



ASSESSMENT and
QUALIFICATIONS
ALLIANCE

Mark scheme

June 2003

GCE

Electronics

Unit ELE2

Copyright © 2003 AQA and its licensors. All rights reserved.

ELE2 – Further Electronics

- 1 (a) Summing amplifier or mixer ✓ (1mark)
- (b) Output of circuit needs to be amplified by 5 ✓
 Calculation or reasoned deduction of feedback resistor changes ✓
 R_f changed to $500k\Omega$ ✓
 {gain of circuit needs to be increased ✓}
 {increase value of feedback resistor ✓} (3 marks)
- (c) (i) Resistor ✓
 connected to inverting input terminal ✓ (2 marks)
- (ii) Guitar needs to be amplified four times more than other inputs ✓
 Calculation or reasoned deduction of feedback resistor changes ✓
 Resistor value of $25k\Omega$ ✓ (3 marks)
- (Total 9)**
- 2 (a) Binary value = 1111. Decimal value is 15 ✓ Hex value is F ✓ (2 marks)
- (b) The three terms for the heater to be on ✓
 ORed together ✓
 to give expression $Q = \overline{D}\overline{C}\overline{B}\overline{A} + \overline{D}\overline{C}B\overline{A} + \overline{D}C\overline{B}\overline{A}$ ✓ (3 marks)
- (c) Two steps of simplification to give $Q = \overline{D}\overline{B}\overline{A} + \overline{D}\overline{C}\overline{B}\overline{A}$ ✓ ✓ (2 marks)
- (Total 7)**
- 3 (a) Voltage gain = $V_{out} / V_{in} = 2 / 0.02 = 100$ ✓
 { $20mV \times 100 = 2V$ ✓} (1 mark)
- (b) (i) P at inverting input ✓ (1 mark)
- (ii) $G_v = -R_f / R_1 = -100 \Rightarrow R = 100 \times 10000$ ✓
 $\Rightarrow R = 1M\Omega$ ✓ (2 marks)
- (iii) $10k\Omega$ ✓ (1 mark)
- (c) Hydrophone has a large output resistance ✓
 Amplifier has a low input resistance ✓
 Input to amplifier only approximately $20 \times 10000 / 1010000 = 0.2mV$ ✓
 Hydrophone internal resistance contributes to input resistance of inverting amp ✓
 So giving unity gain ✓

max (2 marks)

- (d) Input to + input ✓
 resistor from – input to 0V ✓
 feedback resistor $1M\Omega$ and $R_1 = 10k\Omega$ (or appropriate values) ✓
 { R_f must be greater than $10k\Omega$ } ✓

(3 marks)

- (e) Very high input resistance ✓

(1 mark)

(Total 11)

- 4** (a) Push switch pressed, input to first NAND gate goes high ✓
 Output of first NAND gate goes low, output of astable goes high ✓
 Capacitor discharges and charges in opposite direction ✓
 Until voltage at input to first NAND gate $< +V_s/2$ ✓
 Output of astable switches state ✓
 Capacitor charges in opposite direction ✓
 Process repeats as long as switch pressed ✓

max (5 marks)

(b)
$$f = \frac{1}{2RC} = \frac{1}{2 \times 10^4 \times 10^{-7}} = 500\text{Hz} \quad \checkmark \checkmark$$

(2 marks)

- (c) (i) On the rising edge of each clock pulse ✓
 the output of the D-type flip-flop changes state ✓

(2 marks)

- (ii) They flash {alternately so fast that they appear to be continuously lit} ✓

(1 mark)


(Total 10)

- 5** (a) $X_c = 1/2 \times \pi \times 200 \times 15 \times 10^{-9}$ ✓
 $X_c = 53k\Omega$ ✓

(2 marks)

- (b) Use of non-inverting amplifier formula ✓
 If effect of capacitors ignored gain = 58 ✓
 If effect of capacitors taken into account ✓
 Gain around 30 ✓

max (5 marks)

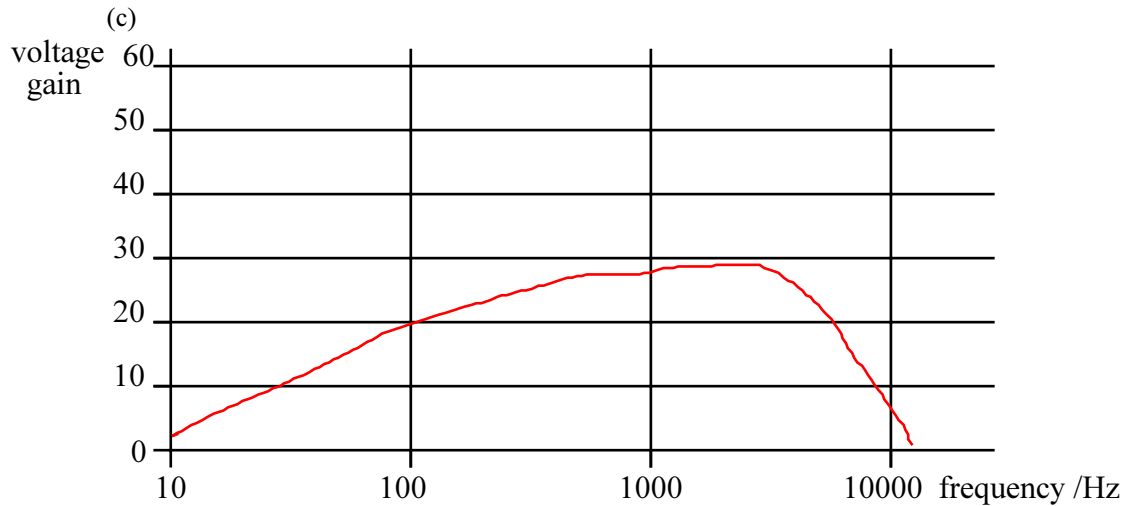

One mark for low freq., one for mid range, one for high freq. ✓ ✓ ✓
 Graph should agree with calculated values for three marks

(3 marks)
(Total 8)

- 6
- (a) Falling edge of clock pulse ✓
 {when its output is low ✓}
- (1 mark)
- (b) (i) Negative going pulse makes output of gate A go high, ✓
 This makes input of gate B high, and output low, ✓
 Capacitor charges through thermistor, ✓
 Until voltage at input of gate B is below half of the supply voltage, ✓
 Output of gate B goes high, output of gate 3 low ✓
 Monostable resets. ✓
- max (5 marks)
- (c) (i) $T = CR = 10^{-8} \times 180 \times 10^3 = 1.8\text{ms}$ ✓
- (1 mark)
- (ii) $T = CR = 10^{-8} \times 10^4 = 0.1\text{ms}$ ✓
- (1 mark)
- (d) The astable triggers the monostable every 2ms and so when cold the monostable provides an almost continuous output to the driver so keeping the heater switched on. ✓
 When the thermistor warms up the output from the monostable is shorter and so the heater is on for less time in every 2ms. ✓
 A temperature will be reached where the length of time that the heater is switched on is just sufficient to maintain the temperature of the thermistor ✓
- max (2 marks)
(Total 9)

- 7 (a) Volume control ✓
 {allows adjustment of the effect of the input ✓ } (1 mark)
- (b) (i) assumption e.g. MOSFETs need V_{GS} of 2V ✓
 11 - 15V ✓ (2 marks)
- (ii) Voltage gain of source follower is 1 ✓
 Inverting amp - gain of -15 ✓ (2 marks)
- (c) (i) Cross-over distortion ✓ (1 mark)
- (ii) Bias the MOSFETs into conduction ✓
 by applying permanent bias voltage to gate ✓
 Use negative feedback ✓
 by incorporating output devices into op-amp feedback loop ✓ (4 marks)
- (iii) Only a noise/sound is needed ✓ (1 mark)
- (d) (i) $W = I^2 \times R = 2.3^2 \times 4 = 21 \text{ W}$ ✓ ✓ (2 marks)
- (ii) {Difference between input power and output} power is dissipated
 as heat in MOSFETs ✓
 Heatsinks prevent MOSFETs from being destroyed by getting too hot ✓ (2 marks)
- (e) Metal - good conduction of heat away from MOSFETs ✓
 Large surface area - good convection and radiation of heat from MOSFETs ✓
 Matt black - good radiation of heat from MOSFETs ✓
 Good thermal contact with MOSFETs ✓
 Fan to improve air circulation ✓

max (3 marks)

(Total 18)

(Paper Total 72 marks)