



ASSESSMENT and  
QUALIFICATIONS  
ALLIANCE

# Mark scheme

# June 2003

---

## GCE

## Electronics


### Unit ELE4

Copyright © 2003 AQA and its licensors. All rights reserved.
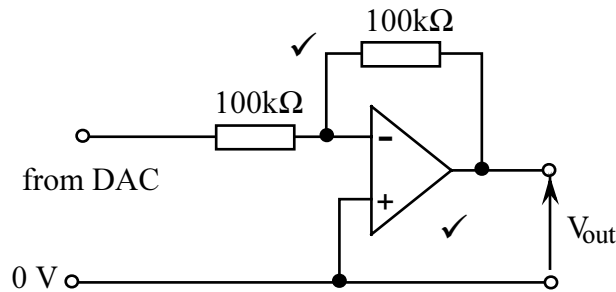
## ELE4 – Electronic Control Systems


- 1
- (a) (i) data in ROM cannot be changed, data in RAM can be ✓  
ROM retains data after power is removed, Ram loses data ✓ etc. (1 mark)  
max (1 mark)
- (ii) basic input and output instructions ✓  
basic operating system commands ✓  
any sensible response (2 marks)
- (b) (i) A bus is a collection of wires along which data is sent and received and to which each section of the microcomputer system is connected ✓ (1 mark)
- (ii) Buses are used to reduce the number of connection routes needed ✓ (1 mark)
- (iii) To enable data to pass to and from the microprocessor (or RAM etc) ✓ (1 mark)
- (c) (i) Memory mapped ports are decoded as memory addresses and accessed as memory elements ✓ (1 mark)
- (ii) I/O mapping has its own separate control line (or commands) to indicate an address is an I/O port. ✓  
I/O mapping does not take up memory allocation (addresses) ✓ (2 marks)
- (Total 9)**
- 2
- (a) (i) a, b, c, d, g ✓ (1 mark)
- (ii) D<sub>0</sub>, D<sub>1</sub>, D<sub>2</sub>, D<sub>3</sub> and D<sub>6</sub> ✓  
i.e. 01001111 (or 79<sub>10</sub>) ✓  
giving 4F ✓ (3 marks)
- (b) (i) 60mA ✓ (1 mark)
- (ii) **5 LEDs** => **5 x 1.9 = 9.5V** ✓  
voltage across R approx. **15 - 9.5 = 5.5V** ✓  
=> **R = 5.5 / 0.06 = 91.7Ω** ✓ max (2 marks)
- (iii) **Power = V x I = 5.5 x 0.06** ✓  
=> **Power = 0.33W** (accept 0.5 or 1W) ✓ (2 marks)
- (Total 9)**

- 3 (a) (i) Digital to Analogue Conversion ✓ (1 mark)
- (ii)  $12.75V / 255$  ✓  
 $\Rightarrow$  change in output for a change of 1 in the input is 0.05V (50mV) ✓ (2 marks)
- (iii)



- (b) (i) **start:** is a label ✓ (1 mark)
- (ii) sends the integer variable  $N\%$  to the output port  $378_{16}$  ✓ (1 mark)
- (c) Enter a number greater than 255 or less than 0 ✓ ✓ (2 marks)
- (Total 9)**

- 4 (a) (i)

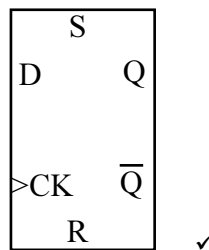

- (ii) whatever value is put on D is transferred to Q ✓  
only on the rising edge of the clock pulse ✓ (1 mark)
- (b) (i) three possible output states ✓  
0, 1, high impedance ✓ (2 marks)
- (ii) to isolate the outputs from the two 4 bit latches ✓ (1 mark)
- (c) (i) Neural networks have lots of very basic processors whereas a PC has a few complex processors ✓  
data is stored through a neural network, whereas a PC stores it centrally ✓ (2 marks)
- (ii) justified reason e.g. No, because ANNs only predictive and are not able to do accurate measurements ✓ (1 mark)
- (Total 9)**

- 5 (a) (i) Whole system built in a single IC ✓  
PICs have separate instruction bus ✓  
(appropriate and sensible response) max (1 mark)
- (ii) Sensible answer e.g. cheap and very versatile ✓ (1 mark)

- (b) Closed loop when system monitors the output and uses state of output to control the input (feedback) ✓ eg.  
 Filling with water requires the amount of water to be monitored and stopped at the required amount - could not do by time because of variation in water pressure ✓  
 Heating could not be done by time because of variation in input water temp ✓  
 max (2 marks)
- (c) (i) Negative feedback is where information from the output is used to adjust the input so that the output remains steady ✓  
 (1 mark)
- (ii) If the speed is too fast the input drive to the motor will be reduced and vice versa if the speed is too slow ✓  
 (1 mark)
- (d) (i) thermistor ✓  
 (1 mark)
- (ii) thermistor is part of a voltage divider circuit which produces a voltage dependent upon the temperature of the thermistor. ✓  
 The op-amp compares this voltage with that from the PIC/AVR and produces a low output when the voltage from the voltage divider exceeds that from the PIC/AVR ✓  
 (2 marks)
- (Total 9)**

- 6 (a) To clean up the pulses,( restoring the logic levels and sharp rise and fall times) ✓  
 (1 mark)
- (b) (i) When the output is at 0V, the voltage divider connected to point A consists of a 47kΩ resistor at the top and two 47kΩ resistors in parallel at the bottom ✓  
 Combined resistance at bottom is 23.5kΩ ✓  
 Voltage divided into ratio of 2:1 => voltage at point A = 4V ✓  
 (3 marks)
- (ii) When output is 12V, there are two 47kΩ resistors at the top of the voltage divider and one 47kΩ resistor at the bottom ✓  
 Combined resistance at top is 23.5kΩ ✓  
 Voltage divided into ratio of 1:2 => voltage at point A = 8V ✓  
 (3 marks)
- (iii) Op-amp has a very large open loop voltage gain so acts as a comparator ✓  
 When the input rises above 8V, the inverting input to the op-amp is greater than the non-inverting input, so the output goes to 0V ✓  
 Similarly when the input voltage goes below 4V when the output is at 12V ✓  
 max (2 marks)
- (Total 9)**

- 7 (a) MOSFET or transistor with coils in drain/collector circuit. ✓  
 Input to gate or base (with series resistor) ✓  
 Protection diode for MOSFET/transistor correctly placed ✓  
 (3 marks)
- (b) (i) A 4 pole stepper motor rotates 7.5° as each successive coil is energised, so with four coils energised in sequence it rotates 30° ✓  
 (1 mark)
- (ii) Reverse the sequence ✓  
 so that D<sub>3</sub> is energised first, then D<sub>2</sub>, then D<sub>1</sub> then finally D<sub>0</sub> ✓  
 (2 marks)
- (iii) Alter the value of the **pause** ✓  
 (1 mark)

- (c) (i) **OUT(&H378)**, is command to write what follows to the parallel port and 4 corresponds to making the bit D<sub>2</sub> logic 1 ✓ (1 mark)
- (ii) **OUT(&H378), 1**  
**GOSUB waitabit**  
**OUT(&H378), 2**  
**GOSUB waitabit**  
**OUT(&H378), 4**  
**GOSUB waitabit**  
**OUT(&H378), 8**  
**STOP** ✓ ✓ ✓ ✓ (4 marks)
- (d) (i) Polled is when the computer monitors a port by regularly reading its value ✓ (1 mark)
- (ii) Interrupt; the computer performs other operations until an external device generates a signal, upon which the computer will stop what it is doing and service the interrupting device. It does not therefore need to continuously monitor the device unlike with polling. ✓ (1 mark)
- (iii) Make the motor rotate one step at a time ✓  
Read in the value of port (&H379) and examine bit 5 ✓  
Repeat this until bit 5 is high, tube A is then aligned with the pipe ✓ (3 marks)
- (e) It would be very difficult to make a conventional motor accurately rotate 30° ✓ (1 mark)
- (Total 18)**

**(Paper Total 72 marks)**