

# GCE 2004

## *June Series*



# Mark Scheme

## Electronics

### *5431/6431 (ELE5)*

---

Mark schemes are prepared by the Principal Examiner and considered, together with the relevant questions, by a panel of subject teachers. This mark scheme includes any amendments made at the standardisation meeting attended by all examiners and is the scheme which was used by them in this examination. The standardisation meeting ensures that the mark scheme covers the candidates' responses to questions and that every examiner understands and applies it in the same correct way. As preparation for the standardisation meeting each examiner analyses a number of candidates' scripts: alternative answers not already covered by the mark scheme are discussed at the meeting and legislated for. If, after this meeting, examiners encounter unusual answers which have not been discussed at the meeting they are required to refer these to the Principal Examiner.

It must be stressed that a mark scheme is a working document, in many cases further developed and expanded on the basis of candidates' reactions to a particular paper. Assumptions about future mark schemes on the basis of one year's document should be avoided; whilst the guiding principles of assessment remain constant, details will change, depending on the content of a particular examination paper.

Further copies of this Mark Scheme are available from:

Publications Department, Aldon House, 39, Heald Grove, Rusholme, Manchester, M14 4NA  
Tel: 0161 953 1170

or

download from the AQA website: [www.aqa.org.uk](http://www.aqa.org.uk)

Copyright © 2004 AQA and its licensors

#### COPYRIGHT

AQA retains the copyright on all its publications. However, registered centres for AQA are permitted to copy material from this booklet for their own internal use, with the following important exception: AQA cannot give permission to centres to photocopy any material that is acknowledged to a third party even for internal use within the centre.

Set and published by the Assessment and Qualifications Alliance.


The Assessment and Qualifications Alliance (AQA) is a company limited by guarantee registered in England and Wales 3644723 and a registered charity number 1073334. Registered address AQA, Devas Street, Manchester. M15 6EX. *Dr Michael Cresswell Director General*

**ELE5 – Communications Systems****1**

- (a) input transducer✓ modulator✓ transmitter✓  
 receiver✓ demodulator✓ output transducer✓ (6 marks)
- (b) any wired system✓ optical fibre✓ radio waves✓ (3 marks)

**(Total 9)****2**

(a)

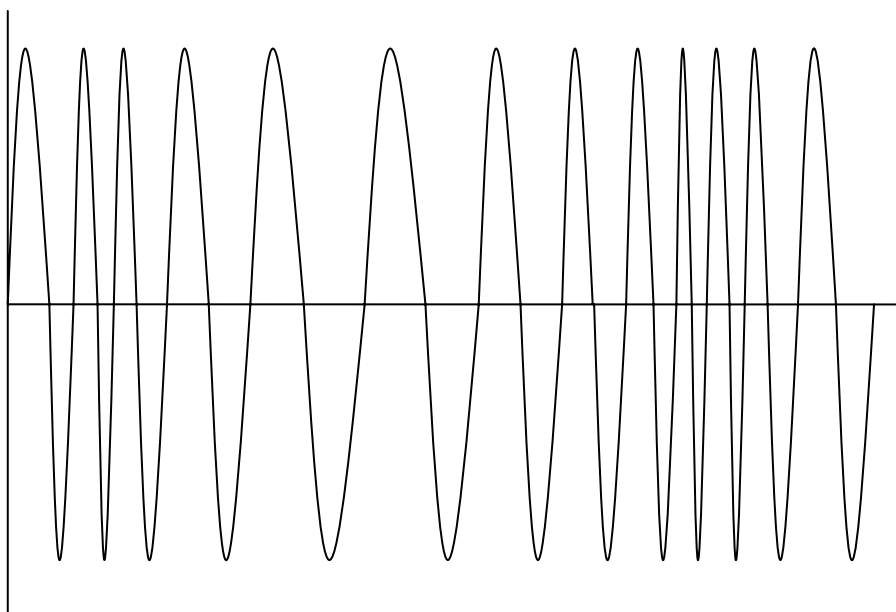

constant amplitude✓ varying frequency✓ in phase with info✓ (3 marks)

- (b)  $2 \times (15 + 75) \checkmark = 180 \text{ kHz} \checkmark$  (2 marks)

- (c) (i)  $\lambda = 3 \times 10^8 / 100 \times 10^6 \checkmark = 3 \text{ m} \checkmark$   
 $3/2 = 1.5 \text{ m} \checkmark$


(ii)  $75 \Omega \checkmark$  (4 marks)

**(Total 9)**

**3**


(a) antenna✓ demodulator✓ audio amp✓ loudspeaker✓ (4 marks)

(b) (i)

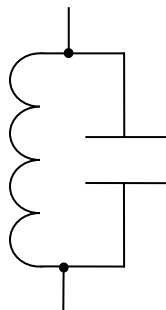

capacitor symbol✓  
inductor symbol✓  
parallel circuit✓

(ii)

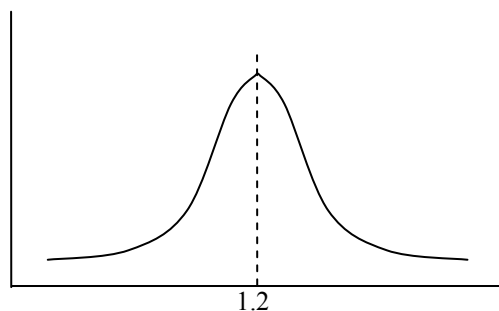

resonant frequency✓  
correct shape✓

(iii)  $L = \frac{1}{4 \pi^2 f^2 C}$  ✓


$= \frac{1}{4 \times 9.87 \times 1.44 \times 10^{12} \times 500 \times 10^{-12}}$  ✓

$= 35 \mu\text{H}$  ✓

(8 marks)

**(Total 12)**


**4**

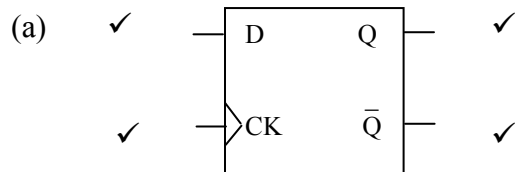

(4 marks)

- (b) data on D input is sent to Q ✓ when clock goes high ✓ (2 marks)
  - (c) all clock inputs wired together ✓ Q to D between stages ✓ (2 marks)
  - (d) serial data into first D input ✓  
parallel data out of all the Q outputs ✓  
after correct number of clock pulses ✓ (3 marks)
- (Total 11)**


**5**

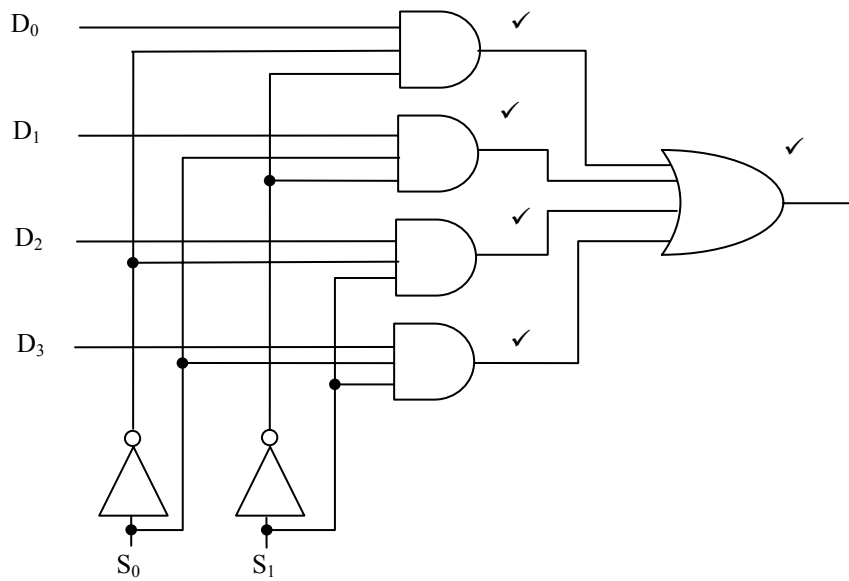

**(Total 5)**

**6**


(a)

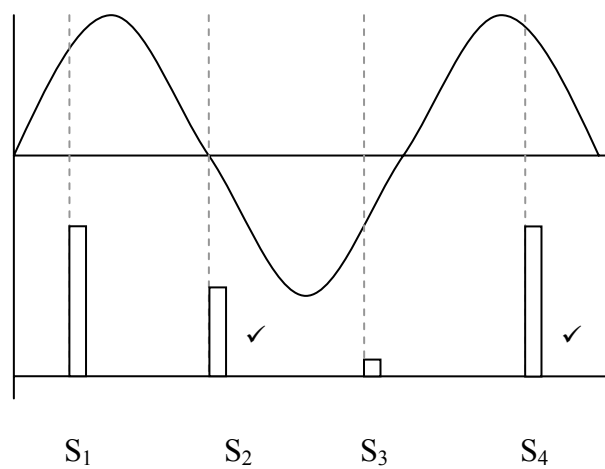

(2 marks)

(b) (i) 256✓

(ii)

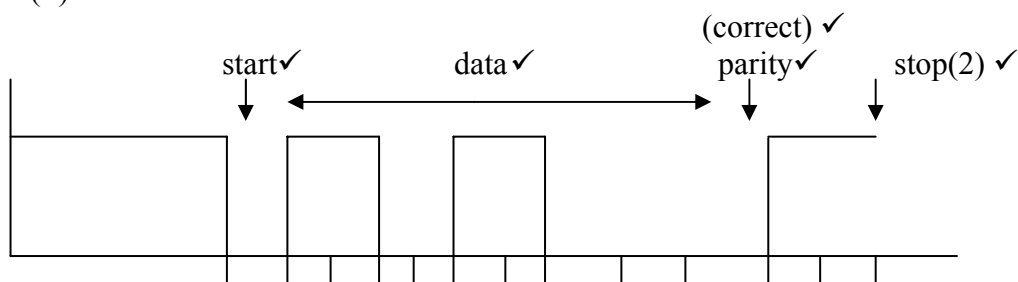

(6 marks)

**(Total 8)**

7


(a) laser diode (allow LED) ✓ (1 mark)

(b) total internal reflection ✓ (1 mark)

(c) photo diode (allow phototransistor) ✓ (1 mark)

(d) absorption ✓ scattering ✓ (2 marks)

(e) (i) e.g.

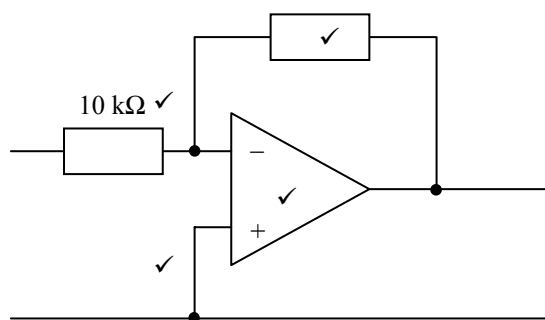


gain;  $1 / 0.025 = 40$  ✓

feedback resistor;  $40 \times 10 \text{ k} = 400 \text{ k}\Omega$  ✓

(ii) gain-bandwidth product ✓ (7 marks)

(f) (i)

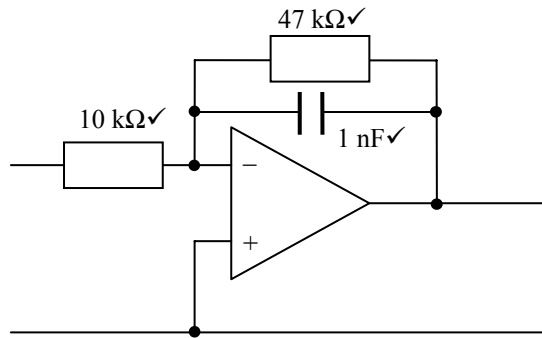

$$\begin{aligned} \text{(ii)} \quad f &= \frac{1}{2\pi RC} \quad \checkmark \\ &= \frac{1}{6.28 \times 47 \times 10^3 \times 10^{-9}} \quad \checkmark \\ &= 3.4\text{ kHz} \quad \checkmark \end{aligned}$$

(6 marks)

**(Total 18)****(Paper Total 72)**