



General Certificate of Education

Electronics 5431/6431

ELE4 Electronic Control Systems

Mark Scheme

2007 examination - June series

Mark schemes are prepared by the Principal Examiner and considered, together with the relevant questions, by a panel of subject teachers. This mark scheme includes any amendments made at the standardisation meeting attended by all examiners and is the scheme which was used by them in this examination. The standardisation meeting ensures that the mark scheme covers the candidates' responses to questions and that every examiner understands and applies it in the same correct way. As preparation for the standardisation meeting each examiner analyses a number of candidates' scripts: alternative answers not already covered by the mark scheme are discussed at the meeting and legislated for. If, after this meeting, examiners encounter unusual answers which have not been discussed at the meeting they are required to refer these to the Principal Examiner.

It must be stressed that a mark scheme is a working document, in many cases further developed and expanded on the basis of candidates' reactions to a particular paper. Assumptions about future mark schemes on the basis of one year's document should be avoided; whilst the guiding principles of assessment remain constant, details will change, depending on the content of a particular examination paper.

Further copies of this Mark Scheme are available to download from the AQA Website: www.aqa.org.uk

Copyright © 2007 AQA and its licensors. All rights reserved.

COPYRIGHT

AQA retains the copyright on all its publications. However, registered centres for AQA are permitted to copy material from this booklet for their own internal use, with the following important exception: AQA cannot give permission to centres to photocopy any material that is acknowledged to a third party even for internal use within the centre.

Set and published by the Assessment and Qualifications Alliance.

- 1**
- (a) (i) A label, gives a reference point within the subroutine/program ✓
- (ii) Reads the contents of port &H379 into the (integer) variable X% ✓
- (iii) Reads port &H379 into X% and masks the three least significant bits ✓
- (4 marks)*
- (b) (i) When called, it reads the keyboard a set number of times and checks to see if a particular key has been pressed, so delaying the computer ✓
- (ii) Change the value passed to the routine in T% ✓
- (iii) When the keyboard has been scanned T% times or when a particular key is pressed (Esc) ✓
- (5 marks)*
- (Total 9 marks)*
-
- 2**
- (a) (i) 0V (since no current passes through the 1MΩ resistor) ✓
- (ii) 3μA passes through 1MΩ resistor so output voltage is - 3V ✓
- (3 marks)*
- (b) (i) Very large voltage gain ✓
- (ii) $2^8 \Rightarrow 256$ ✓
- (2 marks)*
- (c) (i) D_6 is half of $D_5 \Rightarrow 20k\Omega$ ✓
 D_1 is 640kΩ ✓
- (ii) $V_{out} = -R_f \{ V / R \}$ ✓
 $\Rightarrow V_{out} = -10 (5 / 40) = (-)1.25V$ ✓
- (4 marks)*
- (Total 9 marks)*

- 3**
- (a) (i) Conventional motor - 2 connections ✓
 (allow credit for mention of separate field windings etc)
 Stepper motor - at least 4 connections ✓
- (ii) Conventional motor has no control over accuracy of rotation ✓
 Stepper motor - angle of rotation accurate ✓
- (4 marks)*
- (b) (i) Armature moves 7.5° anticlockwise ✓
- (ii) The armature moves 7.5° each time the current is switched
 to the next coil so armature rotates 30°, ✓ clockwise ✓
- (3 marks)*
- (c) To rotate the current has to be continuously switched, in order,
 to coils A, B, C and D ✓
- (1 mark)*
- (d) The speed of rotation can be changed by varying the time that the
 current passes through each coil (or delay between advancing
 current to next coil) ✓
- (1 mark)*
- (Total 9 marks)*
- 4**
- (a) They contain ROM, RAM, CPU, I/O ports etc ✓
 all formed onto a single piece of silicon ✓
- (2 marks)*
- (b) Cheap to purchase ✓
 Easily updated ✓
 small physical size ✓
 reliable - no moving parts etc ✓
- (max 2 marks)*
- (c) Separate instruction bus ✓
- (1 mark)*

- (d) start
input "power setting"
output "power setting to power supply"
input "cooking time"
output "switch on magnetron" ✓
output "display cooking time"
wait one second ←—————→
decrement cooking time
does cooking time remaining equal to zero - no —————→
yes ✓
switch off magnetron
output "Remove Food"
output "turn on buzzer"
has buzzer sounded for 5 seconds yes - stop ✓
no
stop

✓ for valid symbols

(4 marks)

(Total 9 marks)

- 5 (a) (i) connections between neurons, ✓
weighting attached to each connection ✓
- (ii) ANN - simple but lots of them ✓
compared to few but complex ✓
- (iii) When the ANN compares its output with the required
output for a set of inputs and adjusts the weightings etc
of the inputs to create a match ✓
Programmed by providing examples of outputs that
should be gained from given sets of inputs and allowing
the ANN to adjust its neuron weightings ✓

(6 marks)

- (b) PCs better at matching for exact items whereas ANNs are better
to interpret the input data to find patterns ✓

(1 mark)

- (c) lines joining each input layer neuron to each neuron in the hidden
layer ✓✓

(2 marks)

(Total 9 marks)

- 6 (a) Accurate MOSFET symbol ✓ correctly positioned ✓ (2 marks)
- (b) (i) When output of op-amp high, top resistor of voltage divider is effectively $5k\Omega$ so voltage split in ratio 1:2 ✓
=> voltage at non-inverting input of op-amp is 3.33V ✓
- (ii) When output of op-amp low, bottom resistor of voltage divider is effectively $5k\Omega$ so voltage split in ratio 2:1 ✓
=> voltage at non-inverting input of op-amp is 1.67V ✓ (4 marks)
- (c) (i) $T = C R = 4.7 \times 10^6 \times 30 \times 10^{-12} = 1.41 \times 10^{-4} \text{s}$ ✓
- (ii) 63% of 5V = 3.15V ✓ (2 marks)
- (d) Recognition of charging between $\frac{1}{3}$ and $\frac{2}{3}V_s$ taking $0.69RC$ so giving a frequency of 10.3kHz ✓ (1 mark)
- (Total 9 marks)
- 7 (a) Closed loop system because there is feedback ✓ (1 mark)
- (b) (i) correctly labelled virtual earth point on inverting input of op-amp ✓
- (ii) top MOSFET labelled with N ✓
- (iii) rudder and variable resistor rotate in other direction ✓
- (iv) Diodes protect MOSFETs from induced high voltages from motor ✓ (4 marks)
- (c) (i) Op-amp output goes negative ✓
so P channel MOSFET switches on ✓
- (ii) $V_{\text{out}} = -100 \left(\frac{3}{10} - \frac{2.75}{10} \right) = -2.5V$ ✓ ✓
- (iii) This will reduce the speed of the motor ✓
since the voltage has decreased ✓
- (iv) The motor will stop when there is no (very small) voltage across it ✓
which occurs when the voltage from the variable resistor is -3V ✓

(v) voltage from VR is -3V, ✓
output of summing amp goes positive, ✓
motor rotates in opposite direction until VR voltage is 0V ✓
(11 marks)

(d) bias MOSFETs into conduction, ✓
by an appropriate method e.g. voltage dividers to gates of
MOSFETs ✓
include MOSFETs in the op-amp feedback loop ✓
(max 2 marks)

(Total 18 marks)