

Surname		Other Names	
Centre Number		Candidate Number	
Candidate Signature			

For Examiner's Use
--------------------

General Certificate of Education  
 June 2008  
 Advanced Subsidiary Examination



**ELECTRONICS**  
**Unit 1 Foundation Electronics**

**ELE1**

Friday 16 May 2008 9.00 am to 10.30 am

<p><b>For this paper you must have:</b></p> <ul style="list-style-type: none"> <li>• a pencil and a ruler</li> <li>• a calculator.</li> </ul>
---

Time allowed: 1 hour 30 minutes

**Instructions**

- Use black ink or black ball-point pen. Use pencil only for drawing.
- Fill in the boxes at the top of this page.
- Answer **all** questions.
- You must answer the questions in the spaces provided. Answers written in margins or on blank pages will not be marked.
- Do all rough work in this book. Cross through any work you do not want to be marked.
- A *Data Sheet* is provided on pages 3 and 4. Detach this perforated sheet at the start of the examination.

**Information**

- The maximum mark for this paper is 72.
- The marks for questions are shown in brackets.
- You are expected to use a calculator where appropriate.
- You are reminded of the need for good English and clear presentation in your answers.

For Examiner's Use			
Question	Mark	Question	Mark
1		5	
2		6	
3			
4			
Total (Column 1) →			
Total (Column 2) →			
TOTAL			
Examiner's Initials			



**Data Sheet**

- A perforated *Data Sheet* is provided as pages 3 and 4 of this question paper.
- This sheet may be useful for answering some of the questions in the examination.
- You may wish to detach this sheet before you begin work.




## Data Sheet

**Resistors** Preferred values for resistors (E24) series:  
1.0, 1.1, 1.2, 1.3, 1.5, 1.6, 1.8, 2.0, 2.2, 2.4, 2.7, 3.0, 3.3, 3.6, 3.9, 4.3,  
4.7, 5.1, 5.6, 6.2, 6.8, 7.5, 8.2, 9.1 ohms and multiples that are ten  
times greater.

**Resistor Printed Code (BS 1852)** This code consists of letters and numbers:  
R means  $\times 1$   
K means  $\times 1000$  (i.e.  $10^3$ )  
M means  $\times 1\,000\,000$  (i.e.  $10^6$ )  
Position of the letter gives the decimal point  
Tolerances are given by the letter at the end of the code, F =  $\pm 1\%$ ,  
G =  $\pm 2\%$ , J =  $\pm 5\%$ , K =  $\pm 10\%$ , M =  $\pm 20\%$ .

Resistor Colour Code	Number	Colour
	0	Black
	1	Brown
	2	Red
	3	Orange
	4	Yellow
	5	Green
	6	Blue
	7	Violet
	8	Grey
	9	White

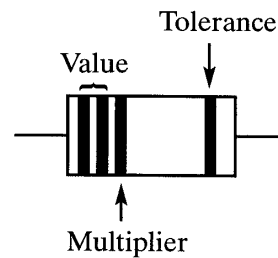

Tolerance, gold =  $\pm 5\%$ , silver =  $\pm 10\%$ , no band =  $\pm 20\%$ .

**Silicon diode**  $V_F = 0.7\text{ V}$

**Silicon transistor**  $V_{be} \approx 0.7\text{ V}$  in the on state  
 $V_{ce} \approx 0.2\text{ V}$  when saturated

**Resistance**  $R_T = R_1 + R_2 + R_3$  series

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$
 parallel

**Capacitance**  $\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$  series

$$C_T = C_1 + C_2 + C_3$$
 parallel

**Time constant**  $T = CR$

**A.C. theory**  $I_{\text{rms}} = \frac{I_o}{\sqrt{2}}$

$$V_{\text{rms}} = \frac{V_o}{\sqrt{2}}$$

$$X_C = \frac{1}{2\pi fC}$$
 reactance

$$X_L = 2\pi fL$$
 reactance

$$f = \frac{1}{T}$$
 frequency, period

$$f_o = \frac{1}{2\pi\sqrt{LC}}$$
 resonant frequency

Turn over ▶




Operational amplifier	$G_V = \frac{V_{\text{out}}}{V_{\text{in}}}$	voltage gain
	$G_V = -\frac{R_f}{R_1}$	inverting
	$G_V = 1 + \frac{R_f}{R_1}$	non-inverting
	$V_{\text{out}} = -R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$	summing
Astable and Monostable using NAND Gates	$f \approx \frac{1}{2RC}$	astable
	$T \approx RC$	monostable
555 Astable and Monostable	$T = 1.1RC$	monostable
	$t_H = 0.7(R_A + R_B)C$ $t_L = 0.7R_B C$ ]	astable
	$f = \frac{1.44}{(R_A + 2R_B)C}$	two resistor circuit
Electromagnetic Waves	$c = 3 \times 10^8 \text{ m s}^{-1}$	speed in vacuo
List of BASIC Commands	<b>DIM</b> variable [(subscripts)] <b>DO</b> [{ <b>WHILE</b>   <b>UNTIL</b> } condition] (statement block) <b>LOOP</b> <b>DO</b> (statement block) <b>LOOP</b> [{ <b>WHILE</b>   <b>UNTIL</b> } condition] <b>FOR</b> counter = start <b>TO</b> end [ <b>STEP</b> increment] (statement block) <b>NEXT</b> counter <b>GOSUB</b> [label   line number] (statement block) <b>RETURN</b> <b>IF</b> condition <b>THEN</b> (statement block 1) <b>ELSE</b> (statement block 2) <b>INKEY\$</b> <b>INP</b> (port %) <b>INPUT</b> [ ; ] ["prompt" ;1, ] variable list (comma separated) <b>LPRINT</b> [expression list] [ { ;1, } ] <b>OUT</b> port%, data% <b>PRINT</b> [expression list] [{;1,}] <b>REM</b> remark	



Answer **all** questions in the spaces provided.

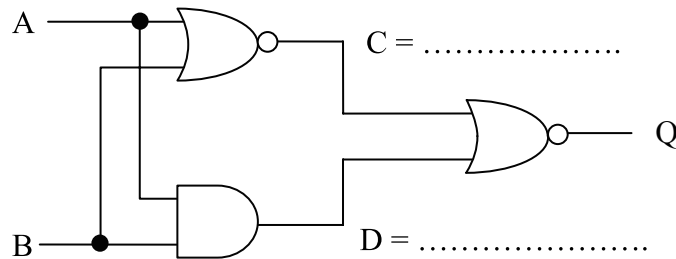1 A logic circuit diagram is shown below.



1 (a) Write the simplest Boolean expressions for the logic signals at points C and D on the diagram above in the spaces provided. (2 marks)

1 (b) (i) Write the simplest Boolean expression for Q in terms of C and D only.

Q = .....

1 (b) (ii) Write a simple Boolean expression for Q in terms of A and B only.

Q = .....

(3 marks)

1 (c) Complete the truth table to show the logic values of C, D and Q for all the combinations of variables A and B.

A	B	C	D	Q
0	0			
0	1			
1	0			
1	1			

(4 marks)


1 (d) Draw a logic circuit diagram in the space below using a single logic gate that would have the same function as the original circuit.

(2 marks)

Turn over ▶



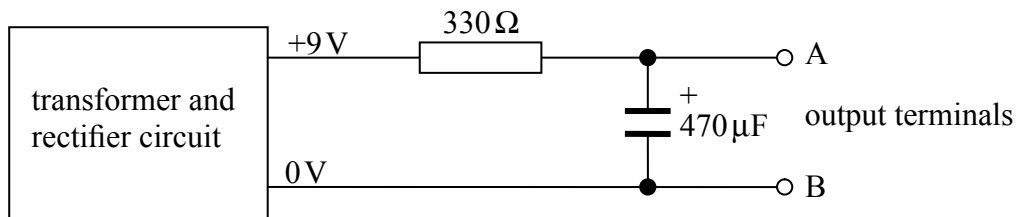2 The output stage of a power supply is shown below.



2 (a) (i) Calculate the current through the resistor when the output terminals are connected together.

.....

2 (a) (ii) Calculate the power dissipation of the resistor at this current.

.....

(4 marks)

2 (b) (i) Calculate the time constant of this circuit, assuming no load is connected to its output.

.....

2 (b) (ii) The 9 V supply is switched on and the capacitor is initially uncharged. Approximately how long will it take for the output voltage to reach 9 V?

.....

2 (b) (iii) A load resistance of 10 kΩ is connected between the output terminals. Calculate the approximate time taken for the output voltage to reach 0 V after the 9 V supply is switched off.


.....

(6 marks)



3 An npn junction transistor is to be used as a switch to control an electromagnetic relay.

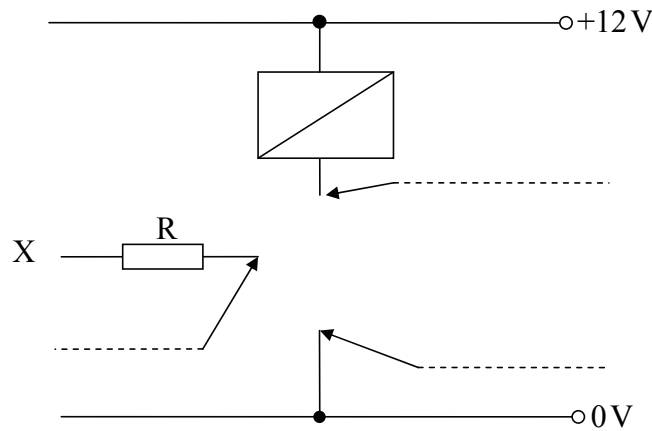3 (a) (i) Complete the circuit diagram to show how the transistor is connected, label the leads of the transistor in the spaces shown.



3 (a) (ii) Add to the diagram the component required to protect the transistor from the back emf of the relay.

(6 marks)

3 (b) The relay coil has a resistance of  $240\ \Omega$ .

3 (b) (i) Calculate the collector current of the transistor when the relay is switched on.

.....  
 .....

3 (b) (ii) The transistor has a current gain (ratio of collector current to base current) of 50. Calculate the minimum base current when the relay is switched on.

.....  
 .....

3 (b) (iii) The input voltage at X which saturates the transistor is 4.7V. Calculate the value of R, the resistor required.

.....  
 .....

3 (b) (iv) Choose the most appropriate value for R from the E24 series.

.....

(5 marks)



- 4 A student designs a very simple light level detector which indicates when the light level falls, as a reminder to switch on a reading lamp to avoid eye strain.

Since the detector is to be battery powered, it must have a **minimum** power consumption.

The following data is gathered about the devices that could be used.

For the input sensor:

LDR type	resistance at 10 lux
a	200 k $\Omega$
b	94 k $\Omega$
c	20 k $\Omega$

For the processing stage:

type	relevant information
NOT gate 4049	Power consumption 0.001 mW
op-amp TL081	Supply current 1.4 mA
op-amp 741	Supply current 1.7 mA

For the output stage:

device	relevant information
filament lamp	6 V 0.06 A
red LED	$V_f$ 2V @ 10 mA

- 4 (a) Choosing from the tables above, select a suitable device and type for each of the subsystems that would result in the lowest current drawn from the battery. Label the system diagram with them.



(3 marks)

- 4 (b) The system could be designed to indicate low light by either switching the output device on or off. Which would be better? Give your reason.

.....

.....

(2 marks)





- 4 (c) The LDR has a resistance of  $150\text{ k}\Omega$  at the light level at which the system should alert the user. The chosen processing stage requires an input voltage of  $4.5\text{ V}$  to switch. Draw the circuit diagram of a voltage divider that would give a rising voltage as the light level falls marking the output connection and suitable value for the component other than the LDR.

\_\_\_\_\_ ○  $+9\text{ V}$

\_\_\_\_\_ ○  $0\text{ V}$

(3 marks)

- 4 (d) The output of the process stage is  $7.3\text{ V}$ , and the minimum output current that will operate the output device is  $3\text{ mA}$  at  $1.9\text{ V}$ .

Calculate the value of a series resistor for the output device.

.....  
.....

(2 marks)

10
----

**Turn over for the next question**


**Turn over ▶**



5 A student designs a noise warning system to alert the user to the presence of a noise level likely to damage hearing. An LED flashes on and off when the noise level exceeds a safe value.

5 (a) Label each subsystem in the system diagram below to show a possible design for the noise warning system using the following subsystems:

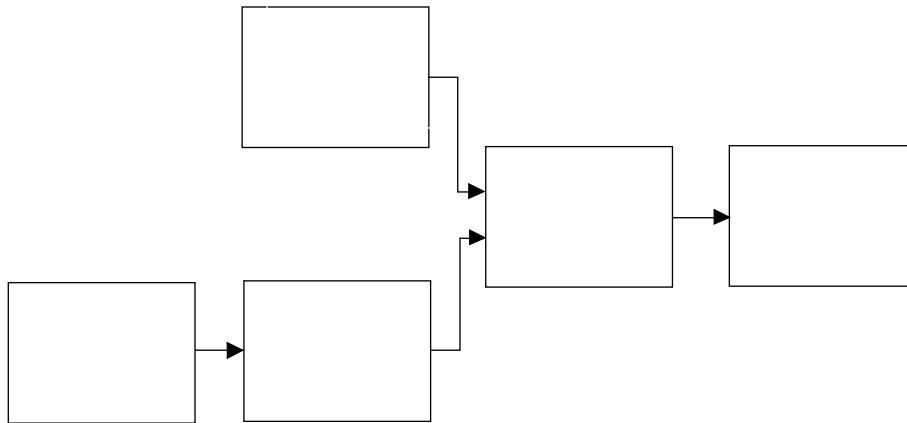**NOR gate      astable      comparator      LED      sound sensor**



(5 marks)


5 (b) In which subsystem could

5 (b) (i) an op-amp be used.....

5 (b) (ii) a 555 IC be used?.....

(2 marks)

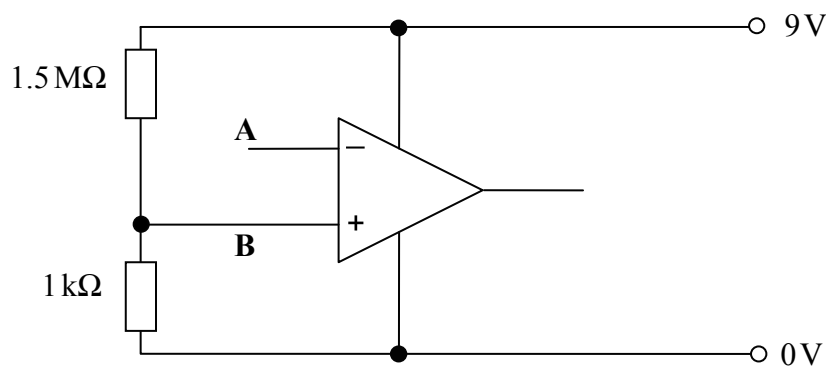5 (c) The comparator circuit diagram is shown below.



5 (c) (i) Calculate the voltage at point **B** in this circuit

.....  
 .....

The signal from the sound sensor is connected to point **A** in the comparator circuit. What voltage would you expect from the output of this circuit when


5 (c) (ii) the voltage at **A** is 4 mV .....

5 (c) (iii) the voltage at **A** rises to 10 mV? .....

(4 marks)

5 (d) Part of the astable circuit diagram is shown below.

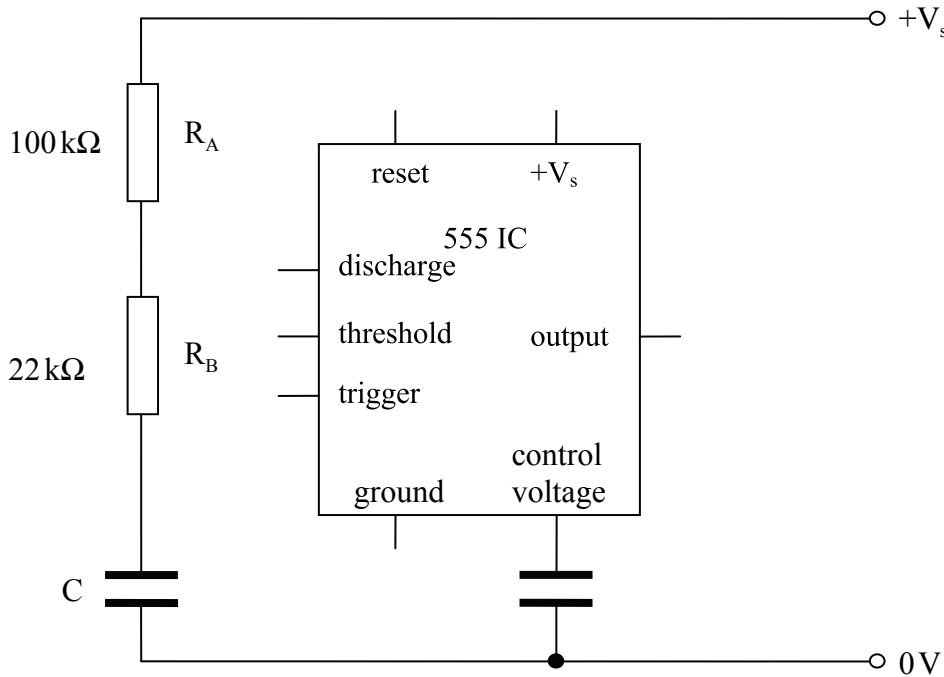5 (d) (i) Complete the circuit by drawing in the wire links required.



5 (d) (ii) Given the values shown on the circuit diagram for  $R_A$  and  $R_B$ , calculate the value of  $C$  required to give an output frequency of 2 Hz.

.....  
 .....

(7 marks)



6 A zener diode is used to regulate the output voltage of a power supply to 5.1 V when an input voltage between 7 V and 9.6 V is applied.

6 (a) Add a zener diode and its current limiting resistor to complete the circuit diagram below.



(4 marks)

6 (b) The minimum zener current should be 5 mA under all conditions. The maximum output current required is 60 mA.

6 (b) (i) Calculate the minimum voltage across the resistor.

.....

6 (b) (ii) What current flows through the resistor when the output current is 60 mA?

.....

6 (b) (iii) Calculate the required resistor value.

.....

6 (b) (iv) Which preferred E24 resistor value should be chosen?

.....

6 (b) (v) Calculate the power dissipated by the resistor when the input voltage is 9.6 V and the output current is 60 mA.

.....

.....

6 (b) (vi) Explain whether a 0.25 W power rating would be suitable for the resistor.

.....

(8 marks)

**END OF QUESTIONS**

