



**General Certificate of Education (A-level)  
June 2013**

**Electronics**

**ELEC4**

**(Specification 2430)**

**Unit 4: Programmable Control Systems**

**Final**

***Mark Scheme***

---

Mark schemes are prepared by the Principal Examiner and considered, together with the relevant questions, by a panel of subject teachers. This mark scheme includes any amendments made at the standardisation events which all examiners participate in and is the scheme which was used by them in this examination. The standardisation process ensures that the mark scheme covers the students' responses to questions and that every examiner understands and applies it in the same correct way. As preparation for standardisation each examiner analyses a number of students' scripts: alternative answers not already covered by the mark scheme are discussed and legislated for. If, after the standardisation process, examiners encounter unusual answers which have not been raised they are required to refer these to the Principal Examiner.

It must be stressed that a mark scheme is a working document, in many cases further developed and expanded on the basis of students' reactions to a particular paper. Assumptions about future mark schemes on the basis of one year's document should be avoided; whilst the guiding principles of assessment remain constant, details will change, depending on the content of a particular examination paper.

Further copies of this Mark Scheme are available from: [aqa.org.uk](http://aqa.org.uk)


Copyright © 2013 AQA and its licensors. All rights reserved.

**Copyright**

AQA retains the copyright on all its publications. However, registered schools/colleges for AQA are permitted to copy material from this booklet for their own internal use, with the following important exception: AQA cannot give permission to schools/colleges to photocopy any material that is acknowledged to a third party even for internal use within the centre.

Set and published by the Assessment and Qualifications Alliance.

Question	Part	Subpart	Marking guidance	Mark
1	(a)		closed because the pressure in the storage tank is monitored, output affects input, there is feedback (because of pressure sensor). and negative because the pressure is kept constant	2
1	(b)		$\approx 5 \times 10^5$ and $\approx 8 \times 10^5$ Pa	2
1	(c)	(i)	evidence of voltage divider calculation 4V	2
1	(c)	(ii)	calculation of resistors in parallel (23.5k) voltage divider calculation leading to 8V	2
1	(c)	(iii)	calculation to show resistance of pressure sensor is 40k $\Omega$ , => pressure is $\approx 600 - 700$ kPa	2
2	(a)		<b>Uses in embedded microcontroller not raw definitions e.g. RAM – memory that can be accessed in any order</b> stores the operating program for the microcontroller stores information which needs to be retained when power is removed, e.g. PIN stores data temporarily while processor is operating , e.g. decoding PIN.	3
2	(b)		keep subsystems synchronised / timing for serial data I/O / determines speed of operation initialise system / restarts program in ROM (NOT Reset alone)	2
2	(c)		<b>During verification of PIN</b> ROM accessed to control processor, handle serial I/O, and contains details of PIN encryption  NVM accessed to recall encrypted PIN  RAM accessed to temporarily store numbers e.g. those involved with processing the PIN	5
3	(a)	(i)	calculation, answer 360, 390 ohms	2

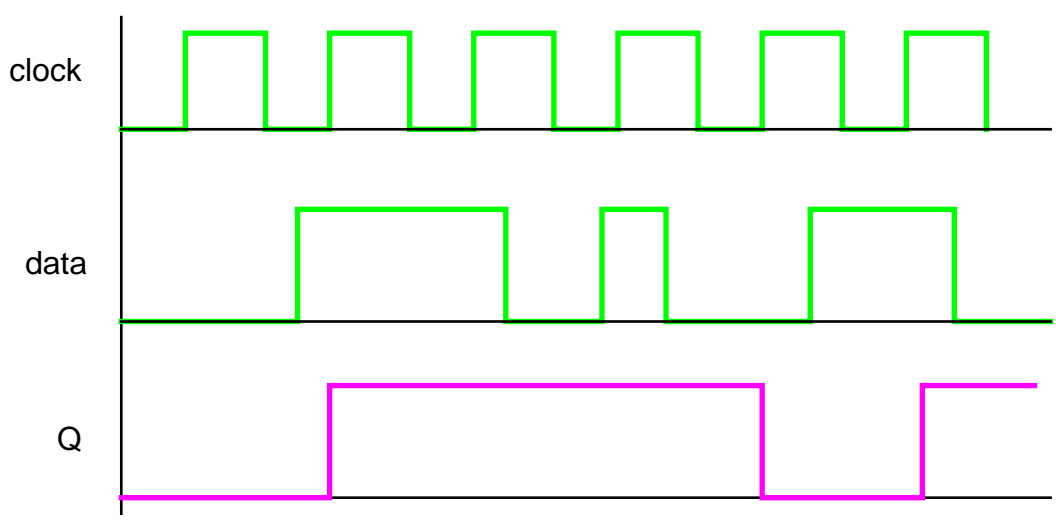3	(a)	(ii)	calculation, answer $1M\Omega < R_p < 25M\Omega$		2
3	(a)	(iii)	single sharp pulse 0 - 5 - 0V		1
3	(b)		 <p>clock</p> <p>data</p> <p>Q</p> <p>rising edge triggered only clock triggered - correct shape</p>		2
3	(c)	(i)	reference to light already going through outer slot, therefore D=1 by the time that the inner slot becomes 1, so activating the clock input		2
3	(c)	(ii)	rotates the other way then Q = 0 because clock rises when no light passes through outer slots		1
4	(a)		finishes current operation, (saves current variables to the stack), jumps to a routine to execute the interrupt request, On return, the variables are recalled from the stack and it continues where it left off.		3

4	(b)	value in PORTB decreases by 1 to a minimum value of 0		<b>2</b>																											
4	(c)	value in PORTB increases by 1 to a maximum value of 255		<b>2</b>																											
4	(d)	MOVRW PORTA, (marked with MOVRW PORTB) ANDW 0x01 ✓ JPZ (label) ✓ MOVRW PORTB ✓		<b>3</b>																											
5	(a)	MOVW 0x00 MOVWR TRISB		<b>2</b>																											
5	(b)	<table border="1"> <thead> <tr> <th>Display</th> <th>Binary</th> <th>Hexadecimal</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>00001110</td> <td>0x06</td> </tr> <tr> <td>2</td> <td><b>01011011</b></td> <td><b>0x5B (ecf)</b></td> </tr> <tr> <td>3</td> <td>01001111</td> <td>0x4F</td> </tr> <tr> <td>4</td> <td>01100110</td> <td>0x66</td> </tr> <tr> <td>5</td> <td><b>01101101</b></td> <td>0x6D</td> </tr> <tr> <td>6</td> <td>01111101</td> <td>0x7D</td> </tr> <tr> <td>7</td> <td>00001111</td> <td><b>0x07</b></td> </tr> <tr> <td>8</td> <td>01111111</td> <td>0x7F</td> </tr> </tbody> </table>	Display	Binary	Hexadecimal	1	00001110	0x06	2	<b>01011011</b>	<b>0x5B (ecf)</b>	3	01001111	0x4F	4	01100110	0x66	5	<b>01101101</b>	0x6D	6	01111101	0x7D	7	00001111	<b>0x07</b>	8	01111111	0x7F		<b>4</b>
Display	Binary	Hexadecimal																													
1	00001110	0x06																													
2	<b>01011011</b>	<b>0x5B (ecf)</b>																													
3	01001111	0x4F																													
4	01100110	0x66																													
5	<b>01101101</b>	0x6D																													
6	01111101	0x7D																													
7	00001111	<b>0x07</b>																													
8	01111111	0x7F																													
5	(c)	continually reads the value in PORTA until a change in input is detected		<b>2</b>																											
5	(d)	1µs and 2µs 3µs (allow 333kHz)		<b>2</b>																											
6	(a)	relevant calculation leading to 63		<b>1</b>																											

6	(b)	feedback resistor, and +ve input to 0V three input resistors, input resistors in the ratio 1:2:4 in the range $1k\Omega < R < 1M\Omega$		<b>3</b>
6	(c)	feedback resistor, and resistor to 0V two input resistors, all given resistors the same in the range $1k\Omega < R < 1M\Omega$		<b>3</b>
6	(d)	first flash ADC converts the input to an approximate value (most significant 3 bits) this value is converted back into a voltage and subtracted from the input voltage the second flash ADC converts the remainder (least significant three bits)		<b>3</b>
7	(a)	data inputs to D data outputs from Q clock inputs joined and sensibly labelled		<b>3</b>
7	(b)	tri-state – three (output) states 0, 1 OR high, low high impedance (NOT On/Off)		<b>3</b>
7	(c)	shared data bus must be only one signal present at a time to avoid bus contention all other devices in high impedance state		<b>4</b>
8	(a)	Dome heavy, needs large torque/power, but does not need to be positioned accurately => conventional motor ✓✓ Telescope needs to be positioned accurately but does not need large force => stepper motor ✓✓		<b>4</b>
8	(b)	tolerant of large surge currents provide isolation from 'mains' voltage (NOT cheap, easy to use etc)		<b>2</b>

8	(c)	protection diode for MOSFET diode round the correct way one NC terminal to Live, opposite NO to Neutral then remaining NC terminal to Neutral, and NO to Live		4
---	-----	--	--	---