

Centre Number						Candidate Number				
Surname										
Other Names										
Candidate Signature										

For Examiner's Use	
Examiner's Initials	
Question	Mark
1	
2	
3	
4	
5	
6	
TOTAL	



General Certificate of Education
Advanced Subsidiary Examination
June 2014

Electronics

ELEC2

Unit 2 Further Electronics

Wednesday 21 May 2014 9.00 am to 10.00 am

For this paper you must have:

- a pencil and ruler
- a calculator
- a Data Sheet (enclosed).

Time allowed

- 1 hour

Instructions

- Use black ink or black ball-point pen.
- Fill in the boxes at the top of this page.
- Answer **all** questions.
- You must answer the questions in the spaces provided. Do not write outside the box around each page or on blank pages.
- Do all rough work in this book. Cross through any work you do not want to be marked.

Information

- The marks for questions are shown in brackets.
- The maximum mark for this paper is 67.



J U N 1 4 E L E C 2 0 1

Answer **all** questions in the spaces provided.

- 1** A student is experimenting with an ultrasound microphone which operates at a frequency of 40 kHz. The microphone produces a maximum output amplitude of 40 mV and has a very large output resistance (greater than 10 M Ω). The student needs to amplify the microphone output to give a signal of 4 V amplitude.

- 1 (a)** Calculate the voltage gain needed from the amplifier.



[2 marks]

.....

- 1 (b)** Complete the circuit diagram of a suitable op-amp based amplifier in **Figure 1**. Include suitable component values.

[4 marks]

Figure 1

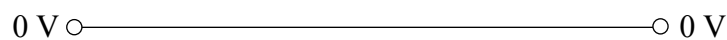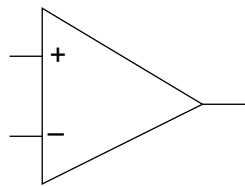

- 1 (c)** When the student tests the amplifier he finds that with an input voltage of 40 mV amplitude, the output is only 1 V amplitude. The student consults the op-amp data sheet and finds that the gain-bandwidth product of the op-amp is 10^6 Hz.

- 1 (c) (i)** Explain the meaning of the term **gain-bandwidth product**.

[1 mark]

.....



1 (c) (ii) Show, using a calculation, why the output of the amplifier is only 1 V.

[2 marks]

.....
.....
.....

1 (c) (iii) Explain how the student can solve the problem by adding a second op-amp circuit.

[2 marks]

.....
.....
.....
.....

11


Turn over for the next question

Turn over ▶



- 2 A resistor and uncharged capacitor are connected in series as in **Figure 2**.


Figure 2

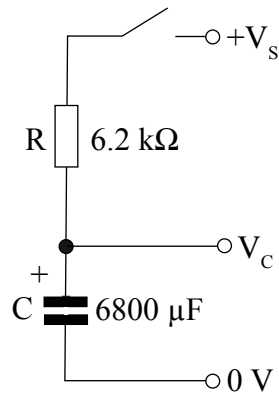

- 2 (a) If the switch is closed at time $t = 0$, sketch on the axes in **Figure 3** how the voltage across the capacitor, V_c , varies with time.

[2 marks]

Figure 3

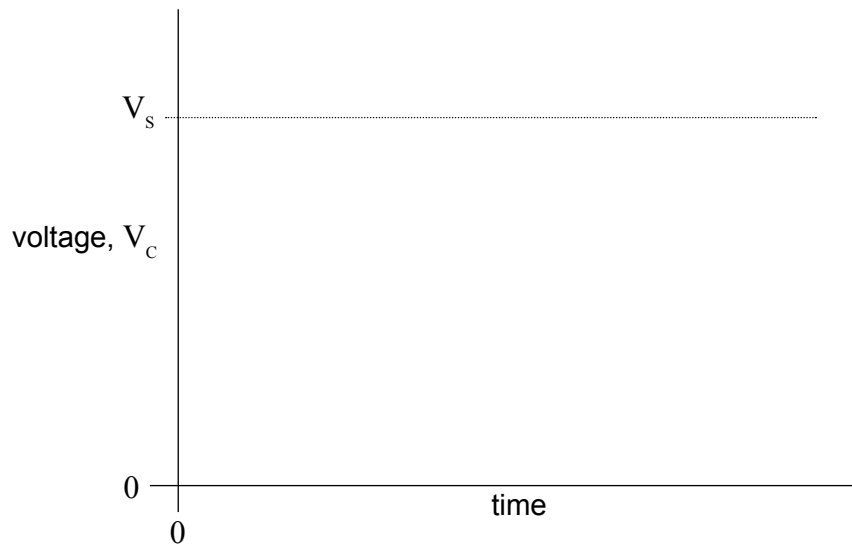

- 2 (b) Calculate the time taken for V_c to be equal to $V_s/2$.

[2 marks]


.....

.....



2 (c) A student decides to use this RC timing circuit as the basis for a kitchen timer project. Figure 4 shows the circuit used.

Figure 4

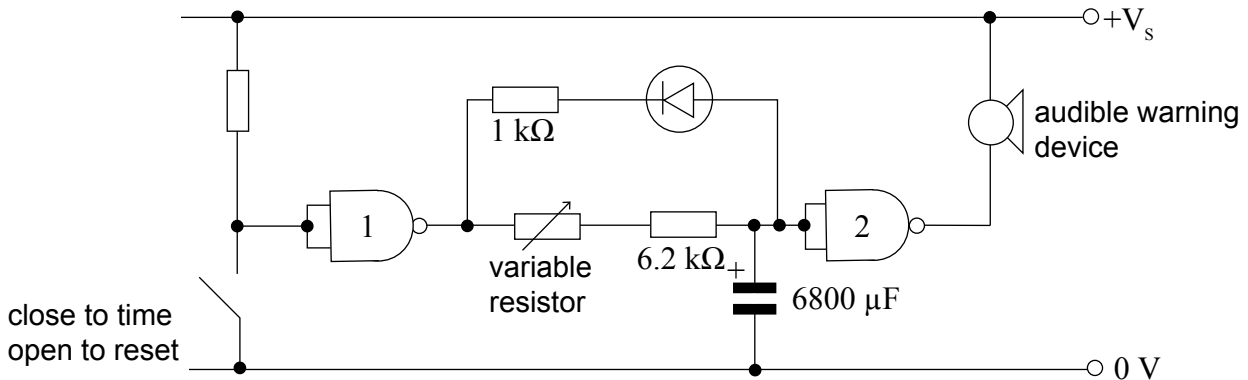

The student wants the maximum time to be about 1 hour. Assuming that the logic gates switch at $V_s/2$, calculate a suitable value for the variable resistor.

[2 marks]

.....

.....

2 (d) When constructed, timings up to a few minutes are accurate but become increasingly too long, until at the maximum setting of the variable resistor, the timer never sounds the audible warning device.

Capacitance $6800 \mu\text{F} \pm 20\%$

Rated voltage 16 V

Leakage current $<50 \mu\text{A} @ 20^\circ\text{C}$

An extract from the data sheet for the capacitor is shown opposite. Explain the likely cause of the timing problem.

[3 marks]

.....

.....

.....

2 (e) When the switch is opened, the timer resets. Describe what happens during this process.

[2 marks]

.....

.....




3 A project needs a subsystem which will produce a pulse output in the range 10 Hz to 200 Hz. The subsystem is to be based on a 555 astable.

3 (a) **Figure 5** shows a partially drawn 555 astable circuit diagram. Add the **three** missing connections.

[3 marks]


Figure 5

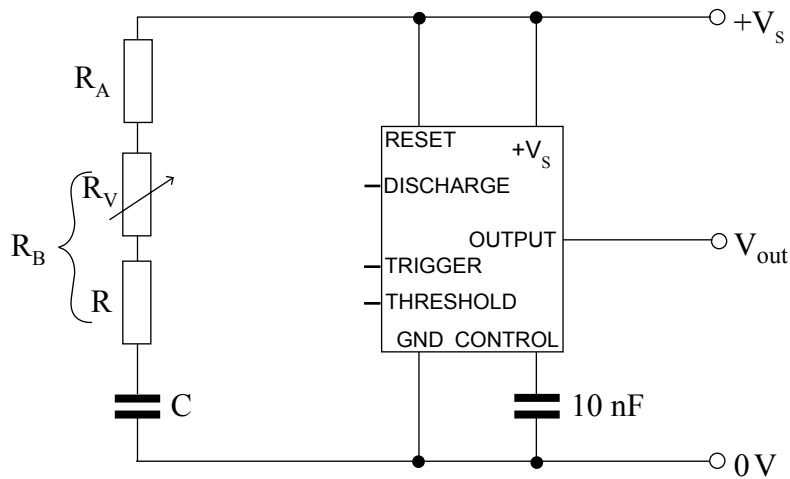

3 (b) **Figure 6** shows how the output voltage, V_{out} , varies with time. Sketch onto the graph how the voltage across the capacitor varies with time.

[3 marks]

Figure 6

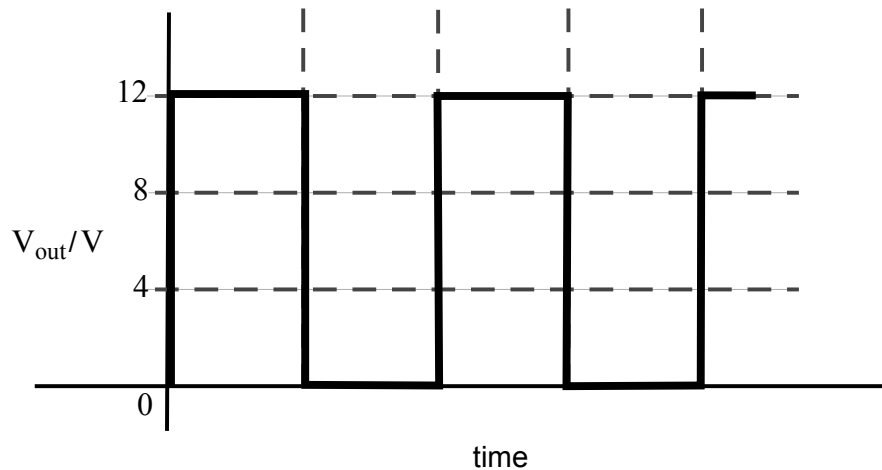

3 (c) If the frequency is 200 Hz, $C = 100 \text{ nF}$ and $R_A = 1 \text{ k}\Omega$, show that the value of the fixed resistor, which is part of R_B , is approximately 36 k Ω .

[3 marks]

.....

.....

.....

.....

3 (d) Calculate a suitable value for R_V so that when set to its maximum value the frequency of the pulses is approximately 10 Hz.

[2 marks]

.....

.....

.....

11


Turn over for the next question

Turn over ▶



- 4 **Figure 7** shows the circuit diagram for a power amplifier. The power amplifier is required to have an overall voltage gain of at least 5 and a power output of 10 W into a 4 Ω loudspeaker.

Figure 7

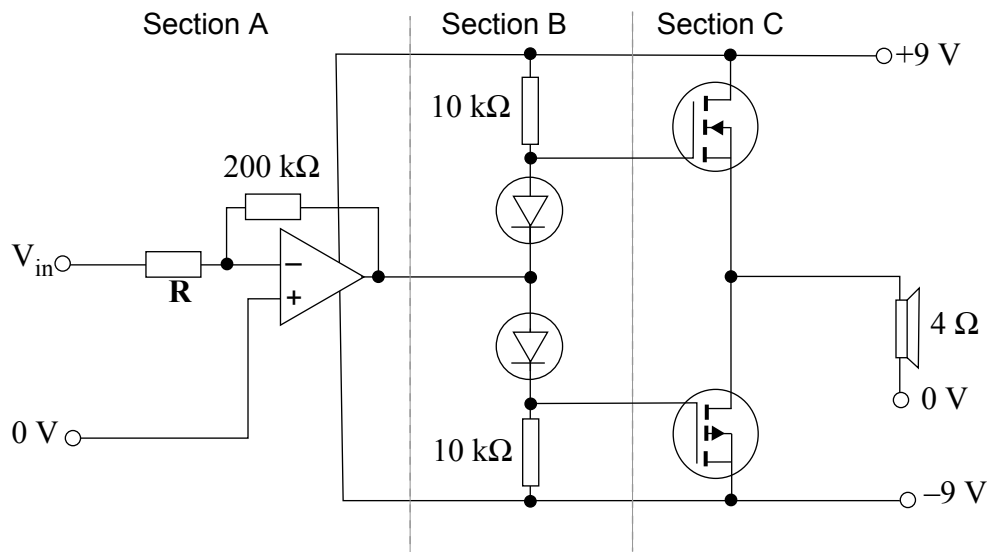

- 4 (a) (i) Put a tick in the box that best describes the function of Section B.

[1 mark]

Provides voltage gain.

Biases the MOSFETs.

Provides power gain.

Sets the voltage gain of the amplifier.

- 4 (a) (ii) Put a tick in the box that best describes the function of Section C.

[1 mark]

Provides voltage gain.

Biases the MOSFETs.

Provides power gain.

Sets the voltage gain of the amplifier.



4 (b) (i) Calculate a value for **R** which will give Section A a voltage gain of 5.

[2 marks]

.....

.....

.....

4 (b) (ii) Explain why the voltage gain of the **overall** circuit is less than 5.

[2 marks]

.....

.....

.....

.....


Question 4 continues on the next page

Turn over ▶



4 (c) A sine wave of amplitude 1.8 V is fed into the amplifier and the voltage across the loudspeaker is shown in **Figure 8**.

Figure 8

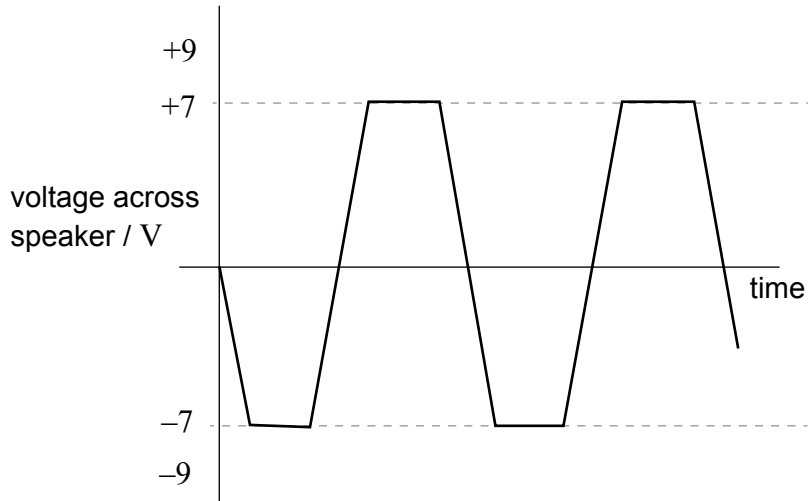

4 (c) (i) Put a tick in the box that best explains why the voltage across the speaker does **not** reach ± 9 V.

[1 mark]

- The input signal voltage to the amplifier is too small.
- The op-amp output does not saturate at the supply voltages.
- The loudspeaker has a resistance that is too large.
- The op-amp does not have sufficient voltage gain.

4 (c) (ii) Estimate the maximum undistorted output power of the amplifier.

[3 marks]

.....

.....

.....



4 (c) (iii) Put a tick in the box that best describes how to increase the undistorted output power of the amplifier.

[1 mark]

Decrease the input signal voltage.

Decrease the power supply voltage.

Increase the power supply voltage.

Increase the loudspeaker resistance.

11

Turn over for the next question

Turn over ▶




5 An industrial process requires chemicals to be exposed to an intense light which then reduces over time to zero. A control system for the light uses a 4-bit down counter and a 4-input summing amplifier.

5 (a) Complete the circuit diagram for a 4-bit down counter in **Figure 9**. Label the clock input.


[4 marks]

Figure 9

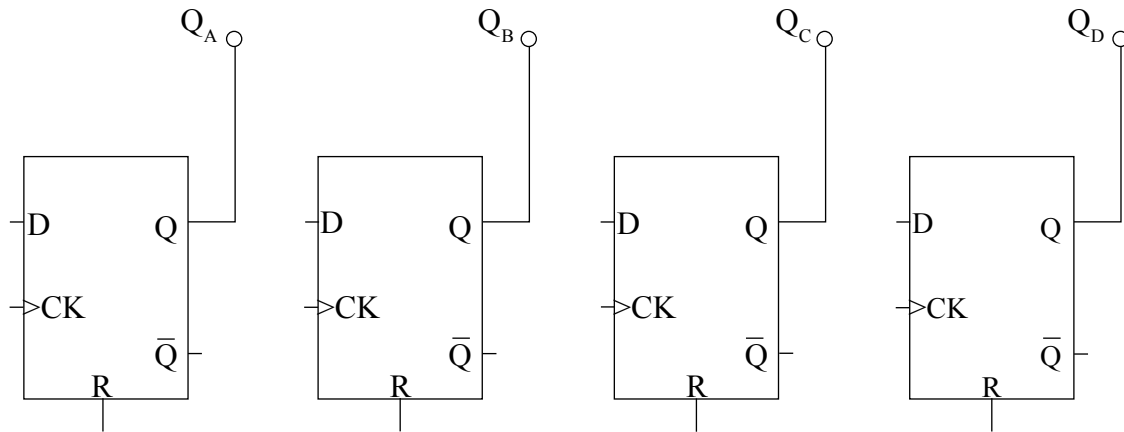

5 (b) **Figure 10** shows the circuit diagram for the summing amplifier.

Figure 10

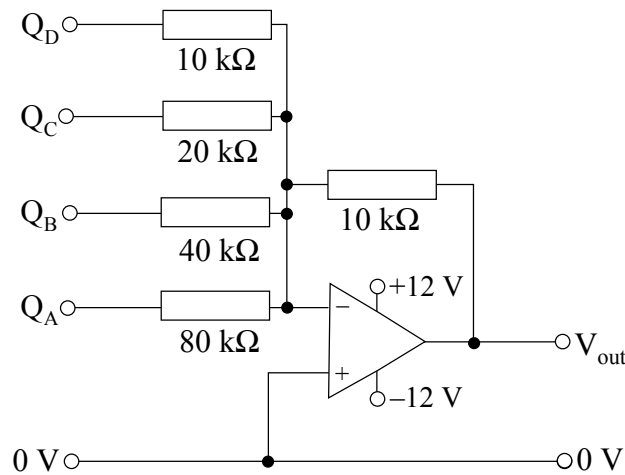

Assume that a logic 1 output from the counter is +5 V and a logic 0 is 0 V. Calculate the output from the summing amplifier when the counter has reached a count of 1011_2 .

[3 marks]

.....

.....


.....



- 5 (c)** The counter is reset to 0000.
Sketch a graph on **Figure 11** to show the output of the summing amplifier for an input of 32 clock pulses to the counter.

[4 marks]

Figure 11

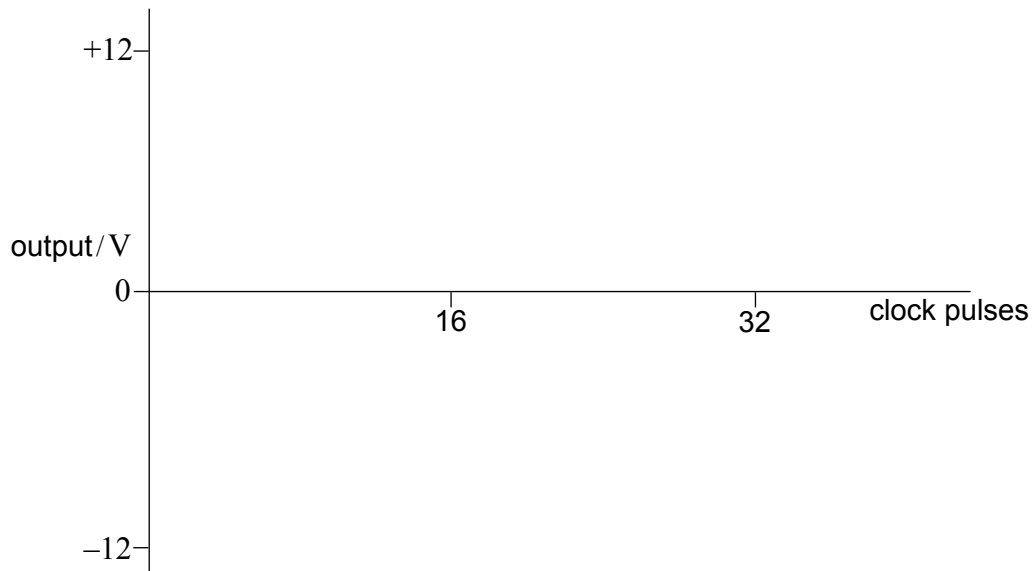

11


Turn over for the next question

Turn over ▶



6 Figure 12 shows the symbol for a D-type flip-flop.

Figure 12

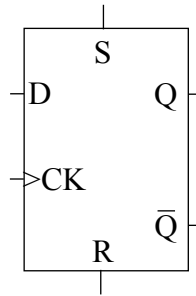

6 (a) Describe the operation of a D-type flip-flop.

[3 marks]

.....

.....


.....

.....

6 (b) Complete the circuit diagram for a 4-bit shift register in Figure 13. Label the serial data input and the clock input.

[4 marks]

Figure 13

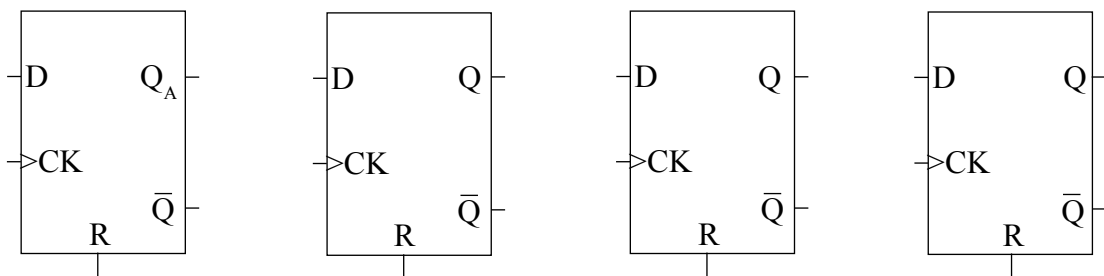

6 (c) Add logic gate(s) to Figure 13 so that when all of the Q outputs of the shift register are logic 0, then the serial data input is a logic 1.


[3 marks]



- 6 (d) With the logic gate(s) added, the shift register is reset.
Show on the axes of **Figure 14** how Q_A changes for 8 clock pulses.

[2 marks]

Figure 14

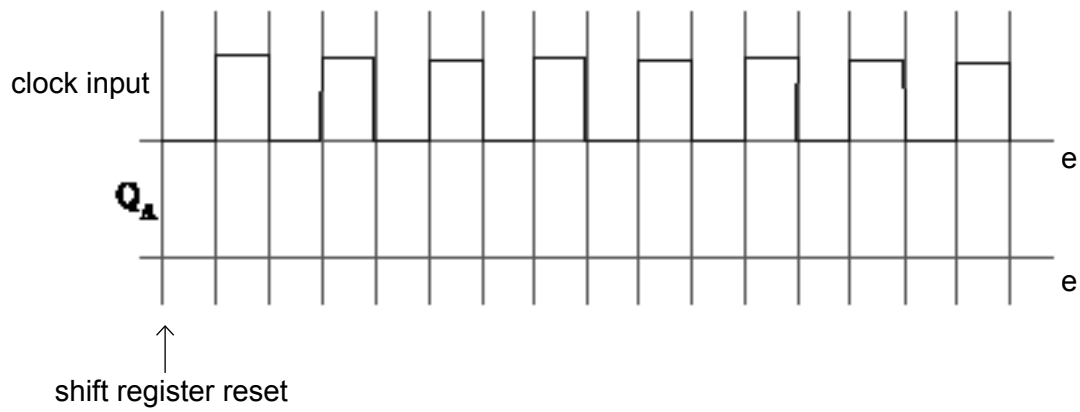

12

END OF QUESTIONS



There are no questions printed on this page

**DO NOT WRITE ON THIS PAGE
ANSWER IN THE SPACES PROVIDED**

