
A-LEVEL ELECTRONICS

Programmable Control Systems ELEC4
Mark scheme

2430
June 2014

Version: 1.0 Final

Mark schemes are prepared by the Lead Assessment Writer and considered, together with the relevant questions, by a panel of subject teachers. This mark scheme includes any amendments made at the standardisation events which all associates participate in and is the scheme which was used by them in this examination. The standardisation process ensures that the mark scheme covers the students' responses to questions and that every associate understands and applies it in the same correct way. As preparation for standardisation each associate analyses a number of students' scripts: alternative answers not already covered by the mark scheme are discussed and legislated for. If, after the standardisation process, associates encounter unusual answers which have not been raised they are required to refer these to the Lead Assessment Writer.

It must be stressed that a mark scheme is a working document, in many cases further developed and expanded on the basis of students' reactions to a particular paper. Assumptions about future mark schemes on the basis of one year's document should be avoided; whilst the guiding principles of assessment remain constant, details will change, depending on the content of a particular examination paper.

Further copies of this Mark Scheme are available from aqa.org.uk

COMPONENT NUMBER: ELEC4

COMPONENT NAME: Programmable Control Systems

Question	Part	Sub part	Marking Guidance	Mark	Comment
1	(a)		Example noisy input signal giving multiple crossing of threshold each period ✓ leading to more pulses being recorded by the counter ✓	2	
1	(b)		Schmitt trigger has two switching levels ✓ Example so signal must go above upper when going positive/below lower going negative OR relevant valid representation on diagram ✓ so preventing the multiple pulses occurring as the signal crosses the 0V point ✓	3	
1	(c)	(i)	input to op-amp inverting input ✓ feedback resistor to non-inverting input ✓ remainder of the circuit all functionally correct AND input and output labelled ✓	3	
1	(c)	(ii)	an appropriate calculation ✓ feedback resistor larger than other resistor ✓ all resistor values 1k – 1MΩ ✓ resistors in the ratio 2:1 ✓	4	
2	(a)	(i)	16μs ✓	1	
2	(a)	(ii)	MOVW 0x0F ✓ MOVWR PRE ✓	2	

2	(b)	(i)	4ms/16µs = 250 ✓ 0xFA ✓	2		
2	(b)	(ii)	MOVRW SR ✓ ANDW 0x02 ✓	2		
2	(c)	(i)	250 ±1 loops to give 1s ✓	1		
2	(c)	(ii)	MOVW 0xFA MOVWR 0xB0 ✓	1		
2	(c)	(iii)	loop1: CALL TIME1 // initiate/call the 4ms subroutine ✓ loop2: MOVRW SR ANDW 0x02 JPZ loop2 // check whether the 4ms delay has finished. DEC 0xB0 MOVRW 0xB0 JPZ end // decrement 0xB0 and check for zero ✓ JMP loop1 // return to loop1 and repeat ✓ end:	loop1: CALL TIME1 // initiate/call the 4ms subroutine ✓ DEC 0xB0 MOVRW 0xB0 JPZ end // decrement 0xB0 and check for zero ✓ JMP loop1 // return to loop1 and repeat ✓ end:	3	<p>First answer includes checking for the 4ms subroutine to end.</p> <p>Both are only examples – examiners will have to check answers carefully and award marks for the three basic steps – as shown by the comments.</p>
3	(a)		closed ✓ there is (negative) feedback ✓	2		

3	(b)		calculation e.g. $50/256 = (0.195^{\circ}\text{C}) \checkmark$ $\approx 0.2^{\circ}\text{C} \checkmark$	2	
3	(c)		Examples a motor whose armature turns through discrete angles when powered \checkmark two coils, not centre tapped \checkmark coils need the current to be reversed \checkmark	3	
3	(d)		one n-channel and one p-channel in each arm \checkmark n-channel on the bottom \checkmark coil between two arms \checkmark input to gates of MOSFETs \checkmark correctly labelled power supply. \checkmark	5	
4	(a)	(i)	calculation $20/40 = \checkmark$ $500\text{mA} \checkmark$	2	
4	(a)	(ii)	sensible calculation \checkmark sensible answer of around $2.5\text{W} \checkmark$	2	
4	(b)		high power density, small physical size, etc \checkmark cost, can explode if damaged, do not like cold temperatures etc \checkmark	2	
4	(c)		recognise that 12.6V is 63% of supply voltage \checkmark calculation $40 \times 4.7 = 188\text{s} \checkmark$	2	
4	(d)	(i)	recognise that 4.7V is 37% of $12.6\text{V} \checkmark$ calculation $1.5/4.7 = 0.319\Omega \checkmark$	1	

4	(d)	(ii)	Example. mean voltage (8.7V), justified voltage used ✓ sensible calculation ✓ 237W ✓ (More accurate answer is 214W)	3	Example if mean power calculated rather than voltage, then 282W.
5	(a)		voltage divider calculation $2.5 = (12.6 \times 10)/(10 + R)$ ✓ 40.4kΩ ✓	2	
5	(b)		Example When capacitor voltage less than 4.7V, voltage divider of 13k and 15k give a voltage of less than 2.5V at D ₁ ✓ microcontroller can detect this as logic 0 ✓	2	
5	(c)		appropriate flow chart with marks for the following key points correct symbols ✓ read D ₀ until D ₀ = 1 (loop) ✓ turn motor on ✓ read D ₁ ✓ read D ₁ until D ₁ = 0 (loop) ✓ return loop with motor turned off ✓	6	
6	(a)		Example ADC-convert analogue signal from the PC to digital signal for transmission ✓ DAC convert received digital signal to analogue signal for the hi-fi ✓	2	
6	(b)		lower resolution ✓ fewer conversion levels ✓ less dynamic range ✓ etc	2 max	

6	(c)		calculation $1 / 44000 = \checkmark$ $22.7\mu\text{s} \checkmark$	2	
6	(d)	(i)	invert the output from op-amp A \checkmark provide unity gain \checkmark	2	
6	(d)	(ii)	0x80 gives D_7 5V \checkmark Example of calculation of summing amplifier leading to \checkmark 10k Ω \checkmark	2 max	
6	(e)		Input value steadily increases, so output voltage steadily increases until count reaches 0xFF \checkmark whereupon it starts again from 0 \checkmark	2	
7	(a)		calculation e.g. 3 LEDs each with 2 bits giving 6 bits \checkmark $2^6 = 64 \checkmark$ Accept 63 – when all of the LEDs are off – not a colour	2	
7	(b)	(i)	only on for 33% of time \checkmark so LED perceived as only being 1/3 as bright or similar \checkmark	2	
7	(b)	(ii)	human eye persistence of vision >50ms \checkmark flash rate \approx 3ms \checkmark	2	
7	(c)	(i)	input bits are 00 01 10 11 \checkmark 0x1B \checkmark	2	
7	(c)	(ii)	red on continuously, green on for 2/3 duty cycle and blue on for 1/3 duty cycle red plus one other correct \checkmark third colour correct \checkmark	2	