



ADVANCED GCE
ELECTRONICS
Unit F611: Simple Systems

F611

* C U P / T E S 5 3 5 8 *

Candidates answer on the question paper

OCR Supplied Materials:

None

Other Materials Required:

- Scientific calculator

Monday 18 May 2009
Morning

Duration: 1 hour 30 minutes



Candidate Forename						Candidate Surname				
--------------------	--	--	--	--	--	-------------------	--	--	--	--

Centre Number						Candidate Number			
---------------	--	--	--	--	--	------------------	--	--	--

INSTRUCTIONS TO CANDIDATES

- Write your name clearly in capital letters, your Centre Number and Candidate Number in the boxes above.
- Use black ink. Pencil may be used for graphs and diagrams only.
- Read each question carefully and make sure that you know what you have to do before starting your answer.
- Answer **all** the questions.
- Do **not** write in the bar codes.
- Write your answer to each question in the space provided, however additional paper may be used if necessary.

INFORMATION FOR CANDIDATES

- The number of marks is given in brackets [] at the end of each question or part question.
- The total number of marks for this paper is **90**.
- You will be awarded marks for the quality of written communication where this is indicated in the question.
- Unless otherwise indicated, you can assume that:
 - op-amps are run off supply rails at +15V and -15V
 - logic circuits are run off supply rails at +5V and 0V
- You are advised to show all the steps in any calculations.
- This document consists of **16** pages. Any blank pages are indicated.



A calculator may
be used for this
paper

Data Sheet

Unless otherwise indicated, you can assume that:

- op-amps are run off supply rails at +15V and -15V
- logic circuits are run off supply rails at +5V and 0V.

resistance	$R = \frac{V}{I}$
power	$P = VI$
series resistors	$R = R_1 + R_2$
time constant	$\tau = RC$
monostable pulse time	$T = 0.7RC$
relaxation oscillator period	$T = 0.5RC$
frequency	$f = \frac{1}{T}$
Boolean Algebra	$A \cdot \bar{A} = 0$ $A + \bar{A} = 1$ $A(B + C) = AB + AC$ $\overline{AB} = \bar{A} + \bar{B}$ $\overline{A + B} = \bar{A} \cdot \bar{B}$ $A + A \cdot B = A$ $A \cdot B = \bar{A} \cdot C = AB + \bar{A} \cdot C + BC$

Answer **all** the questions.

- 1 Fig. 1.1 shows a logic system.

 


Fig. 1.1

- (a) Complete this truth table for the logic system.

B	A	C	D	Q
0	0			
0	1			
1	0			
1	1			

[3]

- (b) Use the truth table to write down a Boolean expression for Q in terms of B and A.

$$Q = \dots \quad [1]$$

- (c) Show in the space below how a logic system made from only NAND gates can replace the circuit of Fig. 1.1.

[2]

- (d) Use Boolean algebra or a truth table to justify your NAND gate circuit.

[2]

[Total: 8]

- 2 The circuit of Fig. 2.1 is part of a sensor circuit.

 


Fig. 2.1

- (a) The circuit contains a thermistor.

(i) Put a circle around the thermistor.

[1]

(ii) Describe the electrical properties of a thermistor.

[2]

- (b) A potentiometer is missing from the circuit of Fig. 2.1.

It allows the voltage at X to be varied from 0V to +15V.

(i) On Fig. 2.1, show how the potentiometer should be connected.

[2]

(ii) Explain what happens to the voltage at Z when the voltage at X is slowly increased from 0V to +15V.

[3]

(iii) On Fig. 2.1, show how a voltmeter should be connected to measure the voltage at Z. [1]

- (c) The network of two resistors and a diode between the output of the op-amp and the NOT gate converts the signal at Z into logic 1 or logic 0.

- (i) Explain why the diode can be ignored when Z is at +13V.

.....
.....
.....

[2]

- (ii) Calculate the voltage at A when Z is at +13V.

voltage = V [3]

- (iii) State the voltage at A when Z is at -13V. Give a reason for your answer.

.....
.....
.....
.....

[3]

- (iv) Use your answers to (ii) and (iii) to comment on the idea that this network provides logic 1 or logic 0 at A.

.....
.....
.....
.....

[2]

[Total: 19]

- 3 The circuit of Fig. 3.1 uses a relaxation oscillator to make a sound.

 


Fig. 3.1

- (a) (i) Suggest values of resistor R and capacitor C which will make the period T of the oscillator $200\mu\text{s}$.

$$R = \dots$$

$$C = \dots \quad [3]$$

- (ii) Calculate the frequency of the oscillator.

$$\text{frequency} = \dots \text{ kHz} \quad [2]$$

- (b) A double-beam oscilloscope is connected to the circuit to monitor the signals at the input and output of the Schmitt trigger NOT gate. The screen of the double-beam oscilloscope is shown in Fig. 3.2.

 


Fig. 3.2

- (i) The timebase is set to $50\text{ }\mu\text{s}$ per division.

The vertical amplifier is set to 2V per division with 0V at the centre of the screen.

Draw on Fig. 3.2 to show the signal at the **output** of the NOT gate. [3]

- (ii) The screen of Fig. 3.2 also shows the signal at the input of the NOT gate.

The trip points of the Schmitt trigger NOT gate are $+2.0\text{V}$ and $+3.0\text{V}$.

Draw on Fig. 3.2 to show the signal at the **input** of the NOT gate. [3]

- (iii) Show on Fig. 3.1 how the oscilloscope should be connected to monitor just the signal at the **input**. [2]

- (c) The circuit of Fig. 3.1 contains a MOSFET.

- (i) Why is the MOSFET necessary?

.....
.....

[1]

- (ii) On Fig. 3.1, label the gate, drain and source of the MOSFET. [1]

.....
.....
.....

[2]

- (d) Calculate the **average** power of the loudspeaker in Fig. 3.1.

$$\text{average power} = \dots \text{W} \quad [3]$$

[Total: 20]

- 4 The circuit of Fig. 4.1 contains a single logic gate.

 


Fig. 4.1

- (a) Fig. 4.1 is an incomplete block diagram for the circuit of Fig. 4.1.

 


Fig. 4.2

- (i) Complete the block diagram of Fig. 4.2.

[3]

- (ii) What do the arrows on a block diagram show?

[1]

- (b) (i) Complete the truth table for the circuit of Fig. 4.1.

switch X	switch Y	B	A	Q	state of LED
open	open	0	0	0	off

[4]

- (ii) Describe the behaviour of the circuit.

.....
.....
.....
.....

[2]

- (c) The LED is connected to the logic gate by a resistor.

- (i) Explain why the resistor is necessary.

.....
.....
.....

[2]

- (ii) The voltage drop across the LED is 1.7V when its power is 5.0mW.

Show that the current in the LED is about 3mA.

[1]

- (iii) Calculate a suitable value for the resistor R .

$$R = \dots \Omega \quad [2]$$

- (d) Fig. 4.1 is a circuit diagram. Suggest why the supply rail connections to the logic gate have not been shown.

.....
.....

[1]

[Total: 16]

10

- 5 Here is the truth table for a logic system. It has inputs C, B and A, and outputs P and Q.

C	B	A	P	Q
0	0	0	1	1
0	0	1	1	0
0	1	0	1	1
0	1	1	1	0
1	0	0	0	0
1	0	1	0	0
1	1	0	1	1
1	1	1	1	0

- (a) (i) Write down a Boolean expression for Q in terms of C, B and A.

[3]

- (ii) Use Boolean algebra to show that $Q = \overline{C}.\overline{A} + B.\overline{A}$.

[3]

- (iii) Show in the space below how the circuit for Q can be assembled from NOT, AND and OR gates.

[3]

(b) A Boolean expression for P is $P = \overline{C} + B$.

(i) Show in the space below how the circuit for P can be assembled from **two** NAND gates.

[2]

(ii) Use Boolean algebra to justify your arrangement of NAND gates.

[2]

(iii) Explain the advantages of assembling a logic system using only NAND gates.


.....
.....
.....

[2]

[Total: 15]

- 6 The circuit of Fig. 6.1 contains an RC network.

 The table shows the behaviour of the logic gate.



signal at A	signal at Q
< 2.5V	+5V
> 2.5V	0 V

Fig. 6.1

- (a) Calculate the time constant of the RC network.

$$\text{time constant} = \dots \text{ s} [2]$$

- (b) Explain why the lamp comes on as soon as the switch is pressed.

.....

 [3]

13

- (c) Explain, in detail, what happens to the lamp when the switch is released.

.....
.....
.....
.....
.....
.....

[4]

Quality of Written Communication [3]

[Total: 12]

END OF QUESTION PAPER

PLEASE DO NOT WRITE ON THIS PAGE

PLEASE DO NOT WRITE ON THIS PAGE

PLEASE DO NOT WRITE ON THIS PAGE



RECOGNISING ACHIEVEMENT

Copyright Information

OCR is committed to seeking permission to reproduce all third-party content that it uses in its assessment materials. OCR has attempted to identify and contact all copyright holders whose work is used in this paper. To avoid the issue of disclosure of answer-related information to candidates, all copyright acknowledgements are reproduced in the OCR Copyright Acknowledgements Booklet. This is produced for each series of examinations, is given to all schools that receive assessment material and is freely available to download from our public website (www.ocr.org.uk) after the live examination series.

If OCR has unwittingly failed to correctly acknowledge or clear any third-party content in this assessment material, OCR will be happy to correct its mistake at the earliest possible opportunity.

For queries or further information please contact the Copyright Team, First Floor, 9 Hills Road, Cambridge CB2 1PB.

OCR is part of the Cambridge Assessment Group; Cambridge Assessment is the brand name of University of Cambridge Local Examinations Syndicate (UCLES), which is itself a department of the University of Cambridge.