

Tuesday 29 May 2012 – Afternoon**A2 GCE ELECTRONICS****F614 Electronics Control Systems**

Candidates answer on the Question Paper.

OCR supplied materials:

None

Other materials required:

- Scientific calculator

Duration: 1 hour 40 minutes

| | | | | | | | | | |
|--------------------|--|--|--|--|-------------------|--|--|--|--|
| Candidate forename | | | | | Candidate surname | | | | |
|--------------------|--|--|--|--|-------------------|--|--|--|--|

| | | | | | | | | | |
|---------------|--|--|--|--|--|------------------|--|--|--|
| Centre number | | | | | | Candidate number | | | |
|---------------|--|--|--|--|--|------------------|--|--|--|

INSTRUCTIONS TO CANDIDATES

- Write your name, centre number and candidate number in the boxes above. Please write clearly and in capital letters.
- Use black ink. HB pencil may be used for graphs and diagrams only.
- Answer **all** the questions.
- Read each question carefully. Make sure you know what you have to do before starting your answer.
- Write your answer to each question in the space provided. Additional paper may be used if necessary but you must clearly show your candidate number, centre number and question number(s).
- Do **not** write in the bar codes.

INFORMATION FOR CANDIDATES

- The number of marks is given in brackets [] at the end of each question or part question.
- The total number of marks for this paper is **110**.
- You will be awarded marks for your Quality of Written Communication.
- You are advised to show all the steps in any calculations.
- This document consists of **20** pages. Any blank pages are indicated.

**A scientific
calculator may be
used for this paper**

Microcontroller instructions

The microcontroller contains eight general purpose registers S_n, where n = 0, 1, 2 ... 7. The microcontroller has an eight bit input port, I, an eight bit output port, Q, and an analogue input, ADC.

In the table of assembler instructions given below, S_d is the destination register and S_s the source register.

| assembler | function |
|------------------------------------|---|
| MOVI S _d ,n | Copy the byte n into register S _d |
| MOV S _d ,S _s | Copy the byte from S _s to S _d |
| ADD S _d ,S _s | Add the byte in S _s to the byte in S _d and store the result in S _d |
| SUB S _d ,S _s | Subtract the byte in S _s from the byte in S _d and store the result in S _d |
| AND S _d ,S _s | Logical AND the byte in S _s with the byte in S _d and store the result in S _d |
| EOR S _d ,S _s | Logical EOR the byte in S _s with the byte in S _d and store the result in S _d |
| INC S _d | Add 1 to S _d |
| DEC S _d | Subtract 1 from S _d |
| IN S _d ,I | Copy the byte at the input port into S _d |
| OUT Q,S _s | Copy the byte in S _s to the output port |
| JP e | Jump to label e |
| JZ e | Jump to label e if the result of the last ADD, SUB, AND, EOR, INC, DEC, SHL or SHR was zero |
| JNZ e | Jump to label e if the result of the last ADD, SUB, AND, EOR, INC, DEC SHL or SHR was not zero |
| RCALL s | Push the program counter onto the stack to store the return address and then jump to label s |
| RET | Pop the program counter from the stack to return to the place the subroutine was called from |
| SHL S _d | Shift the byte in S _d one bit left putting a 0 into the lsb |
| SHR S _d | Shift the byte in S _d one bit right putting a 0 into the msb |

There are three subroutines provided:

- readable – copies the byte in the lookup table pointed at by S7 into S0. The lookup table is labelled table: When S7=0 the first byte from the table is returned in S0
- wait1ms – waits 1ms before returning
- readadc – returns a byte in S0 proportional to the voltage at ADC

Datasheet

| | |
|------------------------------|---|
| resistance | $R = \frac{V}{I}$ |
| power | $P = VI$ |
| series resistors | $R = R_1 + R_2$ |
| time constant | $\tau = RC$ |
| monostable pulse time | $T = 0.7RC$ |
| relaxation oscillator period | $T = 0.5RC$ |
| frequency | $f = \frac{1}{T}$ |
| voltage gain | $G = \frac{V_{out}}{V_{in}}$ |
| open-loop op-amp | $V_{out} = A(V_+ - V_-)$ |
| non-inverting amplifier gain | $G = 1 + \frac{R_f}{R_d}$ |
| inverting amplifier gain | $G = -\frac{R_f}{R_{in}}$ |
| summing amplifier | $-\frac{V_{out}}{R_f} = \frac{V_1}{R_1} + \frac{V_2}{R_2} \dots$ |
| break frequency | $f_0 = \frac{1}{2\pi RC}$ |
| Boolean Algebra | $A \cdot \bar{A} = 0$ $A + \bar{A} = 1$ $A \cdot (B + C) = A \cdot B + A \cdot C$ $\overline{A \cdot B} = \bar{A} + \bar{B}$ $\overline{A + B} = \bar{A} \cdot \bar{B}$ $A + A \cdot B = A$ $A \cdot B + \bar{A} \cdot C = A \cdot B + \bar{A} \cdot C + B \cdot C$ |
| amplifier gain | $G = -g_m R_d$ |
| ramp generator | $\Delta V_{out} = -V_{in} \frac{\Delta t}{RC}$ |

Answer **all** questions.

- 1 Fig. 1.1 shows an incomplete MOSFET voltage follower circuit.

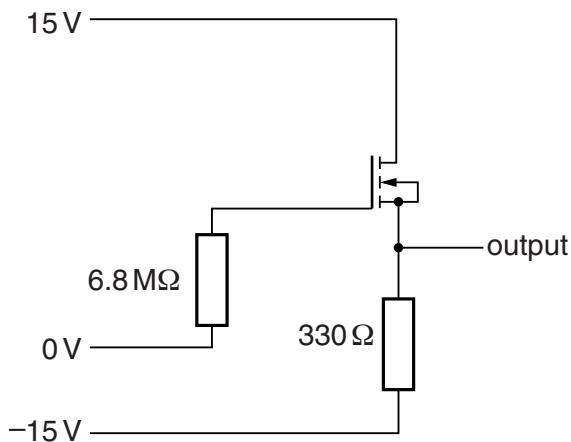




Fig. 1.1

- (a) The voltage at the output is -2V . Calculate the drain-source current through the MOSFET.

$$\text{drain-source current} = \dots \text{mA} [4]$$

- (b) Draw a capacitor on Fig. 1.1 to show how an ac signal can be input to the voltage follower.
Write 'input' at the input connection. [2]
- (c) Explain why voltage follower circuits are used.
-
.....
..... [2]

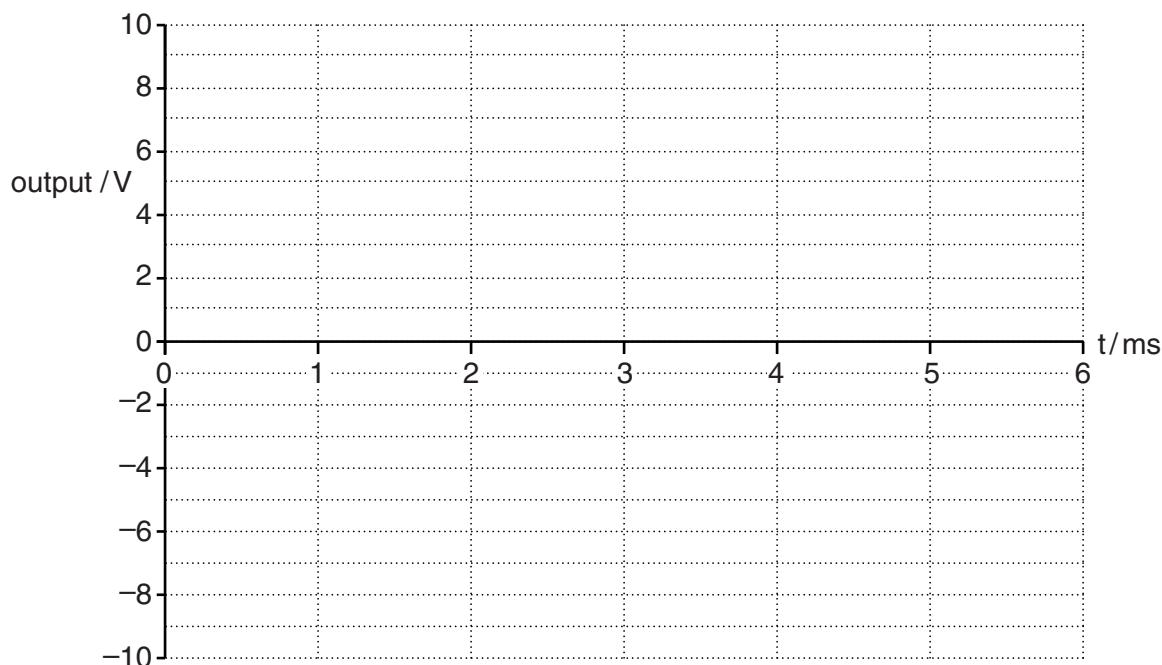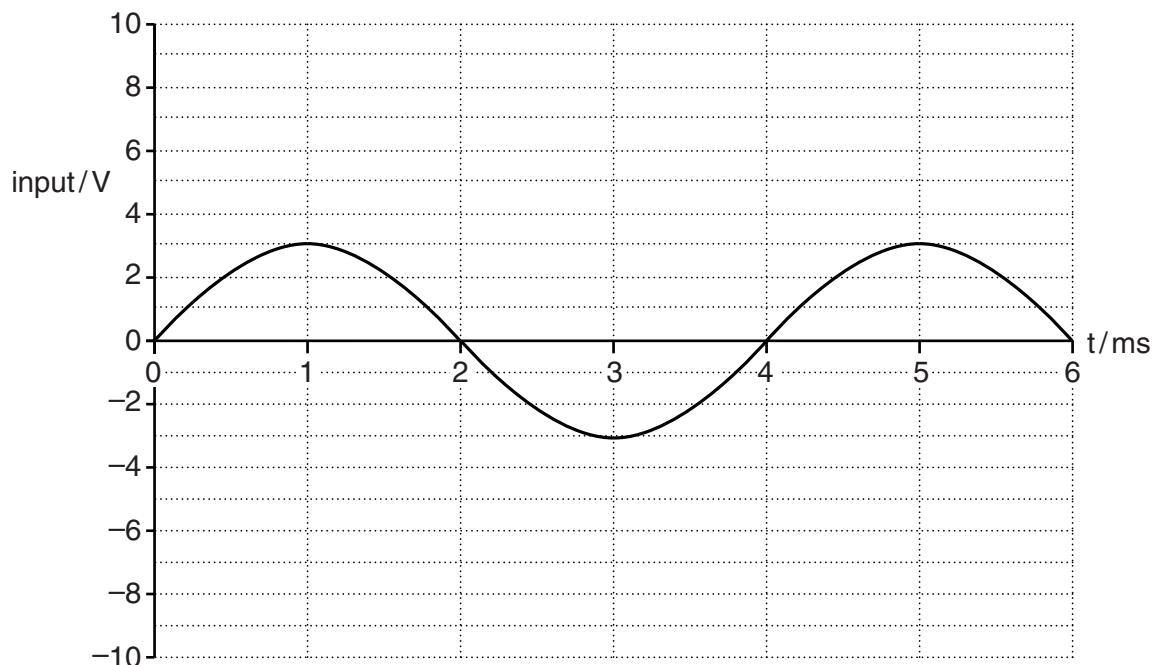- (d) The graph below shows how the voltage at the input varies with time. Draw on the axes to show how the output voltage varies with time.



[3]

[Total 11]

- 2 Part of a circuit for controlling the temperature of a soldering iron is shown in Fig. 2.1.

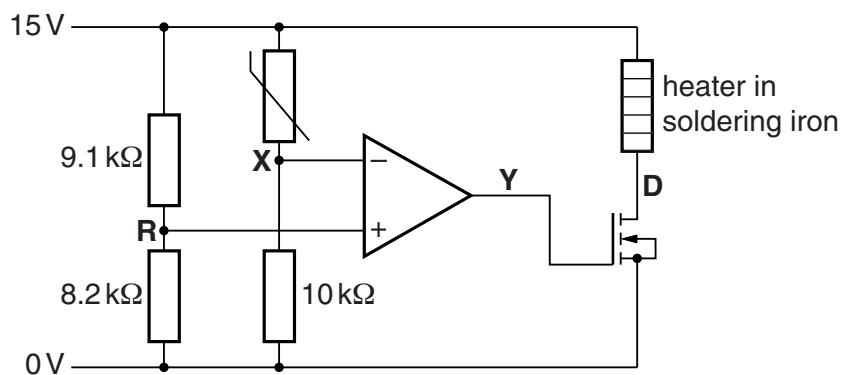


Fig. 2.1

- (a) The circuit uses a thermistor to sense the temperature of the soldering iron.
Draw a ring around the thermistor on Fig. 2.1.

[1]

- (b) Show that the voltage at **R** is about 7V.

[3]



- (c) When the soldering iron is cold the voltage at **X** is 3V.
Explain why the heater is on. Refer to the voltages in the circuit in your answer.

[4]

- (d) (i) Explain why the temperature of the soldering iron reaches a constant average value but never stops changing.

.....
.....
.....
.....
..... [4]

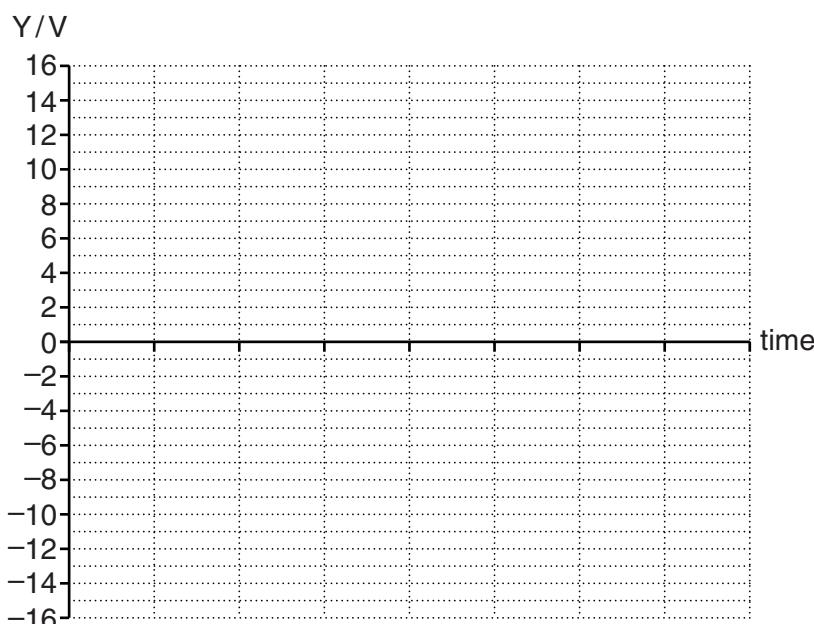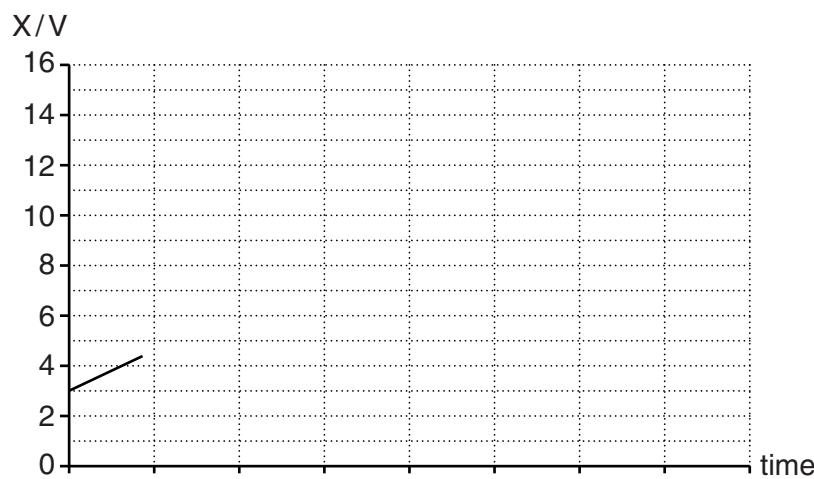- (ii) Complete the voltage-time graphs for **X** and **Y** to illustrate your answer to (d). Assume the graph starts when the soldering iron is switched on from cold.



[4]

[Total 16]

- 3** Fig. 3.1 shows a memory module.

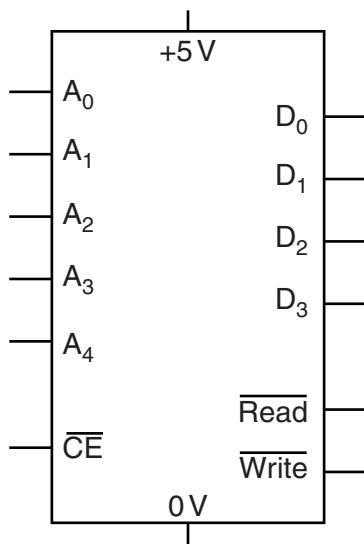


Fig. 3.1

- (a) Calculate the number of memory locations in the memory module.

number of memory locations = [2]

- (b) State the largest decimal number that each memory location can hold.

largest decimal number = [1]

- (c) State the voltages on each address line and control line when memory address 03 is being read.

$$A_4 = \dots V \quad A_3 = \dots V \quad A_2 = \dots V \quad A_1 = \dots V \quad A_0 = \dots V$$

CE =V Read =V Write =V [5]

- (d) Describe the sequence of signals required to store the decimal number 2 at memory location 04.

[5]

- (e) Fig. 3.2 shows a larger memory module.

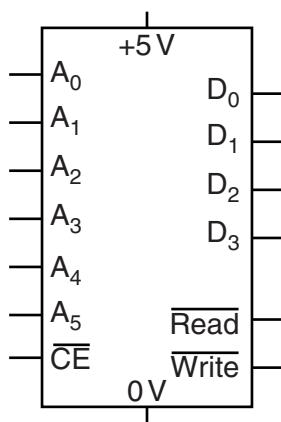


Fig. 3.2

Complete the diagram below to show how the larger memory module can be made from memory modules which are the same as Fig. 3.1 and logic gates.

| | |
|----------------|-------|
| 5 V | _____ |
| A ₀ | _____ |
| A ₁ | _____ |
| A ₂ | _____ |
| A ₃ | _____ |
| A ₄ | _____ |
| A ₅ | _____ |

| | |
|----------------|-------|
| D ₀ | _____ |
| D ₁ | _____ |
| D ₂ | _____ |
| D ₃ | _____ |
| CE | _____ |
| Read | _____ |
| Write | _____ |
| 0 V | _____ |

[6]

[Total 19]

Turn over

PLEASE DO NOT WRITE ON THIS PAGE

4 This question is about microcontrollers.

(a) Describe what the **address bus** is in a microcontroller and what it is used for.

.....
.....
.....
.....

[3]

(b) State the location and describe the function of the **program counter** in a microcontroller.

.....
.....
.....
.....
.....

[4]

(c) Show how a 4-bit output port of a microcontroller can be made from D flip-flops. Label the inputs from the data bus and the outputs.

[4]

(d) State the function of the **reset** pin on a microcontroller.

.....
.....
.....

[1]

[Total 12]

- 5 The circuit in Fig. 5.1 is used as part of an in-car phone charger.

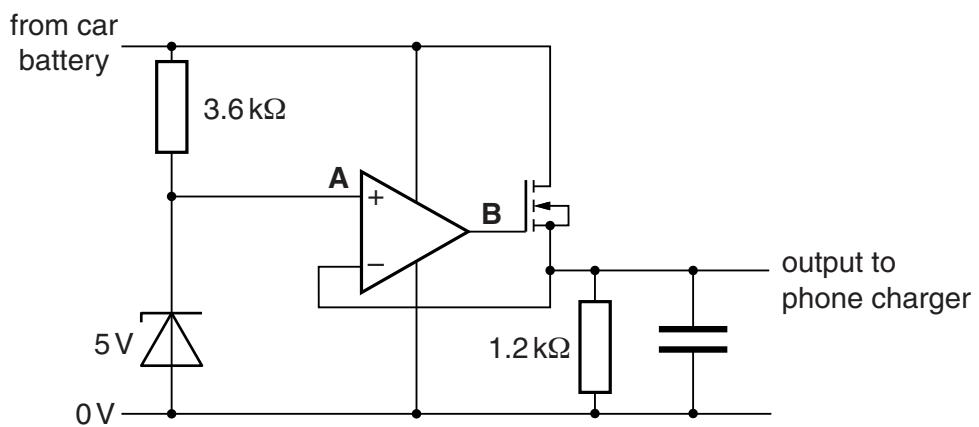


Fig. 5.1

- (a) Explain why the output voltage of the circuit is 5V when the voltage from the car battery is 14V. Refer to the voltages at **A** and **B** in your answer. The threshold voltage of the MOSFET is 3V.

.....
.....
.....
.....

[5]

- (b) Show that the current through the MOSFET is about 4mA when there is nothing connected to the output of the circuit and the voltage from the car battery is 14V.

[2]

- (c) Calculate the power dissipated in the MOSFET when the voltage from the car battery is 14V and there is nothing connected to the output.

power in MOSFET = W [3]

- (d) Explain why the MOSFET is needed in the circuit.

.....
.....
.....

[2]


- (e) Suggest why the circuit only works well when the voltage from the car battery is at least 10V.

.....
.....
.....

[2]

[Total 14]

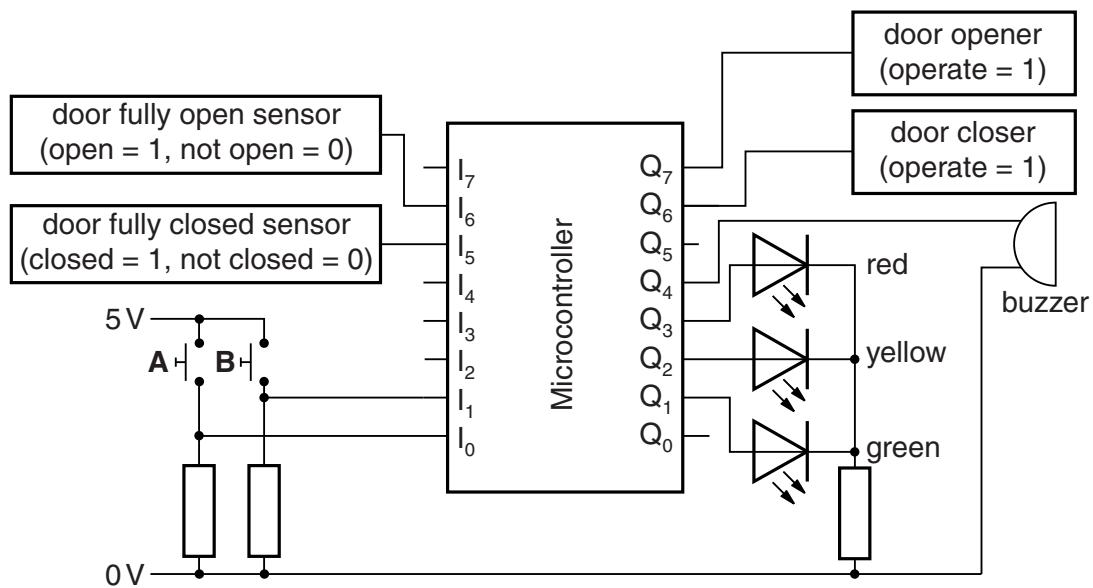- 6 The microcontroller circuit and program in Fig. 6.1 operate the sliding doors on a train. The main program calls a number of subroutines to operate the train doors, LEDs and buzzer.



```

main:  RCALL opendoor
       RCALL switcha
       RCALL warn
       RCALL closedoor
       RCALL switchb
       JP      main

```

Fig. 6.1

- (a) The subroutine `opendoor` opens the train doors. Explain what each part of the subroutine does by filling in the explanation on each line. Look at Fig. 6.1 and refer to the electronic devices connected to the inputs and outputs in your explanations. The first one has been done for you.

| Label | Instruction | Explanation |
|------------------------|--------------------------|---------------------------------|
| <code>opendoor:</code> | MOVI S4, 88 OUT Q, S4 | turn on door opener and red LED |
| | MOVI S3, 40 | |
| <code>loop:</code> | IN S2, I | |
| | AND S2, S3 | |
| | JZ loop | |
| | MOVI S4, 08 OUT Q, S4 | |
| | RET | |

[6]

- (b) The subroutine `warn` is shown below.

```

warn: MOVI S5, 02
loop: MOVI S6, 10
      OUT Q, S5
      RCALL wait10s
      SHL S5
      SUB S6, S5
      JNZ loop
      RET
  
```

The subroutine `wait10s` produces a delay of 10 seconds.

Explain the effect of the subroutine `warn` on the circuit.

.....

 [4]

- (c) The subroutine `switcha` waits until switch A has been pressed and then returns to the main program. Write the code for the subroutine `switcha`.

`switcha:`

.....

 [5]

- (d) Write the subroutine `wait10s` to produce a delay of 10 seconds. You should use the instruction `RCALL wait1ms` which produces a delay of 1 ms in your code.

.....

 [6]

[Total 21]

- 7 An engineer designs an electronic volume control for the music system in a supermarket. The electronic volume control circuit and the graph of the MOSFET characteristics are shown in Fig. 7.1.

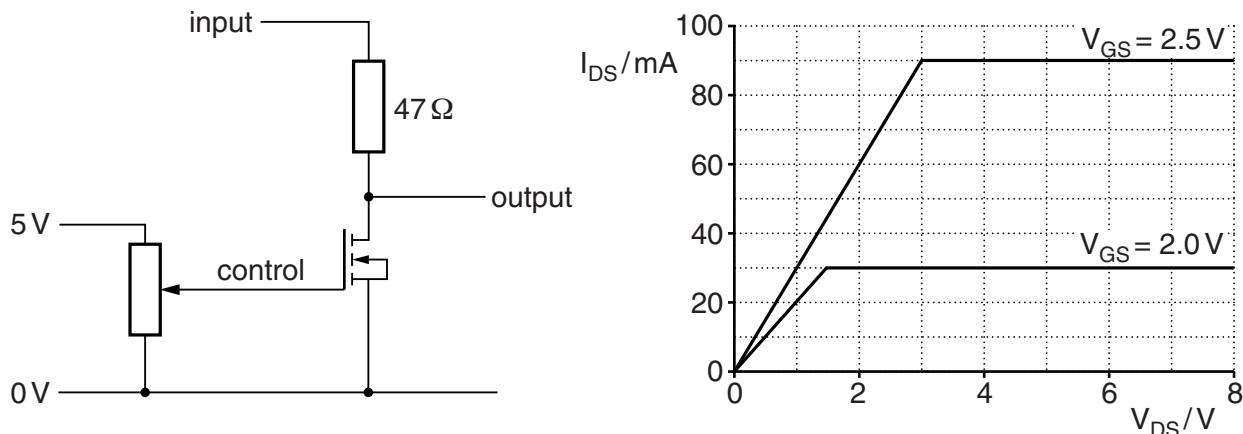


Fig. 7.1

- (a) Mark the drain, gate and source on the MOSFET in Fig. 7.1 with the letters **D**, **G** and **S**. [2]
- (b) Do a calculation to show that the resistance of the MOSFET is about 30Ω when the voltage at **control** is 2.5V and **input** is small.

$$\text{resistance of MOSFET} = \dots \Omega [2]$$

- (c) Calculate the amplitude of **output** when voltage at **control** is 2.5V and the amplitude of **input** is 0.8V .

$$\text{amplitude of output signal} = \dots \text{V} [2]$$

- (d) Explain what happens to **output** when **control** is reduced to 2V without changing **input**.

.....
.....
.....

[2]

- (e) Explain why the electronic volume control will only work well for small input signals. Refer to the graph of characteristics in your answer.

.....
.....
.....

[2]

- (f) Explain what will happen to **output** when voltage at **control** is 2.5V and the amplitude of **input** is increased slowly from 0.8V to 8V.

.....
.....
.....
.....
.....

[4]

[Total 14]
Quality of Written Communication [3]

PLEASE DO NOT WRITE ON THIS PAGE

PLEASE DO NOT WRITE ON THIS PAGE

PLEASE DO NOT WRITE ON THIS PAGE



Copyright Information

OCR is committed to seeking permission to reproduce all third-party content that it uses in its assessment materials. OCR has attempted to identify and contact all copyright holders whose work is used in this paper. To avoid the issue of disclosure of answer-related information to candidates, all copyright acknowledgements are reproduced in the OCR Copyright Acknowledgements Booklet. This is produced for each series of examinations and is freely available to download from our public website (www.ocr.org.uk) after the live examination series.

If OCR has unwittingly failed to correctly acknowledge or clear any third-party content in this assessment material, OCR will be happy to correct its mistake at the earliest possible opportunity.

For queries or further information please contact the Copyright Team, First Floor, 9 Hills Road, Cambridge CB2 1GE.

OCR is part of the Cambridge Assessment Group; Cambridge Assessment is the brand name of University of Cambridge Local Examinations Syndicate (UCLES), which is itself a department of the University of Cambridge.