

Thursday 6 June 2013 – Afternoon

A2 GCE ELECTRONICS

F614/01 Electronics Control Systems

Candidates answer on the Question Paper.

OCR supplied materials:

None

Other materials required:

- Scientific calculator

Duration: 1 hour 40 minutes



Candidate forename		Candidate surname	
-----------------------	--	----------------------	--


Centre number						Candidate number				
---------------	--	--	--	--	--	------------------	--	--	--	--

INSTRUCTIONS TO CANDIDATES

- Write your name, centre number and candidate number in the boxes above. Please write clearly and in capital letters.
- Use black ink. HB pencil may be used for graphs and diagrams only.
- Answer **all** the questions.
- Read each question carefully. Make sure you know what you have to do before starting your answer.
- Write your answer to each question in the space provided. Additional paper may be used if necessary but you must clearly show your candidate number, centre number and question number(s).
- Do **not** write in the bar codes.

INFORMATION FOR CANDIDATES

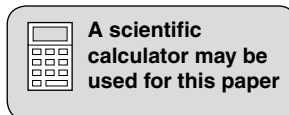- The number of marks is given in brackets [] at the end of each question or part question.
- The total number of marks for this paper is **110**.
- You will be awarded marks for your Quality of Written Communication.
- You are advised to show all the steps in any calculations.
- This document consists of **20** pages. Any blank pages are indicated.



Microcontroller instructions

The microcontroller contains eight general purpose registers S_n , where $n = 0, 1, 2 \dots 7$. The microcontroller has an eight bit input port, I, an eight bit output port, Q, and an analogue input, ADC.

In the table of assembler instructions given below, S_d is the destination register and S_s the source register.

assembler	function
MOVI S_d, n	Copy the byte n into register S_d
MOV S_d, S_s	Copy the byte from S_s to S_d
ADD S_d, S_s	Add the byte in S_s to the byte in S_d and store the result in S_d
SUB S_d, S_s	Subtract the byte in S_s from the byte in S_d and store the result in S_d
AND S_d, S_s	Logical AND the byte in S_s with the byte in S_d and store the result in S_d
EOR S_d, S_s	Logical EOR the byte in S_s with the byte in S_d and store the result in S_d
INC S_d	Add 1 to S_d
DEC S_d	Subtract 1 from S_d
IN S_d, I	Copy the byte at the input port into S_d
OUT Q, S_s	Copy the byte in S_s to the output port
JP e	Jump to label e
JZ e	Jump to label e if the result of the last ADD, SUB, AND, EOR, INC, DEC, SHL or SHR was zero
JNZ e	Jump to label e if the result of the last ADD, SUB, AND, EOR, INC, DEC SHL or SHR was not zero
RCALL s	Push the program counter onto the stack to store the return address and then jump to label s
RET	Pop the program counter from the stack to return to the place the subroutine was called from
SHL S_d	Shift the byte in S_d one bit left putting a 0 into the lsb
SHR S_d	Shift the byte in S_d one bit right putting a 0 into the msb

There are three subroutines provided:

- readtable – copies the byte in the lookup table pointed at by S_7 into S_0 . The lookup table is labelled table: When $S_7=0$ the first byte from the table is returned in S_0
- wait1ms – waits 1ms before returning
- readadc – returns a byte in S_0 proportional to the voltage at ADC

Datasheet

Unless otherwise indicated, you can assume that:

- op-amps are run off supply rails at +15V and -15V
- logic circuits are run off supply rails at +5V and 0V.

resistance	$R = \frac{V}{I}$	
power	$P = VI$	
series resistors	$R = R_1 + R_2$	
time constant	$\tau = RC$	
monostable pulse time	$T = 0.7RC$	
relaxation oscillator period	$T = 0.5RC$	
frequency	$f = \frac{1}{T}$	
voltage gain	$G = \frac{V_{out}}{V_{in}}$	
open-loop op-amp	$V_{out} = A(V_+ - V_-)$	
non-inverting amplifier gain	$G = 1 + \frac{R_f}{R_d}$	
inverting amplifier gain	$G = -\frac{R_f}{R_{in}}$	
summing amplifier	$-\frac{V_{out}}{R_f} = \frac{V_1}{R_1} + \frac{V_2}{R_2} \dots$	
break frequency	$f_0 = \frac{1}{2\pi RC}$	
Boolean Algebra	$A.\bar{A} = 0$	$A + \bar{A} = 1$
		$A.(B + C) = A.B + A.C$
	$\overline{A.B} = \bar{A} + \bar{B}$	$\overline{A + B} = \bar{A}.\bar{B}$
	$A + A.B = A$	$A.B. + \bar{A}.C = A.B + \bar{A}.C + B.C$
amplifier gain	$G = -g_m R_d$	
ramp generator	$\Delta V_{out} = -V_{in} \frac{\Delta t}{RC}$	

Answer **all** questions.

1 Fig. 1.1 shows an incomplete MOSFET amplifier circuit.

 


Fig. 1.1

- (a) Add components and connections to Fig. 1.1 to show how an a.c. signal can be input and output from the amplifier.
Label the input and the output of the amplifier. [2]
- (b) Calculate the value of **R** to make $V_G = 3V$.

$R = \dots\dots\dots k\Omega$ [3]

(c) The graph in Fig. 1.2 shows how the drain current, I_{DS} through the MOSFET depends on the voltage at V_G .

 


Fig. 1.2

(i) Use the graph to find the threshold voltage of the MOSFET.

threshold voltage = $\dots\dots\dots V$ [1]

(ii) Show that the voltage at V_D is about 7V when V_G is 3V.

[3]

(iii) Use information from the graph to calculate the transconductance of the MOSFET.

transconductance = S [3]

(iv) Show that the gain of the amplifier is -6.

[2]

(d) The graph below shows how the voltage V_G varies with time t .

(i) Draw on Fig. 1.1 to show how an oscilloscope can be connected to measure the voltage V_D . [1]

(ii) Draw on the axes of Fig. 1.3 to show how the voltage V_D varies with time.

 


Fig. 1.3

[3]

(iii) Use the graph to find the frequency of V_G .

frequency = Hz [1]

[Total: 19]
Turn over

2 Fig. 2.1 shows an incomplete block diagram of a switched mode power supply.

(a) Use the words below to complete the block diagram.

comparator opto-isolator oscillator rectifier reference smoother transformer

 


Fig 2.1

[6]

(b) Fig. 2.2 shows the circuit diagram of the full-wave rectifier in Fig. 2.1.

 


Fig. 2.2

Fig. 2.3 shows how the voltage at V_{in} varies with time t .

 


Fig. 2.3

Draw on the axes of Fig. 2.3 to show the voltage V_{out} from the rectifier in Fig. 2.2.

[4]

- (c) The opto-isolator contains an LED and a phototransistor.
Explain how an opto-isolator works by referring to the function of each of these components.

.....
.....
..... [2]

- (d) Explain the function of the transformer in the power supply.

.....
.....
..... [2]

[Total: 14]

3 Fig 3.1 shows the incomplete block diagram of a system containing a microcontroller.

 


Fig. 3.1

(a) Complete the block diagram of the microcontroller by drawing and labelling: the address bus, control bus and data bus. Put arrow heads at the end of the buses to show the direction of flow of information. [6]

(b) Describe what happens in the CPU during one machine cycle.
.....
.....
.....
.....
.....
..... [5]

[Total: 11]

BLANK PAGE

PLEASE DO NOT WRITE ON THIS PAGE

4 Fig 4.1 shows the circuit and main program for the door bell in a house.

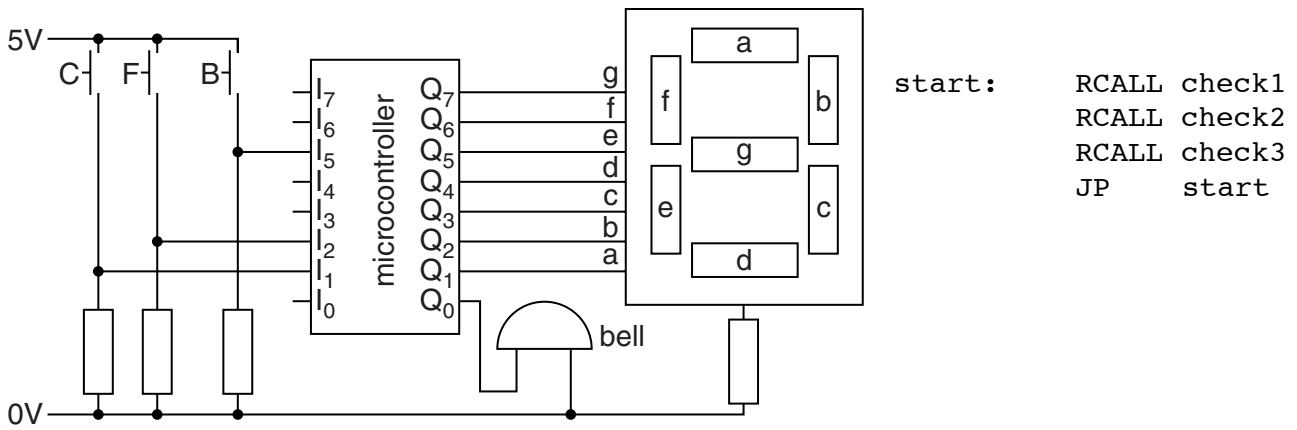


Fig. 4.1

(a) Complete the subroutine `check1` so that the subroutines `show1` and `show2` are called when switch F is pressed otherwise the subroutine returns to the main program.

```

check1: .....
        .....
        .....

        JZ   endf
        RCALL show1
        RCALL show2
endf:   RET
    
```

[4]

(b) Complete the subroutine `show1` to display **F** on the 7-segment display and turn the bell off.

```

show1:  MOVI S2, .....
        .....
        .....
    
```

[3]

(c) The subroutine `wait200ms` produces a delay of 200ms. Complete the subroutine `wait200ms`.

```

wait200ms: .....

delay:   RCALL wait1ms
        DEC   S5
        JNZ  delay
        RET
    
```

[2]

(d) Describe the effect of the subroutine `show2` on the output devices shown in Fig. 4.1.

```
show2:  MOVI  S3, 01 .....  
        MOVI  S4, 06 .....  
loop:   EOR   S2, S3 .....  
        OUT   Q, S2 .....  
        RCALL wait200ms .....  
        DEC   S4 .....  
        JNZ   loop .....  
        RET   .....  
.....  
.....  
.....  
.....  
.....
```

[4]

(e) Write a subroutine to turn the bell on for 600 ms without affecting the display.

[8]

[Total: 21]

5 Fig 5.1 shows the circuit diagram for a full adder.

 


Fig. 5.1

(a) Complete the truth table for the full adder.

C	B	A	F	S
0	0	0		

[2]

(b) Fig 5.2 shows a system for adding binary numbers together.

 


Fig. 5.2

- (i) Complete the circuit in Fig. 5.3 for a 4-bit register for the parallel processing of binary words.
- Label the following:
 - inputs A_0, A_1, A_2, A_3
 - outputs Q_0, Q_1, Q_2, Q_3
 - the signal X which makes the register store the word at the inputs


 


Fig. 5.3

[3]

 - (ii) Fill in the boxes to show the addition of the two binary numbers 0111 0110 and 0101 0100.



[3]

(c) Show how the decimal number -42 can be obtained using two's complement.

[3]

[Total: 11]

Turn over

6 A circuit for controlling the position of a satellite dish is shown in Fig. 6.1.

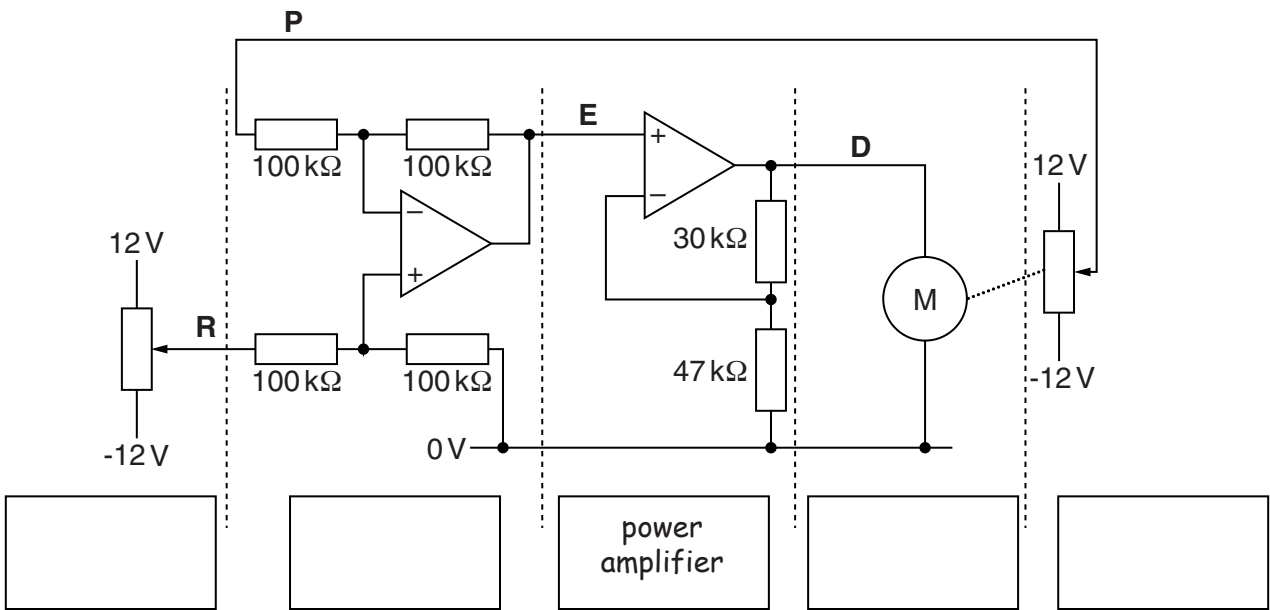


Fig. 6.1

(a) Label the sections of circuit diagram in Fig 6.1 using the labels. One of the labels has already been written in for you:

difference amplifier **motor** **position sensor** **power amplifier** **reference** [1]

(b) Show that the voltage gain of the power amplifier is about 1.6. [2]

(c) Name the component used to control the voltage at **R**. [1]

.....

(d) **P** is initially 5V. Then the user moves the dish by changing **R** to 2V. For **R** = 2V and **P** = 5V:

(i) calculate the voltage at **E**

voltage at **E** = V [2]

(ii) calculate the voltage at **D**

voltage at **D** = V [1]

(iii) Explain how the circuit works to move the satellite dish to the set position. Refer to the voltages at R, P, E and D in your answer.

.....
.....
.....
.....
..... [4]

(e) Explain why the circuit uses proportional feedback instead of on-off feedback for controlling the position of the satellite dish.

.....
.....
.....
.....
..... [4]

[Total: 15]

7 Fig. 7.1 shows the circuit diagram of a volatile memory cell.

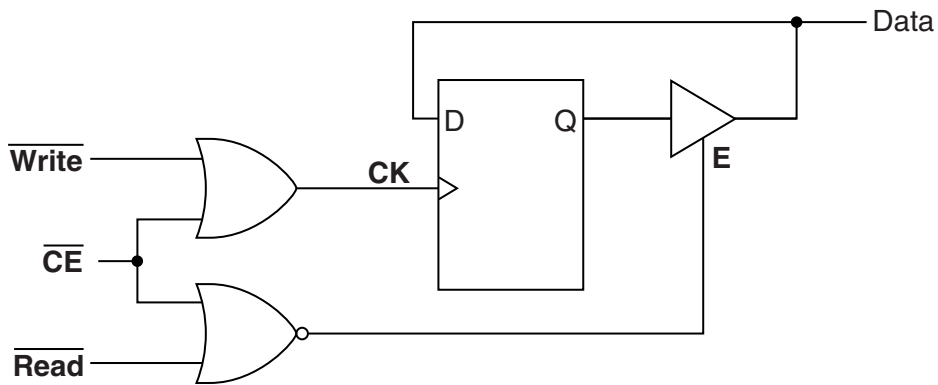


Fig. 7.1

(a) State what the word 'volatile' means in reference to a memory cell.

.....
 [1]

(b) Complete the truth table for the logic system in the memory cell.

\overline{CE}	\overline{Read}	\overline{Write}	CK	E

[3]

(c) Describe the sequence of logic levels needed on \overline{CE} , Data, \overline{Read} and \overline{Write} to store a logic 1 in the memory cell.

.....

 [5]

- (d) Fig. 7.2 shows a memory module.
Explain why the memory module contains 6 memory cells.

 


Fig 7.2

.....

 [2]

- (e) Complete the circuit diagram in Fig. 7.3 to show how the memory module in Fig. 7.2 can be built from memory cells and other components.

 
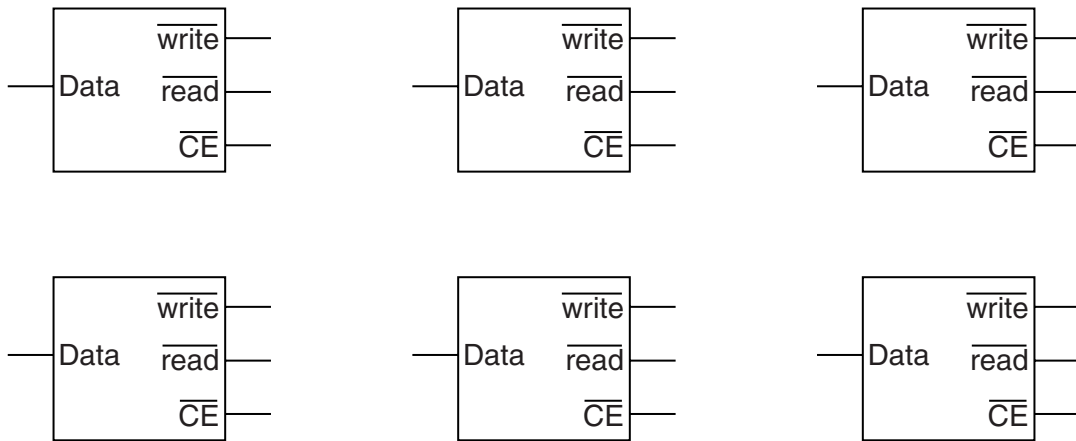
 


Fig. 7.3

[5]

[Total: 16]

Quality of Written Communication [3]

END OF QUESTION PAPER

18
BLANK PAGE

PLEASE DO NOT WRITE ON THIS PAGE

BLANK PAGE

PLEASE DO NOT WRITE ON THIS PAGE

PLEASE DO NOT WRITE ON THIS PAGE



Copyright Information

OCR is committed to seeking permission to reproduce all third-party content that it uses in its assessment materials. OCR has attempted to identify and contact all copyright holders whose work is used in this paper. To avoid the issue of disclosure of answer-related information to candidates, all copyright acknowledgements are reproduced in the OCR Copyright Acknowledgements Booklet. This is produced for each series of examinations and is freely available to download from our public website (www.ocr.org.uk) after the live examination series.

If OCR has unwittingly failed to correctly acknowledge or clear any third-party content in this assessment material, OCR will be happy to correct its mistake at the earliest possible opportunity.

For queries or further information please contact the Copyright Team, First Floor, 9 Hills Road, Cambridge CB2 1GE.

OCR is part of the Cambridge Assessment Group; Cambridge Assessment is the brand name of University of Cambridge Local Examinations Syndicate (UCLES), which is itself a department of the University of Cambridge.