



GCE MARKING SCHEME

SUMMER 2016

**ELECTRONICS ET5
1145/01**

INTRODUCTION

This marking scheme was used by WJEC for the 2016 examination. It was finalised after detailed discussion at examiners' conferences by all the examiners involved in the assessment. The conference was held shortly after the paper was taken so that reference could be made to the full range of candidates' responses, with photocopied scripts forming the basis of discussion. The aim of the conference was to ensure that the marking scheme was interpreted and applied in the same way by all examiners.

It is hoped that this information will be of assistance to centres but it is recognised at the same time that, without the benefit of participation in the examiners' conference, teachers may have different views on certain matters of detail or interpretation.


WJEC regrets that it cannot enter into any discussion or correspondence about this marking scheme.

1. (a)

State	Current Outputs			Next Outputs		
	C	B	A	D _C	D _B	D _A
0	1	1	1	1	0	0
1	1	0	0	1	0	1
2	1	0	1	0	0	1
3	0	0	1	0	1	1
4	0	1	1	1	1	1
5	0	0	0	1	1	1
6	0	1	0	1	1	1
7	1	1	0	1	0	0

Five correct 'current' states identified 1 mark
 Correct progression into 'Next Output' 1 mark
 States in correct order in table 1 mark
 ('Next Outputs = 0 0 0' for state 4 = 1 mark total.)

(b)

 


Completely correct 1 mark

(c) "An unused state is not part of the main sequence." or equivalent. 1 mark

(d) A stuck state does not allow progression to the main sequence, or equivalent. 1 mark

 (e) (i) $D_B = \overline{C}$ 1 mark
 $D_C = B + \overline{A}$ or $\overline{A \cdot \overline{B}}$ one mark per term 2 marks
 (Must be simplest for 2 marks. Any other correct = 1 mark.)




Allow ecf from (e) for D_B and D_C
 Clock connections correct 1 mark
 D_C correct 1 mark
 D_B correct 1 mark
 D_A correct 1 mark
 Use of \overline{Q} 1 mark
 (Allow ecf from (e) for D_B and D_C)

Total for Q1

14

2. (a)

 

Capacitor in series with resistor
RC network in input circuit
Remainder of circuit correct

1 mark
1 mark
1 mark

(b) (i) Correct multipliers in break frequency formula
Break frequency = 995 Hz (accept 994.7 Hz).

1 mark
1 mark

(ii) Low frequency voltage gain = 12 (or -12)

1 mark

(c) (i) Filter = treble boost

1 mark

(ii) Break frequency = 3 kHz

1 mark

Total for Q2

8

3. (a) (i) Voltage at X = 0.1 V

1 mark

(ii) Binary output = 10

1 mark

(iii) Smallest $V_{IN} = 0.4 V$ (accept " $>0.4 V$ ")

1 mark

(b) (i) Resolution = 0.0625 V (=1/16 V) (accept 0.063 V)

1 mark

(ii) $V_{REF} = 1.0 V$

1 mark

(iii) No. of resistors = 16

1 mark

Total for Q3

6

4. (a) Answer = D (00011)

1 mark

(b) `movlw b'10010XXX'` (X = don't care)

Enable GIE (set bit 7)

1 mark

Enable INTE and disable all others (set bit 4, reset bits 6, 5, 3)

1 mark

(Answer must be 8 bits)

(c)

220	alarm	movwf	protect	; store contents of W in register called 'protect';
221		bsf	PORTA, 2	; output logic 1 to switch on buzzer;
222		call	tensec	; call ten second delay subroutine;
223		btfs	PORTA, 0	; test reset switch - ignore next instruction if pressed;
224		goto	alarm	; jump back to line 220;

One mark per correct line


5 marks

(Lower case used in 'PORTA' or upper case in 'alarm' loses 1 mark)

Total for Q4

8

5. (a)

 

Correct input impedance on both channels ($>10k\Omega$)
 Correct max voltage gain on **both** channels
 Rest of circuit correct
 (Resistor values may differ from specimen answer.)

1 mark
 1 mark
 1 mark

(b) Output = $-[(10 \times 2) + (-4 \times 1)] = -16\text{mV}$
 Correct value (16 mV)
 Correct sign (-)
 (Allow ecf from (a))

1 mark
 1 mark

Total for Q5 5

6. (a) (i) $V_{\text{OUT}} = 7.2\text{V}$

1 mark

(ii) New $V_{\text{OUT}} = \mathbf{6.96\text{V}}$ (accept 7.0V)

1 mark

(b) (i) $V_{\text{DIFF}} = (6 - 7.2) = -1.2\text{V}$ - allow ecf from (a)

Correct value

1 mark

Correct sign

1 mark

(Allow ecf from (a))


(ii) $V_{\text{DIFF}} = (5.8 - 7.0) = -1.2\text{V}$ - allow ecf from (i)

1 mark

(c) Advantage such as **immunity to electrical noise**

1 mark

(d)

 


Inverting input at mid-point of voltage divider as shown
 Non-inverting input at mid-point of voltage divider as shown
 Correct ratio to give voltage gain of 100

1 mark
 1 mark
 1 mark

Total for Q6 9

7. (a)

 

- (i) Correct connection for switch, labelled A and resistor 1 mark
- (ii) Correct connection for switch, labelled B 1 mark
- Resistor in series with switch 1 mark
- Correct connection for capacitor 1 mark
- (b) (i) Voltage at X = 0V 1 mark
- (ii) Voltage above switch B drops from 48V to 0V when switch is pressed 1 mark
- so voltage at X drops by 48V to -48V 1 mark
- thyristor is momentarily reverse biased and switches off, or equivalent 1 mark
- (c) Advantage such as no moving parts so no wear from friction 1 mark

Total for Q7

9

8. (a)

Link S

(Other links included - zero marks)

1 mark

(b)

$$R_1 = R_2$$

1 mark


(c)

(i) $V_{OUT} = 2.3V$

(ii) Power dissipation = 0.66 W (accept 0.7 W)

1 mark

(iii)

 


Signal centred on +2.3V

1 mark

Sinusoidal signal of amplitude 2V

1 mark

(d) (i)

 

Use of complementary pair

1 mark

Common emitter connection to output

1 mark

Common base connection to input

1 mark

(ii) Max. power dissipation = 18 W

1 mark

(iii) Advantage such as zero quiescent power dissipation

1 mark

Total for Q8

11