



GCE MARKING SCHEME

**ELECTRONICS
AS/Advanced**

SUMMER 2015

INTRODUCTION

The marking schemes which follow were those used by WJEC for the Summer 2015 examination in GCE ELECTRONICS. They were finalised after detailed discussion at examiners' conferences by all the examiners involved in the assessment. The conferences were held shortly after the papers were taken so that reference could be made to the full range of candidates' responses, with photocopied scripts forming the basis of discussion. The aim of the conferences was to ensure that the marking schemes were interpreted and applied in the same way by all examiners.

It is hoped that this information will be of assistance to centres but it is recognised at the same time that, without the benefit of participation in the examiners' conferences, teachers may have different views on certain matters of detail or interpretation.

WJEC regrets that it cannot enter into any discussion or correspondence about these marking schemes.

| | Page |
|-----|-------------|
| ET1 | 1 |
| ET2 | 6 |
| ET4 | 9 |
| ET5 | 14 |

ET1

| Question | | | Marking detail | Marks available | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
|----------|-----|----------|--|-----------------|---|---|---|---|---|---|----------|----------|---|---|----------|----------|----------|---|----------|---|----------|----------|----------|---|---|----------|----------|---|---|---|----------|---|---|---|----------|---|---|---|----------|---|
| 1. | (a) | | <p>One mark for each correct column X, Y and Q no ecf</p> <table border="1" style="margin-left: auto; margin-right: auto; border-collapse: collapse; text-align: center;"> <thead> <tr> <th>B</th> <th>A</th> <th>X</th> <th>Y</th> <th>Q</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> <td>0</td> <td>0</td> </tr> </tbody> </table> | B | A | X | Y | Q | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 3 | | | | | | | | | | | |
| B | A | X | Y | Q | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 0 | 0 | 1 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 1 | 1 | 1 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 0 | 1 | 1 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 1 | 1 | 0 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| | (b) | | Correct NAND gate replacement for OR gate drawn. | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| | | | | 4 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 2. | (a) | (i) | <table border="1" style="margin-left: auto; margin-right: auto; border-collapse: collapse; text-align: center;"> <thead> <tr> <th>C</th> <th>B</th> <th>A</th> <th>Q</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table> | C | B | A | Q | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 2 |
| C | B | A | Q | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 0 | 0 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 0 | 1 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 1 | 0 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 0 | 1 | 1 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 0 | 0 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 0 | 1 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 1 | 0 | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 1 | 1 | 1 | 0 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| | | (ii) | <p>Completely correct 2 marks. Reverse order 1 mark only</p> <p>$Q = \bar{C}.B.\bar{A} + C.\bar{B}.\bar{A} + C.B.\bar{A}$ allow correct simplification (one error award 1 mark) ecf (a)(i)</p> | 2 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| | (b) | | By altering the connections between the D inputs <u>and</u> the power rails. | 1 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| | | | | 5 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |

| Question | | Marking detail | Marks available |
|----------|-----|--|-----------------|
| 3. | (a) | Output Logic 1 between first falling-edge of A and first-rising edge of B Output logic 1 when A is logic 0 for final time. (-1 mark for each additional transition up to a maximum of 2 marks) | 1 1 |
| | (b) | EXNOR, XNOR | 1 |
| | | | 3 |
| 4. | (a) | To keep the input X at logic 1 when switch A is open. (accept 'it acts as a pull-up resistor')/ To prevent short-circuit of power rails. | 1 |
| | (b) | $Y = [\text{logic}] 0$ | 1 |
| | (c) | Inputs from switches to NOR gate Output of NOR and Pulses to AND gate Output of AND gate to Q (Possible alternative OR then NOR) | 1 1 1 |
| | | | 5 |

| Question | | | Marking detail | Marks available |
|----------|---|--|------------------------|-----------------|
| 5. | (a) | (i) | $\overline{C}.0 = 0$ | 1 |
| | | (ii) | $D + \overline{D} = 1$ | 1 |
| | (b) | <p>Correct map Two groups of 4 and one of 2 identified (ecf map) Any correct term from groups identified on the map Simplest overall expression $Q = \overline{D}.C + C.A + \overline{D}.B.\overline{A}$</p> | 1 1 1 1 | |
| (c) | $Q = (B.A) + \overline{A}$ 1 mark (DeMorgan) $B + \overline{A}$ 1 mark (simplification) Alternative solution: $\overline{(\overline{B+A}).A} = \overline{\overline{B}.A} = B + \overline{A}$ | 2 | | |
| | | | | 8 |
| 6. | (a) | (i) | Binary 11101101 | 1 |
| | | (ii) | BCD 0010 0011 0111 | 1 |
| | (b) | Band D selected and connected to logic gate inputs Single AND gate chosen with output to R | 1 1 | |
| | | | | 4 |

| Question | | Marking detail | Marks available | |
|----------|------|---|---|--------|
| 7 | (a) | $\bar{Q} = [\text{logic}] 1$ | 1 | |
| | (b) | <p>Q responds correctly to:</p> <ul style="list-style-type: none"> ▪ Clock/data (3 correct = 2 marks, 2 correct = 1 mark) ▪ Reset ▪ Set <p>(-1 mark for each additional transition up to a maximum of 2 marks)</p> | 2 1 1 | |
| | | | 5 | |
| 8. | (a) | <ul style="list-style-type: none"> ▪ \bar{Q} to D $\times 3$ ▪ clock inputs correct $\times 3$ ▪ Q to resistor/LED $\times 3$ | 1 1 1 | |
| | | (b) | Switch and resistor across power rails with correct orientation. Correct connection of switch unit to 3 resets | 1 1 |
| | | (c) (i) | 120 | 1 |
| | (ii) | 15 ecf from (c)(i) (i.e. $\frac{1}{8}$ of the answer) | 1 | |
| | | | 7 | |

| Question | | Marking detail | Marks available | |
|----------|---|---|--|-------------|
| 9. | (a) | <ul style="list-style-type: none"> ▪ Inverse sloping line through (0,0) ▪ Correct gradient (passes through 100, -7.5) ▪ Saturation at $18V \times 2$ (240, -18) | 1 1 1 | |
| | | (b) | (i) BW = 48 k[Hz] or 0.048 M[Hz] or 48 000 [Hz] | 1 |
| | | | (ii) Horizontal line at gain 75 Sloping line through (48,53) ecf from (b)(i) | 1 1 |
| | (c) | (i) | <ul style="list-style-type: none"> ▪ Operational amplifier with negative feedback resistor drawn correctly ▪ Resistor between V_{IN} and inverting input ▪ Non-inverting input to 0V | 1 1 1 |
| | | | (ii) R_F and R_I in ratio 75:1 (both 1 k Ω or greater as requested) Correctly assigned and identified on the circuit diagram. | 1 1 |
| | | | | 11 |
| 10. | (a) | Voltage gain = 7 | 1 | |
| | (b) | 2.0×10^{12} [Ω] or 2 T[Ω] | 1 | |
| | (c) | (i) $40 \times 9 = 360$ [mV] | 1 | |
| | | (ii) <u>Sine wave</u> of correct frequency and phase Voltage peaks at ± 360 mV ecf from (c) (i) | 1 1 | |
| | (d) | $\frac{13.5}{9} = 1.5$ [V] or 1 500 m[V] | 1 | |
| (e) | $\frac{27}{6} = 4.5$ (1 mark) μs (1 mark) (unit consistent with number) | 2 | | |
| | | | 8 | |




ET2

| Question | | | Answers/Explanatory Notes * Indicates that ECF will be allowed from a previous part | Marks Available |
|----------|---|------------------------------|---|--------------------------|
| 1 | a | (i) (ii) | 0.5 k Ω (1) 1.5 k Ω (1) | 2 |
| | b | (i) (ii) (iii) (iv) | $I_1 = 8 \text{ mA}$ (1) * $I_2 = 4 \text{ mA}$ (1) * $V_1 = 4 \text{ V}$ (1) $V_2 = 8 \text{ V}$ (1) * | 4 [6] |
| 2. | a | (i) (ii) (iii) | $V_{OC} = 6.75 \text{ V}$ (1) $I_{SC} = 0.069 \text{ A}$ (1) $R_O = 97.5 \Omega$ (1) * | 3 |
| | b | | Voltage drop across 120 Ω resistor = 3 V (1) Current through 120 Ω resistor = 0.025 A (1) Minimum value of load resistance = 200 Ω (1) * | 3 [6] |
| 3. | a | (i) (ii) | 5.5 V (1) 3 V (1) [allow 1 mark if answers reversed] | 2 |
| | b | (i) (ii) | Resistor connected between i/p and o/p of Schmitt (1) Capacitor connected between 0 V and Schmitt i/p (1) Suitable method (1) Correct values (1) Any combination of R and C with a period of 5 ms e.g. $R = 1 \text{ k}\Omega$; $C = 5 \mu\text{F}$ | 2 2 [6] |
| 4. | a | (i) (ii) (iii) | Graph 3 (1) Graph 4 (1) Graph 2 (1) | 3 |
| | b | (i) (ii) | Correct position and symbol for capacitor (1) 3 correct connections (1) 16.6 V (1) | 2 1 [6] |

| Question | | | Answers/Explanatory Notes * Indicates that ECF will be allowed from a previous part | Marks Available |
|----------|---|----------------------|--|---------------------|
| 5. | a | | Correct components in voltage divider (1) Correct orientation (with pull up resistor) (1) | 2 |
| | b | | Substitution with correct multipliers (1) 5.17 secs (1) | 2 |
| | c | (i) (ii) | Voltage across R = 4 V (1) $R = \frac{4}{24\text{mA}} = 167\Omega$ (1) * 180Ω (1) * | 3 [7] |
| 6. | a | | Diode in inverse parallel across solenoid (1) | 1 |
| | b | | Substitution (1) 4.8 V (1) * | 2 |
| | c | | Substitution (1) 18.72 W (1) | 2 [5] |
| 7. | a | (i) | Appropriate scales (1) Quality of curve (1) At least 5 accurate points (1) | 3 |
| | | (ii) | 4 kΩ (accept 3.8 – 4.2 kΩ) (1) * | 1 |
| | b | (i) (ii) (iii) | Two 10 kΩ resistors in voltage divider connected to V- (1) 2.08 V (accept 2– 2.1 V / * allow ecf from a(ii)) (1) LED off : V- larger than V+ (1) | 3 [7] |


| Question | | | Answers/Explanatory Notes * Indicates that ECF will be allowed from a previous part | Marks Available |
|--------------|--|---|--|-----------------|
| 8. | a | (i) | $I_B = \frac{120}{80} = 1.5 \text{ mA} \text{ (1)}$ | 3 |
| | | (ii) | Voltage across base resistor = $3.4 - 0.7 = 2.7 \text{ V} \text{ (1)}$ $R = \frac{2.7\text{V}}{1.5\text{mA}} = 1.8 \text{ k}\Omega \text{ (1) *}$ | |
| | b | Shape (1) Plotting point (0.7, 9) (1) Plotting point (3.4, 0) (1) | 3 | |
| | c | (i) $V_{\text{OUT}} = 3 \pm 0.5 \text{ V} \text{ (1) *}$ (ii) $3 \text{ V} \times 80 \text{ mA} = 240 \text{ mW} \text{ (1)}$ | 2 | |
| d | Resistor and LDR in voltage divider (1) LDR at bottom (1) | 2 | | |
| | | | | [10] |
| 9. | a | $15 - 5.6 = 9.4 \text{ V} \text{ (1)}$ $\frac{9.4}{20} = 0.47 \text{ A} = 470 \text{ mA} \text{ (1)}$ | 2 | |
| | b | $470 - 6 = 464 \text{ mA} \text{ (1) *}$ | 1 | |
| | c | Voltage across 20Ω resistor = $600 \text{ mA} \times 20 \Omega = 12 \text{ V} \text{ (1)}$ $V_{\text{LOAD}} = 3 \text{ V} \text{ (1)}$ | 2 | |
| | d | Horizontal line at 5.6 V until $I = 464 \text{ mA} \text{ (1) *}$ Gradual downward slope thereafter (1) | 2 | |
| | | | | [7] |
| TOTAL | | | | 60 |

ET4
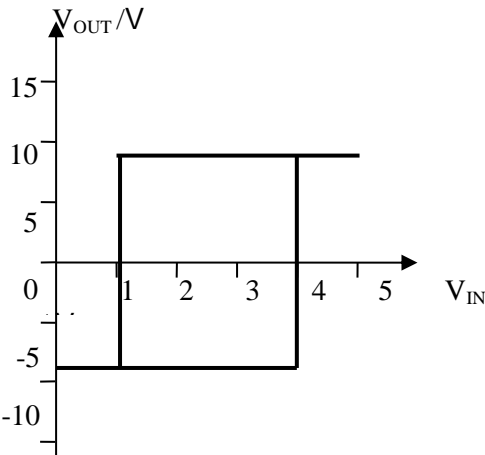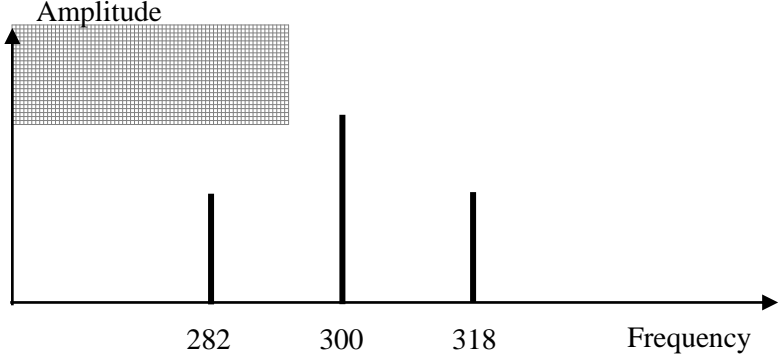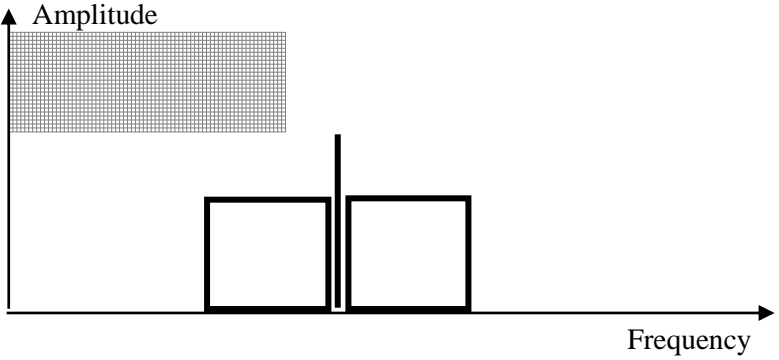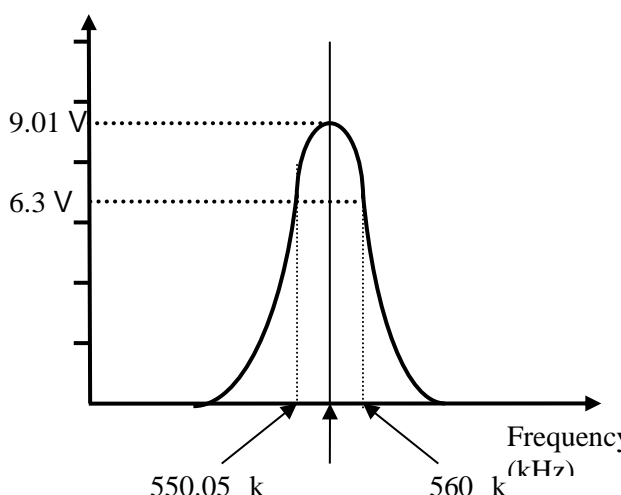
| Question | Marking details | Marks Available |
|---|--|--|
| <p>1</p> <p>(a)</p> <p>(b)</p> | <p>Non-Inverting</p>  <p>Saturation Levels at $\pm 9\text{ V}$</p> <p>Switching thresholds at 1 V and 4 V</p> <p>Non-inverting characteristic</p> | <p>1</p> <p>1</p> <p>1</p> <p>1</p> <p>[4]</p> |
| <p>2</p> <p>(a)</p> <p>(b)</p> <p>(i)</p> <p>(ii)</p> |  <p>Line spectrum</p> <p>Correct carrier frequency</p> <p>Correct side band frequencies</p>  <p>Continuous band spectrum</p> <p>36 kHz</p> | <p>1</p> <p>1</p> <p>1</p> <p>1</p> <p>1</p> |

| Question | | Marking details | Marks Available |
|----------|-----|---|-----------------|
| 2. | (c) | (i) $f_c = \frac{1}{14.28 \times 10^{-6}} = 70\,000 \text{ Hz} = 70 \text{ kHz} (\pm 0.2 \text{ kHz})$ | 1 |
| | | (ii) $f_i = \frac{1}{200 \times 10^{-6}} = 5\,000 \text{ Hz} = 5 \text{ kHz}$ | 1 |
| | | (iii) Modulation Depth = $\frac{V_{\max} - V_{\min}}{V_{\max} + V_{\min}} \times 100\%$ $= \frac{3-0.4}{3+0.4} \times 100\% = 76.5\% \text{ (Accept 71-77\%)}$ | 1 |
| | | | [8] |
| 3. | (a) | (i) T | 1 |
| | | (ii) Q | 1 |
| | | (iii) R & S | 1 |
| | | (iv) P or R or S | 1 |
| | (b) | (i) Poor Selectivity – The inability to reject nearby stations. | 1 |
| | | (ii) Poor Sensitivity – The inability to detect weak stations. | 1 |
| | (c) | (i) 1.680 MHz / 2.145 MHz / 3.825 MHz / 0.465 MHz or 465 kHz All 4 Correct = 2 marks 3 Correct = 1 mark | 2 or 1 |
| | | (ii) 0.465 MHz or 465 kHz | 1 |
| | | | [9] |


| Question | | Marking details | Marks Available | | | | | | | | | | | | | | | | | | | | | | | | |
|--|----------------|--|-----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|---|---|---|---|---|---|---|---|---|---|---|---|---|---|
| 4. | (a) | (i) <div style="text-align: center;"> <p>Logic level</p> <p>1 mark for each correct label</p> </div> | 3 | | | | | | | | | | | | | | | | | | | | | | | | |
| | | (ii) Character transmitted = "W", No marks for "U" | 1 | | | | | | | | | | | | | | | | | | | | | | | | |
| | (b) | (i) <table border="1" style="margin-left: auto; margin-right: auto;"> <tr> <td>P₄</td> <td>P₃</td> <td>P₂</td> <td>P₁</td> <td>P₀</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> <td>0</td> <td>0</td> </tr> </table> <p style="text-align: right;">All five correct = 2 marks All five inverted = 1 mark</p> | P ₄ | P ₃ | P ₂ | P ₁ | P ₀ | 1 | 1 | 1 | 0 | 0 | 2 or 1 | | | | | | | | | | | | | | |
| | | P ₄ | P ₃ | P ₂ | P ₁ | P ₀ | | | | | | | | | | | | | | | | | | | | | |
| 1 | 1 | 1 | 0 | 0 | | | | | | | | | | | | | | | | | | | | | | | |
| (ii) <p>(I) P₀ and P₄ fail the parity check</p> <p>(II) P₀ and P₄ fail the parity check – common to D₃, so this is where the error is.</p> <table border="1" style="margin-left: auto; margin-right: auto;"> <tr> <td>D₇</td> <td>D₆</td> <td>D₅</td> <td>D₄</td> <td style="background-color: yellow;">D₃</td> <td>D₂</td> <td>D₁</td> <td>D₀</td> <td>P₄</td> <td>P₃</td> <td>P₂</td> <td>P₁</td> <td>P₀</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> <td>0</td> <td style="background-color: yellow;">0</td> <td>1</td> <td>0</td> <td>0</td> <td>1</td> <td>0</td> <td>0</td> <td>1</td> <td>0</td> </tr> </table> | D ₇ | D ₆ | D ₅ | D ₄ | D ₃ | D ₂ | D ₁ | D ₀ | P ₄ | P ₃ | P ₂ | P ₁ | P ₀ | 0 | 1 | 1 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |
| D ₇ | D ₆ | D ₅ | D ₄ | D ₃ | D ₂ | D ₁ | D ₀ | P ₄ | P ₃ | P ₂ | P ₁ | P ₀ | | | | | | | | | | | | | | | |
| 0 | 1 | 1 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | | | | | | | | | | | | | | | |
| [8] | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 5. | (a) | | 1 | | | | | | | | | | | | | | | | | | | | | | | | |
| | | | 1 | | | | | | | | | | | | | | | | | | | | | | | | |
| | (b) | <p style="text-align: center;">Correct Method in each case (2 x 1) Consistent Application in each case (2 x 1)</p> | 1 | | | | | | | | | | | | | | | | | | | | | | | | |
| | | <p>No of levels required = $\frac{5}{500 \times 10^{-6}} = 10\,000$</p> <p>13 bits provide $2^{13} = 8\,192$ levels, 14 bits provide $2^{14} = 16\,384$ levels, so 14 bits would be suitable.</p> | 1 | | | | | | | | | | | | | | | | | | | | | | | | |
| [6] | | | | | | | | | | | | | | | | | | | | | | | | | | | |

| Question | | Marking details | Marks Available |
|----------|-----|---|--|
| 6. | (a) | $f_o = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.02 \times 10^{-3} \times 4 \times 10^{-9}}}$ $= 562\,698 \text{ Hz} \cong 560 \text{ kHz}$ | <p style="text-align: right;">multipliers answer</p> <p style="text-align: right;">1 1</p> |
| | (b) | $R_D = \frac{L}{r_L C} = \frac{0.02 \times 10^{-3}}{2.5 \times 4 \times 10^{-9}} = 2\,000 \, \Omega = 2 \text{ k}\Omega$ | <p style="text-align: right;">correct substitution in correct formula answer</p> <p style="text-align: right;">1 1</p> |
| | (c) | $V_{\text{OUT}} = \frac{10 \times 2\,000}{220 + 2\,000} = 9.01 \text{ V}$ | <p style="text-align: right;">Substitution in formula answer</p> <p style="text-align: right;">1 1</p> |
| | (d) | $Q = \frac{2\pi f_o L}{r_L} = \frac{2\pi \times 562\,698 \times 0.02 \times 10^{-3}}{2.5}$ $= 28.3 \text{ (28.1 for 560k)}$ | <p style="text-align: right;">answer</p> <p style="text-align: right;">1</p> |
| | (e) | $\text{bandwidth} = \frac{f_o}{Q} = \frac{562\,698}{28.3} = 19\,883 \text{ Hz} = 19.9 \text{ kHz}$ | <p style="text-align: right;">answer only</p> <p style="text-align: right;">1</p> |
| | (f) |  <ul style="list-style-type: none"> • Shape (1) • Peak output voltage 9 V (1) • Correct resonant frequencies and use of $0.7 \times$ peak to plot bandwidth (1) | <p style="text-align: right;">3</p> |
| | | | [11] |

| Question | | Marking details | Marks Available |
|----------|-----|--|--|
| 7. | (a) | $\frac{12 - V_{IN}}{9} = \frac{12 - 1}{6.8}$ $12 - V_{IN} = \frac{9 \times 11}{6.8}$ $12 - V_{IN} = 14.56$ $V_{IN} = 12 - 14.56 = -2.56 \text{ V}$ <p style="text-align: right;">correct formula / substitution correct answer</p> | <p style="text-align: right;">1 1</p> |
| | (b) | $\frac{-12 - V_{IN}}{9} = \frac{-12 - 1}{6.8}$ $-12 - V_{IN} = \frac{9 \times -13}{6.8}$ $-12 - V_{IN} = -17.21$ $V_{IN} = -12 + 17.21 = 5.21 \text{ V}$ <p style="text-align: right;">correct formula / substitution correct answer</p> | <p style="text-align: right;">1 1 [4]</p> |

ET5

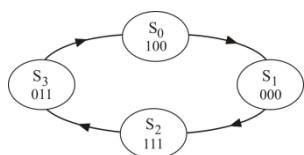1. (a) One count not completely registered before next pulse arrives (or equivalent.) 1 mark
 (b) (i)




- Completely correct 1 mark
 (ii) '001' (only correct answer) 1 mark
 (iii) Any unused state, such as '010' 1 mark
 (iv) State 5 progresses through '110' to main sequence, or equivalent 1 mark
 Timing information 1 mark
 State 4 loops back to itself continuously, or equivalent 1 mark

Total for Q1

7

2. (a)

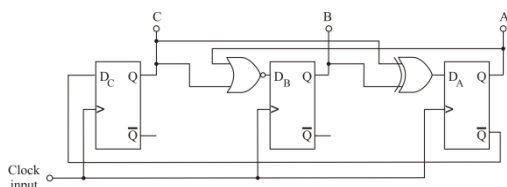

- Clock connections correct 1 mark
 D_C correct 1 mark
 D_B correct 1 mark
 D_A correct 1 mark
 Use of \bar{Q} 1 mark

- (b)

| State | Current state | | | | Next state | | | |
|-------|---------------|------|--------|----------|------------|------|--------|----------|
| | Light | Pump | Paddle | Solenoid | Light | Pump | Paddle | Solenoid |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 |
| 2 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 0 |
| 3 | 1 | 1 | 1 | 0 | 1 | 0 | 1 | 1 |
| 4 | 1 | 0 | 1 | 0 | 1 | 0 | 0 | 1 |
| 5 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |

- Buzzer correct 1 mark
 Pump correct 1 mark
 Paddle correct 1 mark
 Solenoid correct 1 mark

Total for Q2


9

3. (a) (i) Grey code 1 mark
 (ii) Binary can give false readings when near segment boundaries/moving between segments causing either false alarms, or missing alarm conditions, or equivalent. 1 mark
 (b) $Q = Z \cdot X$, or equivalent 1 mark
 Correct operator 1 mark
 Correct signals 1 mark
 (c) Any application in which speed is monitored, or equivalent. 1 mark

Total for Q3

5

4. (a) (i)

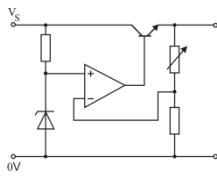

Zener sub-system correct

1 mark

Non-inv amp correct

1 mark

Emitter follower correct

1 mark


(ii) Line regulation keeps output voltage steady when supply voltage varies

1 mark

(iii) As V_S increases, voltage across resistor increases, but output of zener, and so V_{REF} , remains constant, or equivalent

1 mark

(b) (i)

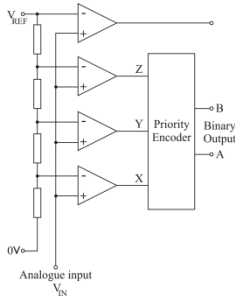

Use of three comparators

1 mark

Correct input and output connections to comparators

1 mark

(ii) All resistor values equal

1 mark

All resistor values $>1\text{ k}\Omega$

1 mark

(iii) $V_{REF} = 1.00\text{ V}$

1 mark

(iv) $B = 1_2$ $A = 0_2$

1 mark

Total for Q4

11

5. (a)

04 goto **warn**

1 mark

(b)

100 warn movlw b'1000000'

1 mark

101 **movwf** PORTB

1 mark

(c)

Instruction at address 103 switches off the lamp, or equivalent

1 mark

(d)

Working register contains '4'

1 mark

(e) (i)

99 warn **movwf** **Wstore**

107 **movf** **Wstore,0**

correct use of Wstore

1 mark

correct destination

1 mark


(ii) Flag indicates that interrupt has been serviced or equivalent

1 mark

Total for Q5

8

6. (a)

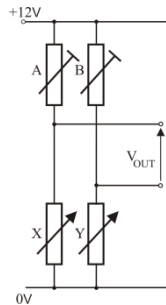


Two voltage dividers each having strain gauge and variable resistor
Correct orientation / use of correct symbols

1 mark
1 mark

- (b) Both strain gauges warm up equally. Both increase in resistance equally.
Produces same change in output of each voltage divider.
Changes cancel each other out, (or equivalent.)

1 mark

(c) (i)

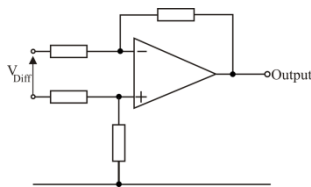

Inverting input at mid-point of voltage divider as shown
Non-inverting input at mid-point of voltage divider as shown

1 mark
1 mark

- (ii) Correct ratio of feedback to input resistor, AND values > 1 kΩ
Values symmetrical on inverting and non-inverting inputs
(iii) Output = 200 × 3.5 = 700 mV

1 mark
1 mark
1 mark

Total for Q6

8

7. (a) (i) **A, F, H**

All three conditions, and no others

1 mark

(ii) **C**

All three conditions (and no other)

1 mark

(b) (i) **X = 12 V AND Y = 12 V**

1 mark

(ii) **X = 0 V AND Y = 12 V**

1 mark

(iii) I **X = -12 V AND Y = 0 V**

1 mark

II Reverse biases the thyristor, causing it to switch off, or equivalent

1 mark

Total for Q7

6

8. (a) (i) **Signal 4**

1 mark

(ii) **Signal 5**

1 mark

(iii) **Signal 2**

1 mark

(b) (i) **Diac**

1 mark

(ii) **C**

1 mark

(c) Phase shift = $\tan^{-1}\left(\frac{R}{X_C}\right)$

1 mark

Evidence of correct interpretation of multipliers and/or X_C
= 88.4°

1 mark


Total for Q8

7

9. (a) (i) Break frequency = 195 Hz (or 195.04 Hz)
(ii) Voltage gain = 5
(iii)

1 mark

1 mark

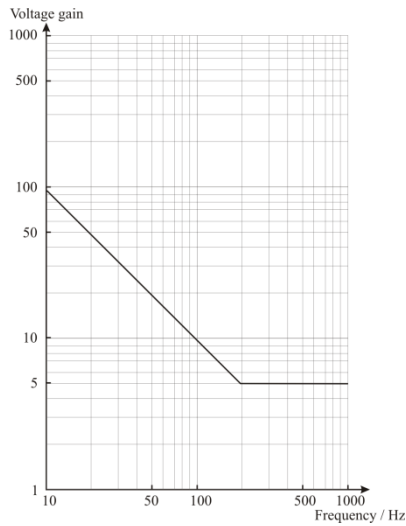

Correct shape for bass boost filter

1 mark

Break frequency as in (a)(i)


1 mark

Voltage gain as in (a)(ii)

1 mark

- (b) (i) Remove crossover distortion, or equivalent

1 mark

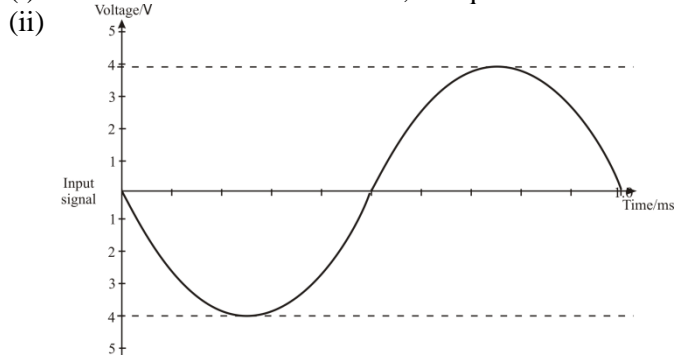

No crossover distortion

1 mark

Correct amplitude

1 mark

(iii) Max output power = $\frac{V_s^2}{8R_L}$
= 1.13 W (Accept 1 W)

1 mark

Total for Q9

9



WJEC
245 Western Avenue
Cardiff CF5 2YX
Tel No 029 2026 5000
Fax 029 2057 5994
E-mail: exams@wjec.co.uk
website: www.wjec.co.uk