Centre No.					Pape	er Refer	ence			Surname	Initial(s)
Candidate No.			6	7	3	2	/	0	1	Signature	

Paper Reference(s)

6732/01 **Edexcel GCE**

Physics

Advanced Subsidiary

Unit Test PHY2

Wednesday 17 January 2007 – Afternoon

Time: 1 hour 15 minutes

Materials required for examination	Items included with question papers
Nil	Nil

Instructions to Candidates

In the boxes above, write your centre number, candidate number, your surname and initials and your

Answer ALL questions in the spaces provided in this question paper.

In calculations you should show all the steps in your working, giving your answer at each stage. Calculators may be used.

Include diagrams in your answers where these are helpful.

Information for Candidates

The marks for individual questions and the parts of questions are shown in round brackets.

There are seven questions in this paper. The total mark for this paper is 60.

The list of data, formulae and relationships is printed at the end of this booklet.


Advice to Candidates

You will be assessed on your ability to organise and present information, ideas, descriptions and arguments clearly and logically, taking account of your use of grammar, punctuation and spelling.

is publication may be reproduced only in accordance with

N23600A W850/R6732/57570 6/6/6/6/4/7700



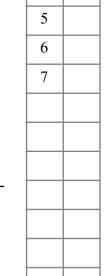

Examiner's use only

Team Leader's use only

Question Number

2

3

4

Turn over


Total



advancing learning, changing lives

		Leave blank
1.	The relationship between physical quantities can be expressed as a word equation .	
	For example	
	$Current = \frac{Charge}{Time}$	
	Time	
	Complete the following word equations.	
	Pressure =	
	Resistivity =	
	Pressure × Volume = of an ideal gas	
		Q1
	(Total 5 marks)	

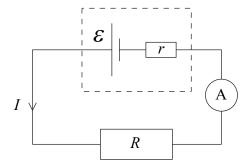
3. A student sets up the following circuit using a cell of e.m.f. \mathcal{E} and internal resistance r.



(a) Complete the equation for the total e.m.f. ${\pmb {\cal E}}$ in terms of the other quantities given in the diagram.

$$\mathcal{E} =$$
 (1)

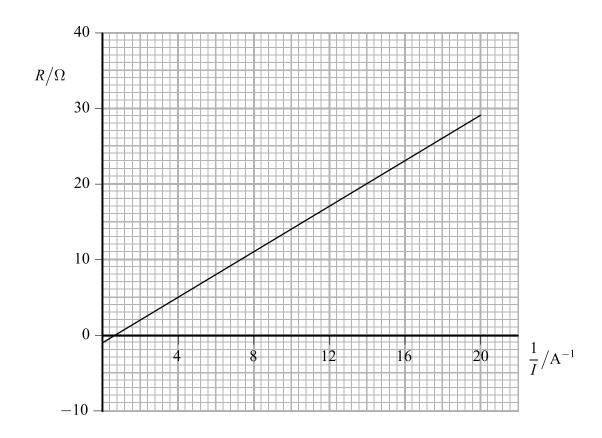(b) He measures the current I for different values of resistance R. He then plots a graph of R against 1/I.



4

Leave blank


The equation for this graph is

(i) Show how this equation is derived from the one you have stated above. (ii) Use the graph to determine the value for the e.m.f. of the cell. Show all your working. (iii) Use the graph to determine the value for the e.m.f. of the cell. Show all your working. (2) (iii) Show that when the external resistance is 5 Ω the power dissipated in that resistance is about 0.3 W. (3) (5) The student repeats the experiment adding an identical cell in series. Draw on the graph the result of this experiment.		$R = \frac{\mathcal{E}}{I} - r$
(ii) Use the graph to determine the value for the e.m.f. of the cell. Show all your working. E.m.f. =	(i)	Show how this equation is derived from the one you have stated above.
(ii) Use the graph to determine the value for the e.m.f. of the cell. Show all your working. E.m.f. =		
(ii) Use the graph to determine the value for the e.m.f. of the cell. Show all your working. E.m.f. =		
working. E.m.f. =	<i>(</i> ::\	
E.m.f. =	(11)	
E.m.f. =		
 (iii) Show that when the external resistance is 5 Ω the power dissipated in that resistance is about 0.3 W. (3) (a) (b) The student repeats the experiment adding an identical cell in series. Draw on the graph the result of this experiment. (3) 		
resistance is about 0.3 W. (3) C) The student repeats the experiment adding an identical cell in series. Draw on the graph the result of this experiment. (3)		
(c) The student repeats the experiment adding an identical cell in series. Draw on the graph the result of this experiment. (3)	(iii	
(c) The student repeats the experiment adding an identical cell in series. Draw on the graph the result of this experiment. (3)		
(c) The student repeats the experiment adding an identical cell in series. Draw on the graph the result of this experiment. (3)		
graph the result of this experiment. (3)		
		(3)
(Total 10 marks)		e student repeats the experiment adding an identical cell in series. Draw on the
		e student repeats the experiment adding an identical cell in series. Draw on the ph the result of this experiment.
		e student repeats the experiment adding an identical cell in series. Draw on the aph the result of this experiment. (3)
		e student repeats the experiment adding an identical cell in series. Draw on the aph the result of this experiment. (3)
		e student repeats the experiment adding an identical cell in series. Draw on the aph the result of this experiment. (3)
		e student repeats the experiment adding an identical cell in series. Draw on the aph the result of this experiment. (3)
		e student repeats the experiment adding an identical cell in series. Draw on the aph the result of this experiment. (3)

4. A variable resistor consisting of a wire and sliding contact has three terminals labelled K, L and M.


Leave blank

Figure 1

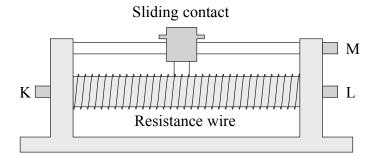

The variable resistor is connected in series with a 6.0 V supply of negligible internal resistance, an ammeter and a 20 Ω fixed resistor.

Figure 2

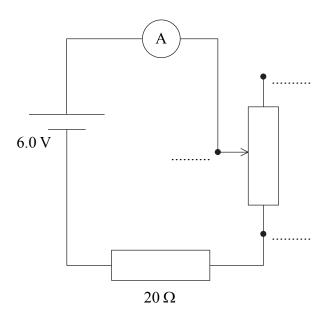

(a) Label the terminals K, L and M on Figure 2.

(1)

(b) (i)	The variable resistor has a maximum resistance of 10Ω . The resistance of the fixed resistor is 20Ω . Determine the potential difference across the resistor when the sliding contact is at the mid-point of the variable resistor.
	Potential difference =(3)
(ii)	What assumption have you made about the ammeter?
(c) The	
c) Th	What assumption have you made about the ammeter? (1) e same components can be used in a second circuit to vary the potential difference oss the fixed resistor fully from 0 V to 6.0 V. Draw the circuit diagram for this
c) The	What assumption have you made about the ammeter? (1) e same components can be used in a second circuit to vary the potential difference oss the fixed resistor fully from 0 V to 6.0 V. Draw the circuit diagram for this
c) Th	What assumption have you made about the ammeter? (1) e same components can be used in a second circuit to vary the potential difference oss the fixed resistor fully from 0 V to 6.0 V. Draw the circuit diagram for this

(b) A student heats 400 g of water from 0 °C until it has all changed to steam.

(i) Show that the energy required to raise the temperature of 400 g of water from 0 °C to its boiling point is approximately $2 \times 10^5 \, \mathrm{J}$. The specific heat capacity of water is $4200 \, \mathrm{J \, kg^{-1} \, K^{-1}}$.

.....


(

(ii) Calculate the energy required to change 400 g of water, at its boiling point, to steam. The specific latent heat of vaporisation of water is $2.3 \times 10^6 \, \mathrm{J \, kg^{-1}}$.

Energy =

(iii) Use the axes below to plot a graph of energy transferred to the water against temperature.

Energy transferred / 10⁵ J

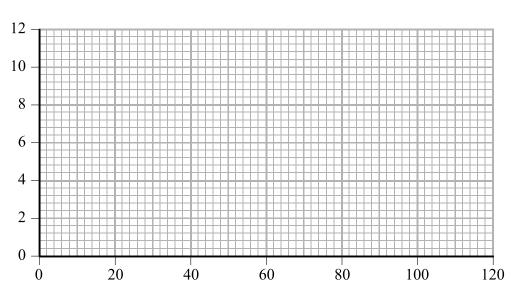


Temperature / °C

(2)

(Total 10 marks)

Leave blank

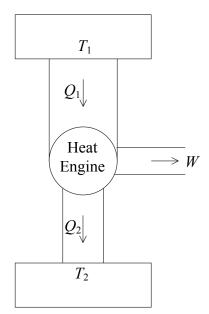6. (a) The diagram can be used to illustrate the principle of a heat engine.



State what each of the following symbols represents.

T_1	
T_2	
W	
O_2	
\mathcal{Q}_2	(4)


(b) (i) A steam engine is a type of heat engine. The maximum thermal efficiency of a certain steam engine is 24% when the steam enters at a temperature of $227\,^{\circ}$ C.

Calculate the temperature at which the st	leam leaves.
To	amparatura —
Te	emperature =
	(3)


(ii) State one way in which the efficiency of the steam engine could be increased.

(1) Q6

(Total 8 marks)

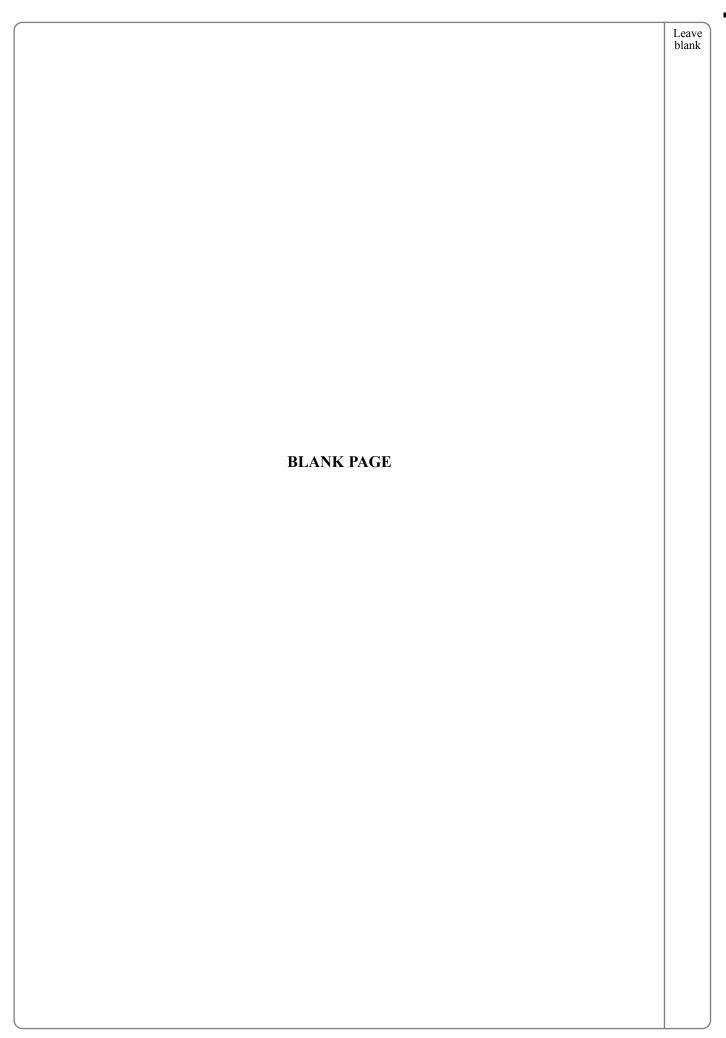

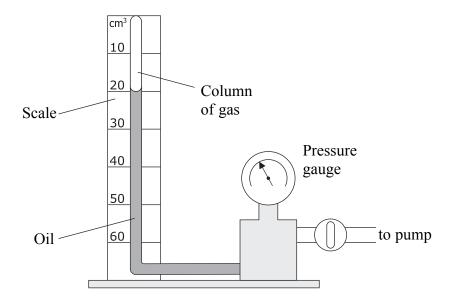A student uses the following apparatus to measure the volume occupied by a fixed mass of gas at different pressures. The temperature of the gas remains at 22 °C throughout the experiment.



(a) The volume of the gas is 20 cm^3 when the gas pressure is $200 \times 10^3 \text{ Pa}$. Calculate the pressure exerted by the gas when its volume decreases by 5.0 cm³.

Pressure = **(3)**

(b) The column of oil in the tube has a cross-sectional area of 7.9×10^{-5} m². Calculate the force exerted on the surface of the oil when the gas pressure is $200 \times 10^3 \, \text{Pa}$.

Force =

(2)

12

20 cm ³ of the gas at 35 °C. What value does she obtain? Pressure =		(Total 10 marks)
(i) She then correctly uses the pressure law to calculate the pressure exerted by 20 cm³ of the gas at 35 °C. What value does she obtain? Pressure =		
(i) She then correctly uses the pressure law to calculate the pressure exerted by 20 cm³ of the gas at 35 °C. What value does she obtain? Pressure =	(ii)	
(i) She then correctly uses the pressure law to calculate the pressure exerted by 20 cm ³ of the gas at 35 °C. What value does she obtain?		(3)
(i) She then correctly uses the pressure law to calculate the pressure exerted by		Pressure =
(i) She then correctly uses the pressure law to calculate the pressure exerted by		
	(i)	
		V
p		p A

List of data, formulae and relationships

Data

Speed of light in vacuum $c = 3.00 \times 10^8 \,\mathrm{m \ s^{-1}}$

Acceleration of free fall $g = 9.81 \,\mathrm{m \, s^{-2}}$ (close to the Earth) Gravitational field strength $g = 9.81 \,\mathrm{N \, kg^{-1}}$ (close to the Earth)

Elementary (proton) charge $e = 1.60 \times 10^{-19} \text{ C}$ Electronic mass $m_e = 9.11 \times 10^{-31} \text{ kg}$ Electronvolt $1 \text{ eV} = 1.60 \times 10^{-19} \text{ J}$ Planck constant $h = 6.63 \times 10^{-34} \text{ Js}$ Molar gas constant $R = 8.31 \text{ J K}^{-1} \text{ mol}^{-1}$

Rectilinear motion

For uniformly accelerated motion:

v = u + at

 $x = ut + \frac{1}{2}at^2$

 $v^2 = u^2 + 2ax$

Forces and moments

Moment of F about $O = F \times (Perpendicular distance from F to O)$

Sum of clockwise moments about any point in a plane = Sum of anticlockwise moments about that point

Dynamics

Force $F = m \frac{\Delta v}{\Delta t} = \frac{\Delta p}{\Delta t}$

Impulse $F\Delta t = \Delta p$

Mechanical energy

Power P = Fv

Radioactive decay and the nuclear atom

Activity $A = \lambda N$ (Decay constant λ)

Half-life $\lambda t_{\frac{1}{2}} = 0.69$

Electrical current and potential difference

Electric current I = nAQvElectric power $P = I^2R$

Electrical circuits

Terminal potential difference $V = \mathcal{E} - Ir$ (E.m.f. \mathcal{E} ; Internal resistance r)

Circuit e.m.f. $\Sigma \mathcal{E} = \Sigma IR$

Resistors in series $R = R_1 + R_2 + R_3$

Resistors in parallel $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$

Heating matter

Change of state: energy transfer = $l\Delta m$ (Specific latent heat or specific enthalpy change l)
Heating and cooling: energy transfer = $mc\Delta T$ (Specific heat capacity c; Temperature change ΔT)

Celsius temperature $\theta/^{\circ}C = T/K - 273$

Kinetic theory of matter

 $T \propto$ Average kinetic energy of molecules

Kinetic theory $p = \frac{1}{3} \rho \langle c^2 \rangle$

Conservation of energy

Change of internal energy $\Delta U = \Delta Q + \Delta W$ (Energy transferred thermally ΔQ ; Work done on body ΔW)

Efficiency of energy transfer $= \frac{\text{Useful output}}{\text{Input}}$

For a heat engine, maximum efficiency $=\frac{T_1-T_2}{T_1}$

Mathematics

 $\sin(90^{\circ} - \theta) = \cos\theta$

Equation of a straight line y = mx + c

Surface area cylinder = $2\pi rh + 2\pi r^2$

sphere = $4\pi r^2$

Volume cylinder = $\pi r^2 h$

sphere = $\frac{4}{3}\pi r^3$

For small angles: $\sin \theta \approx \tan \theta \approx \theta$ (in radians)

 $\cos\theta \approx 1$

Experimental physics

Percentage uncertainty $= \frac{\text{Estimated uncertainty} \times 100\%}{\text{Average value}}$

