

1(a)(i)	Ammeter		B1
(ii)	Voltmeter		B1
(b)	$I$ : current		B1
	$\Delta t$ : time (interval / duration)		B1
(c)(i)	$I = 7.5 \times 10^3 / 1500$ $I = 5.0$ (A)		C1 A1
(ii)	$V = P / I$ $V = 1.2 \times 10^3 / 5.0$ $V = 240$ (V)	(allow other variants) (possible e.c.f) (-1 for missing k or $10^3$ factor)	C1 C1 A1
(iii)	$E = 1.2 \times 10^3 \times 1500$ $E = 1.80 \times 10^6$ (J)	(-1 for missing k or $10^3$ factor) penalise once only in (ii) & (iii)	C1 A1
(iv)	units = $1500/3600 \times 1.2 = 0.5$ cost = $0.5 \times 6.4 = 3.2$ (p)	units = $1.8 \times 10^6 / 3.6 \times 10^6 = 0.5$ (possible (e.c.f if (iii) used)	C1 A1
2(a)	$R = V / I$ symbols defined: $R$ = resistance, $V$ = p.d. / voltage and $I$ = current ( $V = IR$ with all symbols defined scores 1/ 2) ( $R$ = p.d. / voltage per unit current scores 2/2) ( $R$ = p.d. / voltage per unit amp / A scores 1/ 2)		C1 A1
(b)	Resistance decreases as temperature increases. Correct <u>curve</u> with $R$ decreasing as temperature increases.		B1 B1
(c)(i)	Resistance increases (as $V$ increases) Temperature increases / atoms vibrate more / more electron collisions (with atoms)		B1 B1
(ii)	1. $P = 24 \times 2$ $P = 48$ (W)		C1 A1
	2. $V = 12$ (V) when current is 2.0 (A)	(Allow $V = 11.0$ V from graph)	C1
	$R = 12 / 2.0 = 6.0$ ( $\Omega$ )		A1
	3. $R_T = 6.0 + 5.0 = 11.0$ ( $\Omega$ )	(possible e.c.f)	B1
	4. $V_L = 11.0 \times 2.0 = 22$ (V) $r = (24-22) / 2.0 = 1.0$ ( $\Omega$ )	$R_{circuit} = 48 / 2.0^2 = 12$ ( $\Omega$ ) $r = 12.0 - 11.0 = 1.0$ ( $\Omega$ )	C1 A1
3(a)	$\rho = RA / L$ Symbols defined: $\rho$ = resistivity, $A$ = <u>cross-sectional area</u> , $R$ = resistance and $L$ = length ( $R = \rho L/A$ with all symbols defined scores 1/ 2)		M1 A1
(b)(i)	$A = \rho L / R$ $A = 4.3 \times 10^{-6} \times 1.2 \times 10^2 / 5.0$ $A = 1.0(3) \times 10^{-8}$ ( $m^2$ )	(-1 for using $L$ as 2.0 mm)	C1 C1 A1
(ii)	$t = 1.0(3) \times 10^{-8} / 2.0 \times 10^{-3}$ $t = 5.1(6) \times 10^{-6}$ (m)	(possible e.c.f)	B1

- 4(a) Sum of currents = zero (at junction) /  
sum of currents in = sum of currents out (at junction) B1  
 Charge is conserved. B1
- (b)(i)  $V = V_0 \times R_2 / (R_1 + R_2)$  |  $R = V / I$  and  $R = R_1 + R_2$  C1  
 $V = 6.0 \times 400 / (1200 + 400)$  |  $I = 6.0 / 1600 = 3.75 \times 10^{-3}$  (A) C1  
 $V = 1.5$ (V) |  $V = 3.75 \times 10^{-3} \times 400$  A0  
 (Answer of 4.5 (V) scores 1/ 2) |  $V = 1.5$ (V)
- (ii) 1.  $R_D = 1.5 / 0.1 = 15$  ( $\Omega$ ) C1  
 $R = R_1 R_2 / (R_1 + R_2) / 1/R_T = \sum 1/R_i$  C1  
 $R = 400 \times 15 / (400 + 15) = 14.5 = 15$  ( $\Omega$ ) (possible e.c.f) A1
2.  $V \approx 6.0 \times 15 / (1200 + 15)$  |  $I \approx 6.0 / 1200 + 15 \approx 4.98 \times 10^{-3}$  (A) C1  
 $V \approx 0.07$  (V) |  $V \approx 4.98 \times 10^{-3} \times 15 = 0.07$  (V) A1  
 (Answer of 5.93 (V) scores 1/ 2)
3. Resistance of device is small(er) / current in device is small(er) /  
 p.d. across device is small(er) B1
- 5(a) Fig. 5.1: (long straight) wire / conductor B1  
 Fig. 5.2: (single) coil / two (parallel) wires B1
- (b)(i) Zero B1  
 (ii) 1.  $F = BIL$  C1  
 $F = 1.2 \times 10^{-2} \times 0.30 \times 1.5 \times 10^{-2}$  C1  
 $F = 5.4 \times 10^{-5}$  (-1 for L = '1.5') A1  
 Unit: newton / N (do not allow n) B1  
 2.(Fleming's) L.H.R B1
- 6(a) (Moving) electrons behave like a wave B1
- (b)(i)  $\lambda = h / p$  |  $\lambda = h / mv$  M1  
 $\lambda = \text{wavelength, } p = \text{momentum}$  |  $\lambda = \text{wavelength, } m = \text{mass}$   
 and  $v = \text{velocity / speed}$  A1
- (ii) 1.  $E = 0.01 \times 10^6 \times 1.6 \times 10^{-19}$   
 $10^6$  factor in answer M1  
 use of  $1\text{eV} = 1.6 \times 10^{-19}$  (J) in answer M1  
 $E = 1.6 \times 10^{-15}$  (J) A0
2.  $E_k = \frac{1}{2} m v^2$  C1  
 $1.6 \times 10^{-15} = 0.5 \times 9.1 \times 10^{-31} \times v^2$  C1  
 $v = 5.9(3) \times 10^7$  ( $\text{ms}^{-1}$ ) A1
3.  $\lambda = 6.63 \times 10^{-34} / 9.1 \times 10^{-31} \times 5.9(3) \times 10^7$  C1  
 $\lambda = 1.2(3) \times 10^{-11}$  (m) (possible e.c.f) A1
- (c) Shorter wavelength B1  
 Mass of proton is larger (than an electron's). B1

7(a) Any five from: B1 x 5

- Photons are involved /  $E = hf$
- Surface electrons are involved.
- One-to-one exchange of energy between photon and electron
- Electrons carry negative charge, therefore removal means reduction in (negative) charge (of plate).
- Electron released when photon energy > workfunction (energy).
- Electron emission related to threshold frequency.
- Energy conserved in the interaction (between photon and electron).
- Einstein's equation mentioned ( $hf = \frac{1}{2}mv^2 + \phi$ ).

Any two from:

More photons (in a given time).

More electrons are removed (in a given time)

The plate loses charge quicker.

B1 x 2

- (b)(i) 1.  $f = 3.0 \times 10^8 / 6.3 \times 10^{-7}$  C1  
 $f = 4.7(6) \times 10^{14}$  A1  
 unit: hertz / Hz B1  
 $2.E = hf$  C1  
 $E = 6.63 \times 10^{-34} \times 4.76 \times 10^{14} = 3.1(6) \times 10^{-19}$  (J) (possible e.c.f) A1  
 (ii)  $N = 1 \times 10^{-3} / 3.16 \times 10^{-19}$  (possible e.c.f) C1  
 $N = 3.1(7) \times 10^{15}$  (s<sup>-1</sup>) A1  
 (iii) Energy of photon is greater/ blue light has shorter wavelength. B1  
 Reduced (rate) of photons / fewer photons (in a given time) B1

8 Any two from: B1 x 2

- Travel at the speed of light /  $3 \times 10^8$  (ms<sup>-1</sup>)(in vacuum).
- Travel in vacuum / space.
- Transverse waves.
- Oscillating electric and magnetic fields.
- Can be reflected / diffracted / refracted / polarized etc.

Principal radiation named.

B1 x 3

Correct wavelength. (see guide below)

B1 x 3

Guide:	$\gamma$ -rays	$10^{-16} - 10^{-12}$ m
	X-rays	$10^{-11} - 10^{-9}$ m
	u.v	$\sim 10^{-8}$ m
	visible	$\sim 10^{-7}$ m
	i.r	$\sim 10^{-6}$ m
	microwaves	$10^{-4} - 10^{-2}$ m
	radio waves	$> 10^{-1}$ m

(If unit for wavelength not given, then penalty of -1)

QWC applied to Q7 & Q8

Maximum of 4 marks