

Question	Expected Answers	Marks
<p>1</p> <p>(a)</p> <p>(b)</p> <p>(c)</p>	<p>10^{-3} to 10^{-1} (m) (Allow range: 0.0005 m to 0.15 m)</p> <p>Any <u>one</u> from:</p> <ol style="list-style-type: none"> 1. Travels at the speed of light / 3×10^8 (ms^{-1} in vacuum) 2. Travel in vacuum (Allow 'free space' but not just 'space') 3. Transverse (wave) / can be polarised 4. Consists of oscillating electric and magnetic fields 5. Can be reflected / refracted / diffracted / shows interference 6. (Behave as) photon(s) 7. Warms food <p>(e.m.f. =) $\frac{W}{Q}$ / (e.m.f. =) $\frac{78}{24}$</p> <p>(e.m.f. =) $3.25 \approx 3.3$ (V)</p>	<p>B1</p> <p>B1</p> <p>C1</p> <p>A1</p> <p>[Total: 4]</p>
<p>2</p> <p>(a)</p> <p>(b)</p>	<p><u>Energy</u> (transformed by a device working) at 1 kW for 1 hour</p> <p>$E = Pt$ / $5.8 = 0.12 \times \text{time}$ / (time =) 48.3 (hr)</p> <p>(time =) $1.74 \times 10^5 \approx 1.7 \times 10^5$ (s)</p>	<p>B1</p> <p>C1</p> <p>A1</p> <p>[Total: 3]</p>

Question	Expected Answers	Marks
3		
(a)	Line crosses 'y-axis' at 1.4 (V) / $V = E$ or 1.4(V) when $I = 0$ $V = E - Ir$, since $I = 0$ (Hence $V = E$ or 1.4(V))	B1
(b)(i)	(Graph extrapolated to give) current = 2.0 (A) (Allow tolerance $\pm 0.1A$)	B1
(b)(ii)	$E = I_{(\max)} r$ gradient = r (Ignore sign) $(r = \frac{1.4}{2.0})$ (Attempt made to find gradient) $r = 0.7(0) (\Omega)$ $r = 0.7(0) (\Omega)$ (Possible ecf)	C1 A1
(b)(iii)	(excessive) heating of <u>cell</u> / energy wasted <u>internally</u> / cell might 'explode' / <u>cell</u> goes 'flat' (quickly)	B1
		[Total: 5]

Question	Expected Answers	Marks
4		
(a)	Correct circuit for both lamps in parallel (ignore ammeter here) Ammeter placed correctly in <u>series</u> with P	B1 B1
(b)(i)	The resistance of LDR/circuit changes (as light intensity changes) When blade blocks light, resistance of LDR/circuit is large(r) (ora) Correct statement about p.d (Possible ecf)	B1 B1 B1
(b)(ii)1.	(V = 5.0 – 3.0) 2.0 (V) (Allow 1 sf answer)	B1
(b)(ii)2.	$V = \frac{R_2}{R_1 + R_2} \times V_0$ $(3.0 = \frac{R}{R + 2200} \times 5.0)$ $R = 3300 (\Omega)$ <div style="display: inline-block; vertical-align: middle; margin-left: 20px;"> $I = 2.0/2200 / 9.1 \times 10^{-4} (A)$ $(R = 3.0 / 9.1 \times 10^{-4})$ $R = 3300 (\Omega) \quad \text{Possible ecf}$ </div> <p>(For $V_{LDR} = 2.0 \text{ V}$, $R = 1.47 \text{ k}\Omega$. This scores 1/2) (If 3.5 V given in (b)(ii)1., then $R = 940 \Omega$. This scores 2/2)</p>	C1 A1
		[Total: 8]

Question	Expected Answers	Marks
5 (a)	(resistance =) p.d./current (Allow use of 'voltage') ((resistance =) ratio of p.d. to current 2/2) ((resistance =) voltage per (unit) current 2/2) ((R =) V/I scores 1/2) ((resistance =) voltage per (unit) ampere scores 1/2)	B2
(b)(i)	Parallel	B1
(b)(ii)1.	$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$ / $\frac{1}{R} = \frac{3}{18}$ (R =) 6.0 (Ω) (Allow 1 sf answer)	C1 A1
(b)(ii)2.	$P = \frac{V^2}{R}$ (Allow $P = VI$ or $P = I^2R$) ($P = \frac{12^2}{6}$) $P = 24$ (W) (Possible ecf from (b)(ii)1.) (If 18 Ω used, $P = 8$ (W). Allow 1/2)	C1 A1
(b)(ii)3.	$R = \frac{\rho L}{A}$ (Allow other subject) $18 = \frac{6.9 \times 10^{-6} \times 0.85}{A}$ $A = 3.26 \times 10^{-7} \approx 3.3 \times 10^{-7} \text{ (m}^2\text{)}$ ($3.3 \times 10^{-5} \text{ (m}^2\text{)}$ scores 2/3) (If $R = 6.0 \Omega$ then $A = 9.8 \times 10^{-7} \text{ (m}^2\text{)}$. This scores 2/3)	C1 C1 A1 [Total: 10]

Question	Expected Answers	Marks
6		
(a)	Arrow towards the cloud	B1
(b)	Into the page (No ecf from (a))	B1
(c)(i)1.	$I = \frac{\Delta Q}{\Delta t}$ (Allow other subject, with or without Δ) (charge =) 7800×0.23 $1.794 \times 10^3 \approx 1.8 \times 10^3$ (C) (Ignore minus sign) $(1.8 \times 10^6$ (C) scores 2/3)	C1 C1 A1
(c)(i)2.	(number =) $\frac{1.79 \times 10^3}{e}$ (Possible ecf) (number =) $1.12 \times 10^{22} \approx 1.1 \times 10^{22}$	C1 A1
(c)(ii)	$F = BIL$ (F =) $42 \times 10^{-6} \times 7800 \times 250$ (F =) $81.9 \approx 82$ (8.2×10^7 scores 2/3) newton / N / TAm / Jm ⁻¹	C1 C1 A1 B1
		[Total: 11]

Question	Expected Answers	Marks
7 (a)	Any <u>five</u> from: <ol style="list-style-type: none"> 1. Photoelectric (effect) mentioned 2. Photon(s) mentioned in correct context / $E = hf$ 3. One-to-one 'interaction' between photon & electron 4. Surface electrons are involved 5. Electron released / photoelectric (effect) when photon energy $> / =$ work function (energy) 6. Electrons emitted / photoelectric (effect) when frequency $> / =$ threshold frequency 7. Energy is conserved (in the 'interaction' between photon and electron) 8. Reference to Einstein's equation: $hf = \phi + KE_{(\max)}$ 	B1 × 5
	[QWC: Spelling and Grammar]	B1
(b)(i)1.	(energy of photon = 2.2 + 0.3) 2.5 (eV)	B1
(b)(i)2.	(energy =) $2.5 \times \frac{1.6 \times 10^{-19}}{4.0 \times 10^{-19}}$ (Possible ecf from (b)(i)1.) 4.0×10^{-19} (J) (Allow 1 sf answer)	C1 A1
(b)(ii)	$(f =) \frac{4.0 \times 10^{-19}}{h}$ (Possible ecf) $(f =) \frac{4.0 \times 10^{-19}}{6.63 \times 10^{-34}}$ $(f =) 6.03 \times 10^{14} \approx 6.0 \times 10^{14}$ (Hz) (Allow 6×10^{14})	C1 A1
(c)	Each photon has more energy / There are fewer photons (in a given time because intensity is the same) Smaller current	B1 B1 [Total: 13]

Question	Expected Answers	Marks
8	<p>Any <u>five</u> from:</p> <ol style="list-style-type: none">1. Electrons travel / move as a wave2. Electrons show diffraction / interference (effects)3. Diffraction (is noticeable) when λ comparable to 'gap' size4. Mention of de Broglie equation: $\lambda = \frac{h}{mv}$5. λ, h, m and v correctly identified in 4. above6. Graphite / matter / atoms / nuclei / small gap(s) needed to diffract electrons7. Experimental evidence: '(diffraction) rings' / 'fringes' (Can score on a diagram) <p>[QWC: Organisation]</p>	<p>B1 × 5</p> <p>B1</p> <p>[Total: 6]</p>