

ELECTRICAL CIRCUITS

2022/01	Mark Scheme	June 2001
1. (a)(i)	Coulomb / C (Allow Ampere second / As)	B1
(i)	Voltmeter	B1
(c)(i)	$P = VI$ $V = 36 / 3.0$ p.d. = 12 (V)	(Allow other variant) C1 C1 A1
(ii)	$E = 36 \times 600$ energy = $2.1(6) \times 10^4$ (J) = 2.2×10^4 (J)	C1 A1
(i)	$\Delta Q = IVt / Q = It$ $\Delta Q = 3.0 \times 600$ charge = 1.8×10^3 (C)	(Allow other variant) C1 C1 A1
(v)	$N = 1.8 \times 10^3 / 1.6 \times 10^{-19}$ (Possible ECF) number = $1.1(3) \times 10^{22} \approx 1.1 \times 10^{22}$	C1 A1
		[Total 12]
2. (a)	$R = V/I$ Symbols defined: R = resistance, V = p.d. and I = current (Allow use of 'voltage' instead of 'p.d.') (Resistance = p.d. per (unit) current scores 2/2) ($V = IR$ with all symbols defined scores 1/2) (Resistance = p.d. <u>per</u> (unit) amp / A scores 1/2) (Resistance = volts <u>per</u> (unit) current scores 1/2) (Resistance = volts <u>per</u> (unit) ampero scores 0/2)	M1 A1
(c)(i)	$\propto V/I \Rightarrow V = \text{constant}$ Current \propto p.d. / p.d. \propto current = constant and (metallic conductor at) constant temperature (Allow symbols n (c)(i) if defined in (a))	C1 A1
(i)	One correct response scores 1/2 Three correct responses scores 2/2	
(c)	Ammeter in series Voltmeter across cell or the thermistor (No credit if the meters or their positions are contradictory)	B1 B1
		[Total 8]

3. (a)(i) $R = 50 \Omega$ C1
 $I = 3.0 / 50$ C1
 current = 0.06 (A) A1

(i) $P = V^2 / R = 3.0^2 / 50$ C1
 power = 3.0×0.06
 power = 0.18 (W) (Possible ECF) A1

(b)(i) 'Constant temperature implied (w/e)' B1
 (Do not allow reference to Ohm's law or to 'heating')

(ii) 1. 40Ω B1
 2. $A = \pi \times (1.0 \times 10^{-3})^2 = 3.1(4) \times 10^{-6} (\text{m}^2)$ B1
 $R = \rho L/A$ (A low other variant) C1
 $40 = 5.4 \times 10^{-8} \times L / 3.1(4) \times 10^{-6}$ (Possible ECF) C1
 $L = 0.23(3) (\text{m}) \approx 0.23 (\text{m})$ A1
 Length is 9000 larg, therefore must be scaled (w/e) B1

(Total 12)

4. (a)(i) p.d. = Energy 'lost' by charge(s)/electron(s) (as heat / light) B1
 e.m.f. = Energy 'gained' by charge(s)/electron(s) (as electrical) B1
 (p.d. linked to energy transfer to heat/light and e.m.f. to energy transfer to electrical scores 1/2)

(ii) Tick only for $\vee C$ B1

(b) (Sum of) e.m.f.s = sum / total of p.d.s / sum of voltages (in a loop) B1
 (Do not allow equation unless the symbols are defined)
 Energy is conserved B1

(c)(i) $R = 1.28 / 0.80$ C1
 resistance = 1.6(3) (Ω) A1

(ii) $R = R_0 + R_1 / 1.60 = r + 1.10 / r = (1.28 - 0.8 \times 1.1) / 0.8$ C1
 $r = 0.5(2) (\Omega) = 0.5 (Ω)$ (Possible ECF) A1

(iii) p.d. = $1.10 \times 0.80 = 0.88 (\text{V})$ (Possible ECF) B1

(Total 16)

5. (a)(i)	Decreases	B1
(i)	Decreases	B1
(ii)(i)	$V = V_s \times R_2 / (R_1 + R_2)$ $V = 5.0 \times 420 / (1000 + 420)$ p.d. = 1.4(*) (V) = 1.5 (V) (Answer of 3 b(2) (V) scores 2/3)	$V = R$ and $R = R_1 + R_2$ $I = 5.0 / 1420 = 3.52 \times 10^{-3}$ (A) p.d. = $3.52 \times 10^{-3} \times 420 = 1.5$ (V) A1
(ii)	1. $R = R_1 R_2 / R_1 + R_2 = 420 \times 50 / 420 + 50 = 30$ (= 44.7 (0)) 2. $V = 5.0 \times 45 / (1000 + 45)$ p.d. = 0.21(*) (V) = 0.22 (V) (Allow $V = 0.2$ (V) as long as working is shown)	B1 C1 C1 A1
		[Total: 6]
6. (a)(i)	Correct direction of field (clockwise) Concentric circles round wire (Judge by eye) Increasing separation between successive circles (> three incs)	B1 M1 A1
(i)	1. (Fleming's) Left hand rule B1 2. To the left / Towards the other wire (No ECF from (a)(i)) Can score on Fig.6.1	B1
(b)(i)	$B = F / IL$ F = force, I = current and L = length of conductor / wire(in the field) (B = force per (unit) current length of conductor scores 2/2) (F = BIl , with symbols defined scores 1/2) (B = force per (unit) ampere metre scores 1/2) (B = force when current is 1A and length is 1m scores 3/2)	M1 A1
	The conductor / wire normal to field	A1
(ii)	$F = 2.5 \times 10^{-3} \times 3.0 \times 2.0$ force = 1.5×10^{-3} (N)	C1 A1
		[Total: 10]

7. (a)	hf	Photon energy / quantum of energy	B1
	ϕ	Work function (energy for the metal)	B1
	$\frac{1}{2}mv_{\text{cut}}^2$	Maximum K.E. of electron	B1
(b)(i)	$f = 3.0 \times 10^{14} / 6.5 \times 10^{-19}$		C1
	frequency = $4.6(2) \times 10^{14} \approx 4.6 \times 10^{14}$		A1
	unit: hertz / Hz / s		B1
(ii)	$E = hf$		C1
	$\phi = 6.63 \times 10^{-34} \times 4.62 \times 10^{14} = 3.0(6) \times 10^{-19} \text{ J} = 3.1 \times 10^{-18} \text{ J}$ (Possible ECF)		C1
	$\phi = 3.0(6) \times 10^{-19} / 1.6 \times 10^{-19}$		C1
	work function energy = $1.9(4) \text{ eV}$		A0
	(Answer of 1.81(eV) without supporting calculations scores 2/3)		
(c)	(Rate of / number of) electrons / photons increases		C1
	(Rate of / number of) photons double, ∴ (Rate of / number of) electrons double		A1
		[Total: 11]	
8.	Electrons behave like a wave		C1
	Moving / travelling electrons behave like a wave		A1
	Interference / diffraction effects are associated with 'waves'		H1
	Wavelength of electron is 'comparable to' / same as / atomic size / separation		B1
	Sensible experimental detail, e.g.: 'Diffraction rings' or 'Diffracted by carbon'		B1
	$\lambda = h/p$ / $\lambda = h/mv$		B1
	λ for the person calculated, $\lambda = 10^{-18} \text{ m}$		B1
	λ of person (very) small (compared with gap to show diffraction)		B1
		[Total: 8]	

- Q. Any one from: B'x1
- Travel at the speed of light / $3 \times 10^8 \text{ ms}^{-1}$ (in vacuum)
 - Travel in vacuum
 - Transverse waves
 - Consists of oscillating electric and magnetic fields
 - Can be reflected / diffracted / refracted / polarised etc.

Practical radiation named M'1x3
 One sensible application for each (See guide below) A'x3

Guide:

γ -rays	Sterilization (of food) / radiotherapy / treatment of cancer
X-rays	(X-ray) pictures of bones / flaws in pipes
U.V.	Sterilization (equipment) / fluoresce (powders/paint) / sunbeds
visible	Photography / seeing things with eye
I.R.	Security / I.R. camera / (TV) remote control
microwaves	microwave oven for cooking / communication / mobile phones
radio (waves)	Communication / commercial broadcast ('not just radio') / TV

[Total: 7]

QWC applied to Q8 and Q9
 (See marking criteria) [4]