

1. (a) resistors in series add to  $20\ \Omega$  and current is  $0.60\ \text{A}$   
*accept potential divider stated or formula* B1

so p.d. across XY is  $0.60 \times 12 (= 7.2\ \text{V})$   
*gives  $(12/20) \times 12\ \text{V} (= 7.2)\ \text{V}$*  B1

(b) (i) the resistance of the LDR decreases M1  
 (so total resistance in circuit decreases) and current increases A1

(ii) resistance of LDR and  $12\ \Omega$  (in parallel)/across XY decreases B1  
 so has smaller share of supply p.d. (and p.d. across XY falls)  
*alternative  $I$  increases so p.d. across  $8.0\ \Omega$  increases; so p.d. across XY falls* B1

[6]

2. (a) Line crosses 'y-axis' at  $1.4\ (\text{V}) / V = E$  or  $1.4(\text{V})$  when  $I = 0$   
 $V = E - Ir$ ; since  $I = 0$  (Hence  $V = E$  or  $1.4(\text{V})$ ) B1

(b) (i) (Graph extrapolated to give) current =  $2.0\ (\text{A})$   
 (Allow tolerance  $\pm 0.1\ \text{A}$ ) B1

(ii)  $E = I_{(\text{max})} r$       gradient =  $r$  (Ignore sign) C1  
 $(r = \frac{1.4}{2.0})$       (Attempt made to find gradient)  
 $r = 0.7(0)\ (\Omega)$        $r = 0.7(0)\ (\Omega)$       (Possible ecf) A1

(iii) (excessive) heating of cell / energy wasted internally /  
 cell might 'explode' / cell goes 'flat' (quickly) B1

[5]

3.	(a)	No current (in circuit) / 'open' circuit / p.d. between X and Y is 5.0 V	B1	
	(b)	$V = \frac{R_2}{R_1 + R_2} \times V_0$ / $\frac{V_1}{V_2} = \frac{R_1}{R_2}$ / $I = \frac{3.4}{168} (= 2.02) \times 10^{-2}$ mA	C1	
		$3.4 = \frac{168}{168 + R} \times 5.0$ / $\frac{1.6}{3.4} = \frac{R}{168}$ / $R = \frac{1.6}{2.02 \times 10^{-2}}$	C1	
		resistance $\approx 79$ (k $\Omega$ ) (Total resistance of 250 k $\Omega$ scores 2/3)	A1	[4]
4.	(a)	<u>Energy</u> (transformed by a device working) at 1 kW for 1 hour	B1	
	(b)	$E = Pt / 5.8 = 0.12 \times \text{time} / (\text{time} =) 48.3$ (hr)	C1	
		(time =) $1.74 \times 10^5 \approx 1.7 \times 10^5$ (s)	A1	[3]
5.	(a)	(i) Correctly selected and re-arranged: $\rho = RA/L$ ; symbols defined: $A =$ <u>cross-sectional</u> area, $R =$ resistance, $L =$ length	M1 A1	
		(ii) $\rho$ is independent of dimensions of the specimen of the material/AW	B1	
	(b)	$R = 1.7 \times 10^{-8} \times 0.08 / 3.0 \times 10^{-4}$	C1	
		$R = 4.5(3) 10^{-6}$ ( $\Omega$ )	A1	[5]
6.	(a)	(i) $Q = It$ with knowledge of what the symbols mean (1) $= 0.050 \times 4.0 \times 3600$ (1) $= 720$ (C) (1)	3	
		(ii) $E = QV$ with knowledge of what the symbols mean (1) $= 720 \times 6.0 = 4320$ (J) (1)	2	
	(b)	chemical (potential) (energy) (1)	1	
	(c)	(i) $I = 4.0/48 = 0.5/r$ (ie by proportion or by finding current) (1) $r = 24/4 = 6$ ( $\Omega$ ) (1)	2	
		(ii) $E = V^2t/R$ with knowledge of what the symbols mean (1) $= 4.02 \times 2700 / 48$ (1) $= 900$ (J) (1)	3	

(iii)  $900/4320 = 5/24 = (0.208)$  (1) 1

(d) because the p.d. across it (4.5 – 4.0) is known only to 1 sig.fig. 1

[13]

7. (i) **M** marked at the end of the graph B1

(ii) current is 5 (A) and p.d is 6 (V) C1

$$P = VI \setminus p = 6.0 \times 5.0$$

$$(Allow \ p = I^2 R \text{ or } p = V^2 \setminus R)$$

power = 30 (W) A1

(iii) 1.  $V_L = 1.0$  (V) (From the  $I/V$  graph)  $\setminus R_L = 1.0/2.0$  or  $0.5$  ( $\Omega$ ) M1

$$V_R = 1.2 \times 2.0 \setminus R_T = 1.2 + 0.5$$
 M1

$$V = 1.0 + 2.4 \setminus V = 1.7 \times 2.0$$
 A1

voltmeter reading = 3.4 (V) A0

2.  $V_r = 4.5 - 3.4$  (= 1.1 V)  $\setminus 4.5 = 2.0r + 3.4$  (Possible ecf) C1

$$r = \frac{1.1}{2.0}$$

$r = 0.55$  ( $\Omega$ ) (1.05  $\Omega$  scores 0/2 since the lamp is ignored) A1

[9]

8. (i) p.d.: energy transferred per unit charge from electrical form (into other forms, e.g. light/heat) B1

e.m.f.: energy transferred per unit charge into electrical form (from other forms, e.g. chemical/mechanical) B1

(ii)  $J C^{-1}$  B1

[3]

9. (a) (i) resistance decreases/falls/drops (with increase in temperature) B1

(ii)  $100 \pm 10 \Omega$  B1

(iii) for low temps  $\Delta R$  is large for  $\Delta\theta$  and at high temps  $\Delta R$  is small for same  $\Delta\theta$ ; so sensitivity decreases (continuously) from low to high temperatures B1

- |     |       |   |    |
|-----|-------|---|----|
| (b) | (i)   | correct circuit symbol                      | B1 |
|     | (ii)  | connections in parallel with fixed resistor | B1 |
|     | (iii) | $R_{th} = 100$ to $105 \Omega$              | B1 |
|     |       | $R_{tot} = 200 + R_{th}$                    | M1 |
|     |       | $I = V/R_{tot} = 6/R_{tot}$ (= 0.02 A)      | A1 |
|     | (iv)  | $(V = IR = 0.02 \times 200) = 4.0$ (V)      | A1 |

**[10]**

- |            |  |    |
|------------|--|----|
| <b>10.</b> | Current is (directly) proportional to potential difference (for a metal conductor) provided the temperature \ (all) physical condition(s) remains constant | M1 |
|            |  | A1 |

**[2]**