

**ADVANCED SUBSIDIARY GCE UNIT
D&T: SYSTEMS AND CONTROL TECHNOLOGY**

2521/02

**INSERT
WEDNESDAY 10 JANUARY 2007**

Morning
Time: 48 minutes



INSERT – FORMULAE SHEET

INSTRUCTIONS TO CANDIDATES

- This insert is to be used as required.

This document consists of **4** printed pages.

General

Area of rectangle	$= l \times w$
Area of triangle	$= \frac{b \times h}{2}$
Area of circle	$= \frac{\pi d^2}{4}$
Circumference of circle	$= \pi d$
Volume of rectangular prism	$= l \times w \times h$
Volume of cylinder	$= \text{area of base circle} \times h$
Volume of cone	$= \frac{\text{area of base circle} \times h}{3}$

Electrical and Electronic Systems

$$V = I \times R$$

$$W = V \times I$$

Resistors in series	$R_{total} = R_1 + R_2 + R_3 \text{ etc.}$
---------------------	--

Resistors in parallel	$\frac{1}{R_{total}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \text{ etc.}$
-----------------------	--

OR

$$R_{total} = \frac{R_1 \times R_2}{R_1 + R_2}$$

Potential Divider	$V_{out} = V_{in} \times \frac{R_2}{R_1 + R_2}$
-------------------	---

Capacitor time constant	$T = C \times R$
-------------------------	------------------

Capacitors in series	$\frac{1}{C_{total}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \text{ etc.}$
----------------------	--

Capacitors in parallel	$C_{total} = C_1 + C_2 + C_3 \text{ etc.}$
------------------------	--

Mark space ratio $= \frac{T_{on}}{T_{off}}$

Astable frequency (f) $= \frac{1}{1.4 \times C_1 \times R_1}$

555 astable frequency (f) $= \frac{1.44}{(R_a + 2R_b)C}$

output high time $= 0.693(R_a + R_b)C$

output low time $= 0.693(R_b)C$

555 monostable time constant

on time $= 1.1R_a C$

Voltage gain $= \frac{V_{out}}{V_{in}}$

Non inverting amplifier $V_{out} = V_{in} \times \frac{(R_f + R_{in})}{R_{in}}$

Inverting amplifier $V_{out} = -V_{in} \times \frac{R_f}{R_{in}}$

Summing amplifier $V_{out} = -R_f \times \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$ etc.

Differential amplifier $V_{out} = \frac{-R_f}{R_a} \times (V_2 - V_1)$

MOSFET $g_m = \frac{\Delta I_d}{\Delta V_{gs}}$

Battery life battery capacity = current x time

Mechanical Systems

Moment = force x perpendicular distance

Stress $= \frac{\text{force}}{\text{cross sectional area}}$

Strain $= \frac{\text{change in length}}{\text{original length}}$

Young modulus of elasticity $= \frac{\text{stress}}{\text{strain}}$

Work done = force x distance moved

Power = force x velocity

Work done = torque x angle turned

Power = torque x angular velocity

Pneumatic Systems

Force = pressure x area

Compression ratio = $\frac{\text{gauge pressure} + \text{atmospheric pressure}}{\text{atmospheric pressure}}$

Volume of air used = area x stroke x compression ratio

Lifting load = vacuum level x area