

ADVANCED GCE UNIT

2525/01

D&T: SYSTEMS AND CONTROL TECHNOLOGY

UNIT 8: Systems and Control Technology 2
INSERT – FORMULAE SHEET
JANUARY 2007



INSTRUCTIONS TO CANDIDATES	
•	This insert is to be used as required.

This document consists of 4 printed pages.

SP (NH) T21873/6 © OCR 2007 [K/100/3470] OCR is an exempt Charity **[Turn over**

General

Area of rectangle
$$= l \times w$$

Area of triangle
$$= \frac{b \times h}{2}$$

Area of circle
$$= \frac{\pi d^2}{4}$$

Circumference of circle
$$=\pi d$$

Volume of rectangular prism
$$= l \times w \times h$$

Volume of cylinder = area of base circle
$$x h$$

Volume of cone =
$$\frac{\text{area of base circle x } h}{2}$$

Electrical and Electronic Systems

$$V = I \times R$$

$$W = V \times I$$

Resistors in series
$$R_{total} = R_1 + R_2 + R_3$$
 etc.

Resistors in parallel
$$\frac{1}{R_{total}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \ \ \text{etc.}$$

OR

$$R_{total} = \frac{R_1 \times R_2}{R_1 + R_2}$$

Potential Divider
$$V_{out} = V_{in} \times \frac{R_2}{R_1 + R_2}$$

Capacitor time constant
$$T = C \times R$$

Capacitors in series
$$\frac{1}{C_{total}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \text{ etc.}$$

Capacitors in parallel
$$C_{total} = C_1 + C_2 + C_3$$
 etc.

$${\rm Mark\ space\ ratio} \qquad \qquad = \frac{T_{on}}{T_{off}}$$

Astable frequency (f)
$$= \frac{1}{1.4 \times C_1 \times R_1}$$

555 astable frequency (f)
$$= \frac{1.44}{(R_a + 2R_b)C}$$

output high time =
$$0.693(R_a + R_b)C$$

output low time =
$$0.693(R_h)C$$

555 monostable time constant

on time =
$$1.1R_aC$$

$$\text{Voltage gain } = \frac{V_{out}}{V_{in}}$$

Non inverting amplifier
$$V_{out} = V_{in} \times \frac{(R_f + R_{in})}{R_{in}}$$

Inverting amplifier
$$V_{out} = -V_{in} \times \frac{R_f}{R_{in}}$$

Summing amplifier
$$V_{out} = -R_f \times (\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}) \ \ \text{etc.}$$

Differential amplifier
$$V_{out} = \frac{-R_f}{R_a} \times (V_2 - V_1)$$

MOSFET
$$g_{m} = \frac{\Delta I_{d}}{\Delta V_{\sigma_{S}}}$$

Battery life battery capacity = current x time

Mechanical Systems

Moment = force x perpendicular distance

Stress =
$$\frac{\text{force}}{\text{cross sectional area}}$$

Strain
$$= \frac{\text{change in length}}{\text{original length}}$$

Young modulus of elasticity =
$$\frac{\text{stress}}{\text{strain}}$$

Work done = force x distance moved

Power = force x velocity

Work done = torque x angle turned

Power = torque x angular velocity

Pneumatic Systems

Force = pressure x area

Compression ratio = (gauge pressure + atmospheric pressure)

atmospheric pressure

Volume of air used = area x stroke x compression ratio

Lifting load = vacuum level x area

Permission to reproduce items where third-party owned material protected by copyright is included has been sought and cleared where possible. Every reasonable effort has been made by the publisher (OCR) to trace copyright holders, but if any items requiring clearance have unwittingly been included, the publisher will be pleased to make amends at the earliest possible opportunity.

OCR is part of the Cambridge Assessment Group. Cambridge Assessment is the brand name of University of Cambridge Local Examinations Syndicate (UCLES), which is itself a department of the University of Cambridge.