

|                     |  |                  |  |
|---------------------|--|------------------|--|
| Surname             |  | Other Names      |  |
| Centre Number       |  | Candidate Number |  |
| Candidate Signature |  |                  |  |

|                    |
|--------------------|
| For Examiner's Use |
|--------------------|

General Certificate of Education  
 June 2008  
 Advanced Subsidiary Examination



**ELECTRONICS**  
**Unit 2 Further Electronics**

**ELE2**

Friday 16 May 2008 9.00 am to 10.30 am

|   |
|---|
| <p><b>For this paper you must have:</b></p> <ul style="list-style-type: none"> <li>• a pencil and a ruler</li> <li>• a calculator.</li> </ul> |
|---|

| For Examiner's Use  |      |          |      |
|---------------------|------|----------|------|
| Question            | Mark | Question | Mark |
| 1                   |      | 5        |      |
| 2                   |      | 6        |      |
| 3                   |      | 7        |      |
| 4                   |      |          |      |
| Total (Column 1)    |      | →        |      |
| Total (Column 2)    |      | →        |      |
| TOTAL               |      |          |      |
| Examiner's Initials |      |          |      |

Time allowed: 1 hour 30 minutes

**Instructions**

- Use black ink or black ball-point pen. Use pencil only for drawing.
- Fill in the boxes at the top of this page.
- Answer **all** questions.
- You must answer the questions in the spaces provided. Answers written in margins or on blank pages will not be marked.
- Do all rough work in this book. Cross through any work you do not want to be marked.
- A *Data Sheet* is provided on pages 3 and 4. Detach this perforated sheet at the start of the examination.

**Information**

- The maximum mark for this paper is 72.
- The marks for questions are shown in brackets.
- You are expected to use a calculator where appropriate.
- Any correct electronic solution will gain credit.
- You are reminded of the need for good English and clear presentation in your answers.



### Data Sheet

- A perforated *Data Sheet* is provided as pages 3 and 4 of this question paper.
- This sheet may be useful for answering some of the questions in the examination.
- You may wish to detach this sheet before you begin work.




## Data Sheet

**Resistors** Preferred values for resistors (E24) series:  
1.0, 1.1, 1.2, 1.3, 1.5, 1.6, 1.8, 2.0, 2.2, 2.4, 2.7, 3.0, 3.3, 3.6, 3.9, 4.3,  
4.7, 5.1, 5.6, 6.2, 6.8, 7.5, 8.2, 9.1 ohms and multiples that are ten  
times greater.

**Resistor Printed Code** This code consists of letters and numbers:  
(BS 1852) R means  $\times 1$   
K means  $\times 1000$  (i.e.  $10^3$ )  
M means  $\times 1\,000\,000$  (i.e.  $10^6$ )  
Position of the letter gives the decimal point  
Tolerances are given by the letter at the end of the code, F =  $\pm 1\%$ ,  
G =  $\pm 2\%$ , J =  $\pm 5\%$ , K =  $\pm 10\%$ , M =  $\pm 20\%$ .

| Resistor Colour Code | Number | Colour |
|----------------------|--------|--------|
|                      | 0      | Black  |
|                      | 1      | Brown  |
|                      | 2      | Red    |
|                      | 3      | Orange |
|                      | 4      | Yellow |
|                      | 5      | Green  |
|                      | 6      | Blue   |
|                      | 7      | Violet |
|                      | 8      | Grey   |
|                      | 9      | White  |

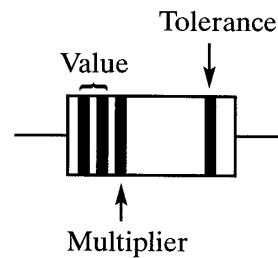

Tolerance, gold =  $\pm 5\%$ , silver =  $\pm 10\%$ , no band  $\pm 20\%$ .

**Silicon diode**  $V_F = 0.7\text{ V}$

**Silicon transistor**  $V_{be} \approx 0.7\text{ V}$  in the on state  
 $V_{ce} \approx 0.2\text{ V}$  when saturated

**Resistance**  $R_T = R_1 + R_2 + R_3$  series

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$
 parallel

**Capacitance**  $\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$  series

$$C_T = C_1 + C_2 + C_3$$
 parallel

**Time constant**  $T = CR$

**A.C. theory**  $I_{\text{rms}} = \frac{I_o}{\sqrt{2}}$

$$V_{\text{rms}} = \frac{V_o}{\sqrt{2}}$$

$$X_C = \frac{1}{2\pi fC}$$
 reactance

$$X_L = 2\pi fL$$
 reactance

$$f = \frac{1}{T}$$
 frequency, period

$$f_o = \frac{1}{2\pi\sqrt{LC}}$$
 resonant frequency

Turn over ▶



|  |  |                      |
|--|--|----------------------|
| Operational amplifier                      | $G_V = \frac{V_{\text{out}}}{V_{\text{in}}}$   | voltage gain         |
|  | $G_V = -\frac{R_f}{R_1}$   | inverting            |
|  | $G_V = 1 + \frac{R_f}{R_1}$  | non-inverting        |
|  | $V_{\text{out}} = -R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$   | summing              |
| Astable and Monostable<br>using NAND Gates | $f \approx \frac{1}{2RC}$  | astable              |
|  | $T \approx RC$   | monostable           |
| 555 Astable and<br>Monostable              | $T = 1.1RC$  | monostable           |
|  | $t_H = 0.7(R_A + R_B)C$<br>$t_L = 0.7R_B C$ ]  | astable              |
|  | $f = \frac{1.44}{(R_A + 2R_B)C}$   | two resistor circuit |
| Electromagnetic Waves                      | $c = 3 \times 10^8 \text{ m s}^{-1}$   | speed in vacuo       |
| List of BASIC Commands                     | <b>DIM</b> variable [(subscripts)]<br><b>DO</b> [{ <b>WHILE</b>   <b>UNTIL</b> } condition]<br>(statement block)<br><b>LOOP</b><br><b>DO</b><br>(statement block)<br><b>LOOP</b> [{ <b>WHILE</b>   <b>UNTIL</b> } condition]<br><b>FOR</b> counter = start <b>TO</b> end [ <b>STEP</b> increment]<br>(statement block)<br><b>NEXT</b> counter<br><b>GOSUB</b> [label   line number]<br>(statement block)<br><b>RETURN</b><br><b>IF</b> condition <b>THEN</b><br>(statement block 1)<br><b>ELSE</b><br>(statement block 2)<br><b>INKEY\$</b><br><b>INP</b> (port %)<br><b>INPUT</b> [ ; ] ["prompt" {;1,}] variable list (comma separated)<br><b>LPRINT</b> [expression list] [ { ;1, } ]<br><b>OUT</b> port%, data%<br><b>PRINT</b> [expression list] [{;1,}]<br><b>REM</b> remark |                      |



Answer **all** questions in the spaces provided.

- 1 Temporary traffic lights are used to control the traffic at roadworks. The traffic lights have a 16-step binary sequence as shown in the table below where R = red, Y = amber, G = green.

| D | C | B | A | traffic lights 1 | traffic lights 2 |
|---|---|---|---|------------------|------------------|
| 0 | 0 | 0 | 0 | R                | G                |
| 0 | 0 | 0 | 1 | R                | G                |
| 0 | 0 | 1 | 0 | R                | G                |
| 0 | 0 | 1 | 1 | R                | G                |
| 0 | 1 | 0 | 0 | R                | G                |
| 0 | 1 | 0 | 1 | R                | G                |
| 0 | 1 | 1 | 0 | R                | Y                |
| 0 | 1 | 1 | 1 | R, Y             | R                |
| 1 | 0 | 0 | 0 | G                | R                |
| 1 | 0 | 0 | 1 | G                | R                |
| 1 | 0 | 1 | 0 | G                | R                |
| 1 | 0 | 1 | 1 | G                | R                |
| 1 | 1 | 0 | 0 | G                | R                |
| 1 | 1 | 0 | 1 | G                | R                |
| 1 | 1 | 1 | 0 | Y                | R                |
| 1 | 1 | 1 | 1 | R                | R, Y             |

- 1 (a) State the value of the step, in hexadecimal, when only the amber lamp is illuminated in **traffic lights 1**.

.....  
(1 mark)

**Question 1 continues on the next page**

**Turn over ▶**



- 1 (b) Explain why the Boolean expression when the green lamp of **traffic lights 1** is illuminated is given by

$$G = D \cdot \bar{C} \cdot \bar{B} \cdot \bar{A} + D \cdot \bar{C} \cdot \bar{B} \cdot A + D \cdot \bar{C} \cdot B \cdot \bar{A} + D \cdot \bar{C} \cdot B \cdot A + D \cdot C \cdot \bar{B} \cdot \bar{A} + D \cdot C \cdot \bar{B} \cdot A$$

.....

.....

.....

.....

.....

(2 marks)

- 1 (c) Show that the expression in part (b) simplifies to:

$$G = D \cdot \overline{B \cdot C}$$

.....

.....

.....

.....

.....

.....

.....

.....

.....

(3 marks)



- 1 (d) Draw a circuit diagram to show how you would implement the simplified logic expression using several 2-input NAND gates.

(3 marks)


|   |
|---|
|   |
| 9 |

**Turn over for the next question**

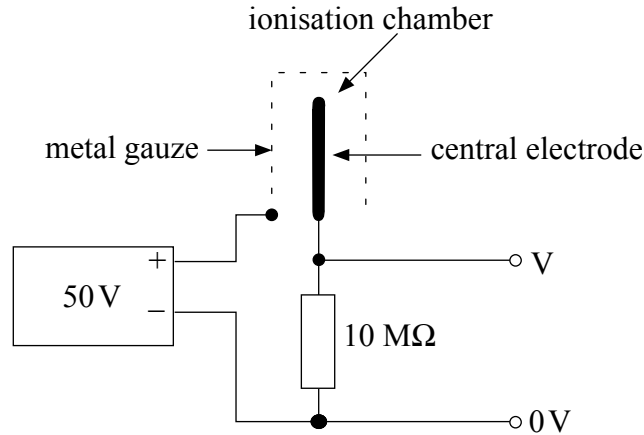**Turn over ▶**



- 2 An ionisation chamber for detecting radioactivity consists of a metal gauze cylinder surrounding a central electrode. The metal gauze is held at a voltage of +50 V with respect to the central electrode. When radiation enters the chamber the gas is ionised and a very small current flows which is directly related to the strength of the radiation. This small current passes through a  $10\text{ M}\Omega$  resistor.



- 2 (a) (i) The maximum current that the detector can produce is  $2 \times 10^{-10}\text{ A}$ . Calculate the corresponding voltage across the  $10\text{ M}\Omega$  resistor.

.....

.....

- 2 (a) (ii) The voltage is to be displayed on a digital meter which has a maximum sensitivity of 200 mV. Calculate the voltage gain required for an amplifier to interface the digital meter to the ionisation chamber.

.....

.....

(4 marks)

- 2 (b) It is decided to use a non-inverting op-amp amplifier to provide this gain. State and explain what important property makes a non-inverting amplifier a suitable choice.

.....

.....


.....

(2 marks)





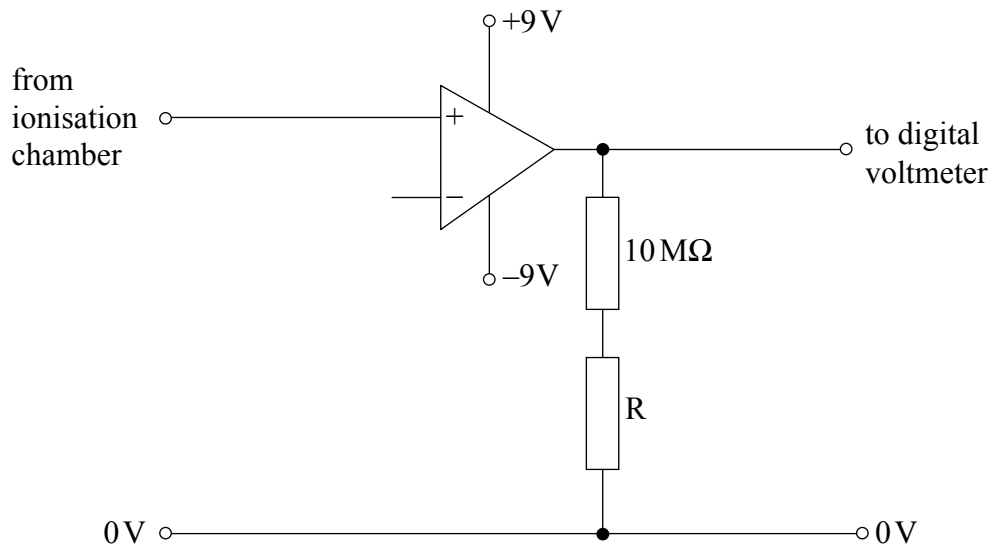The partly drawn circuit diagram for a non-inverting amplifier is shown below.



- 2 (c) (i) Complete the circuit diagram by adding the missing connection.
- 2 (c) (ii) Calculate the value of R needed to produce the voltage gain you have calculated in part (a)(ii).

.....

.....

.....

.....

(3 marks)

**Turn over for the next question**


|   |
|---|
| 9 |
|---|

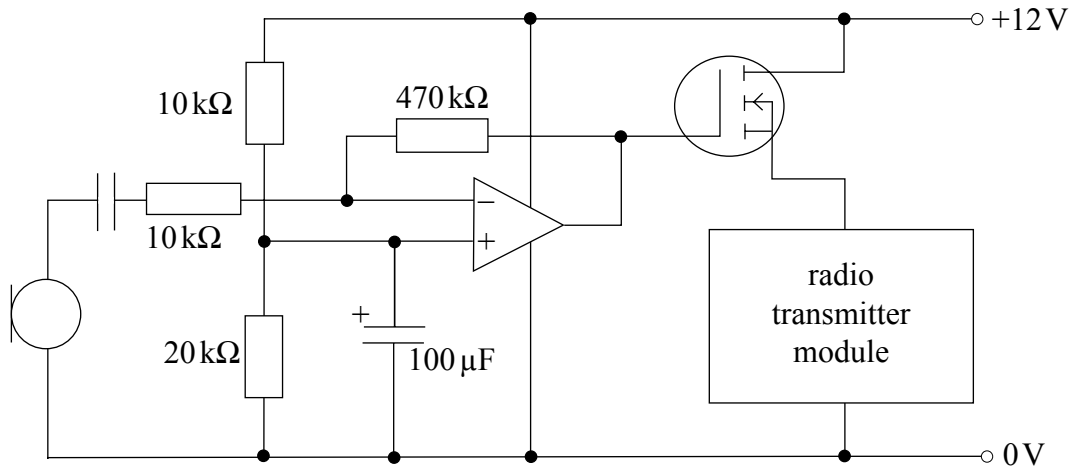**Turn over ▶**



3 Part of the circuit diagram for a low power radio transmitter is shown below.

The audio amplifier controls the current through the radio transmitter module.



3 (a) (i) Label the source connection of the MOSFET with an S.

3 (a) (ii) What is the name for the circuit arrangement in which the MOSFET is being used?

.....  
 (2 marks)

3 (b) (i) Show that the voltage at the non-inverting input of the op-amp is 8 V.

.....  
 .....

3 (b) (ii) With no input signal from the microphone, explain why the voltage on the gate of the MOSFET is also 8 V.

.....  
 .....

3 (b) (iii) If the turn on value of  $V_{gs}$  for the MOSFET is 2 V, what is the voltage across the radio transmitter module, when there is no signal from the microphone?

.....  
 (4 marks)



3 (c) (i) Calculate the voltage gain of the op-amp amplifier.

.....  
.....

3 (c) (ii) If the microphone gives an output of 40 mV, estimate the voltage change that occurs across the radio transmitter module, showing your working.

.....  
.....  
.....  
.....

*(3 marks)*


|   |
|---|
|   |
| 9 |

**Turn over for the next question**

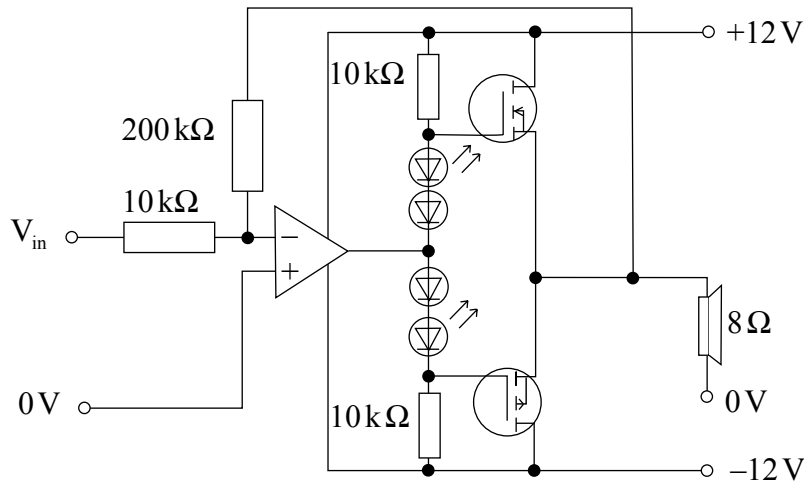**Turn over ▶**



- 4 A student wants to amplify the output from the sound card on his computer so that he can use loudspeakers instead of headphones. His sound card gives a maximum peak output voltage of 500 mV. He wants to use an amplifier circuit that he has found on a website, but needs to decide if it will be suitable. The circuit diagram is shown below.



- 4 (a) Show that the peak voltage developed across the loudspeaker will be approximately 10 V when there is an input of 500 mV.

.....  
 .....  
 (2 marks)

- 4 (b) Calculate the rms output power into the loudspeaker under these conditions.

.....  
 .....  
 (2 marks)

The student is concerned that the amplifier will suffer from *cross-over distortion*.

- 4 (c) (i) Explain what is meant by cross-over distortion.

.....  
 .....  
 .....



4 (c) (ii) State what measures have been taken to reduce cross-over distortion in the circuit.

.....  
.....

(3 marks)

4 (d) With the circuit constructed and working, the student finds that the MOSFETs become very hot. His teacher recommends that he should bolt each MOSFET to a heatsink.

State **two** important features of an efficient heatsink.

.....  
.....

(2 marks)

|   |
|---|
|   |
| 9 |

**Turn over for the next question**

**Turn over ▶**



5 All of the electrical activity of the brain occurs at low frequencies, the alpha rhythm having the highest frequency of 8 – 13 Hz. In order to isolate this electrical activity from that of the muscles, which occurs at a higher frequency, the electrical signals are passed through a *low pass filter* with a *break point frequency* of 20 Hz.

5 (a) (i) What is meant by the term low pass filter?


.....  
 .....

5 (a) (ii) What is meant by the term break point frequency?

.....  
 .....

(3 marks)

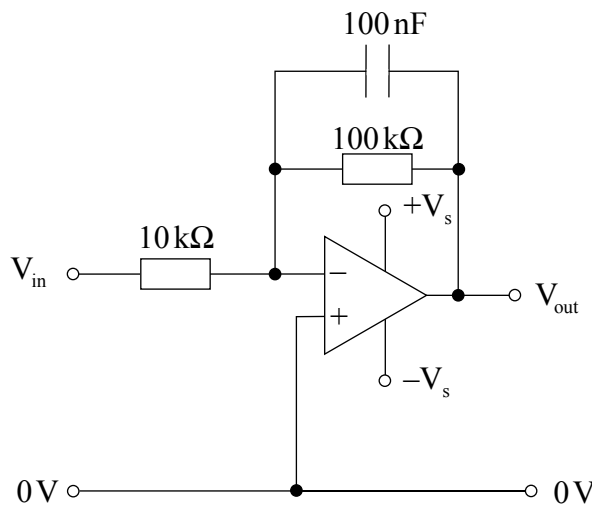5 (b) The circuit diagram of the low pass filter is shown below.



Calculate the reactance of the 100 nF capacitor at a frequency of 20 Hz.


.....  
 .....

(3 marks)



- 5 (c) Sketch onto the grid below how the voltage gain of this filter circuit varies with frequency.

voltage gain

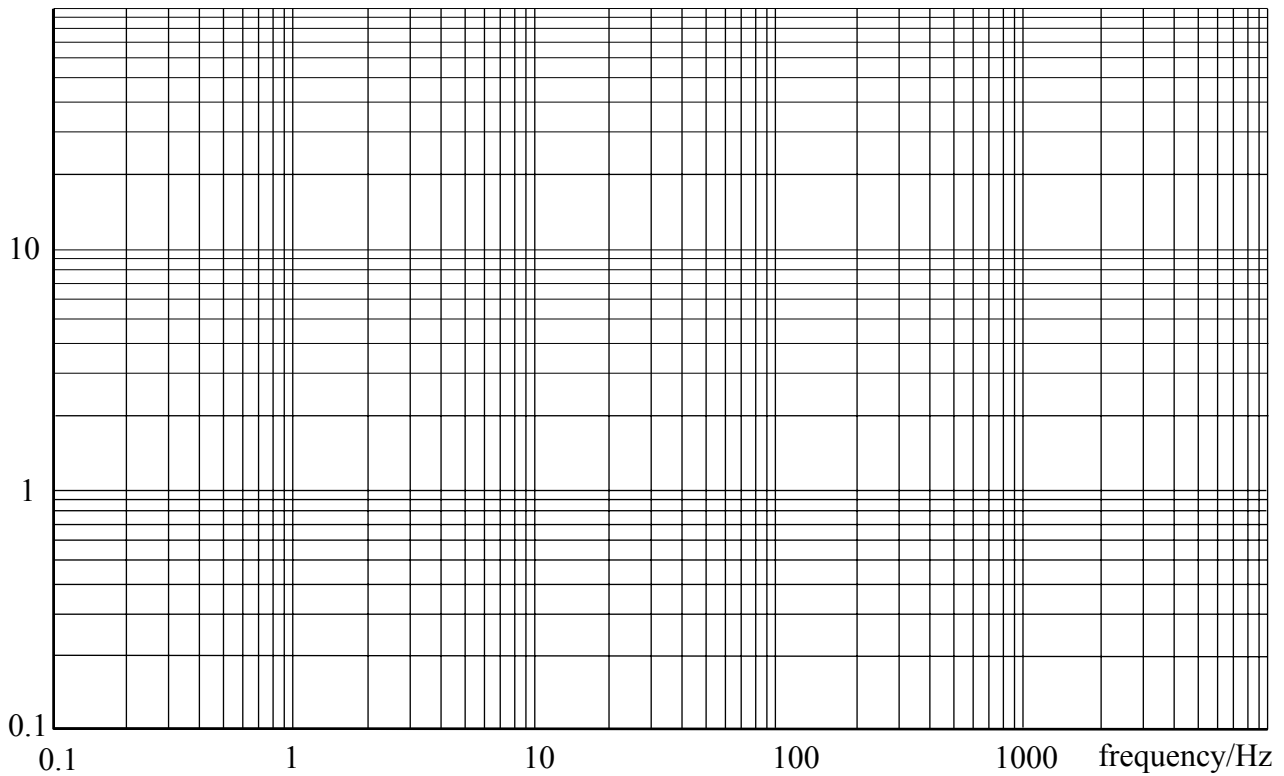

(3 marks)


|   |
|---|
|   |
| 9 |

**Turn over for the next question**

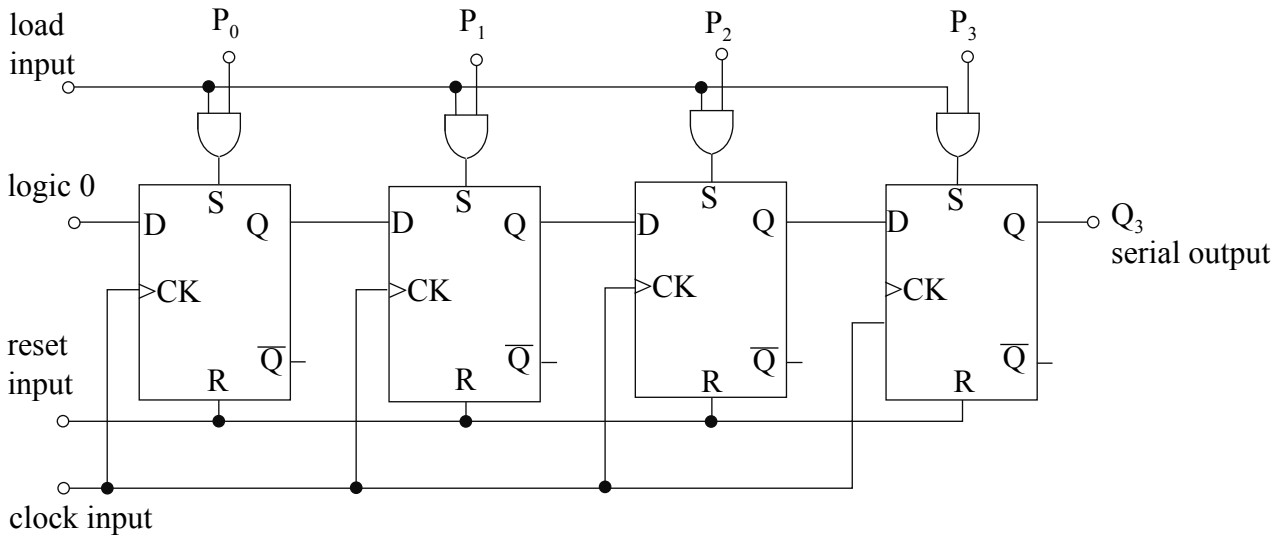**Turn over ▶**



6 The shift register circuit below is used by a student to convert parallel data to serial data. The parallel data is sent to  $P_0$ ,  $P_1$ ,  $P_2$  and  $P_3$  and the serial output is taken from  $Q_3$ .



6 (a) Explain how a shift register works.

.....

.....

.....

(3 marks)

6 (b) (i) Explain why it is necessary in this circuit to reset the shift register before loading new parallel data.

.....

.....

6 (b) (ii) State the logic level of the load input for parallel data to be loaded into the shift register.

.....


.....

(2 marks)






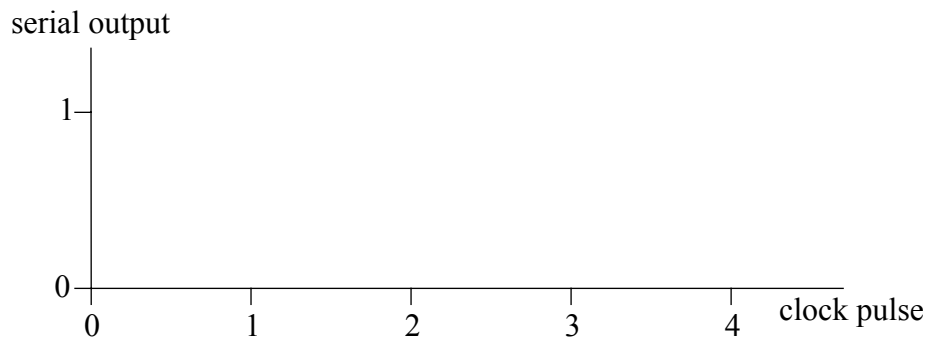- 6 (c) The hexadecimal number **B** is loaded into the shift register. Sketch onto the diagram below the serial output.



(4 marks)

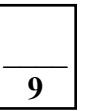


**Turn over for the next question**

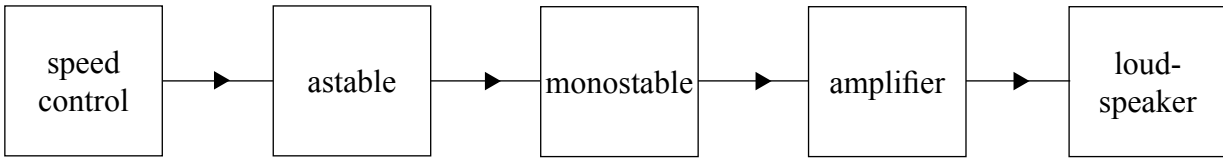
**Turn over ▶**



7 A metronome is a device used by musicians to help keep in time. It produces a click to time the beat of the music. The system diagram of a simple metronome is shown below.



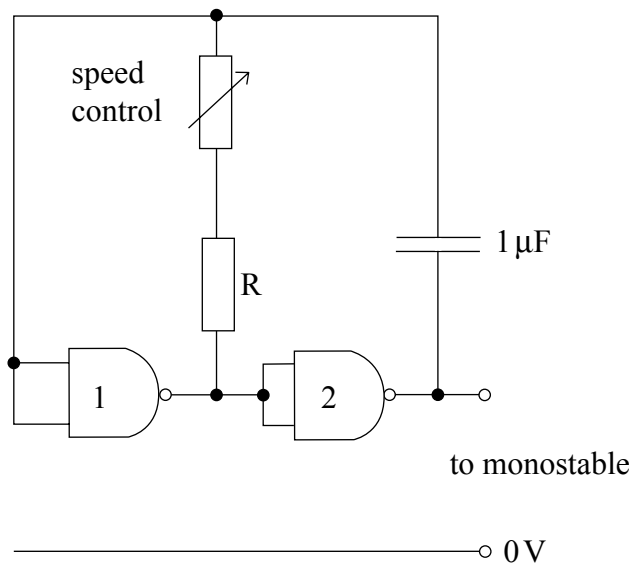The circuit diagram for the astable is shown below.



7 (a) (i) The metronome produces a maximum rate of 240 clicks per minute. What is the required frequency of the astable?

.....

7 (a) (ii) Calculate a suitable value for R using the formula on the Data Sheet.

.....

.....

(3 marks)

7 (b) If the minimum number of clicks per minute is 30, calculate a suitable value for the speed control variable resistor.


.....

.....

(2 marks)



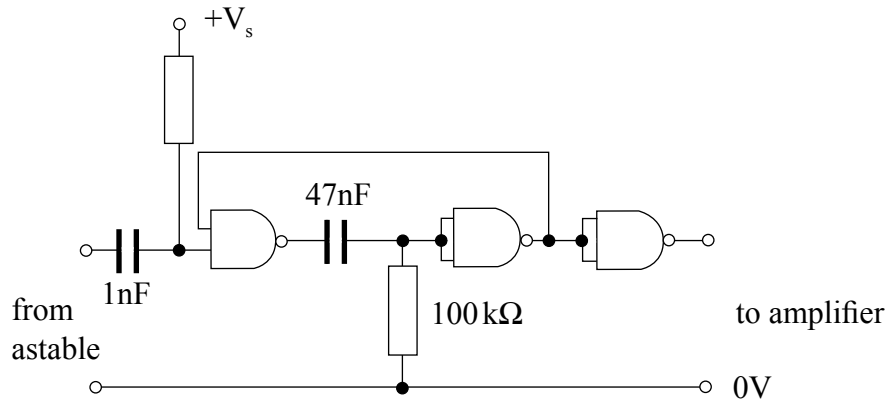The circuit diagram for the monostable is shown below.



- 7 (c) (i) Calculate the time period of the pulse from the monostable using the formula on the Data Sheet.

.....  
 .....

- 7 (c) (ii) Explain how the monostable circuit operates once it has been triggered.

.....  
 .....  
 .....  
 .....  
 .....  
 .....


(6 marks)

**Question 7 continues on the next page**

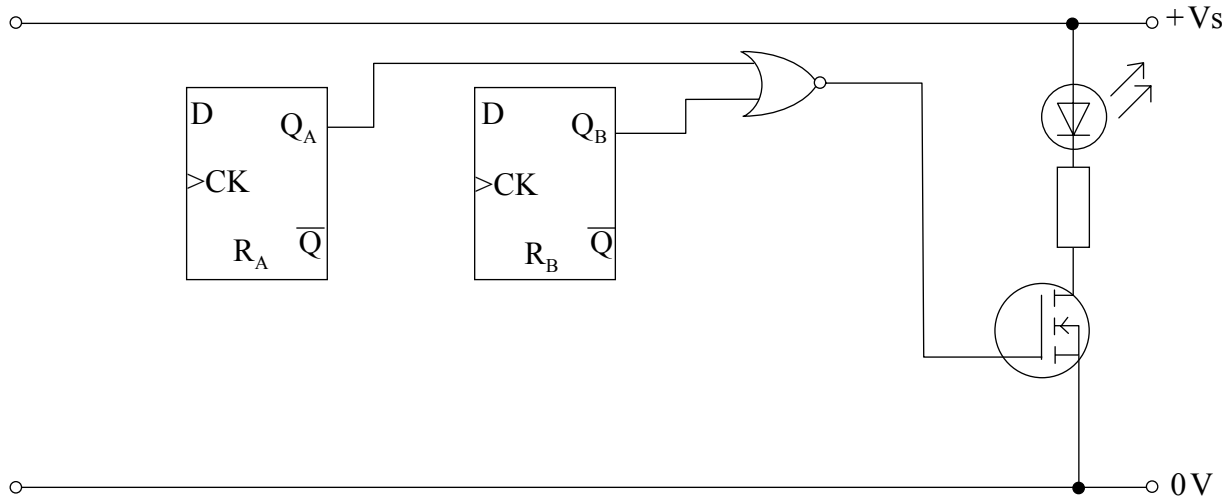**Turn over ▶**



Having built the metronome, a student decides to modify it so that it flashes a LED every two, three or four clicks. He decides to build a 2-bit counter using D-type flip-flops. The diagram below shows two D-type flip-flops and the LED flashing circuit.



7 (d) (i) Add the connections necessary to make the two flip-flops into a 2-bit up-counter and show where the output from the monostable would be connected in order to make them count.

7 (d) (ii) Explain under what conditions the LED will light.

.....  
 .....

(4 marks)

7 (e) In order to make the LED flash every two, three or four clicks, it is necessary to design a logic circuit to control the reset terminals, R, of the flip-flops. Complete the table below for the logic states that must be applied to each of the reset pins. Choose from 0, 1 or  $Q_A \cdot Q_B$

| No of clicks | $R_A$ | $R_B$ |
|--------------|-------|-------|
| 2            | 0     | 1     |
| 3            |       |       |
| 4            |       |       |

(3 marks)

**END OF QUESTIONS**

