



General Certificate of Education

Electronics 5431/6431

ELE4 Electronic Control Systems

Mark Scheme

2008 examination – June series

Mark schemes are prepared by the Principal Examiner and considered, together with the relevant questions, by a panel of subject teachers. This mark scheme includes any amendments made at the standardisation meeting attended by all examiners and is the scheme which was used by them in this examination. The standardisation meeting ensures that the mark scheme covers the candidates' responses to questions and that every examiner understands and applies it in the same correct way. As preparation for the standardisation meeting each examiner analyses a number of candidates' scripts: alternative answers not already covered by the mark scheme are discussed at the meeting and legislated for. If, after this meeting, examiners encounter unusual answers which have not been discussed at the meeting they are required to refer these to the Principal Examiner.

It must be stressed that a mark scheme is a working document, in many cases further developed and expanded on the basis of candidates' reactions to a particular paper. Assumptions about future mark schemes on the basis of one year's document should be avoided; whilst the guiding principles of assessment remain constant, details will change, depending on the content of a particular examination paper.

Further copies of this Mark Scheme are available to download from the AQA Website: www.aqa.org.uk

Copyright © 2008 AQA and its licensors. All rights reserved.

COPYRIGHT


AQA retains the copyright on all its publications. However, registered centres for AQA are permitted to copy material from this booklet for their own internal use, with the following important exception: AQA cannot give permission to centres to photocopy any material that is acknowledged to a third party even for internal use within the centre.

Set and published by the Assessment and Qualifications Alliance.

- 1 (a) The voltage across the resistor is $12 - 4.2 = 7.8\text{V}$ ✓
 $\Rightarrow R = 7.8 / 0.045 = 173\Omega$ ✓
 \Rightarrow increase to preferred value is 180Ω ✓
- (b) (i) Virtual earth point at inverting input to op-amp ✓
(ii) **Photodiode** between inverting input and negative supply ✓
cathode connected to inverting input of op-amp ✓
anode connected to the negative supply ✓
- (c) The current through the feedback resistor will be $5\mu\text{A}$ ✓
 \Rightarrow the output voltage will be $5\mu\text{A} \times 1\text{M}\Omega = 5\text{V}$ ✓

Total – 9

- 2 (a) (i) Very large open loop voltage gain ✓
(ii) V_{in} must be between 0V and 7.5V ✓
- (b) (i) Feedback resistor in parallel with top $47\text{k}\Omega$ resistor giving $23.5\text{k}\Omega$ ✓
 \Rightarrow voltage at non-inverting input terminal is 10V ✓
 \Rightarrow for output to be at $+15\text{V}$, the input voltage must be less than 10V ✓ (max 2)
- (ii) Feedback resistor in parallel with bottom $47\text{k}\Omega$ resistor giving $23.5\text{k}\Omega$
 \Rightarrow voltage at non-inverting input terminal is 5V
 \Rightarrow for output to be at 0V , the input voltage must be greater than 5V ✓
- (c)

 

General shape ✓
Correct switching levels ✓

- (d) (Capacitor charges and discharges between $\frac{1}{3}$ and $\frac{2}{3}$ of supply voltage)
 (This is the same as the 555 timer)
 $\Rightarrow T = 1.4 R C \checkmark$
 $\Rightarrow T = 1.4 \times 10^4 \times 10^{-7} = 1.4\text{ms} \checkmark$

Total – 9

- 3** (a) (i) e.g. Information is stored in the connections between neurons in an ANN whereas it is stored at specific locations in the NAS \checkmark
- (ii) e.g. The NAS is limited by the number of locations at which to store information
 The ANN is essentially unlimited since there are so many possible interconnections between neurons \checkmark
- (iii) e.g. The information in a NAS is more reliable than an ANN since connections between neurons are not stable, while that of the magnetic field is (relatively) \checkmark
- (b) (i) e.g. ANN information processed in parallel by many neurons, in a computer it is processed in a few processors serially $\checkmark \checkmark$
- (ii) e.g. ANNs can learn and adapt to maximise traffic flow, whereas PCs cannot. $\checkmark \checkmark$
- (c) e.g. ANNs unsuitable for applications which require precision since they operate essentially through probability (fuzzy logic). $\checkmark \checkmark$

Total – 9

- 4** (a) (i) $360 / 16 = 22.5^\circ \checkmark$
- (ii) $360 / 16 = 22.5^\circ \checkmark$
- (iii) (Add more rings), each with twice as many divisions (bits) as the previous \checkmark
- (b) Absolute position and direction $\checkmark \checkmark$
- (c) e.g. Accuracy of rotation + explanation $\checkmark \checkmark$
 Speed of response + explanation $\checkmark \checkmark$


Total – 9

- 5 (a) Closed loop + reason ✓
- (b) (i) Eliminate reverse voltages generated as the motor coils switch off ✓
- (ii)

Input A	Input B	Motor
0	0	Stop – 0
0	1	Rotate in one direction – 1
1	0	Rotate in the other direction – 0
1	1	Stop – 0

First and last row ✓
 Middle two rows ✓ ✓

(c) e.g.

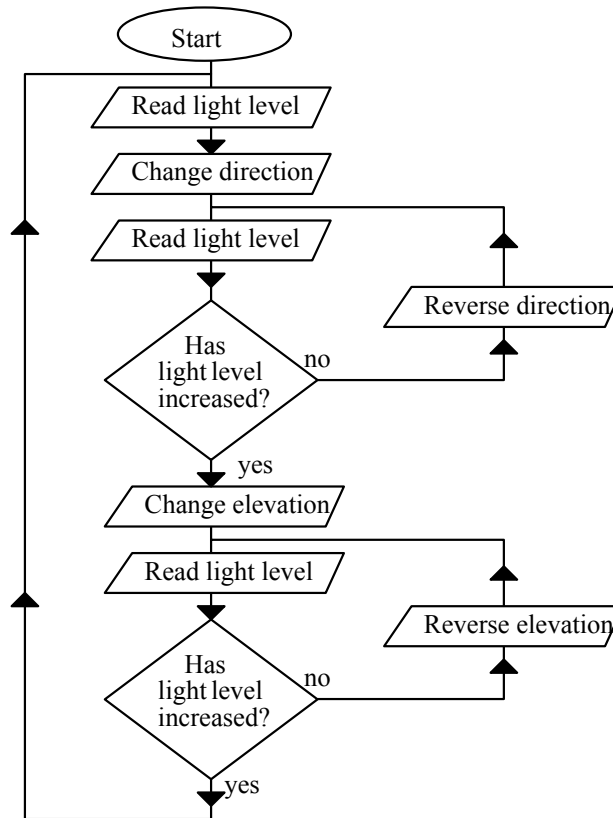

Horizontal direction changes ✓
 Vertical direction changes ✓
 Appropriate elements to flow chart ✓
 Largely correct symbols ✓


Total – 9

6 (a)

tray sensor	reservoir sensor	pump	LED
wet	wet	0	0
wet	dry	0	1
dry	wet	1	0
dry	dry	0	1

Minus 1 per row. ✓ ✓ ✓

(b)

 

- (c) Very large input resistance – (so it does not load the output of the logic gates) ✓
 Very large power gain – (so that a logic gate can readily control the pump) ✓

Total – 9

7 (a) e.g. Computer inputs are digital and only accept two voltage levels ✓
 which is not compatible with the wide range of voltages from an analogue sensor ✓

- (b) (i) Tristate - three output states - 0, 1 ✓
 and high impedance ✓
- (ii) The tristate (buffer) outputs are active low ✓
 When D_6 is 1, output enable of the most significant nibble tristate buffer is logic 1 and so disabled and the output enable of the least significant nibble tristate buffer is logic 0 and so enabled ✓

(c) $15300 / 255 = 60$ ✓
 so resolution is 60 lux ✓

- (d) SC is taken low to start the conversion. ✓
 PC waits until EoC goes high ✓
 D_6 high - least significant nibble read ✓
 D_6 low - most significant nibble read and added to least significant. ✓

- (e) (i) &H379 ✓
- (ii) Masks the least significant three bits ✓
to avoid errors from undefined bits ✓
- (f) (i) Sets bit D_6 to logic 1 without affecting the other bit values ✓
- (ii) It moves the bits in Y% to the right, changes bits on D_4 to D_7
to D_0 to D_3 ✓
- (iii) It sets D_6 to logic 0 ✓

Total – 18

Paper Total – 72