



## **General Certificate of Education**

# **Electronics 1431/2431**

## **ELEC1      Introductory Electronics**

# **Mark Scheme**

*2009 examination – June series*

Mark schemes are prepared by the Principal Examiner and considered, together with the relevant questions, by a panel of subject teachers. This mark scheme includes any amendments made at the standardisation meeting attended by all examiners and is the scheme which was used by them in this examination. The standardisation meeting ensures that the mark scheme covers the candidates' responses to questions and that every examiner understands and applies it in the same correct way. As preparation for the standardisation meeting each examiner analyses a number of candidates' scripts: alternative answers not already covered by the mark scheme are discussed at the meeting and legislated for. If, after this meeting, examiners encounter unusual answers which have not been discussed at the meeting they are required to refer these to the Principal Examiner.

It must be stressed that a mark scheme is a working document, in many cases further developed and expanded on the basis of candidates' reactions to a particular paper. Assumptions about future mark schemes on the basis of one year's document should be avoided; whilst the guiding principles of assessment remain constant, details will change, depending on the content of a particular examination paper.

Further copies of this Mark Scheme are available to download from the AQA Website: [www.aqa.org.uk](http://www.aqa.org.uk)

Copyright © 2009 AQA and its licensors. All rights reserved.

#### COPYRIGHT

AQA retains the copyright on all its publications. However, registered centres for AQA are permitted to copy material from this booklet for their own internal use, with the following important exception: AQA cannot give permission to centres to photocopy any material that is acknowledged to a third party even for internal use within the centre.


Set and published by the Assessment and Qualifications Alliance.

- 1 (a)  $D = \overline{A}$  ✓       $E = \overline{\overline{A} \cdot B}$  ✓  
 Bars are Vital    Consequential marking
- (b) (i)  $Q = \overline{C + E}$  ✓  
 Bars are Vital    Consequential marking
- (ii)  $Q = \overline{\overline{A} \cdot B} + C$  ✓  
 Bars are Vital    Consequential marking
- (c) A and C must be logic 0 and B must be logic 1 ✓  
 Marking points in bold
- (d)

A	B	C	D	E	Q
0	0	0	<b>1</b>	<b>1</b>	<b>0</b>
0	0	1	<b>1</b>	<b>1</b>	<b>0</b>
0	1	0	<b>1</b>	<b>0</b>	<b>1</b>
0	1	1	<b>1</b>	<b>0</b>	<b>0</b>
1	0	0	<b>0</b>	<b>1</b>	<b>0</b>
1	0	1	<b>0</b>	<b>1</b>	<b>0</b>
1	1	0	<b>0</b>	<b>1</b>	<b>0</b>
1	1	1	<b>0</b>	<b>1</b>	<b>0</b>

(11 marks)

2 (a)

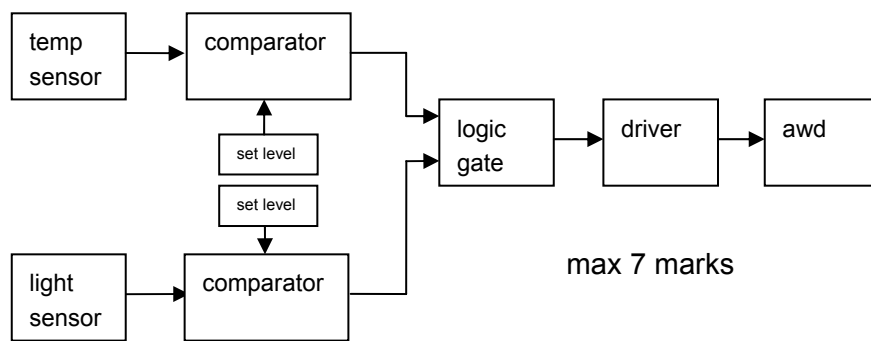

max 7 marks

One per correct subsystem, comparators plus set level count as one

- (b) (i) driver ✓  
 (ii) comparator ✓  
 (iii) temperature sensor ✓
- (c) (i)  $160 - 10 = 150\text{mA}$  ✓  
 (ii)  $9\text{V} \times 160\text{mA}$  ✓       $= 1.44\text{W}$  ✓  
 Or answer plus correct unit

(13 marks)

3 (a)  $R_1 = 2.7k\Omega$  ✓  
 $R_2 = 6.3k\Omega$  ✓


(b) comparator ✓

(c)

voltage of battery to be tested	voltage at X	voltage at Y	
less than 6.3V	0	0	✓
between 6.3 and 9.0V	0	12	✓
more than 9.0V	12	12	✓

One mark per correct line


(d) (i)

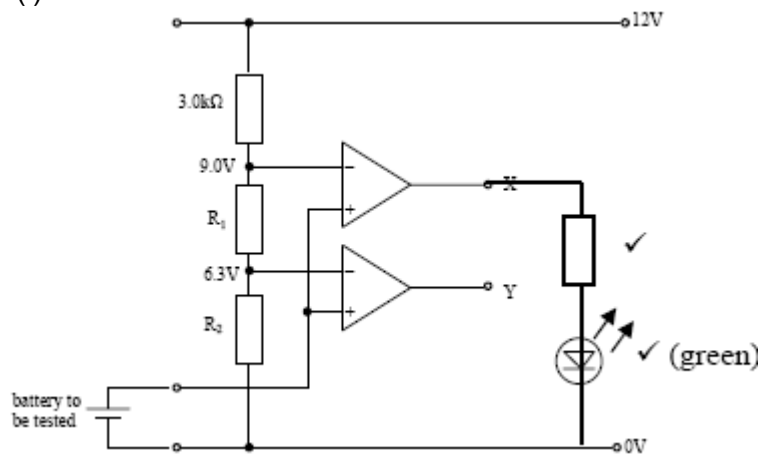

(ii) To limit LED current ✓


(iii) resistor voltage =  $12 - 2 = 10V$  ✓  
 $R = V \div I = 10 \div 20mA = 500\Omega$  ✓ ecf

(e)

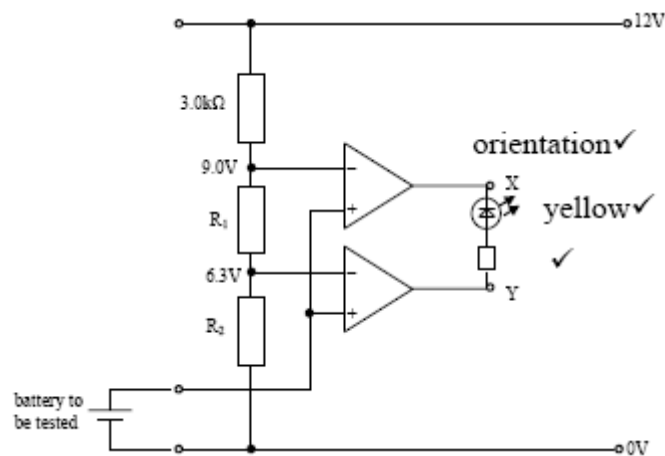


(15 marks)


4 (a)

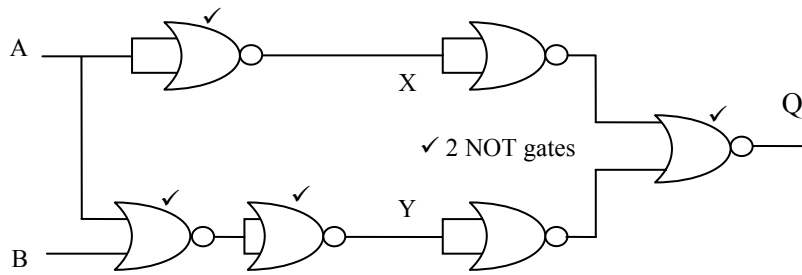

(b)

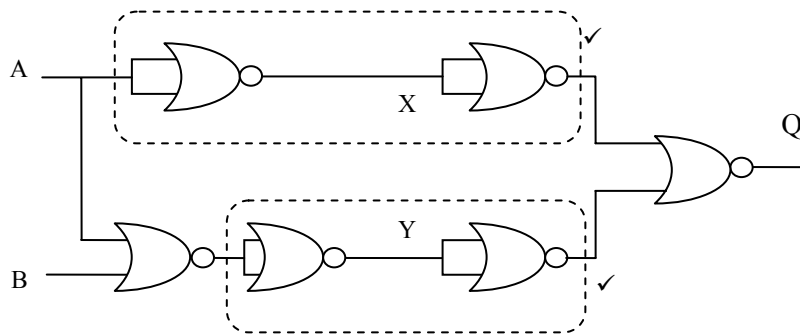


(c) (i)

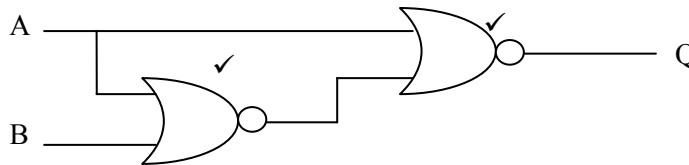

(ii) Any **two** reasons from: only one type of IC need be stocked, cheaper, simpler, less current/power, less complex ✓✓ (11 marks)

5 (a)

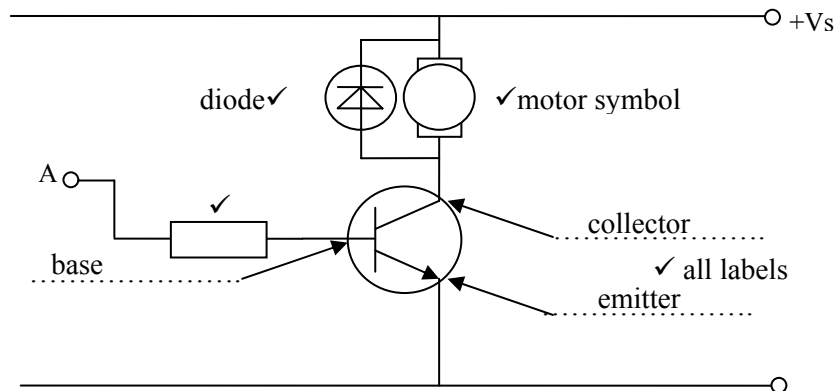


Npn junction transistor ✓

(b) (i)  $300 \div 60 = 5\text{mA}$  ✓

(ii)  $V$  across resistor  $5.6 - 0.6 = 5\text{V}$  (or  $0.7\text{V}$ ) ✓  
 $R = 5 \div 0.005 = 1\text{k}\Omega$  ✓ ecf

(9 marks)

6 (a)

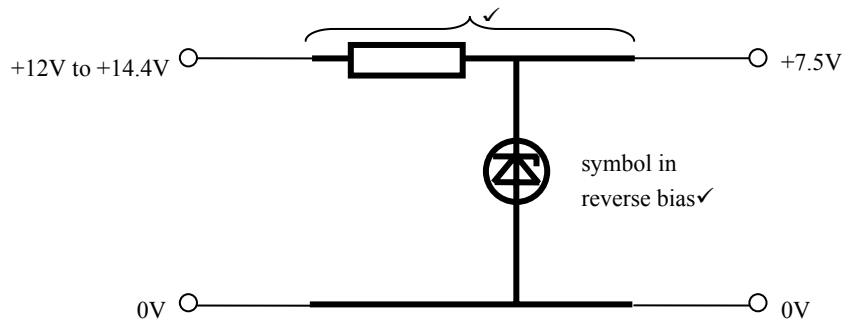

- (b) (i)  $12 - 7.5 = 4.5V$  ✓  
 (ii)  $100 + 10 = 110mA$  ✓  
 (iii)  $4.5 \div 0.11 = 41\Omega$  ✓ ecf  
 (iv)  $39\Omega$  ✓ ecf  
 (v) orange white ✓ black gold ✓ ecf

(8 marks)