



**General Certificate of Education (A-level)
June 2011**

Electronics

ELEC1

(Specification 2430)

Unit 1: Introductory Electronics

Final

Mark Scheme

Mark schemes are prepared by the Principal Examiner and considered, together with the relevant questions, by a panel of subject teachers. This mark scheme includes any amendments made at the standardisation events which all examiners participate in and is the scheme which was used by them in this examination. The standardisation process ensures that the mark scheme covers the candidates' responses to questions and that every examiner understands and applies it in the same correct way. As preparation for standardisation each examiner analyses a number of candidates' scripts: alternative answers not already covered by the mark scheme are discussed and legislated for. If, after the standardisation process, examiners encounter unusual answers which have not been raised they are required to refer these to the Principal Examiner.

It must be stressed that a mark scheme is a working document, in many cases further developed and expanded on the basis of candidates' reactions to a particular paper. Assumptions about future mark schemes on the basis of one year's document should be avoided; whilst the guiding principles of assessment remain constant, details will change, depending on the content of a particular examination paper.

Further copies of this Mark Scheme are available from: aqa.org.uk

Copyright © 2011 AQA and its licensors. All rights reserved.

Copyright

AQA retains the copyright on all its publications. However, registered centres for AQA are permitted to copy material from this booklet for their own internal use, with the following important exception: AQA cannot give permission to centres to photocopy any material that is acknowledged to a third party even for internal use within the centre.

Set and published by the Assessment and Qualifications Alliance.

Question	Part	Subpart	Marking guidance	Mark
1	(a)		<p> humidity sensor ✓ comparator ✓ latch ✓ astable ✓ driver ✓ awd ✓ reset switch ✓ set level ✓ </p>	8
1	(b)	(i)	Set level ✓	1
1	(b)	(ii)	Comparator ✓	1
1	(b)	(iii)	Driver ✓	1
2	(a)		$D = A.C$ ✓ $E = A.B$ ✓ $F = B.C$ ✓	3
2	(b)		$G = A.C + A.B$ ✓ $Q = A.C + A.B + B.C$ ✓	2

2	(c)	5

2	(d)	Output is a logic 1 when at least 2 inputs are at logic 1✓	1
3	(a)	(i) zener diode✓	1
3	(a)	(ii) 4.7V✓	1
3	(a)	(iii) reverse✓	1
3	(b)	(i) 5 + 100 = 105mA✓	1
3	(b)	(ii) 10 - 4.7 = 5.3V✓	1
3	(b)	(iii) 5.3 ÷ 0.105✓ = 50.5Ω✓	2
3	(b)	(iv) 47Ω✓	1
3	(c)	(i) 14.4 - 4.7 = 9.7V✓ 9.7 ÷ 33 = 294mA✓	2
3	(c)	(ii) 4.7 × 0.294 = 1.38W✓	1

4	(a) & (b)		5
---	--------------	--	---

4	(c)	thermistor 20kΩ at 20°C ✓ 2 : 1 ratio (or calc) ✓ R = 10kΩ ✓	3
---	-----	--	---

4	(d)	(i) 0V ✓	1
---	-----	----------	---

4	(d)	(ii) >0 – 3V ✓	1
---	-----	----------------	---

5	(a)	base ✓ gate ✓	2
---	-----	---------------	---

5	(b)	MOSFET ✓	1
---	-----	----------	---

5	(c)	needed to limit the current to a safe value ✓ in the base ✓	2
---	-----	---	---

5	(d)	(i) protection diode – correct symbol and position ✓ correct way round ✓	2
---	-----	---	---

5	(d)	(ii)	protection diode/back emf diode ✓ to prevent damage to transistor/prevent back emf when MOSFET switches off ✓	2
5	(e)		MOSFET has high input resistance ✓ so less current needed from input ✓ because logic circuit can't provide enough current for NPN transistor ✓ larger current gain needed for motor switch than for light switch ✓ (max 3)	3
6	(a)		Logic 1 on top line only, all rest are zeroes. ✓	1
6	(b)		One term per line that gives $P=1$ ✓ 7 terms in all ✓ Each term has all four variables, ✓ with bars where values are zero All "OR"ed together ✓ (✓✓ max)	2

6	(c)	<p> $\checkmark \bar{D}.A$ $\checkmark \bar{D}.\bar{C}.B$ $\checkmark \bar{C}.\bar{B}.A$ $\checkmark \bar{C}.\bar{B}.A$ \checkmark (or Boolean algebra $\checkmark \checkmark \checkmark$) </p>	4
<p>The Boolean Algebra solution is obtained by adding redundant terms into the expression for P; term 3 is repeated three times and term 4 twice.</p> <p>Dbar.A is then obtained by factorising terms 1,3,4 and 5, which contain all possible combinations of variable B and C which can therefore be removed.</p> <p>Cbar.B.A is obtained by factorising terms 3 and 6, variable D is removed as D + Dbar is equivalent to logic 1, which anded with the remaining variables, goes out.</p> <p>C.Bbar.A is obtained from terms 4 and 7, variable D is removed as D + Dbar is equivalent to logic 1, which anded with the remaining variables, goes out.</p> <p>Dbar.Cbar.B is obtained from terms 2 and 3, variable A is removed as A + Abar is equivalent to logic 1, which anded with the remaining variables, goes out.</p>			

6	(d)		5
---	-----	--	---

UMS conversion calculator: www.aga.org.uk/umsconversion