



**General Certificate of Education (A-level)
June 2013**

Electronics

ELEC2

(Specification 2430)

Unit 2: Further Electronics

Final

Mark Scheme

Mark schemes are prepared by the Principal Examiner and considered, together with the relevant questions, by a panel of subject teachers. This mark scheme includes any amendments made at the standardisation events which all examiners participate in and is the scheme which was used by them in this examination. The standardisation process ensures that the mark scheme covers the students' responses to questions and that every examiner understands and applies it in the same correct way. As preparation for standardisation each examiner analyses a number of students' scripts: alternative answers not already covered by the mark scheme are discussed and legislated for. If, after the standardisation process, examiners encounter unusual answers which have not been raised they are required to refer these to the Principal Examiner.

It must be stressed that a mark scheme is a working document, in many cases further developed and expanded on the basis of students' reactions to a particular paper. Assumptions about future mark schemes on the basis of one year's document should be avoided; whilst the guiding principles of assessment remain constant, details will change, depending on the content of a particular examination paper.

Further copies of this Mark Scheme are available from: aqa.org.uk

Copyright © 2013 AQA and its licensors. All rights reserved.

Copyright

AQA retains the copyright on all its publications. However, registered schools/colleges for AQA are permitted to copy material from this booklet for their own internal use, with the following important exception: AQA cannot give permission to schools/colleges to photocopy any material that is acknowledged to a third party even for internal use within the centre.

Set and published by the Assessment and Qualifications Alliance.

Question	Part	Subpart	Marking guidance	Mark
1	(a)		Feedback resistor from output to –ve input Correct inverting or non-inverting amplifier circuit For inverting, 4.7kΩ and 470kΩ in the correct place For non-inverting, 4.7Ω input resistor AND two resistors in ratio of 99/100	4
1	(b)		Formula 120mV 0.12V (No unit error if obvious)	2
1	(c)		<p>Open loop voltage gain.</p> <p>Positive gradient = no marks Correct intercept on vertical axis Correct intercept on horizontal axis Straight line joining</p>	3

1	(d)		(No possible ecf from (c)) Calculation 10kHz		2
2	(a)	(i)	D to \overline{Q} Input to CK Outputs Q or \overline{Q}		3
2	(a)	(ii)	Output half the frequency of the input Output only changes on rising edge of input		2
2	(b)	(i)	Sensible calculation 2.4 (kHz)		2
2	(b)	(ii)	\overline{Q} to next clock D to \overline{Q} AND inputs to 1 and 4 AND output to joined Resets		4
3	(a)		Resistor between $+V_s$ and discharge Resistor between discharge and trigger Trigger and threshold connected C between threshold and 0V		4
3	(b)		Formula Correct substitution 477.6 Hz (Not 480Hz)		3
3	(c)		Formula Substitution 108 - 109k Ω (108.591k Ω)		3

3	(d)		(Do not accept changes to R_A) Mention of variable resistor ✓ Replace R_B with next smallest preferred value and put a small value variable resistor in series. ✓✓ (Sensible answer with variable capacitor ✓✓)		2
4	(a)		Any mention of RxC ✓ $T = RC = 32s$ ✓ $T = 5RC = 160s$ ✓		3
4	(b)		$T = RC$ only $T = 5 \times 4.7$ 23.5s		3
4	(c)		Formula Substitution 2.35F		3
4	(d)		Different leakage currents (or mention of the resistance of the dielectric) Large tolerance so different values.		2
5	(a)	(i)	Calculation Answer (400Hz)		2
5	(a)	(ii)	Calculation Answer (0.15V) (Accept 0.14V) (P to P = 0.3V, one mark only)		2
5	(a)	(iii)	Calculation Answer (3.52W) (7W, one mark only)		2
5	(b)		Cross over distortion (Negative) feedback from output (MOSFET sources), (speaker) Bias output transistors into conduction (implication) (Allow mention of diode/LEDs if cross over distortion mentioned)		3

5	(c)		50% of maximum power output Giving answer of 20Hz to around 300kHz (If 70% 50Hz – 100kHz then 1 max only)		2
6	(a)		Feedback resistor to inverting input Series inverting input resistor Series non-inverting input resistor Resistor from non- inverting input to 0V – same value as R_f All resistors in range 1k Ω to 1M Ω Must have negative feedback then ratio of gain resistors = 100		6
6	(b)	(i)	3V		1
6	(b)	(ii)	0V No difference The same		1
6	(c)		e.g. New resistor values of 198 Ω and 202 Ω (1% change) Calculation of change in voltage $\frac{6 \times 198}{400} = 3.03V$ so change is 0.03V New output voltage = 0.03 x 100 = 3V		3