



Please write clearly in block capitals.

Centre number

--	--	--	--	--

Candidate number

--	--	--	--

Surname

Forename(s)

Candidate signature

AS ELECTRONICS

Unit 1 Introductory Electronics

Tuesday 17 May 2016

Afternoon

Time allowed: 1 hour

Materials

For this paper you must have:

- a pencil and a ruler
- a calculator
- Data Sheet (enclosed).

Instructions

- Use black ink or black ball-point pen.
- Fill in the boxes at the top of this page.
- Answer **all** questions.
- You must answer the questions in the spaces provided. Do not write outside the box around each page or on blank pages.
- Do all rough work in this book. Cross through any work you do not want to be marked.

Information

- The marks for each question are shown in brackets.
- The maximum mark for this paper is 67.



J U N 1 6 E L E C 1 0 1


IB/M/Jun16/E4

ELEC1

Answer **all** questions in the spaces provided.

- 1** The logic diagram in **Figure 1** shows how two inputs **A** and **B** produce an output **Q**.

Figure 1

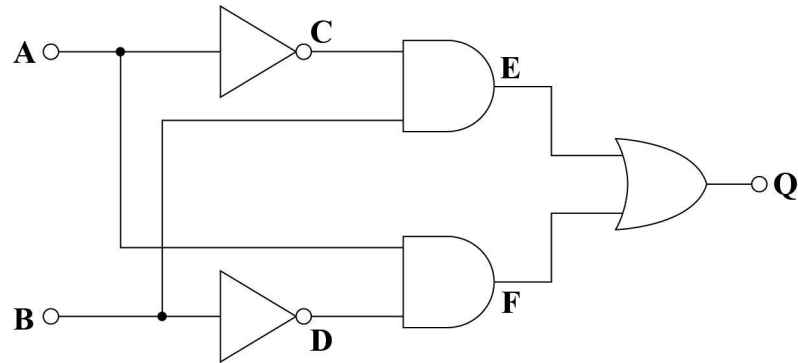

- 1 (a)** Complete the truth table shown in **Table 1** for this logic diagram.

[5 marks]

Table 1

B	A	C	D	E	F	Q
0	0					
0	1					
1	0					
1	1					

- 1 (b) (i)** Write the Boolean expression for point **E** in **Figure 1** in terms of inputs **A** and **B** only.

[1 mark]

E = _____



1 (b) (ii) Write the Boolean expression for point **F** in **Figure 1** in terms of inputs **A** and **B** only.

[1 mark]

F = _____

1 (b) (iii) Write the Boolean expression for the output **Q** in **Figure 1** in terms of inputs **A** and **B** only.

[2 marks]

Q = _____

1 (c) Circle the single logic gate that could be used to replace the function represented in **Figure 1**.

[1 mark]

AND

EXOR

NOR

NAND

OR

Turn over for the next question

10



2 The information below describes how smart washing machines warn people that there is too much washing in the drum and that the machine is overloaded.

- A load sensor detects the weight of washing in the drum and produces an output voltage.
- The load sensor output voltage increases as the weight of washing detected increases.
- When the weight of washing exceeds a preset maximum, a logic 1 is produced by a comparator circuit.
- The comparator output is gated together with a logic level audio frequency signal and a slow astable signal.
- The overall effect is to generate a pulsed tone, which warns of an overload.

2 (a) Using the following subsystems, draw a possible design for this system.

adjustable voltage reference

audio frequency generator

comparator

driver

load sensor

loudspeaker

3-input logic gate

slow astable

[7 marks]

2 (b) (i) Name the subsystem most likely to contain a MOSFET.

[1 mark]

2 (b) (ii) Name the subsystem most likely to contain a potentiometer.

[1 mark]


2 (b) (iii) Name the subsystem most likely to contain an operational amplifier.

[1 mark]

10



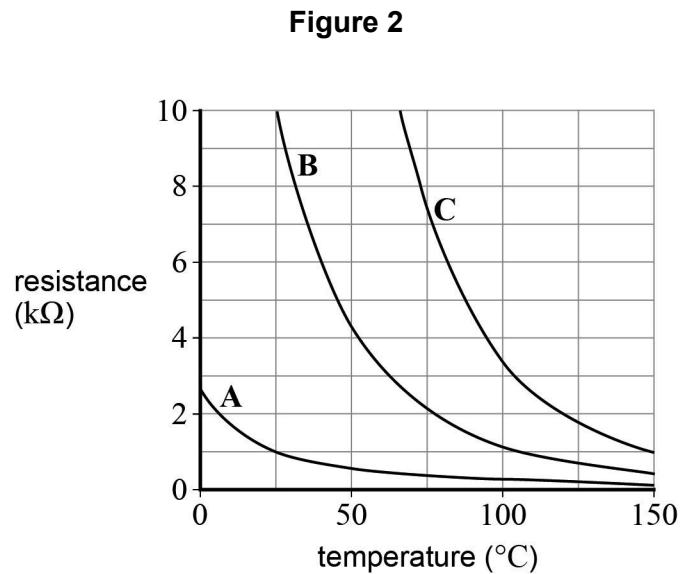- 3** **Figure 2** shows the characteristic curves of three different NTC thermistors, **A**, **B** and **C**.



- 3 (a) (i)** State what the letters NTC stand for.

[1 mark]

- 3 (a) (ii)** State how you can tell from the characteristic curves that **A**, **B** and **C** are NTC thermistors.

[1 mark]

- 3 (b)** A particular industrial process needs a thermistor that has a high sensitivity to small temperature variations in the 75–100 °C temperature range.

State with a reason which thermistor, **A**, **B** or **C**, should be used.

[2 marks]

Thermistor _____

Reason _____



3 (c) Thermistor **A** is selected to monitor another stage in the process.

In this stage, an operational amplifier is used as a comparator to control a red LED and a green LED.

The circuit is designed to:


- only turn on the red LED when the temperature of a liquid is above 25 °C
- only turn on the green LED when the temperature of a liquid is below 25 °C.

Complete the circuit diagram in **Figure 3** showing the following:

- a 2 k Ω resistor, which together with the thermistor forms a voltage divider to produce a voltage that changes as the detected temperature changes
- two resistors arranged as a voltage divider to provide a fixed reference voltage
- suitable values for these two resistors
- correct connections from the voltage dividers to the operational amplifier inputs.

[5 marks]

Figure 3

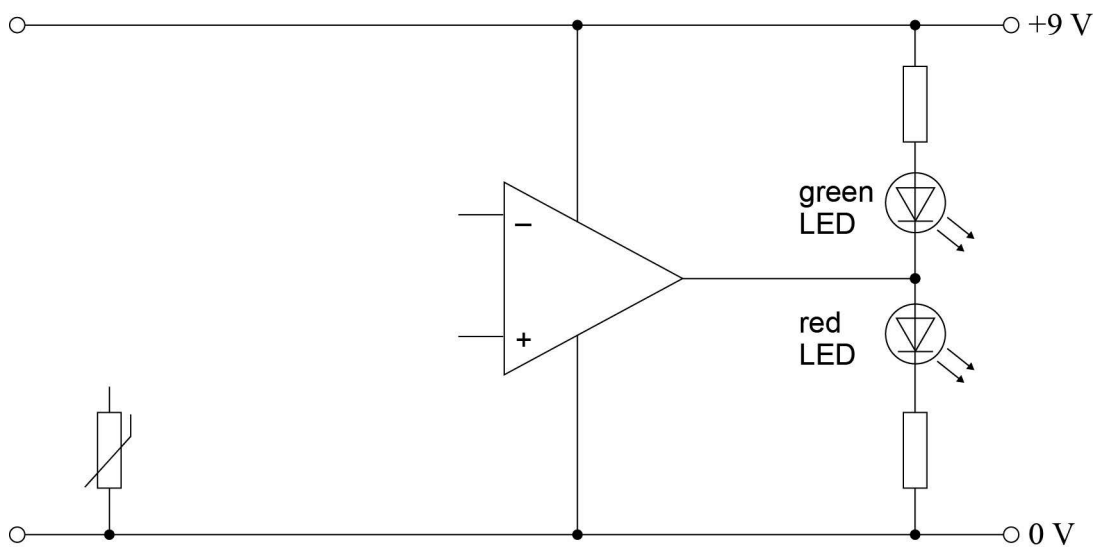

- 3 (d)** When the circuit was built and tested, the green LED performed as expected but the red LED stayed on dimly even when the temperature was below 25°C.

The LEDs used have the characteristics shown in **Table 2**.

Table 2

	Wavelength	Minimum voltage to turn LED on
Green	470–505 nm	2.5 V
Red	630–660 nm	1.7 V

Explain why the red LED did **not** switch off completely whereas the green LED did.

Use the information in **Table 2** and your knowledge of **real** operational amplifiers to help explain your answer.

[3 marks]


Turn over for the next question

12



- 4 The graph in **Figure 4** shows part of the characteristic for a Zener diode.

Figure 4

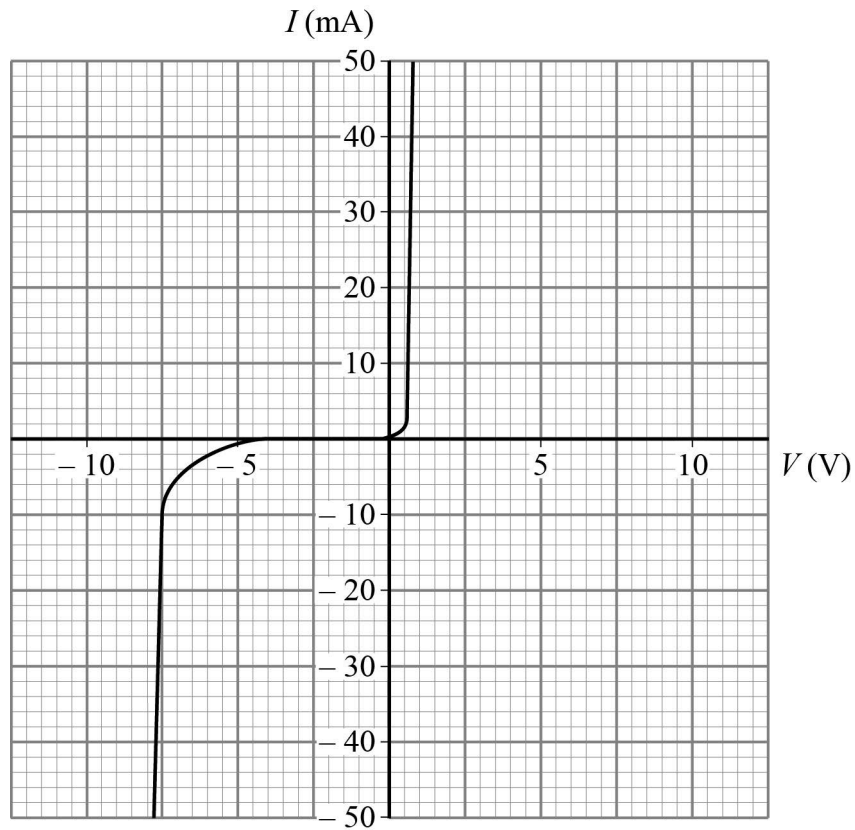

- 4 (a) (i) Estimate from the graph in **Figure 4** the Zener voltage of this Zener diode.

[1 mark]

- 4 (a) (ii) Estimate from the graph in **Figure 4** the minimum current at which this Zener diode should be used.


[1 mark]



- 4 (b)** A student designs a 5 V power supply with a USB socket for use in her car.
- The power supply runs off the car's battery and contains a simple voltage regulator.
- The regulator includes a resistor and a 5.1 V Zener diode.
- Draw on **Figure 5** the Zener diode in the correct position to complete the voltage regulator circuit.

[3 marks]

Figure 5

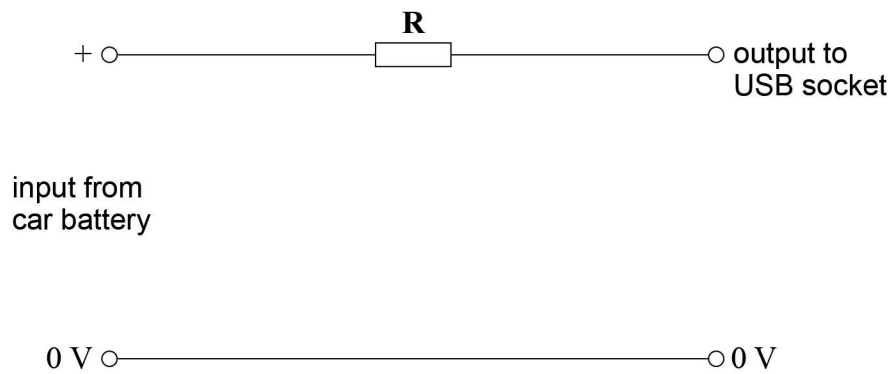

Question 4 continues on the next page



4 (c) The power supply must be capable of providing a current of 500 mA to any device that is plugged into it.

The chosen Zener diode needs 5 mA to maintain the 5.1 V Zener voltage.

4 (c) (i) Assume that the car's battery voltage is 12 V.

Calculate the theoretical value of resistor **R** needed for the regulator circuit.

[3 marks]

4 (c) (ii) Select a suitable resistor value for **R** from the E24 series.

Give a reason for your choice.

[3 marks]

E24 series resistor value _____

Reason _____

4 (c) (iii) Calculate the maximum power that would be dissipated by the Zener diode.


[3 marks]

14



- 5 **Figure 6** shows the relay circuit stage for an outdoor security light. The light is powered by the mains and activated by a Passive Infrared (PIR) detector. The relay (in the dotted box) is shown in its unpowered state.

Figure 6

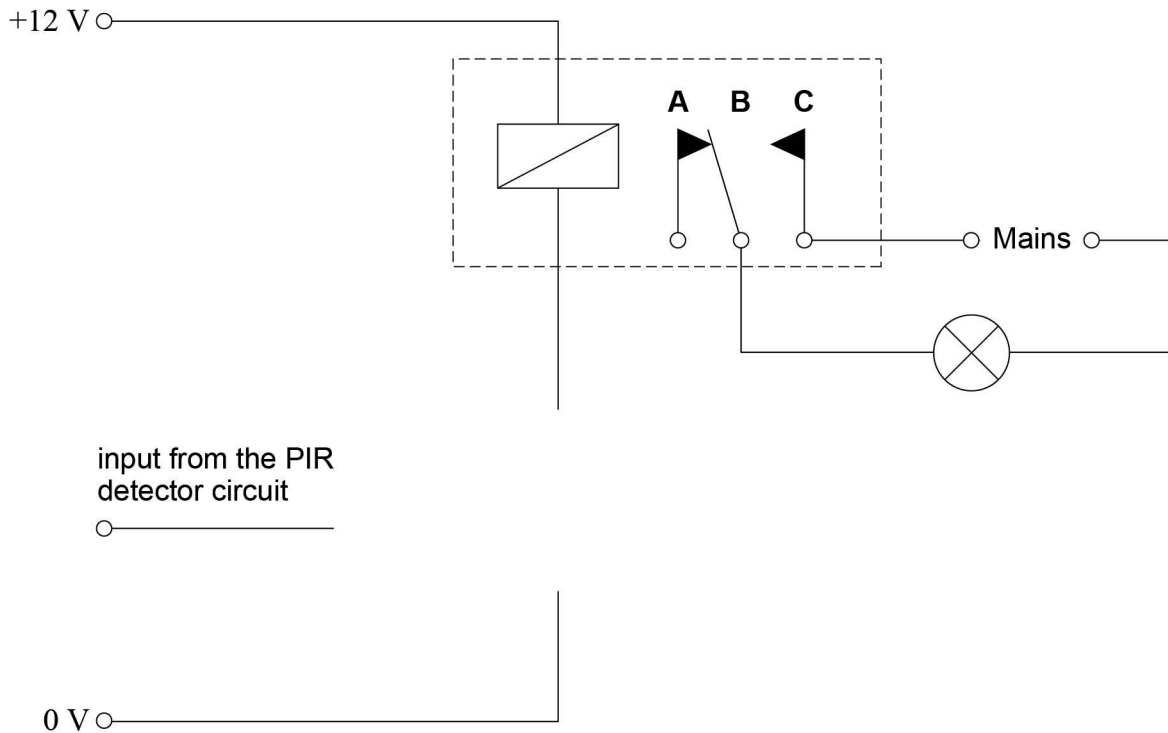

- 5 (a) (i) Draw on **Figure 6** an npn bipolar transistor together with its input resistor, so it can act as a driver for the relay. [2 marks]
- 5 (a) (ii) Draw on **Figure 6** the diode needed to protect the transistor. [2 marks]
- 5 (a) (iii) Explain why diode protection is needed **and** how the diode achieves this. [2 marks]



5 (b) The relay coil has a resistance of 160Ω and must be used on a 12 V supply to operate correctly. The PIR detector circuit can only supply 0.5 mA.

Show that the current gain (I_c / I_b) for the transistor must be at least 150 for the circuit to work.

[3 marks]

5 (c) Tick (✓) the box next to the row of information in **Table 3** that best describes the relay being used in this application.

[1 mark]

Table 3

Contact A	Contact B	Contact C	Configuration	
NC	COM	NO	SPST	
COM	NC	NO	SPDT	
NC	COM	NO	SPDT	
NO	COM	NC	SPDT	
NO	COM	NC	SPST	

5 (d) State **one** advantage of using an n-channel MOSFET instead of the npn bipolar transistor as the driver in **Figure 6**.

[1 mark]

11



6 A small company has a total of 60 shares that are held by three shareholders.

- Mr **A**ndrews holds **10** shares (voting button **A**).
- Mrs **B**rown holds **20** shares (voting button **B**).
- Mrs **C**larke holds **30** shares (voting button **C**).

At a board meeting, each shareholder may vote to cast **all** their shares in support of the plan being discussed by pressing their voting button.

For the plan to be passed, **at least 30 shares** in total must be cast.

A student has been asked to design a logic system that will turn on an LED to indicate when at least 30 shares have been cast in favour of a plan.

6 (a) The logic system works as follows:

- When a voting button is pressed, a logic 1 is produced.
- When at least 30 shares are cast, a logic 1 is produced at output **Q**.

Complete the truth table shown in **Table 4** for this logic system.

[1 mark]

Table 4

C	B	A	Q
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	



- 6 (b)** Explain how the following expression for **Q** represents the correctly completed truth table in part **6 (a)**.

$$Q = A.B.C + \bar{A}.B.C + A.\bar{B}.C + \bar{A}.\bar{B}.C + A.B.\bar{C}$$

[2 marks]

- 6 (c)** Show that the expression for **Q** in part **6 (b)** can be simplified to $Q = (A.B) + C$

You may use either Boolean algebra **or** a Karnaugh map to show how you have arrived at your answer.

[3 marks]



- 6 (d)** **Figure 7** shows the inputs and output for a logic diagram.
When completed it will represent the expression $Q = (A.B) + C$

- 6 (d) (i)** Complete **Figure 7** using the **minimum** number of 2-input logic gates to correctly represent the expression for **Q**.

[2 marks]

Figure 7

A ○ —————

B ○ —————

C ○ —————

————— ○ Q

- 6 (d) (ii)** Complete **Figure 8** to correctly represent the expression **Q** using **NAND** gates only.

[2 marks]

Figure 8

A ○ —————

B ○ —————

C ○ —————

————— ○ Q

10

END OF QUESTIONS



There are no questions printed on this page

**DO NOT WRITE ON THIS PAGE
ANSWER IN THE SPACES PROVIDED**

Copyright Information

For confidentiality purposes, from the November 2015 examination series, acknowledgements of third party copyright material will be published in a separate booklet rather than including them on the examination paper or support materials. This booklet is published after each examination series and is available for free download from www.aqa.org.uk after the live examination series.

Permission to reproduce all copyright material has been applied for. In some cases, efforts to contact copyright-holders may have been unsuccessful and AQA will be happy to rectify any omissions of acknowledgements. If you have any queries please contact the Copyright Team, AQA, Stag Hill House, Guildford, GU2 7XJ.

Copyright © 2016 AQA and its licensors. All rights reserved.

