

Electronics

Advanced GCE

Unit **F615**: Communications Systems

Mark Scheme for June 2012

OCR (Oxford Cambridge and RSA) is a leading UK awarding body, providing a wide range of qualifications to meet the needs of candidates of all ages and abilities. OCR qualifications include AS/A Levels, Diplomas, GCSEs, OCR Nationals, Functional Skills, Key Skills, Entry Level qualifications, NVQs and vocational qualifications in areas such as IT, business, languages, teaching/training, administration and secretarial skills.

It is also responsible for developing new specifications to meet national requirements and the needs of students and teachers. OCR is a not-for-profit organisation; any surplus made is invested back into the establishment to help towards the development of qualifications and support, which keep pace with the changing needs of today's society.

This mark scheme is published as an aid to teachers and students, to indicate the requirements of the examination. It shows the basis on which marks were awarded by examiners. It does not indicate the details of the discussions which took place at an examiners' meeting before marking commenced.

All examiners are instructed that alternative correct answers and unexpected approaches in candidates' scripts must be given marks that fairly reflect the relevant knowledge and skills demonstrated.

Mark schemes should be read in conjunction with the published question papers and the report on the examination.

OCR will not enter into any discussion or correspondence in connection with this mark scheme.

© OCR 2012

Any enquiries about publications should be addressed to:

OCR Publications
PO Box 5050
Annesley
NOTTINGHAM
NG15 0DL

Telephone: 0870 770 6622
Facsimile: 01223 552610
E-mail: publications@ocr.org.uk

Question			Answer	Mark	Guidance
1	a	i	$2^6 = 64$ (which is greater than 42);	1	accept $\log_2 42 = 5.4$ (which rounds up to 6) look for use of the 2^n rule to justify 6 bits not just $2^5 = 32$ (so need 6 bits)
1	a	ii	any three of the following, [1] each: <ul style="list-style-type: none"> • extra bits on either side of (six-bit) data word; • start bit to tell screen that word is about to arrive; • stop bit to allow next start bit to be recognised / restores line to resting state; • start is 0, stop is 1 / start and stop have different values; 	3	ignore references to function of six-bit word not just extra bits are called start and stop accept receiver
1	a	iii	word rate = $1024 \times 1280 \times 40 = 5.243 \times 10^7 \text{ s}^{-1}$; bit rate = $5.243 \times 10^7 \times 8 = 4.194 \times 10^8 \text{ s}^{-1}$; bandwidth = 209.7 MHz	1 1 1	ecf incorrect word rate ecf incorrect bit rate accept 210 / 209 MHz
1	b		any three of the following, [1] each: <ul style="list-style-type: none"> • raster scan delivers (video) signal to each LED in turn; • from one end of a row to the other (owtte); • line sync signal indicates start of the next row; • frame sync signal indicates start of the next frame; 	3	accept pixel for LED accept start of first line instead of new frame
1	c		one cable each for red and blue signals; to control intensity of red and blue LEDs / pixels; (full colour) requires red, blue and green;	1 1 1	accept separate cables for red, green and blue look for stepped analogue not binary signal accept RGB
2	a	i	amplitude = 10 mV; period = 200 μs frequency = 5 kHz	1 1 1	ecf incorrect period
2	a	ii	bandwidth = 10 kHz	1	ecf: 2×frequency from (i) for [1]

Question			Answer	Mark	Guidance
2	b	i		3	carrier spike at 400 kHz [1] sideband spikes, same size, less than (half size of) carrier spike [1] at 407 kHz and 393 kHz (by eye) [1]
2	b	ii		4	correct circuit symbols [1] correct circuit, including labels and 0 V [1] use of $f_0 = 1/2\pi RC$ to justify values [1] $1.6 \mu s (f_0 = 100 \text{ kHz}) \leq RC \leq 16 \mu s (f_0 = 10 \text{ kHz})$ [1] accept any value of $R \geq 1k\Omega$ accept
3	a		frequency of carrier; fixed by voltage of signal;	1	
3	b		<input checked="" type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> <input checked="" type="checkbox"/>	2	correct pattern for [2] one mistake for [1]

Question			Answer	Mark	Guidance
3	c	i		3	correct first box for [1] accept logic gate / limiter / inverter for Schmitt trigger correct second box for [1] correct third box for [1] accept smoother / filter for treble cut filter accept monostable anywhere before filter for [2] accept monostable anywhere for [1]
3	c	ii	Schmitt trigger (removes noise by) converting signal to a square wave; monostable produces a fixed length pulse (at start of each cycle); filter removes frequency components above audio frequency / removes carrier;	1 1 1	each correct description of a stage for [1], no ecf on 3ci
4	a			4	each correct entry for [1]
4	b	i	$(+3 \times 1.5 - 3 \times 1.0) / 2.5 = 0.60 \text{ V}$	1	look for calculation of average voltage
4	b	ii	(PWM) sampling frequency = $1/2.5 \times 10^{-3} = 400 \text{ Hz}$; must sample (at least) twice in each cycle;	1 1	look for working out of frequency from graph accept working backwards from 400 Hz to 2.5 ms not just $200 = 400 / 2$ accept reference to Nyquist criterion

Question			Answer	Mark	Guidance
5	c			3	each correct link for [1] reject multiple links
5	d		any three of the following, [1] each <ul style="list-style-type: none"> • Schmitt triggers / limiters; • can remove noise / recover information; • for FM and PWM but not AM / FM and PWM have greater SNR than AM; • noise affects amplitude more than frequency • FM and PWM are digital, AM is analogue (owtte) 	3	accept interference as noise not cleans up signal
6	a	i		2	correct circuit [1] input, output and 0 V correctly labelled on correct circuit [1]
6	a	ii	$L = \frac{1}{f^2 4\pi^2 C};$ $f = 750 \text{ kHz}$ $f = 750 \times 10^3 \text{ Hz}, C = 47 \times 10^{-12} \text{ F}$ $L = 958 \text{ } \mu\text{H}$	1 1 1 1	evidence of correct rearrangement [1] correct value from graph from 745 to 755 kHz for [1] look evidence of correct units conversion accept 960 μH , ecf incorrect f and units conversion

Question			Answer	Mark	Guidance
6	a	iii	any three of the following for [1] each: <ul style="list-style-type: none"> • at resonant frequency, impedance of LC much larger than R; • so most of signal appears across LC / little signal across R; • above and below resonant frequency, impedance of LC much smaller than R; • so most of signal appears across R / little signal across LC /; • at low frequencies inductor reactance is small, at high frequencies capacitor reactance is small; • L and C only same impedance at resonance, otherwise one always smaller than the other; 	3	look for high quality detail to earn each mark
6	b	i		5	modulators in first two boxes on left [1] correct summing amp [1] correct cable [1] both filters correct [1] demodulator after filter in last pair of boxes [1] accept swapped filters and demodulators for [1]
6	b	ii	bandwidth per channel = $2 \times 5 = 10$ kHz; channels = $12000/10 = 1200$;	1 1	ecf incorrect bandwidth e.g 2400 channels for [1]
7	a			2	correct circuit [1] output and 0 V / earth / ground indicated on correct circuit [1] accept variable capacitor

Question			Answer	Mark	Guidance
7	b		EITHER increase size of rf signal / voltage / current; to detect weak stations / improve sensitivity; OR reduce current / power drawn from tuned circuit; to improve selectivity / reduce bandwidth of tuned circuit;	1 1	not just amplifies / boosts signal not make output louder
7	c		filter centre frequency = 0.35 MHz local oscillator = 27.62 + 0.35 = 27.97 MHz;	1 1	ecf incorrect IF (between 0.40 and 0.30 MHz) for [1] accept 27.62 - 0.35 = 27.27 MHz for [2] look for 4 sig.figs. accept anything from 28.02 MHz to 27.92 MHz for [1] accept anything from 27.32 MHz to 27.22 MHz for [1]
7	d			5	correct circuit [1] input resistor 22 kΩ [1] feedback resistor 35 times input resistor [1] use of $C = 1/2\pi Rf_0$ [1] capacitor 723 pF (accept 700-750 pF) [1] no ecf on incorrect filter circuit for value and justification of C look for $RC = 16 \mu s$
8	a	i	- 0.4;	1	
8	a	ii	A at +5 V; E at $-5 \times 5 \times 10^3 / 40 \times 10^3 = -0.625$ V; resolution = $-0.4 \times -0.625 = 0.25$ V;	1 1 1	ecf from 8ai ecf: A = 1 V gives 0.05 V for [2]
8	a	iii	CBA = 111 and use of summing amplifier formula; top of range is 1.75 V; bottom of range is 0 V;	1 1 1	alternative: $2^3 = 8$ levels so max output = $(8-1) \times 0.25$; ecf on incorrect resolution: top of range = 7 x resolution) for [2], 8 x resolution for [1] ecf: A, B and C at 1 V gives 0.35 V for [1]

Question			Answer	Mark	Guidance
8	b	i		4	all five correct for [4] three or four correct for [3] two correct for [2] one correct for [1]
8	b	ii	<p>any two of the following, [1] each</p> <ul style="list-style-type: none"> • information about setting of multiplexer (X); • so that demultiplexer (Y) is set correctly; • either by adding a destination address to each packet of data; • or by sending synchronisation signals between packets of data; • so that signals at one input always arrive at the correct output • start and stop bits • so that SPC knows when a word arrives (owtte) 	2	ignore references to parity / checksum / data bits
9	a	i	128 kHz	1	

Question			Answer	Mark	Guidance
9	a	ii	any two of the following, [1] each <ul style="list-style-type: none"> • crystal oscillator gives more stable frequency; • transmitter needs to contain matched oscillator; • resistors and capacitors change value with time; • relaxation oscillator would need adjusting to obtain correct value of frequency; • easier to obtain desired frequency than selecting R and C component values; 	2	not more accurate / precise / reliable frequency
9	b	i	any four of the following: <ul style="list-style-type: none"> • \bar{Q} initially high; • counter reset (and ignores pulses) when (its) R is high; • (until pulse at start) copies (1 at) D to Q; • so \bar{Q} goes to 0 • counter no longer reset (and reacts to pulses); • flip-flop resets when C and F both high; • making \bar{Q} high and resetting counter; 	4	
9	b	ii		3	correct square wave for C for [1] D changes on each falling edge of CK for [1] PL goes low and stays low when D goes high for [1] apply ecf from one row to the next one down.
9	c			4	PL correct [1] CK correct [1] Q to either mux input, D from mux output [1] other multiplexer input to c, b, a, 0 and correct output label [1] accept mux inputs in reverse order, ignore second input to first mux
Q			sample from 1b, 1c, 5b, 5d and 9bi		

Quality of Written Communication

3	The candidate expresses complex ideas extremely clearly and fluently. Sentences and paragraphs follow on from one another smoothly and logically. Arguments are consistently relevant and well structured. There will be few, if any, errors of grammar, punctuation and spelling.
2	The candidate expresses straightforward ideas clearly, if not always fluently. Sentences and paragraphs may not always be well connected. Arguments may sometimes stray from the point or be weakly presented. There may be some errors of grammar, punctuation and spelling, but not such as to suggest a weakness in these areas.
1	The candidate expresses simple ideas clearly, but may be imprecise and awkward in dealing with complex or subtle concepts. Arguments may be of doubtful relevance or obscurely presented. Errors in grammar, punctuation and spelling may be noticeable and intrusive, suggesting weaknesses in these areas.
0	The language has no rewardable features.

OCR (Oxford Cambridge and RSA Examinations)
1 Hills Road
Cambridge
CB1 2EU

OCR Customer Contact Centre

Education and Learning

Telephone: 01223 553998

Facsimile: 01223 552627

Email: general.qualifications@ocr.org.uk

www.ocr.org.uk

For staff training purposes and as part of our quality assurance programme your call may be recorded or monitored

Oxford Cambridge and RSA Examinations
is a Company Limited by Guarantee
Registered in England
Registered Office; 1 Hills Road, Cambridge, CB1 2EU
Registered Company Number: 3484466
OCR is an exempt Charity

OCR (Oxford Cambridge and RSA Examinations)
Head office
Telephone: 01223 552552
Facsimile: 01223 552553

© OCR 2012

