


**GCE**  
**AS and A Level**

# **Physics A**

**AS exams 2009 onwards**  
**A2 exams 2010 onwards**

## **Unit 6T: Approved specimen question paper**

**Version 1.0**

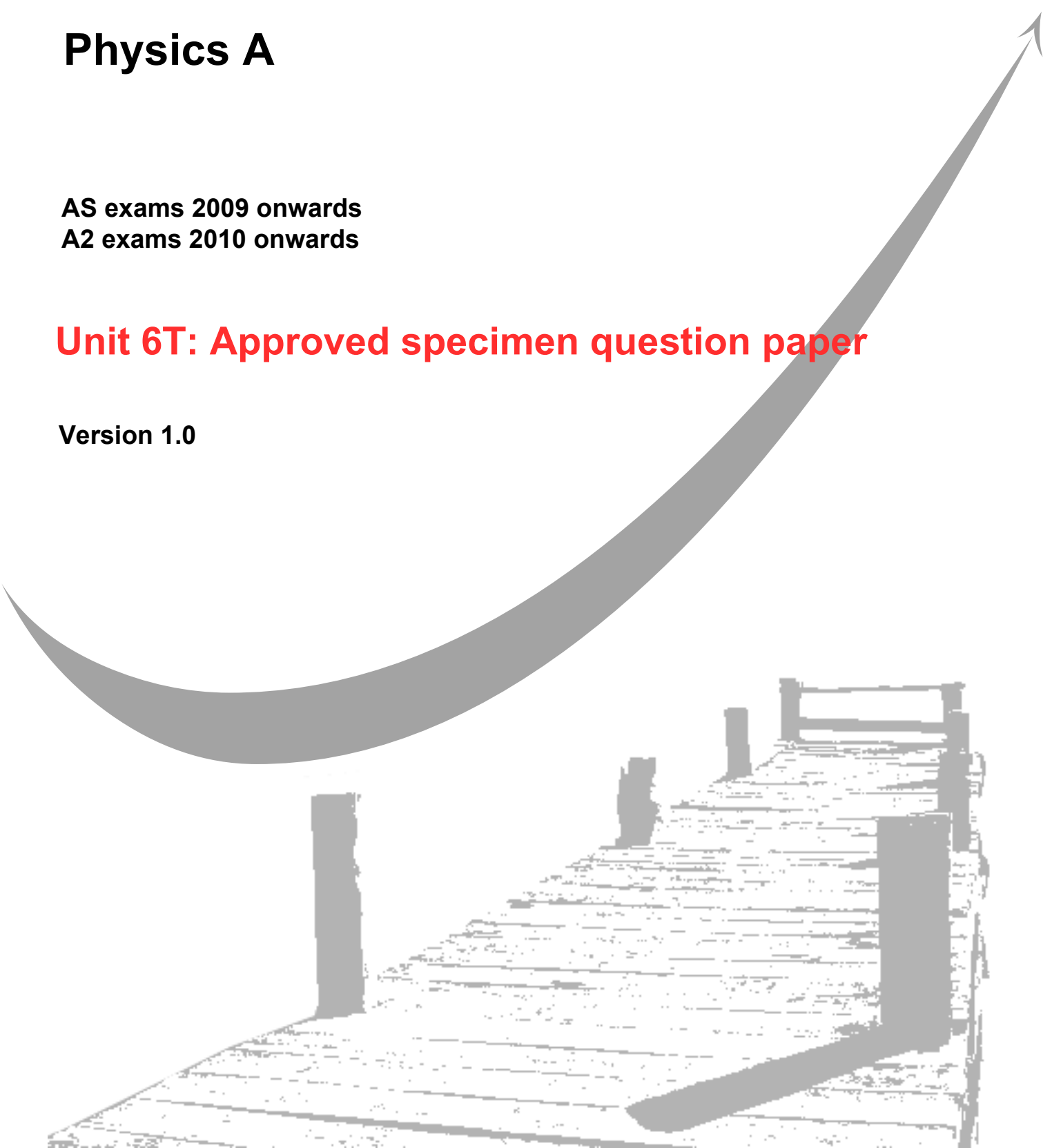

Surname					Other Names				
Centre Number					Candidate Number				
Candidate Signature									

Leave blank

General Certificate of Education  
2010  
Advanced Level Examination



version 1.0

**PHYSICS**  
**Investigative and Practical Skills in A2 Physics**

**Unit 6 ISA**

**PHA6T**

SPECIMEN PAPER

**For this paper you must have:**

- a calculator
- a ruler
- a protractor
- your completed documentation from stage 1

Time allowed: 1 hour

**Instructions**

- Use blue or black ink or ball-point pen.
- Fill in the boxes at the top of this page.
- Answer **all** questions.
- Answer the questions in the spaces provided. A separate sheet of graph paper is required. Attach your graph to this book before handing it to the invigilator at the end of the examination.
- Show all your working.
- Do all rough work in this book. Cross through any work you do not want to be marked.

**Information**

- The maximum mark for this paper is 41.
- The marks for the questions are shown in brackets.

For Examiner's Use			
Sec A	Mark	Sec B	Mark
1		1	
2		2	
3		3	
4		4	
5		5	
		6	
Total (Sec A)			
Total (Sec B)			
TOTAL			
Examiner's Initials			

**SECTION A**

Answer all questions in the spaces provided.  
You should refer to your documentation from Stage 1 as necessary.

- 1** Justify the range you chose for the independent variable when you plotted your graph of the results in Part 1.

.....  
.....  
.....

*(2 marks)*

- 2** (a) From your graph find the peak value of the potential difference across capacitor  $C_2$  for both values of  $R_2$ .

.....  
.....

- (b) Explain the difference between these two voltages.

.....  
.....

*(2 marks)*

- 3** From your graph find the time  $T_m$  at which the voltage peaked for both values of  $R_2$ .

.....  
.....

*(1 mark)*

- 4** Use your graph to estimate the percentage uncertainty in your answer for  $T_m$  with  $R_2 = 100 \text{ k}\Omega$  and explain how you arrived at this estimate.

.....  
.....  
.....  
.....

*(3 marks)*

**5** What was the most significant source of error when you were obtaining your readings in Part 1?

.....  
.....

*(1 mark)*

**6** Estimate  $T_m$  for  $R_2 = 33 \text{ k}\Omega$ . Explain your reasoning.

.....  
.....

*(2 marks)*

**SECTION B**

Answer all questions in the spaces provided.

**1** Theory predicts that

$$T_m = \frac{T_1 T_2}{(T_1 - T_2)} \ln \left( \frac{T_1}{T_2} \right)$$

where  $T_1 = C_1 \times R_1$  and  $T_2 = C_2 \times R_2$ .

(a) Use the formula to calculate  $T_m$  for the discharge in part 1 when  $R_2 = 100 \text{ k}\Omega$ . Compare this value with your answer in Part 2 (3) with reference to your answer from Part 2 (4).

.....  
.....

(b) What is the significance of the product of capacitance and resistance when a capacitor is discharged through a resistor?

.....  
.....  
.....

*(5 marks)*


**2** Describe how you would attempt to verify the formula given in Part 3 (1).

.....  
.....  
.....

*(3 marks)*

In a separated experiment, data was collected for the variation of voltage  $V$  with time  $t$  as capacitor  $C_1$  discharged through a resistor,  $R$ , using the circuit shown in **Figure 2**.

**Figure 2**

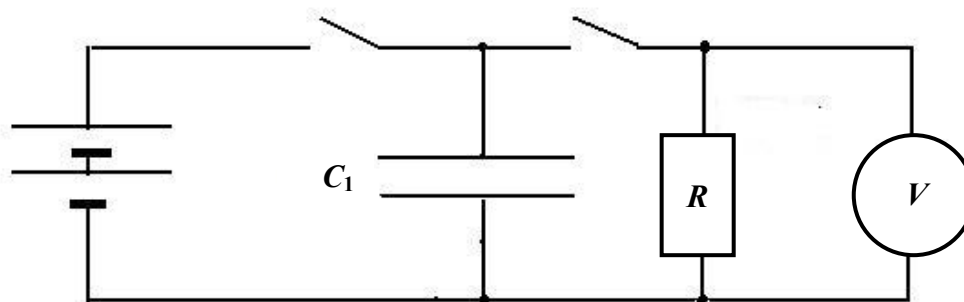

The table in **Figure 3** gives the results from this experiment.

**Figure 3**

$t/s$	0.01	0.02	0.03	0.04	0.05
$V/V$	4.88	3.97	3.23	2.63	2.14

- 3 (a) State what was probably used to obtain these results and explain why?

.....

.....

- (b) Draw a table with three columns for these data. The third column is for  $\ln(V/V)$ .

Complete the table and plot a graph of  $\ln(V/V)$  against  $t$ .

(6 marks)

- 4 (a) Measure the gradient of your graph and hence find a value for the time constant  $\tau$  for the circuit in **Figure 2**, given that

$$V = V_0 e^{-t/\tau}$$

.....  
.....

- (b) Use the graph to find  $V_0$ .

.....  
.....  
.....

*(7 marks)*

- 5 Capacitor discharge is a good model for the nuclear decay of a sample of a radioisotope, since both processes have a constant half-life. Quite often one radioisotope decays into another with a shorter half-life. By considering your results from the experiment in Part 1, suggest the conditions necessary for the number of atoms of the second radioisotope to remain constant for a number of years.

.....  
.....  
.....  
.....

*(2 marks)*

Surname					Other Names				
Centre Number					Candidate Number				
Candidate Signature									

Leave blank



General Certificate of Education  
2010  
Advanced Examination

version 1.0

**PHYSICS A** **PHA6T**  
**Unit 6: Practical and Investigative Skills in A2 Physics**

**Specimen ISA**

Centre Instructions for the Investigation



**PHA6T****Centre instructions for the Investigation**

In this ISA, candidates will be investigating the discharge of a capacitor through an arrangement of two resistors and another capacitor.

The following components will be required for the circuit.

- three resistors; 47 k $\Omega$ , 100 k $\Omega$ , 470 k $\Omega$
- capacitors; 220  $\mu$ F, 100  $\mu$ F
- three switches
- battery (either 3V or 6V)
- voltmeter
- leads
- stopclock or equivalent

**Information for Centres**

Candidates can be told approximately one week before undertaking Stage 1 of the ISA that they will be investigating the discharge of a capacitor through a circuit. Preparation could include the revision of the following topics:

Exponential decay

Capacitor discharge (including time constants)

Radioactive nuclear decay (including half-life)

Stage 2 of the ISA, (the written tests; Section A & B) should be given as soon as possible after the practical investigation.

## PHA6T

## Task Sheet

## Stage 1: Investigation


You are going to investigate the discharge of a capacitor through an arrangement of two resistors and another capacitor.

You are provided with various components.

- Set up the circuit shown in **Figure 1**.

**Ensure that the negative terminals of the capacitors are connected to the negative terminal of the battery as shown on the circuit diagram.**

**Figure 1**

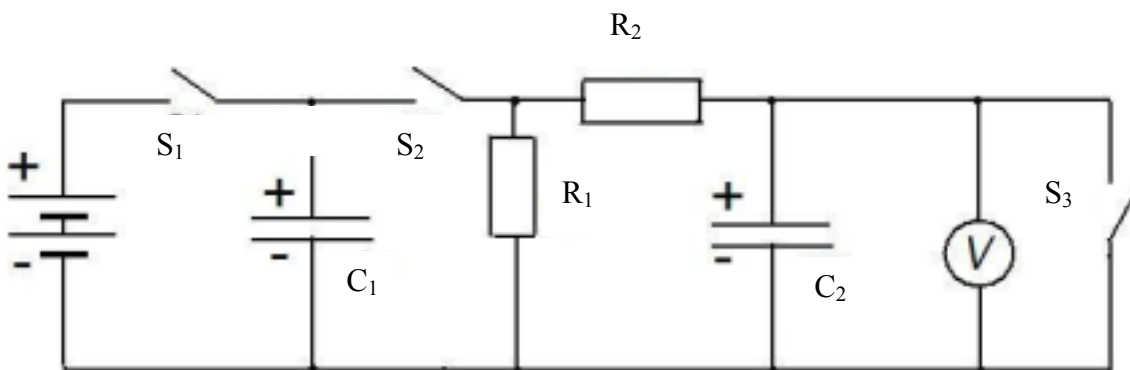

Component values:  $R_1 = 470 \text{ k}\Omega$ ,  $R_2 = 100 \text{ k}\Omega$ ,  $C_1 = 220 \text{ }\mu\text{F}$ ,  $C_2 = 100 \text{ }\mu\text{F}$

You should follow the instructions as listed below;

**Instruction 1**

Open switches S<sub>2</sub> and S<sub>3</sub> and close S<sub>1</sub>. The capacitor C<sub>1</sub> will now be fully charged.

**Instruction 2**

Close S<sub>3</sub>: the voltmeter reading should fall to zero showing that C<sub>2</sub> is fully discharged.

**Instruction 3**

Open S<sub>3</sub>, open S<sub>1</sub> and then close S<sub>2</sub>. C<sub>1</sub> will now discharge through R<sub>1</sub>, R<sub>2</sub> and C<sub>2</sub>. Observe the reading on the voltmeter for the next couple of minutes. This should increase to a maximum value and then start to decrease again.

---

**If the voltmeter reading does not change in this way ask for help from your teacher.**

Repeat **Instructions 1 and 2.**

Using the stopclock provided, take sufficient readings to plot an accurate graph of  $V$  against  $t$ .  $V$  is the potential difference across  $C_2$  and  $t$  is the time after  $S_2$  is closed.

- Present your results in a table.

Replace  $R_2$  with the  $47\text{ k}\Omega$  resistor and repeat the experiment.

- Record your results in a second table.
- Draw your graphs  $V$  against  $t$  using the same axis.

**At the end of the investigation, please hand the following in to your teacher.**

- Your completed answer sheet(s) which should include two results tables.
- A sheet of graph paper with your  $V$ - $t$  graph.

**This documentation will be required for Stage 2 of the ISA. Please ensure you have entered your centre details, candidate number and name on all the sheets you have completed.**