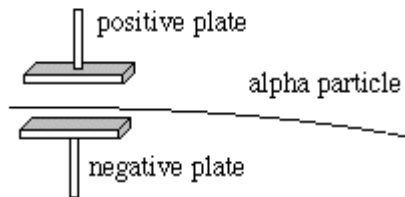


ELECTRIC FIELD & CAPACITOR MODEL SOLUTION

1.



$$\begin{aligned}\text{Electric field, } E &= V / d \\ &= 2000 / 10 \times 10^{-3} \\ &= \underline{2.0 \times 10^5 \text{ V m}^{-1}}\end{aligned}$$

$$\begin{aligned}\text{Electric force, } F &= QE \\ &= [2 \times 1.6 \times 10^{-19}][2.0 \times 10^5] \\ &= \underline{6.4 \times 10^{-14} \text{ N}}\end{aligned}$$

2. Capacitors in Parallel

$$\begin{aligned}\text{Charge on } C_1, Q &= CV \\ &= 12\mu \times 6 \\ &= \underline{72\mu\text{C}}\end{aligned}$$

$$\begin{aligned}\text{Energy} &= \frac{1}{2} CV^2 \\ &= \frac{1}{2} \times 12\mu \times 6^2 \\ &= \underline{216 \mu\text{J}}\end{aligned}$$

Capacitors in Series

$$\begin{aligned}\text{Charge on } C_2, Q &= CV \\ &= [12^{-1} + 12^{-1}]^{-1} \mu \times 6 \\ &= \underline{36 \mu\text{C}}\end{aligned}$$

$$\begin{aligned}\text{Total energy stored on } C_1 \text{ and } C_2 &= \frac{1}{2} [12^{-1} + 12^{-1}]^{-1} \mu \times 6^2 \\ &= \underline{108 \mu\text{J}}\end{aligned}$$

PREPARED BY MR.DERYK NG
UCSI UNIVERSITY
A LEVEL ACADEMY