

- 1 (a) Any **two** from:
 Travel through a vacuum (NOT travel through 'space', but allow 'free space')
 Travel at the speed of light / 3.0×10^8 (ms⁻¹) (in vacuum)
 They consist of photons
 Consist of oscillating electric and magnetic fields
 They are transverse wave / they can be polarised
 They can be diffracted / reflected / refracted / interfered
 (-1 for each contradictory statement) **B1x2**
- (b) $v = f\lambda$ / $c = f\lambda$ (Wave equation with any sub,ect) **C1**
 $\lambda = 3.0 \times 10^8 / 1.6 \times 10^9$ **C1**
 $\lambda = 0.188 = 0.19$ (m) **A1**
- (c) Wavelength in the range 10^{15} to 10^{17} (m) **B1**
 (Allow upper limit of 10^{18} (m) for the wave length) **[Total 6]**
- 2 (a) Arrow (within the lemon and) towards the negative terminal **B1**
- (b)(i) $\Delta Q = I\Delta t$ (Allow other subject, Δt is not necessary) **C1**
 charge = $1.2 \times 10^{-3} \times 6.9 \times 10^6$ **C1**
 charge = 828 = 830 (C); (-1 for 10^6 error and -1 for $t = 8$ days) **A1**
- (ii) $P = VI$ **C1**
 $P = 1.32 \times 1.2 \times 10^3$ (ECF for current from b(i)) **C1**
 $P = 1.58 \times 10^3 = 1.6 \times 10^3$ **A1**
 Unit: W / Js⁻¹ / VA **B1**
- [Total 7]**
- 3 (a) $R = \frac{R_1 R_2}{R_1 + R_2}$ / $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$ / $R = \frac{180 \times 120}{180 + 120}$ / $\frac{1}{R} = \frac{1}{120} + \frac{1}{180}$ **C1**
- $R = 72$ (Ω) (-1 for each error) **A1**
- $R_{\text{ex}} = 72 + 100 = 172$ (Ω) (Allow 170) (Possible ECF) **A1**
- (b) Any **four** marks from:
 Resistance of thermistor decreases as temperature increases (ors) **B2**
 (Resistance of circuit changes with temperature scores 1 mark)
 The voltmeter reading / voltage stays constant / at 4.5 (V) (AW) **B1**
 The ammeter reading / current increases **B1**
 The current is inversely proportional to the resistance of the thermistor **B1**
- One mark for QWC (Spelling and grammar) **B1**
- [Total 8]**

2822

Mark Scheme

June 2003

4	<p>(a) $V = 0.014 \times 160$ $V = 2.24 \text{ V} \approx 2.2 \text{ V}$</p> <p>(b) $V = 12 - 2.24$ $V = 9.76 \text{ (V)} \approx 9.8 \text{ (V)}$</p> <p>(c)(i) area = $\pi \times (4.0 \times 10^{-2})^2$; area = $\pi \times 4.0^2 \times 10^{-4}$ area = $5.03 \times 10^{-4} \text{ (m}^2\text{)} \approx 5.0 \times 10^{-4} \text{ (m}^2\text{)}$</p> <p>(ii) $R = \rho \times l/A$ (Allow any subject); $R = 1.7 \times 10^{-2} \times 0.85 / 5.0 \times 10^{-4}$ C1 $R = 2.9 \times 10^1 \text{ (}\Omega\text{)}$ (1 if $5.0 \times 10^{-4} \text{ (m}^2\text{)}$ is not used from (i)) C1 A1</p> <p>(iii) The resistance decreases by a factor of eight; because area increases by a factor of four and length decreases ($3.6 \times 10^{-3} \text{ (}\Omega\text{)}$ with correct working scores 2/2) ($3.6 \times 10^{-3} \text{ (}\Omega\text{)}$ without working scores 1/2) (Allow 1/2 for 'Resistance decreases by a factor of four because length decreases and area increases by a factor of two scores')</p>	<p>M1 A0</p> <p>B1</p> <p>M1 A0</p> <p>C1 C1 A1</p> <p>M1 A1</p>
[Total 8]		
5	<p>A correct potential divider circuit with LDR, voltmeter (variable) resistor and cell (allow a battery)</p> <p>Correct symbols for LDR, cell (allow battery), variable resistor and voltmeter</p> <p>(-1 for an error or omission)</p> <p>Any five from: (These must be stated and not from the diagram)</p> <p>The (variable) resistor and LDR are connected in series (to the cell)</p> <p>The voltmeter is placed across (variable) resistor / LDR</p> $V = \frac{R_2 V}{R_1 + R_2} \quad ; \quad \frac{V_1}{I_1} = \frac{R_1}{I_1} \quad \text{quoted}$ <p>The resistance of LDR decreases as intensity of light increases (AW); Correct description of how voltage/voltmeter reading changes with light intensity</p> <p>The change in voltage / voltmeter reading is justified in terms of potential divider / ratio of resistance values / $I = V/(R_1 + R_2)$ and $V = IR_2$</p> <p>Correct description of how the (circuit) current is affected by intensity</p> <p>The variable resistor is used for 'sensitivity' / determining 'range' / 'calibration' / (monitor) different light levels</p> <p>One mark for GWC (Organisation)</p>	<p>B1 B1 B1</p> <p>B1 B1</p> <p>B1 B1</p> <p>B1 B1</p> <p>B1</p>
[Total 9]		

6	(a)(i)	Into (plane of) paper	B1
	(ii)	Correct region to the left of the conductor	B1
	(b)	$F = BiL$ (Allow any subject) $B = 3.0 \times 10^{-2} / (0.2 \times 0.027)$ $B = 5.56 \times 10^{-2} \approx 5.6 \times 10^{-2}$ units: tesla / T / NA ⁻¹ / Wb m ⁻²	C1 A1 B1
[Total 5]			
7	(a)	(1 eV) is the work (done) / energy gained / transformed by an electron traveling / accelerated through / across a p.d. / voltage of 1 V (Allow a proton instead of an electron) $1 \text{ eV} = 1.6 \times 10^{-19} \text{ (J)}$ (Ignore omission of unit but NOT $1.6 \times 10^{19} \text{ C}$)	B1 B1
	(b)	energy, photon and (photo)electron respectively (Allow 'momentum' / 'charge' instead of 'energy' for the first marking point)	B1 × 3
	(c)(i)	energy of photon = work function energy / $hf = \phi$ $\phi = 6.63 \times 10^{-34} \times 3.0 \times 10^8 / 3.2 \times 10^{-7}$ / $\phi = 6.63 \times 10^{-34} \times 9.375 \times 10^{14}$ $\phi = 6.22 \times 10^{-19} \text{ (J)}$ / $6.2 \times 10^{-19} \text{ (J)}$ $\phi = 6.22 \times 10^{-19} / 1.6 \times 10^{-19}$ $\phi = 3.88 \text{ (eV)}$ / 3.9 eV Possible ECF	B1 C1 A1 A1
	(ii)	No (photo)electrons Photon energy is less than the work function (energy) / The frequency (ν of the radiation) is less than the threshold frequency / Photons heat the metal	B1 B1
[Total 11]			
8	(a)	$\lambda = \frac{h}{m\nu}$ / $\lambda = \frac{h}{p}$ λ = wavelength, h = Planck constant. m = mass (of particle) and ν = speed / velocity OR p = momentum	M1 A1
	(b)(i)	Neutrons have no charge / Neutrons experiences no electrical forces (or)	B1
	(ii)	$2.6 \times 10^{-15} = 6.63 \times 10^{-34} / m\nu$ / $m\nu = 2.55 \times 10^{-21} \text{ (kgms}^{-1}\text{)}$ $\nu = 6.63 \times 10^{-34} / (2.6 \times 10^{-15} \times 1.7 \times 10^{-27})$ / $\nu = 2.55 \times 10^{21} / 1.7 \times 10^{22}$ $\nu = 1.5 \times 10^3 \text{ (ms}^{-1}\text{)}$ (Allow use of $m_n = 1.67 \times 10^{-27} \text{ kg}$)	C1 C1 A1

[Total 6]