



ASSESSMENT and
QUALIFICATIONS
ALLIANCE

Mark scheme

June 2003

GCSE

Design and Technology Electronic Products

3541 (Full Course)

Foundation

Copyright © 2003 AQA and its licensors. All rights reserved.

Design and Technology: Electronic Products

Full Course: Foundation Tier

Question 1

- (a) series (1 mark)
- (b) (i) 10 (1 mark)
 00 (1 mark)
 1K 1000R 1000Ω (1 mark)
- (ii) equation (1 mark)
 Manipulation/calc (1 mark)
 Answer 1K (1 mark)
- (c) can be +/- % (1 mark)
 all resistors not exact value (1 mark)
 5% below or above

Total 9 marks

Question 2


- (a) (i) **INPUT – Thermistor/Temperature Sensor** (1 mark)
 Transistor – Control/Process potential divider (1 mark)
- (ii) Open loop (1 mark)
- (b) (i) Variable resistor/Potentiometer (1 mark)
 (ii) Thermistor (1 mark)
 (iii) Transistor (1 mark)
 (iv) Relay (1 mark)
 (v) Diode (1 mark)
- (c) (i) Thermistor and VR/Potentiometer OR A & B (2 marks)
 (ii) Resistance lowers (1 mark)
 (iii) Alter the level a which the heater turns on (2 marks)
 (iv) Goes low/Reduces (1 mark)
 (v) 0.6/0.7V (1 mark)
- (d) V to heater (1 mark)
 V to relay (1 mark)
 Relay to heater (1 mark)

Total 18 marks

Question 3


- (a) Astable (1 mark)
 - (b) Pin 3 (1 mark)
 - (c) Capacitor or C (1 mark)
 - (d) (i) To protect the LED from damage (1 mark)
 To protect the LED from too high a current (1 mark)
 Controls the amount of electricity to LED
 - (ii) Formula (1 mark)
 $7-2 = 5$ (1 mark)
 $R = 5 / 0.02$ (1 mark)
 Answer 250Ω (1 mark)
 - (e) Pin 1 to 0V (1 mark)
 LED to 0V (1 mark)
 Pin 4 to +V (1 mark)
 Pin 8 to +V (1 mark)
 Pin 7 to PD (1 mark)
 Pin 2 to C (1 mark)
- Penalise only 1 mark for shared holes

Total 15 marks

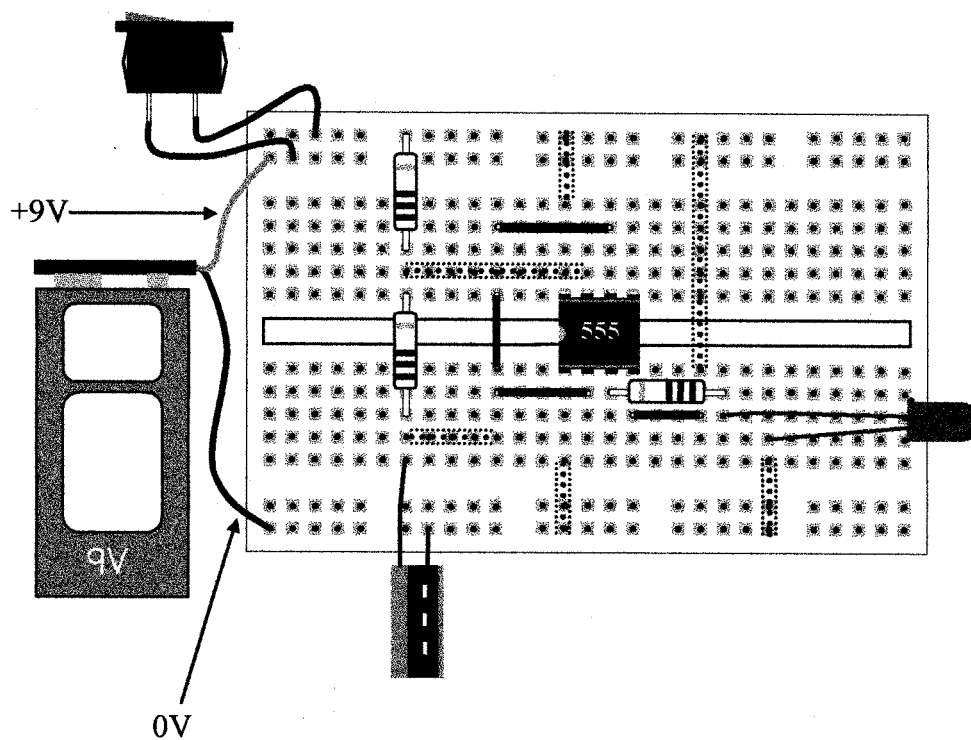

Question 4

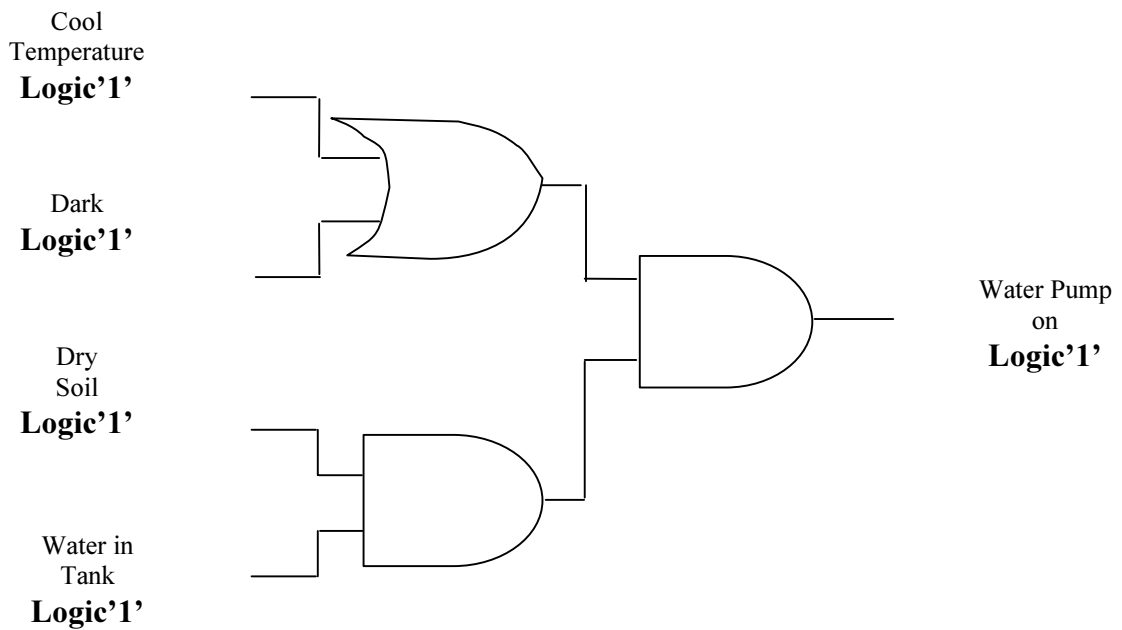- (a) (i) AND (1 mark)
 OR (1 mark)
- (ii) 0 (1 mark)
 0 (1 mark)
 1 (1 mark)
 1 (1 mark)
 Truth label correct for symbol/name
- (b) Temp and Dark to OR gate (1 mark)
 Correct symbol (OR) (1 mark)
 Output of AND and OR to AND (1 mark)
 Correct Symbol (AND) (1 mark)
 AND gate correctly linked to water pump (1 mark)
 Quality of drawing, straight lines, symbols good (1 mark)




- (c) Size of circuit board reduced
 Can be programmed to perform varied tasks
 Can be tested and modified before use, set exactly
 Can replace a complicated circuit any other suitable response
 any 2 (2 marks)
- (d) C 1 correct (1 mark)
 D 2 correct (2 marks)
 A 3 correct/all correct (3 marks)
 B

Total 17 marksQuestion 5

- (a) (i) LDR (1 mark)
 To detect differing light levels/resistance levels
 To determine the switching levels
 any 1 (2 marks)
- (ii) Variable resistor/Potentiometer (1 mark)
 To set the light level at which the light comes on
 To adjust light levels when light comes on.
 any 1 (2 marks)
- (iii) op amp (1 mark)
 to calculate the difference between pins 2/3
 to amplify the difference between pins 2/3 for the output
 to connect analogue input to digital output
 any 1 (2 marks)
- (b) (i) e.g. No damage to components, values changed easily
 Simulation possible, link to CAM any 1 (1 mark)
- (ii) Component library readily available, sizes/spacings accurate. Different
 views available, zoom, easy to change
 (Accept any two advantages) any 2 (2 marks)

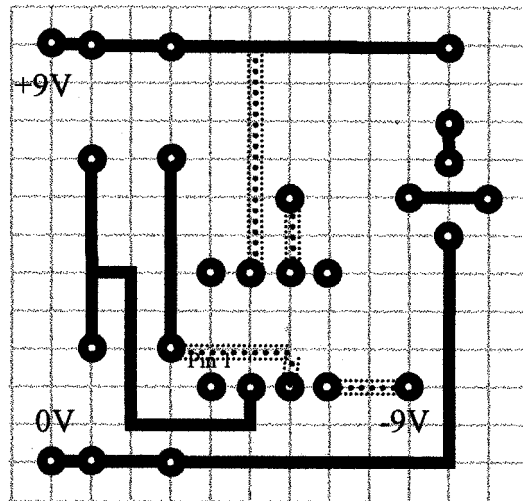- (c) (i) Pin 7 to + rail (1 mark)
- (ii) Pin 6 to resistor (1 mark)
- (iii) Pin 3 to potential divider (1 mark)
- (iv) Pin 4 to -V pad (1 mark)




viewed from the component side.

- (d) Clean track with wire wool
Heat both leg and track
Apply solder when track and legs hot
Apply correct amount of solder
Keep tip of iron clean, wipe on sponge any 2 (2 marks)
- (e) Hot iron – keep in holder
Fumes - ventilation
Lead – wash hands any 2 (4 marks)

Total 22 marks

(d)

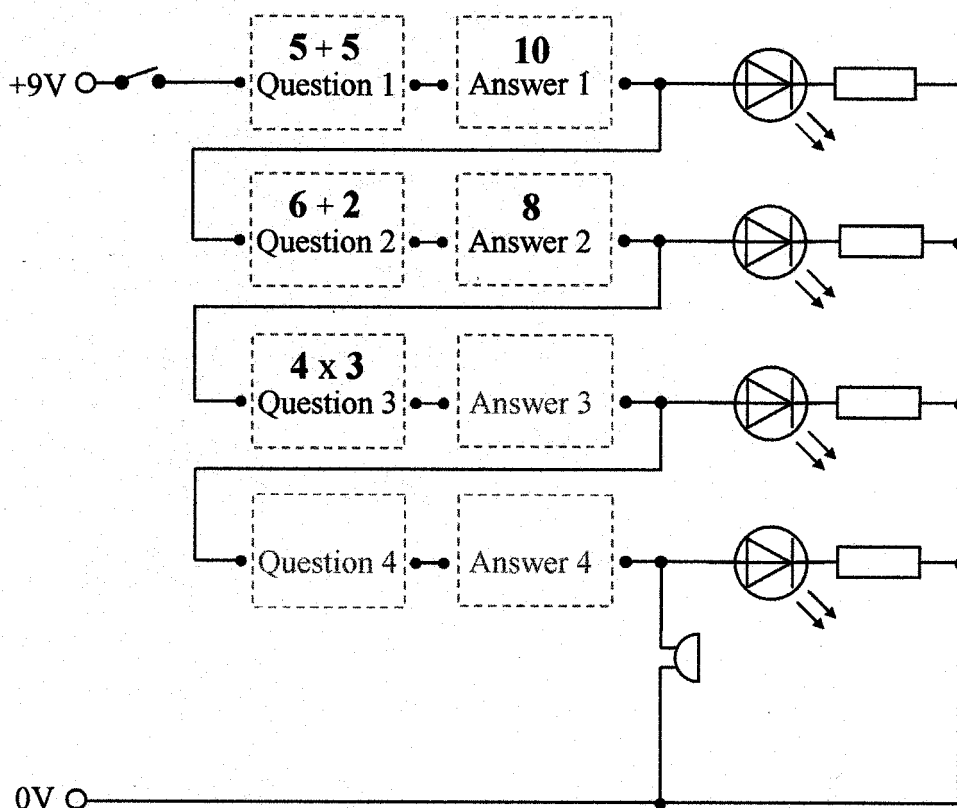

(i) Correct symbol (1 mark)

Parallel with last LED. (1 mark)

(ii) Reed Switch, Push to make, basic contacts, copper tape (1 mark)

Push switch Pressure Pad, LDR etc.
Any other suitable response 1 mark each = 2 marks (1 mark)

(e) To use it as market research, testing the market, Testing the product in use Any 2 (2 marks)

(f) (i) Greater profit margins, long production runs, less staff required, built in QC, etc any 2 Some qualification required (2 marks)

(ii) quality, wider range, competition so better prices etc any 2 some qualification required (2 marks)

(g) Any suitable testing procedure/method but to be related to evaluation (2 marks)

Total 38 marks

Question 7

Workers' conditions, waste disposal, air, noise pollution

Pollution of atmosphere, use of energy

(2 marks)

Energy when being used, pollutants emitted during use

Air, noise pollution,

(2 marks)

Lack of landfill, pollution of earth, atmosphere,

Public health

(2 marks)

Total 6 marks

Total marks for paper 125