Surname				Other	Names				
Centre Nu	mber					Candi	date Number		
Candidate Signature									

Leave blank

AQA	
ASSESSMENT and	
QUALIFICATIONS	
ALLIANCE	

3546/F

General Certificate of Secondary Education Summer 2003

DESIGN AND TECHNOLOGY Systems and Control Technology

FOUNDATION TIER

Thursday 19 June 2003 1.30 pm to 3.30 pm

In addition to this paper you will require:

a pen, pencil, ruler, eraser and pencil sharpener.

Time allowed: 2 hours

Instructions

- Write your name and other details in the spaces provided above.
- Answer either Section A Mechanisms Focus Technology; or Section B – Pneumatics Focus Technology. not both
- Write your answers in this question paper/answer book.

Information

- The maximum mark for this paper is 125.
- A list of formulae is given on page 2 which you may need to use when answering certain questions.
- The number of marks is given in brackets at the end of each question or partquestion.
- Wherever calculations are needed you should show your working.
- All dimensions are given in millimetres unless otherwise stated.
- You are reminded of the need for good English and clear presentation.

Copyright © 2003 AQA and its licensors. All rights reserved.

For Examiner's Use				
SECTION A MECHANISMS FOCUS				
Number	Mark			
A1				
A2				
A3				
A4				
A5				
A6				
A7				
A8				
TOTAL				
SECTION B PNEUMATICS FOCUS				
Number	Mark			
B1				
B2				
B3				
B4				
B4 B5				
B5				
B5 B6				
B5 B6 B7				


Pneumatics			Force = Pressure \times Area		
Ratio of Simple	e Gears		Gear Ratio = $\frac{\text{Number of teeth on driven gear}}{\text{Number of teeth on driver gear}}$		
Velocity Ratio			Velocity Ratio = $\frac{\text{Diameter of driven pulley}}{\text{Diameter of driver pulley}}$		
			Output speed = $\frac{\text{Input speed}}{\text{Gear/Velocity ratio}}$		
Forces			Moments = Force \times Distance		
			Sum of clockwise moments = sum of anti- clockwise moments		
Series Resistan	ce		$\mathbf{R}_{\mathrm{T}} = \mathbf{R}_{1} + \mathbf{R}_{2} + \mathbf{R}_{3}$		
Parallel Resistance			$\frac{1}{R_{T}} = \frac{1}{R_{1}} + \frac{1}{R_{2}} \text{ OR } R_{T} = \frac{R_{1} \times R_{2}}{R_{1} + R_{2}}$		
Potential Differ	rence		$V = I \times R$		
Transistors			$Current Gain = \frac{Collector Current}{Base Current}$		
Amplifier Gain	L		$Av = \frac{Change \text{ in output voltage}}{Change \text{ in input voltage}}$		
Area of circle =	$=\pi r^2$		$\pi = 3.142$		
Resistor Colou	r Code		E12 Resistor preferred values		
Colour Black Brown Red Orange Yellow Green Blue Violet Grey White	Number 0 1 2 3 4 5 6 7 8 9	Number of Zer 0 00 000 0,000 00,000 000,000 0,000,00	ros 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and decades thereafter.		

The following information may be of use to you when answering questions on this paper.

SECTION A – MECHANISMS FOCUS

Answer **all** questions in this section.

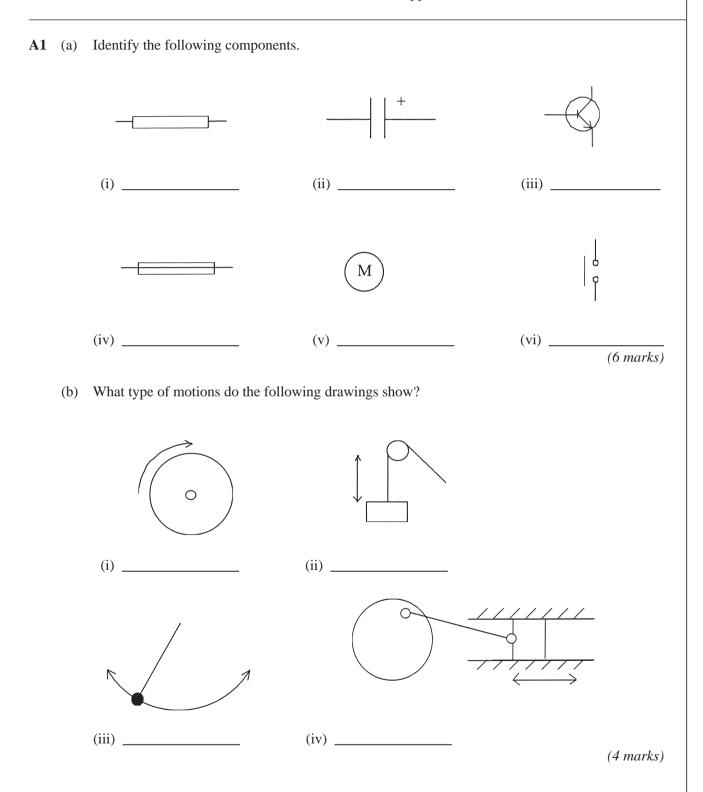Do not answer these questions if you have answered the questions in Section B – Pneumatics Focus (pp. 22–39).



5

(d) In the space below produce a simple design sketch of a microswitch and guard mechanism that could be used on a pillar drill. The switch and mechanism should ensure that the user **could not** operate the machine without the guard in position.

You do not need to draw the pillar drill. Only sketch the idea for how the microswitch and guard will work.

(6 marks)

Turn over ►

TP/0203/3546/F

(c)

- A2 A student has decided to use the monostable circuit shown in **Figure 2** as the timing element in a game being designed. The circuit is based around a 555 timer integrated circuit (IC).
 - (a) Use the information given on the circuit diagram to help you to complete the table in **Figure 2** which describes the pins used for the connection of the 555 timer Integrated Circuit (IC).

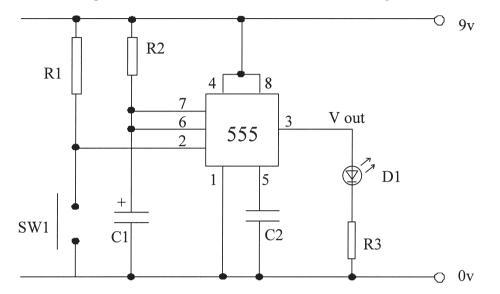


Figure 2

Pin number	Label	Pin number	Label
1		5	Control voltage
2		6	Threshold
3		7	Discharge
4	Reset	8	

Component D1 is a light emitting diode.

It has to be inserted with the correct for it to function correctly. (5 marks)

(b) The unlabelled version of the circuit chosen by the student is shown again below in **Figure 3**. Circle the two components that can be best used to control the timing of the pulse in the circuit shown below.

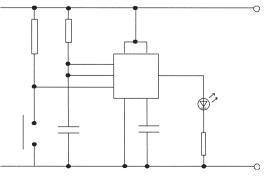


Figure 3

(c)	(i) Resistor 3, (R3), is shown in Figure 4 .
	What is the value of this resistor?
	Orange Gold Ohms (1 mark)
	Figure 4
	(ii) Explain what the Gold band indicates.
	(1 mark)
	(iii) Explain why the resistor is positioned in series with the LED in Figure 3 .
	(2 marks)
(d)	The 555 IC is a DIL integrated circuit. These circuits can easily be damaged when fixing or handling.
	Describe two precautions that can be taken to safeguard against damage.
	1
	(1 mark)
	2

QUESTION A2 CONTINUES ON THE NEXT PAGE

(e) The circuit is to be assembled on a printed circuit board. The student has manufactured the case for the game out of *Medium Density Fibre Board* (MDF). In the space below show a suitable method of fixing the circuit board to the MDF case.

This question is worth 4 marks.

Marks will be awarded as follows:

Method of fixing the circuit board to the MDF case;(2 marks)Quality of drawing.(2 marks)




A3 (a) Identify the type of gear mechanism shown in Figure 5. Rotating shaft Figure 5 Type of mechanism (1 mark)(b) Identify the type of gear used in **Figure 6** to turn rotation through 90 degrees. Output shaft Input shaft Figure 6 Type of gear (1 mark)Will the output shaft in Figure 6 be rotating at the same speed, faster or slower than the input (c) shaft? (1 mark)

TP/0203/3546/F

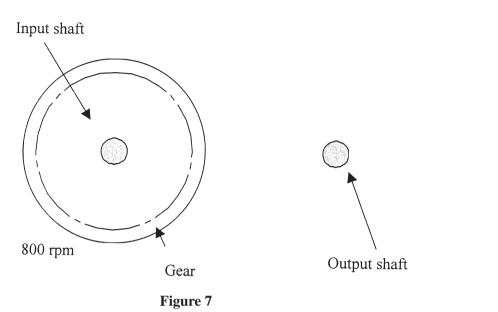(d) Complete the gear system, shown in **Figure 7**, that would allow the output shaft to rotate at 400 rpm and in the same direction as the input shaft.

Indicate on Figure 7 the number of teeth on each gear used in your solution.




(4 marks)

(e) Give **two** safety precautions that are used in gear systems commonly found in workshop machinery.

(1 mark)

10

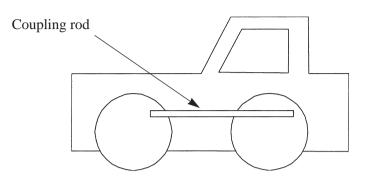A4 The drawing below, Figure 8, shows a toy train that has been manufactured using a variety of different plastic materials.





(a) (i) **Figure 9** shows the coupling rod from the wheel linkage mechanism. It is to be made of plastic (hdp).


What manufacturing process would be best to produce it?

(1 mark)



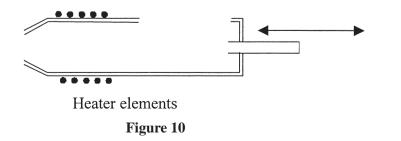(ii) The drawing in **Figure 10** is an incomplete drawing of the process used to manufacture the coupling rods.

Complete the drawing by showing the position of the split mould and the hopper in this manufacturing process.



(2 marks)

(b) Modify the drawing of the component shown in **Figure 9** to show how the component could easily be strengthened. ANSWER BY ADDING LINES TO THE DRAWING GIVEN ON THE PREVIOUS PAGE.


(4 marks)

(c) (i) Which type of plastic is most suitable for recycling – thermoplastic or thermosetting plastic?

(ii) Describe briefly how a manufacturer would recycle this type of plastic.

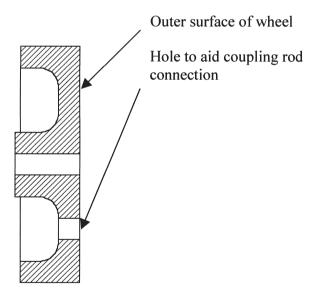(d) On the toy train a coupling rod connects the two wheels. This is shown in **Figure 8** and **Figure 9**.

Sketch a suitable method of fixing this link to the wheel and at the same time allowing it free rotation. You may use the given cross-section of the wheel or re-draw it in the space provided.




Cross section Through wheel

(4 marks)

Turn over ▶

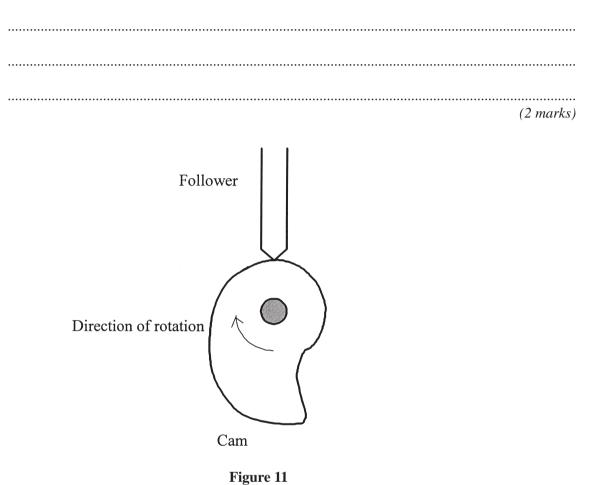
- A5 Many toys use cams to impart motions to give interest to the toy. The profile of a cam determines the type of motion.
 - (a) Describe what happens to the follower when the cam shown in **Figure 11** completes one full rotation.



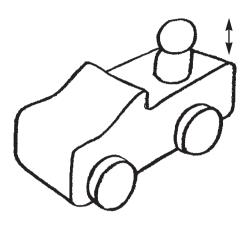(b) (i) In the space below design a cam that could be used to make the driver's head and body in Figure 12 move up and down at the same speed as the toy is pulled along. You may use whatever drawing format you wish.

15

Add notes to your drawing to explain how it works.





(5 marks)

(ii) Fill in the spaces below using words from the list below.

spindle	painting	polishing	wood	plastic
dowel	tubing	axle	friction	temperature

(5 marks)

Turn over ►

- A6 A heating system has been designed for a sauna. It ensures that:
 - the sauna operates within a given temperature range;
 - if the temperature falls below the minimum level a heater is activated;
 - if the temperature exceeds the maximum level the heat source is turned off.

The heater is turned on when the output voltage is high.

- - (ii) In the space below draw the symbol that is used to represent this component.

(2 marks)

(b) The temperature control system flowchart for the process is partially completed in **Figure 13** below.

Complete the flowchart by adding to Figure 13 as required.


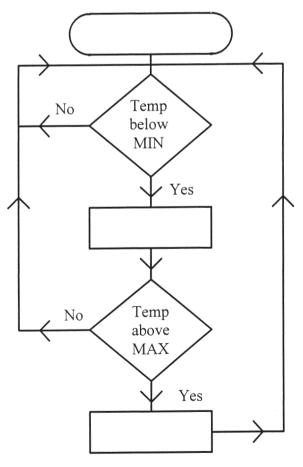


Figure 13

20

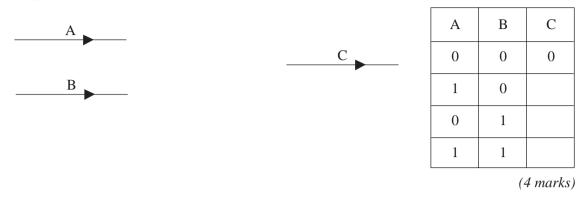
(c) The heating system uses an AND logic gate.

Complete the logic gate symbol and truth table for an AND logic gate.



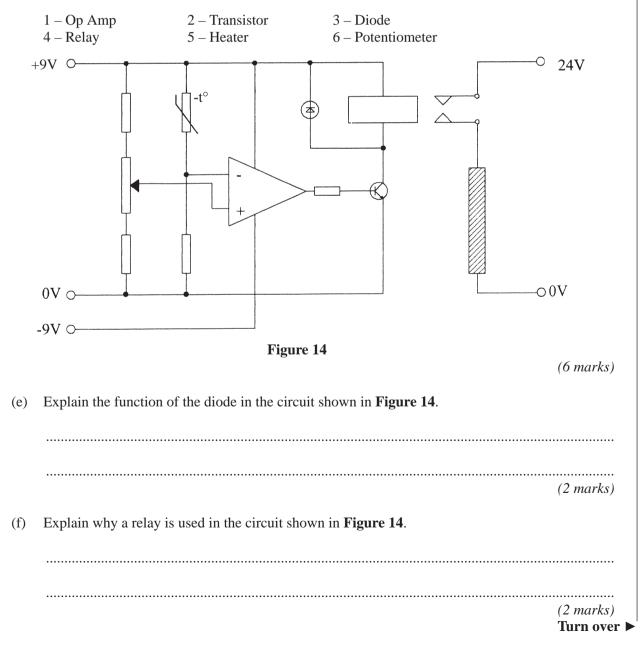(d) A different way of controlling an electronic heating system is to use an Op Amp.

On the circuit shown in **Figure 14** label the indicated components, using the given numbers or words.



A7	(a)	Computer Aided Design (CAD) is often used to design printed circuit boards and for use electronic circuits.	in
		(i) Give two advantages of using CAD.	
		(2 mark	
		(ii) Give one disadvantage of using CAD.	
			 k)
	(b)	When CAD software is bought for use on a PC system the user purchases the license to use the following terms are all related to the purchasing and installation of software.	it.
		Briefly explain what the terms mean.	
		Single user license	•••
		Multi-user license	•••
		Software piracy	
		(3 mark	S)
	(c)	Printed circuit boards can be made using Computer Aided Milling machines.	
		Give two advantages and one disadvantage of producing a printed circuit board in this way.	
		Advantage 1	
		(2 mark	S)
		Advantage 2	
		Disadvantage	••••
		(2 mark	s)

19

(d)	(i)	Give one example of a product that is made using an automated production process	-
			(1 mark)
	(ii)	Give two advantages that arise from the use of automated production machinery chosen product.	for your
		Advantage 1	
			(1 mark)
		Advantage 2	
			(1 mark)
(e)	You	have designed a new product that is quite unique in the market place.	
	Give	four methods of marketing this product so that buyers become aware of it.	
	Meth	nod 1	(1 mark)
	Meth	nod 2	(1 mark)
	Meth	nod 3	
	Meth	nod 4	(1 mark)
	11101		(1 mark)

TURN OVER FOR THE NEXT QUESTION

A8 A local park has a small gauge railway on which children can have rides. In a number of places the railway track crosses a pedestrian pathway. The railway runs between two hedgerows except where it crosses a pedestrian pathway. A typical crossing is shown in **Figure 15**. The park is only open during daylight hours.

The park owners would like a simple barrier crossing designing which is based upon the same idea as barrier crossings used on full size railways. They do not want their barrier crossing to be as complicated but it does have to meet the following criteria:

- It must close the gap when an electrical signal reaches it.
- An audible (sound) alarm must activate until the barrier is raised.
- The barrier must lift when a second electrical signal reaches it.

Use these two pages only to sketch ideas for a design that will satisfy the brief for the barrier.

This question is worth 15 marks.

You will be marked as follows:

Mechanism for raising and lowering barrier;	(5 marks)
Design for audible output;	(5 marks)
Use of suitable materials;	(2 marks)
Quality of drawings.	(3 marks)


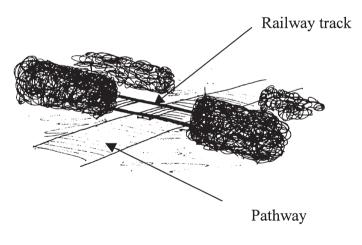


Figure 15


SECTION B – PNEUMATICS FOCUS

Answer **all** questions in this section.

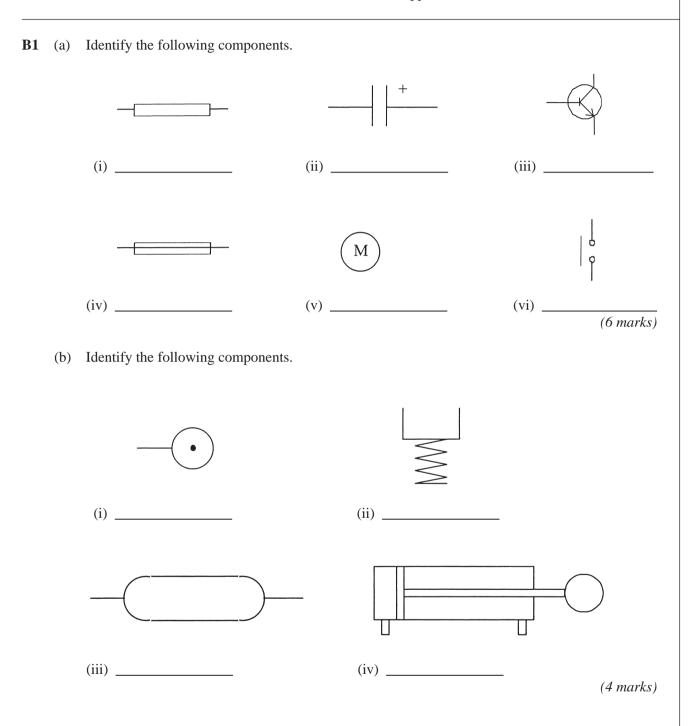Do not answer these questions if you have answered the questions in Section A – Mechanisms Focus (pp. 4–21).



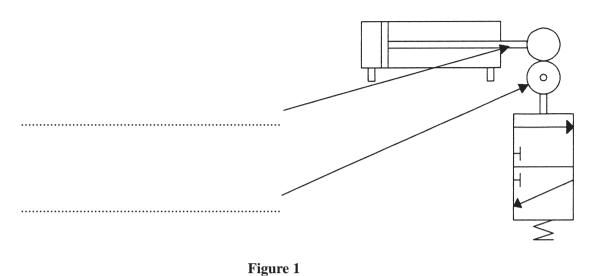(c) Name the **two** parts of the mechanism indicated by the arrows in **Figure 1**.



(2 marks)

(d) Two 3 port control valves form part of a powered Guillotine. This is designed so that the guillotine will only operate when both valves are opened. This is a safety feature that ensures both of the operators hands have to be free of the machine before the guillotine can operate.

In the space below produce a pneumatic circuit diagram for a safety mechanism that would perform this function. This function is an AND function. The arrow below is the final output once the two valves have been activated. Use this as part of your answer.

Output to Guillotine

(6 marks)

B2 A student has decided to use the monostable circuit shown in **Figure 2** as the timing element in a game being designed. The circuit is based around a 555 timer integrated circuit (IC).

24

(a) Use the information given on the circuit diagram to help you to complete the table in **Figure 2** which describes the pins used for the connection of the 555 timer Integrated Circuit (IC).

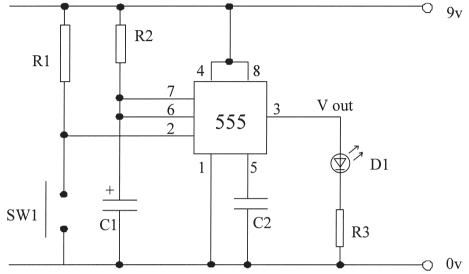


Figure	2
--------	---

Pin number	Label	Pin number	Label
1		5	Control voltage
2		6	Threshold
3		7	Discharge
4	Reset	8	

Component D1 is a light emitting diode.

It has to be inserted with the correct for it to function correctly. (5 marks)

(b) The unlabelled version of the circuit chosen by the student is shown again below in **Figure 3**. Circle the two components that can be best used to control the timing of the pulse in the circuit shown below.

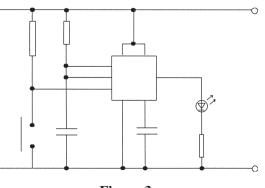


Figure 3

(2 marks)

(c)	(i) Resistor 3, (R3), is shown in Figure 4 .	
	What is the value of this resistor?	
	Orange Gold	Ohms (1 mark)
	Figure 4	
	(ii) Explain what the Gold band indicates.	
		(1 mark)
	(iii) Explain why the resistor is positioned in series with the LED in Figure 3.	
		(2 marks)
(d)	The 555 IC is a DIL chip. These chips can easily be damaged when fixing or handling.	
	Describe two precautions that can be taken to safeguard against damage.	
	1	
		(1 mark)
	2	
		(1 mark)

QUESTION B2 CONTINUES ON THE NEXT PAGE

Turn over ►

(e) The circuit is to be assembled on a printed circuit board. The student has manufactured the case for the game out of *Medium Density Fibre Board* (MDF). In the space below show a suitable method of fixing the circuit board to the MDF case.

This question is worth 4 marks.

Marks will be awarded as follows:

Method of fixing the circuit board to the MDF case;(2 marks)Quality of drawing.(2 marks)

28

B3 (a) Give the full name for the valve illustrated in **Figure 5**.



Figure 5

(b) A large toy shop has decided to produce a moving promotional display. The front of the display is moulded in plastic – (abs). The mechanisms, valves and control lines are attached behind it and are accessible from the rear.

Using the components listed below produce a simple pneumatic circuit drawing that will give a time delay to a piston movement.


single acting cylinder,	flow regulator,	reservoir,	lever operated 3 port valve.
Components:			

(c)	Air going into a cylinder is at a pressure of 0.5 N/mm^2 and the piston is 100 mm in diameter.
	What force does the cylinder exert? Give units where applicable.
	Force produced by cylinder = air pressure \times surface area of piston.
	Area of piston =
	Force =
	$\pi = 3.142 \tag{3 marks}$

TURN OVER FOR THE NEXT QUESTION

Turn over ►

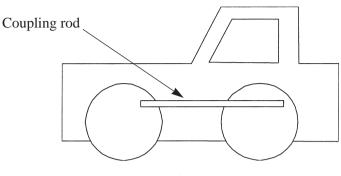B4 The drawing **Figure 6** shows a toy train that has been manufactured using a variety of different plastic materials.






(a) (i) **Figure 7** shows the coupling rod from the wheel linkage mechanism. It is to be made of plastic (hdp).

Which manufacturing process is best to use?

(1 mark)

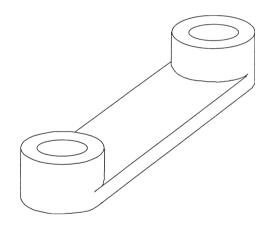



(ii) The drawing in **Figure 8** is an incomplete drawing of the process used to manufacture the coupling rods.

Complete the drawing by showing the position of the split mould and the hopper in this manufacturing process.

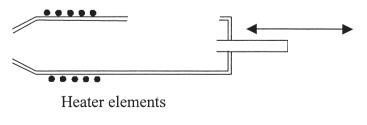


Figure 8

(2 marks)


- (b) Modify the drawing of the component shown in **Figure 7** to show how the component could easily be strengthened. ANSWER BY ADDING LINES TO THE DRAWING GIVEN ON THE PREVIOUS PAGE. (4 marks)
- (c) (i) Which type of plastic is most suitable for recycling thermoplastic or thermosetting plastic.

(1 mark)

(ii) Describe briefly how a manufacturer would recycle this type of plastic.

(2 marks)

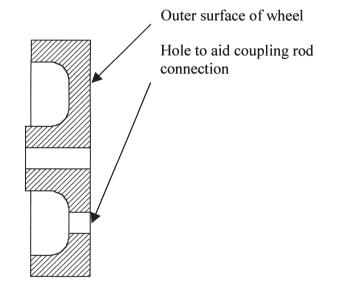(d) On the toy train a coupling rod connects the two wheels. This is shown in **Figures 6 and 7**. Sketch a suitable method of fixing this link to the wheel yet at the same time allowing it free rotation. You may use the given cross-section of the wheel or re-draw it in the space below.



Cross section Through wheel


(4 marks)

Turn over ▶

TP/0203/3546/F

- **B5** A baggage-handling terminal at an airport has pneumatically controlled doors. The circuit diagram shown in **Figure 9** represents the system used.
 - (a) Complete the sentences below to describe what happens in the pneumatic door system shown in **Figure 9**.

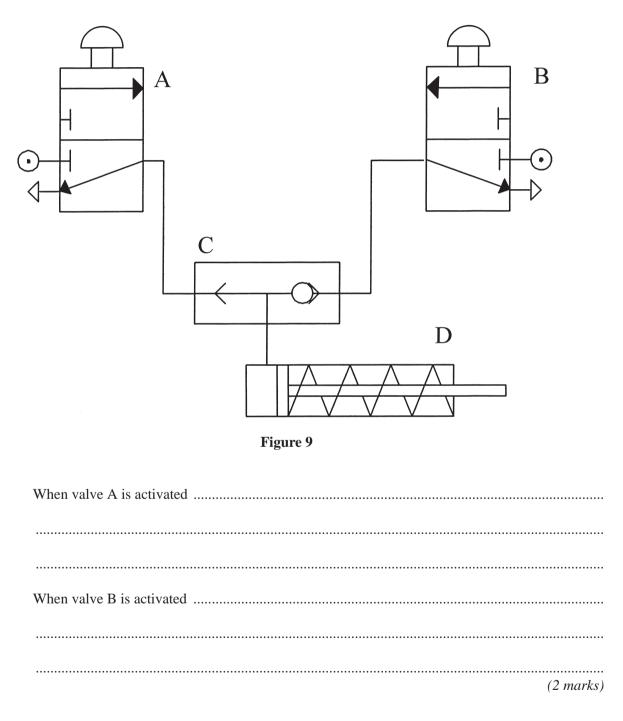You are to use the letters when describing what happens. Eg. when valve A is operated cylinder D will



(b) In operation it was found that the door system would be safer if it could open quickly and close slowly.

In the space below, redraw and modify the pneumatic circuit given in **Figure 9** to allow the door to open quickly and close slowly when either valve is operated.

(5 marks)

(c) Fill in the spaces below using words from the list below.

pneumatics electronics environments	U	DILs mechanics materials	aluminiur steel fabricatio			
Many control sy	stems use a c	combination of				and
		: this is often calle	d mechatror	nics.		
A walking machine	e is a good examp	ble of a mechatron	ic system. V	Valking mac	hines can t	be used
in that are hostile to human beings.						
Plastic materials and are often used in their construction as						
they have good strength to weight ratios.						
The use of		ha	as reduced	the need f	for many	circuit
components and therefore made the control devices much smaller.						

(5 marks)

- **B6** A heating system has been designed for a sauna. It ensures the following:
 - the sauna operates within a given temperature range;
 - if the temperature falls below the minimum level a heater is activated;
 - if the temperature exceeds the maximum level the heat source is turned off.

The heater is turned on when the output voltage is high.


(a) (i) What is the name of a component that senses temperature.

(ii) In the space below draw the symbol that is used to represent this component.

(2 marks)

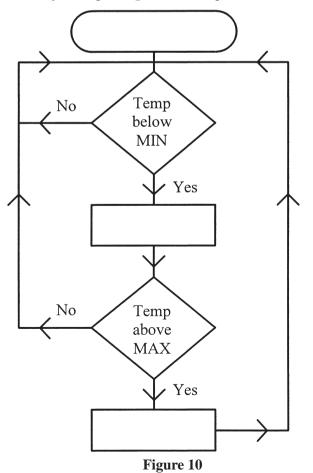
(b) The temperature control system flowchart for the process is partially completed in **Figure 10** below.

Complete the flowchart by adding to Figure 10 as required.



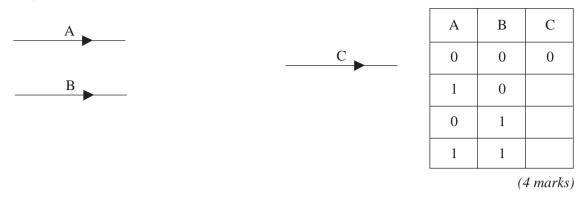
(c) The heating system uses an AND logic gate.

Complete the logic gate symbol and truth table for an AND logic gate.



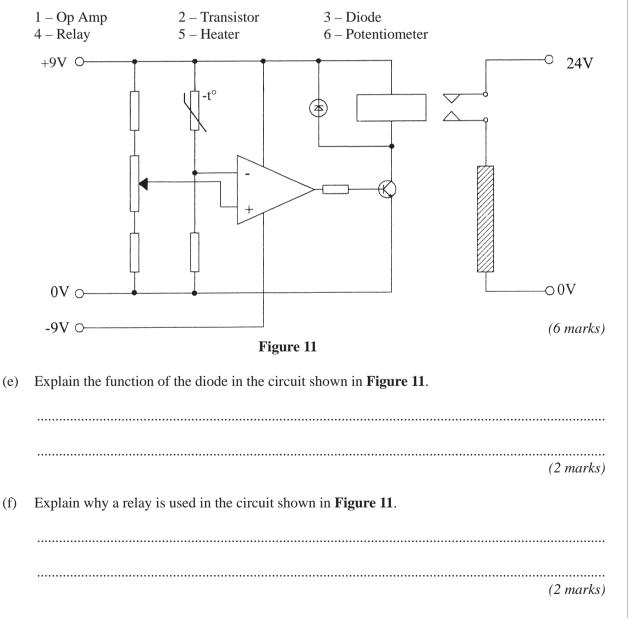(d) A different way of controlling an electronic heating system is to use an Op Amp.

On the circuit shown in **Figure 11** label the indicated components using the given numbers or words.



21

B7	(a)	Computer Aided Design (CAD) is often used to design printed circuit boards and for use in electronic circuits.		
		(i) Give two advantages of using CAD.		
		(2 marks		
		(ii) Give one disadvantage of using CAD.		
	(b)	When CAD software is bought for use on a PC system the user purchases the license to use it The following terms are all related to the purchasing and installation of software.		
		Briefly explain what they mean.		
		Single user license		
		Multi-user license		
		Software piracy		
	(c)	Printed circuit boards can be made using Computer Aided Milling machines.		
		Give two advantages and one disadvantage of producing a printed circuit board in this way.		
		Advantage 1		
		(2 marks		
		Advantage 2		
		Disadvantage		
		(2 marks		

(d)	(i) Give one example of a product that is made using an automated production proc	ess.
		(1 mark)
	(ii) Give two advantages that arise from the use of automated production machine chosen product.	ery for your
	1	(1 mark)
	2	(1 mark)
		, ,
(e)	You have designed a new product that is quite unique in the market place. Give four marketing this product so that buyers become aware of it.	methods of
(e)		
(e)	marketing this product so that buyers become aware of it.	(1 mark)
(e)	marketing this product so that buyers become aware of it. Method 1 Method 2	(1 mark) (1 mark)
(e)	marketing this product so that buyers become aware of it. Method 1	(1 mark) (1 mark)

TURN OVER FOR THE NEXT QUESTION

Turn over ►

- **B8** A local car park has an exit gate which is in the form of a barrier that raises when a car is sensed. The barrier is controlled pneumatically.
 - The barrier must raise when a signal reaches it.
 - It must stay open until a second signal reaches it.
 - It will then lower slowly to the closed position.

Use these two pages only to sketch ideas for a design that will satisfy the brief for the barrier.

This question is worth 15 marks.

You will be marked as follows:

Pneumatic mechanism for raising and lowering barrier;	(5 marks)
Design for pneumatic circuit;	(5 marks)
Use of suitable components;	(2 marks)
Quality of drawings.	(3 marks)

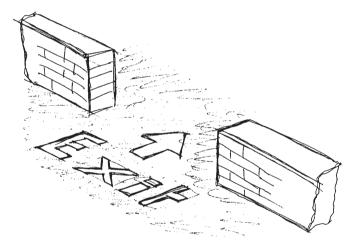


Figure 12

TP/0203/3546/F

END OF QUESTIONS

15