

# Mark scheme June 2003

### **GCSE**

## Design and Technology Electronic Products

3551 (Short Course)
Higher

Copyright © 2003 AQA and its licensors. All rights reserved.

#### **Design and Technology: Electronic Products**

Short Course: Higher Tier


#### Question 1

(a)	(i)	18 000 18k or 18000Ω (correct with unit)	(1 mark) (1 mark) (1 mark)
	(ii)	Tolerance can be +/- % +/- 5%	(1 mark) (1 mark)
(b)	(i)	$5\% = 900\Omega$ 18000 + 900 = 18900 Correct with Units = 18900 or 18.9 or 18K9	(1 mark) (1 mark) (1 mark)
	(ii)	18000 - 900 = 17100 Correct with Units 17100Ω or 17.1 or 17K1 Or correct answer based on (a)(i)	(1 mark) (1 mark)
(c)	(i)	Any correct series connection	(1 mark)
	(ii)	Components can be changed easily (1 mark each) Components can be used again or any other suitable response Or one qualified reason	(2 marks)
	(iii)	R = R1 + R2 $OR$ $12000 + 150$	(1 mark)
		Calculation to arrive at $12150$ Correct with units $12150\Omega$ , $12-15k$ , $12k15$	(1 mark) (1 mark)

**Total 16 marks** 


#### Question 2

(a)	No damage to components, Can link to CAM Values quickly changed Possible greater range of components High outlay/low running cost	1 mark each
	Any other suitable response.	(3 marks)
(b) (c)	Formula $1.44/(R1 + 2R2) \times C$ Working reference to $R1 + 2R2 = 37K$ Ref to $\mu$ ie divide by 1,000,000 or manipulation of 37k Correct working $-38$ Correct answer $389Hz$ One mark for advantage and one mark for qualification. e.g. component size correct $-$ makes it easy to put component in	(1 mark) (1 mark) (1 mark) (1 mark) (1 mark)
	place. Easy to change layout – to fit board size Any other suitable response	(4 marks)
(d)	Pin 1 to 0V Capacitor to loudspeaker Pin 4 to +V Pin 8 to +V Pin 7 to PD Pin 2 to pin 6	(1 mark) (1 mark) (1 mark) (1 mark) (1 mark)

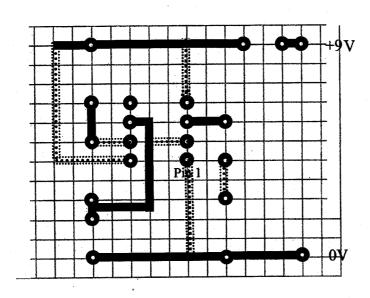

AQA/

(e)	(i)	Mono - Pin 8 to +V	(1 mark)
		Pin1 to 0V	(1 mark)
		Pin 2 to sw/res Junction.	(1 mark)
		Pins 6/7 to Res/cap Junction	(1 mark)
	(ii)	Mono to astable – Pin 3 to pin 4	(2 marks)
		or pin 3 to + V rail	(1 mark)
		0V rail to 0V	(1 mark)
		a V rail 9V or pin 4 to V rail	(1 mark)

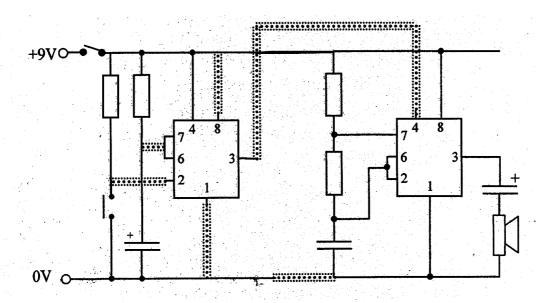

Quality of drawing
Straight lines (1 mark)
Knowledge of Junction dots (1 mark)

(f) Can be programmed and re programmed
Can be programmed to perform varied tasks
Can be tested and modified before use, set exactly
Reduced in size of the circuit
Can replace a complicated circuit
any other suitable response

One mark each
(2 marks)

(g) C
D
1 correct mark
A
2 or 3 correct
B
All correct
3 marks

**Total 33 marks** 



#### Question 3

(a)	V to heater Heater to relay (com/No) relay (Com/No) to V		(1 mark) (1 mark) (1 mark)
(b)	(i) e.g. to protect the trans from too much cur or to bias/set base cur for relay requirement	rrent	(1 mark) (1 mark)
	(ii) To protect the transistor from back emf	r	(1 mark) (1 mark)
(c)	Resistance in thermistor increases Voltage at base of transistor increases above that set by VR Transistor switches Relay activated		(1 mark) (1 mark) (1 mark) (1 mark)

#### **Total 11 marks**

#### Question 4

(a) Basic answer – safe any answer

(1 x 3) (3 marks)

Qualified answer

No sharp edges to catch on skin

Non toxic paint/finish so as not to cause problem if chewed

Material that will not splinter etc etc (3 x 2)

(6 marks)

AQA/

(b)

Information that I need	Where I might find the information
How children learn, degree of difficulty, educational needs, Development levels	Nursery or primary schools
Range, prices, availability, properties and costing of materials	Local Suppliers materials catalogue
A range of toys already on the market	Toys catalogue, magazines, visit toy shops ask assistants
Legal requirements for safety, size for age range, finish requirements, H/S	British Standards Institution
Range of sizes of the age groups to use toy. Hand sizes, what can be gripped easily	Anthropometric Data

1 mark each (maximum 5 marks)

(c)	(i)	Suitable material basic reasons or detailed reason	(1 mark) (1 x 2 marks) (2 marks)	
	(ii)	Suitable shape for overall construction method	chosen.	
		E.g. Vac Form, rounded corners/draft angle or jointing.	details of any	(2 marks)
		A recognised construction method but not fully material	suited to the	(1 mark)
		Detailed provision of the housing for the block the material stated.	s suitable for	(2 marks)
		Reference to provision of the housing for the b	locks	(1 mark)
		Any other details – sizes, fitting of base, finish,	colours etc	(1 mark)
		Clear 3D drawing with or without rendering		(2 marks)
		Drawing that can be interpreted		(1 mark)
	(iii)	Circuit fixed neatly in place Circuit held in place Clear 3D/side/plan/ technical drawing Understood but lacking in quality/detail		(2 marks) (1 mark) (2 marks) (1 mark)



Pollution of atmosphere, use of energy

Air, noise pollution,

Public health

Energy when being used, pollutants emitted during use

Lack of landfill, pollution of earth, atmosphere,

(d)	(i)	Reed Switch, Push to make, basic contacts, microswitch Pressure Pad, LDR or any other suitable response (1 mark for each)	(2 marks)
	(ii)	Detailed sectional view or fully annotated explanation Some evidence of knowledge and annotated detail	(2 marks) (1 mark)
	(iii)	Method that clearly shows how all blocks will work independently and match up	(4 marks)
		Method that shows some probability that all blocks will work independently and match up	(3 marks)
		Method that shows that some blocks will work independently and match up	(2 marks)
		Method that shows that some thought has gone into the positioning of contacts/sensors	(1 mark)
			Total 33 marks
Quest	<u>ion 5</u>		
		y, sustainable use, pollution, waste deposits ninerals/forests can leave top soil very vulnerable to errosion.	(1 mark)
Workers conditions, waste disposal, air, noise  Rellution of atmosphere, use of energy  (2 mark			(2 marks)

**Total 7 marks** 

(2 marks)

(2 marks)

Total mark for paper 100