

Candidate Name	Centre Number	Candidate Number
		0



**GCSE**

298/01

**ELECTRONICS  
 TERMINAL EXAMINATION  
 FOUNDATION TIER**

A.M. TUESDAY, 10 June 2008

1¼ hours

<b>For Examiner's use only</b>	
<b>Total Mark</b>	

**ADDITIONAL MATERIALS**

In addition to this question paper you may need a calculator.

**INSTRUCTIONS TO CANDIDATES**

Write your name, centre number and candidate number in the spaces at the top of this page.

Answer **all** questions.

Write **all** the answers in the spaces provided in this booklet.

**INFORMATION FOR CANDIDATES**

The number of marks is given in brackets at the end of each question or part-question.

## INFORMATION SHEET

This information may be of use in answering the questions.

### 1. Resistor Colour Codes

<b>BLACK</b>	<b>0</b>	<b>GREEN</b>	<b>5</b>
<b>BROWN</b>	<b>1</b>	<b>BLUE</b>	<b>6</b>
<b>RED</b>	<b>2</b>	<b>VIOLET</b>	<b>7</b>
<b>ORANGE</b>	<b>3</b>	<b>GREY</b>	<b>8</b>
<b>YELLOW</b>	<b>4</b>	<b>WHITE</b>	<b>9</b>

The fourth band colour gives the tolerance as follows:

**GOLD**  $\pm 5\%$

**SILVER**  $\pm 10\%$


### 2. Preferred Values for Resistors

<b>E 12 SERIES OF PREFERRED VALUES</b> <b>10; 12; 15; 18; 22; 27; 33; 39; 47; 56; 68; 82 and multiples thereafter</b>
--

3. Resistance =  $\frac{\text{voltage}}{\text{current}}$  ;  $R = \frac{V}{I}$  .

4. Effective resistance, R, of two resistors  $R_1$  and  $R_2$  in series is given by  $R = R_1 + R_2$ .

### 5. Voltage Divider

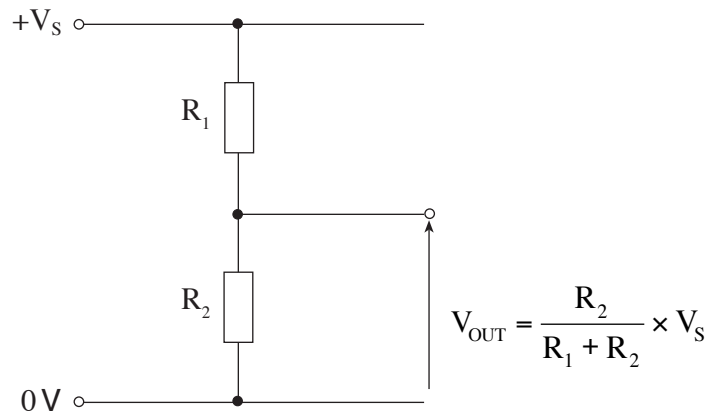

6. Power = voltage  $\times$  current;  $P = VI$

7. LED The forward voltage drop across a LED is 2V.

### 8. Transistors

The forward voltage drop across the base emitter junction is 0.7V.

### 9. Amplifiers

Voltage gain  $A = \frac{V_{OUT}}{V_{IN}}$

Non-inverting amplifier:  $A = 1 + \frac{R_F}{R_1}$  .

Answer **all** questions in the spaces provided.

1. Here is a list of four mechanical switches.

*push*      *reed*      *tilt*      *toggle*

Choose the most appropriate switch from the list for the following jobs.

(a) To be used with a magnet to sense when a door is open.

Answer .....

(b) To be used for a switch to warn the driver of a crane that it is in danger of toppling over.

Answer .....

[2]

2. Four bulbs A, B, C and D are working at the following currents and voltages.

Bulb	Current (A)	Voltage (V)
<b>A</b>	0.1	12
<b>B</b>	0.2	9
<b>C</b>	0.2	6
<b>D</b>	0.3	12

(a) Which bulb uses the **most** power ? .....

[1]


(b) Use the formula in the information sheet on page 2 to calculate the power used by bulb **D**.

[2]

.....  
.....

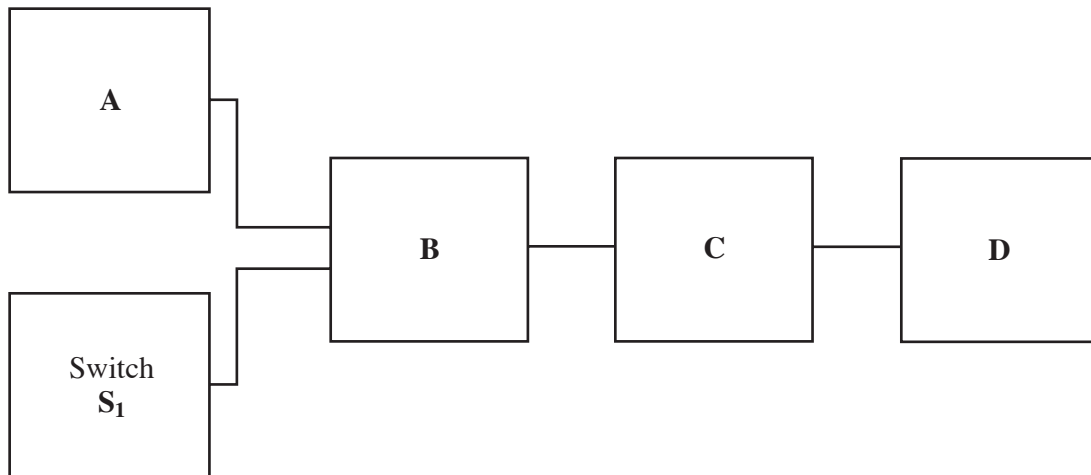3. Here is a system to warn someone that their freezer is too warm.

The output should only come on when switch  $S_1$  is pressed (high) and the output of block A is high.



(a) In each of the following tables place a tick  next to the correct answer:

(i) Which one of the following is the **best** sub-system to use as block A? [1]

Light sensing unit	
Temperature sensing unit	
Pressure sensing unit	

(ii) Which one of the following is the **best** sub-system to use as block B? [1]

AND gate	
OR gate	
Time delay	

(iii) Which one of the following is the **best** sub-system to use as block **C**?

[1]


switch	
Transistor switch/transducer driver	
comparator	

(b) Name a suitable sub-system for block **D**.

[1]

.....

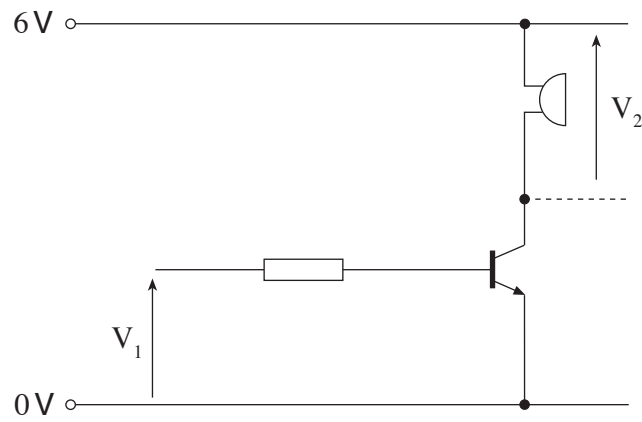4. The following circuit diagram shows part of a system used to switch on a buzzer .



The transistor is **just** saturated when the input voltage  $V_1$  is 2.2V.

Complete the following table to show:


- the voltage  $V_2$  for the input voltages  $V_1$  given,
- whether the buzzer will be **On** or **Off**.

[4]

$V_1$	$V_2$	Buzzer On/Off?
0.3 V		
2.8 V		

**BLANK PAGE**

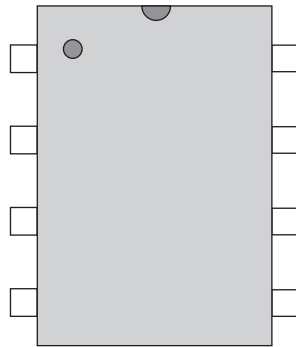
5. (a) The diagram shows a comparator IC seen from above.



(i) Label pin 8 with the number '8'. [1]

(ii) Label pin 5 with the number '5'. [1]

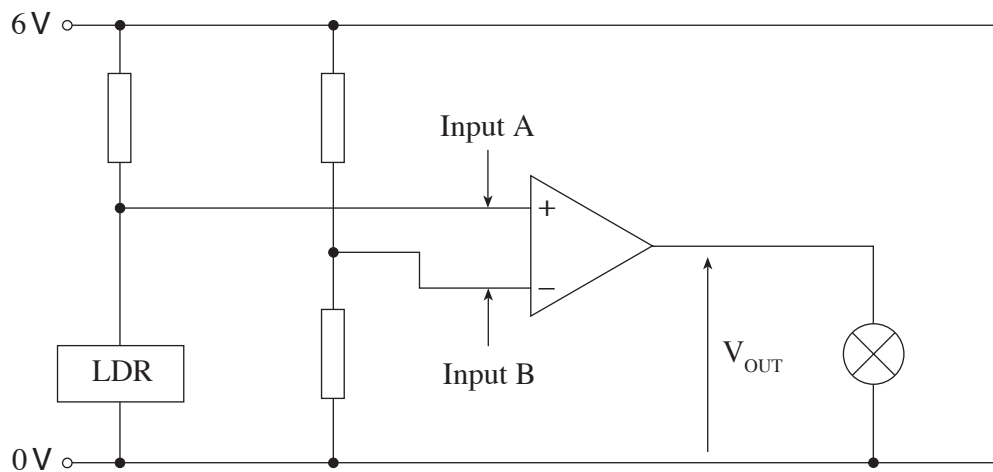- (b) This comparator circuit uses an LDR to switch on a nightlight when it becomes dark. The circuit diagram is shown below.



- (i) The circuit makes use of an LDR. Draw the circuit symbol for an LDR in the space below. [1]





- (ii) The output  $V_{OUT}$  of the comparator saturates at +6V and 0V.

Complete the table for the given values of the input voltages.


[2]

Input A (V)	Input B (V)	Output $V_{OUT}$ (V)
4.2	3.9	
4.5	5.1	

- (c) The circuit is modified by connecting a thyristor between the comparator output and the bulb.

- (i) Draw the circuit symbol for a thyristor in the space below.

[1]

 

- (ii) How will the addition of the thyristor affect the way the circuit behaves?

[1]

.....




6. (a) Which of the following is another name for an astable circuit?

- A Inverter
- B Time delay
- C Pulse generator
- D Latch

Answer .....

[1]

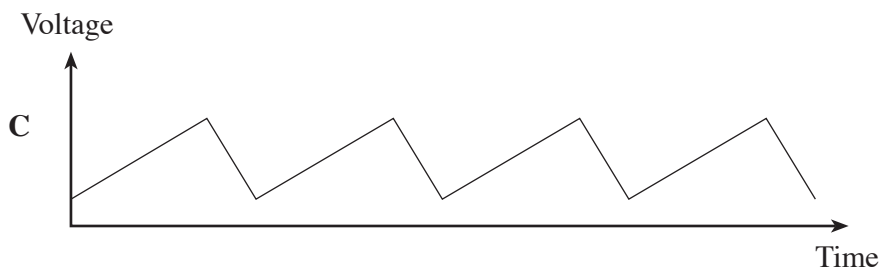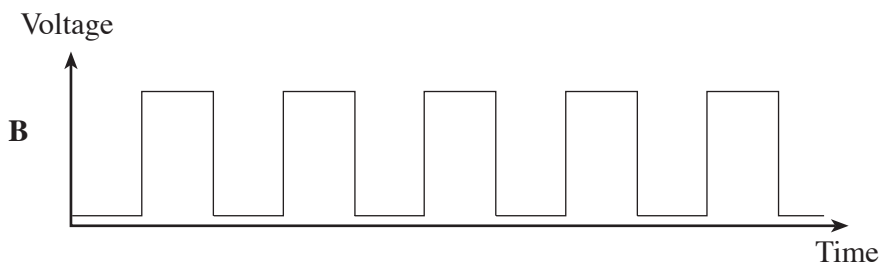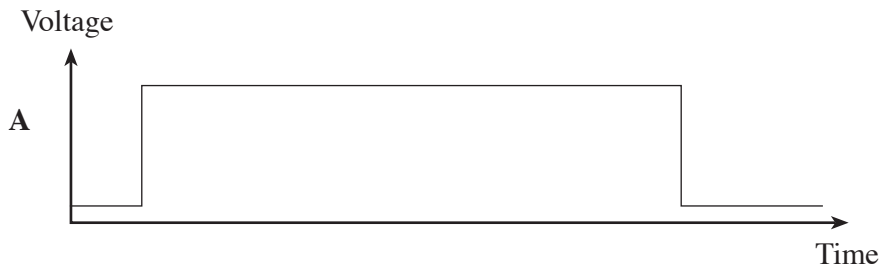(b) Which one of the following is the output signal produced by an astable circuit?



Answer .....

[1]

(c) Give one use of an astable circuit.


[1]

.....

**BLANK PAGE**

7. (a) Write the name of the logic gates in the space provided and complete the truth tables. [4]


(i) Gate 1

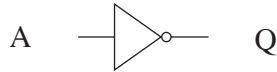

Input		Output
A		Q
0		
1		

Name of gate .....

(ii) Gate 2

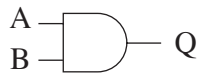

Input		Output
A	B	Q
0	0	
0	1	
1	0	
1	1	

Name of gate .....


(b) (i) Give the name of the logic gate whose output is the **inverse** of the output of Gate 2. [1]

.....

(ii) Draw the symbol of this gate in the space below. [1]


(c) Complete the truth table for the following logic system.

[3]

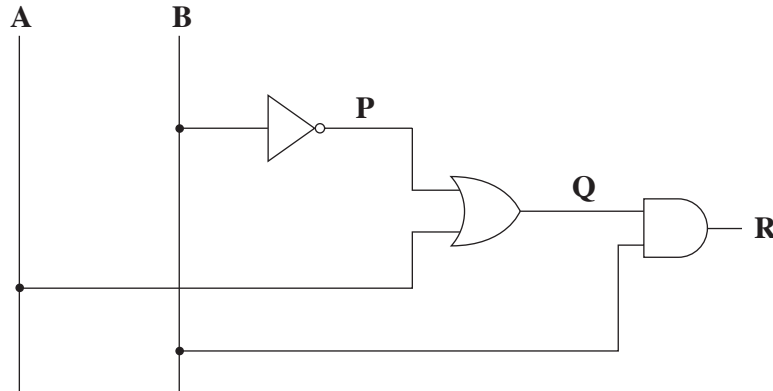

Input		Output		
A	B	P	Q	R
0	0			
0	1			
1	0			
1	1			

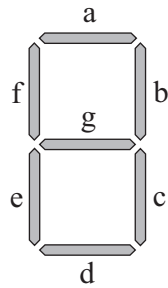
8. Here is a diagram of a seven segment display. It can be used to display numbers or letters.



Complete the following table to show which segments are lit and which number or letter is displayed. [3]

Number or letter	Segment						
	a	b	c	d	e	f	g
4	0	1	1				
H							
	1	0	0	0	1	1	1


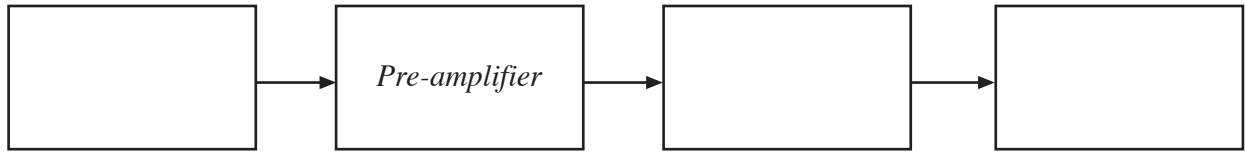
9. The block diagram for a public address system used in a school hall is shown below.



(a) Write the names of the other three blocks in the boxes on the above diagram. Choose from the following list.


*Power amplifier      Loudspeaker      Comparator      Microphone* [3]

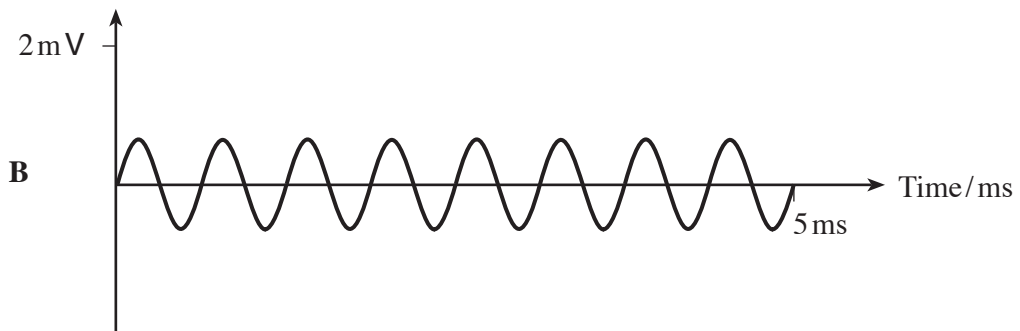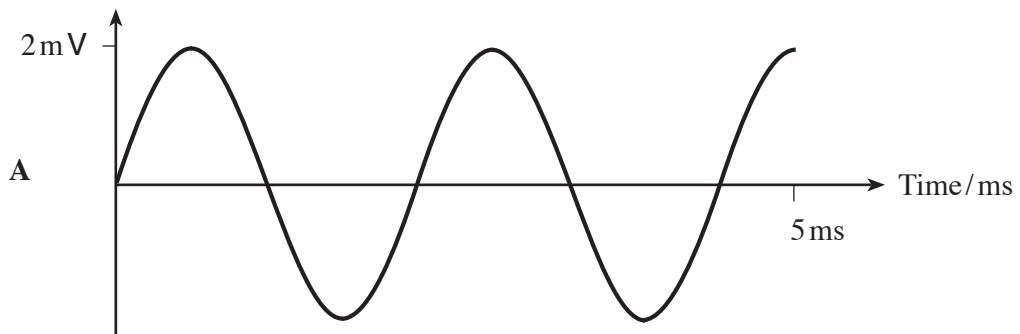(b) The following waveforms were produced by two microphones **A** and **B**.



- (i) Which signal, **A** or **B**, is the **quieter**? ..... [1]
- (ii) Which signal, **A** or **B**, has the **lower** pitch? ..... [1]

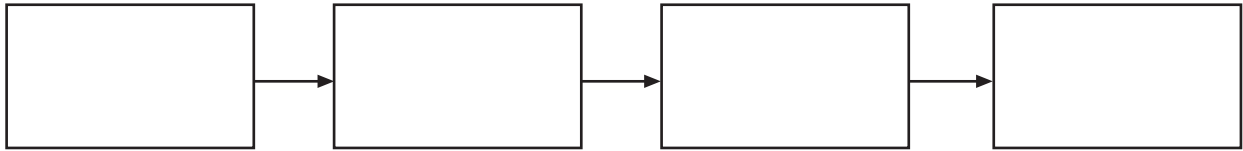10. The following is an incomplete block diagram for a simple radio receiver.



(a) Label the blocks on the diagram above, choosing from the following list of sub-systems. [4]

*tuned circuit          headphones          microphone          aerial          demodulator*


(b) Which of the sub-systems :

- (i) detects the radio waves; .....
- (ii) enables the audio signal to be heard; .....
- (iii) selects the radio station you want to listen to; .....
- (iv) separates the audio signal from the radio signal? .....

[4]




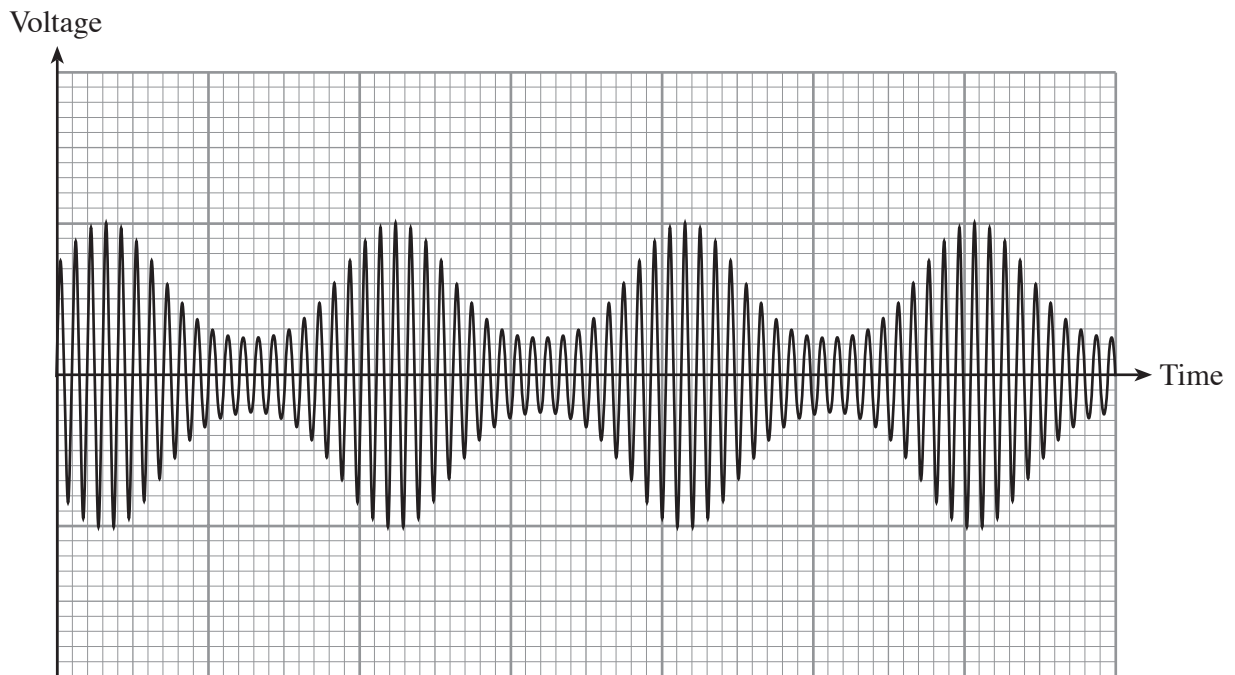(c) The graph shows a modulated carrier wave.




Use this information to sketch the audio signal which is being carried.

[2]

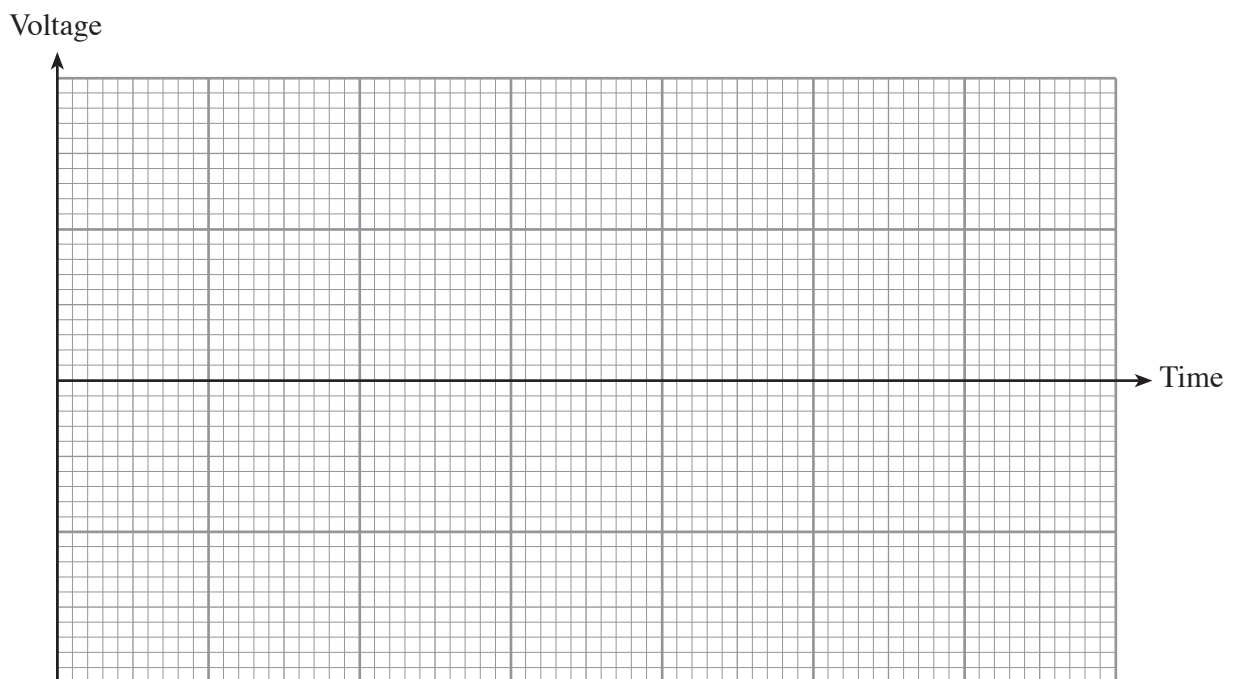

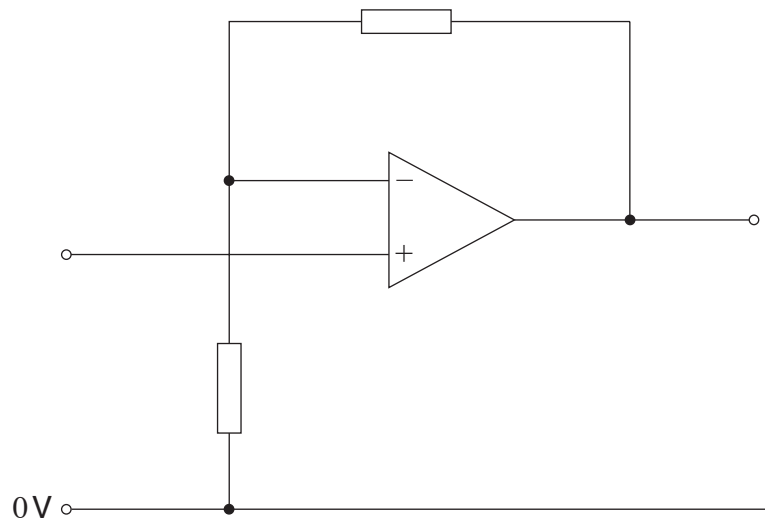11. The following diagram shows a **non-inverting** amplifier.



(a) Label each of the following on the diagram above.

- Feedback resistor (label it  $R_F$ )
- Output voltage (label it  $V_o$ )
- Non-inverting input (label it X)

[3]

(b) The input voltage is 5 mV.  
The output voltage is 500 mV.

Calculate the *voltage gain*.


[2]

.....


.....

.....

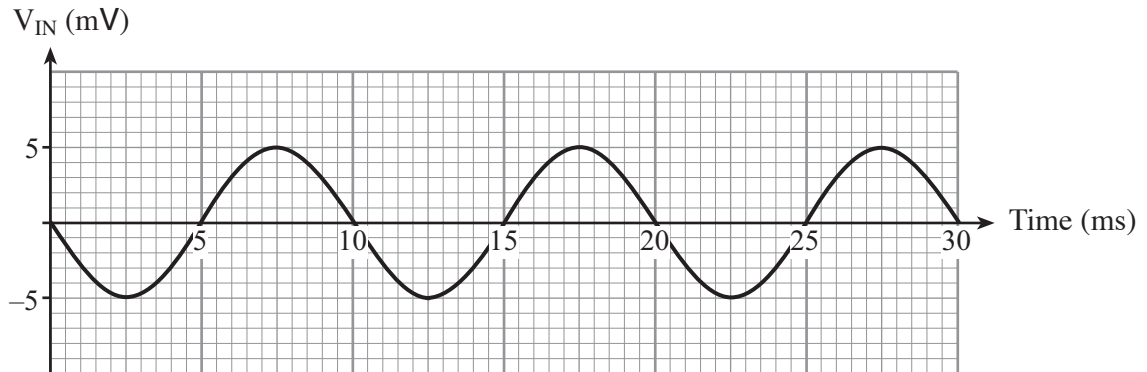- (c) The two resistors are now **changed** to give a gain of **30**.  
The following graph shows the input signal.



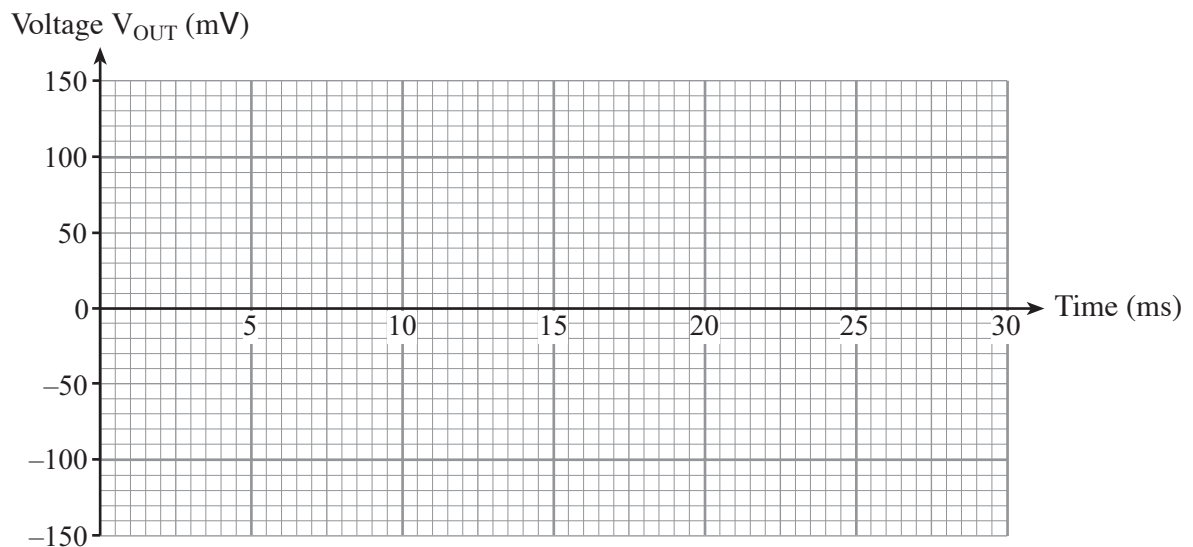
- (i) Use the above graph to find the maximum value of the input voltage  $V_{IN}$  in mV. [1]  
.....
- (ii) Calculate the maximum value of the corresponding output voltage  $V_{OUT}$  in mV. [2]  
.....
- (iii) Draw a graph of this output voltage  $V_{OUT}$ . [3]




12. An analogue signal can be converted into a digital signal and transmitted as a series of binary numbers.

This is done by sampling the analogue signal to make a PAM signal. This is then passed through an ADC to produce a digital signal.


Here are 3 signals:

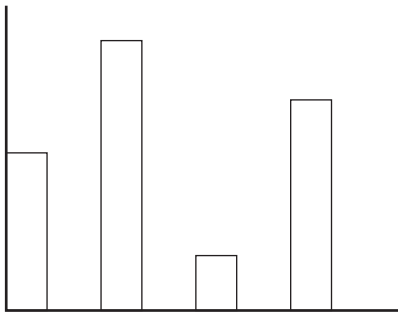

**Signal A**

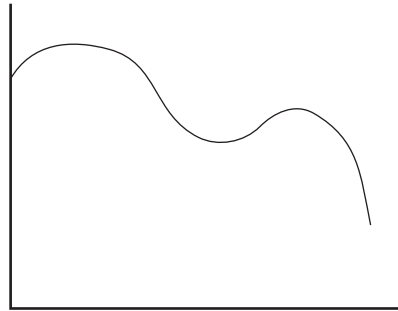

**Signal B**

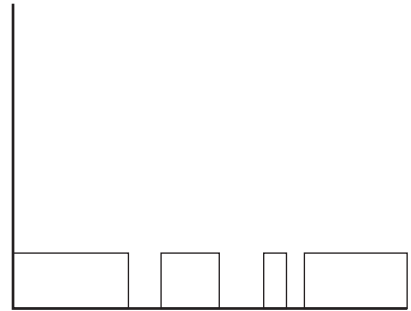

**Signal C**

Which signal, **A**, **B** or **C**, is:

- (i) the analogue input signal, .....
- (ii) the PAM signal, .....
- (iii) the digital output signal? .....

[3]

13. A maximum of 100 cars can enter a car park. A computer program is used to count the number of cars and close a barrier if 100 cars have entered.

(a) Name a suitable sensor to be used at the entrance.

[1]

(b) Complete the following flow chart for the program required by :

- writing the instructions in the empty boxes from the following list:

*Is counter = 100 ?*

*close barrier*

*counter = counter + 1*

- adding correct loops to the decision boxes.

[5]

