

Surname	Centre Number	Candidate Number
Other Names		0



**GCSE**

4162/01

**ELECTRONICS**

**UNIT E2**

**(Paper version of on-screen assessment)**

P.M. THURSDAY, 14 June 2012

1 hour

**Examiner only**

<b>Total Marks</b>	
--------------------	--

**ADDITIONAL MATERIALS**

In addition to this examination paper you may need a calculator.

**INSTRUCTIONS TO CANDIDATES**

Use black ink or black ball-point pen.

Write your name, centre number and candidate number in the spaces at the top of this page.

Answer **all** questions in the spaces provided in this booklet.

**INFORMATION FOR CANDIDATES**

The number of marks is given in brackets at the end of each question or part-question.

4162-010001

## INFORMATION SHEET FOR UNIT E2

This information may be of use in answering the questions.

### 1. Resistor Colour Codes

<b>BLACK</b>	<b>0</b>	<b>GREEN</b>	<b>5</b>
<b>BROWN</b>	<b>1</b>	<b>BLUE</b>	<b>6</b>
<b>RED</b>	<b>2</b>	<b>VIOLET</b>	<b>7</b>
<b>ORANGE</b>	<b>3</b>	<b>GREY</b>	<b>8</b>
<b>YELLOW</b>	<b>4</b>	<b>WHITE</b>	<b>9</b>

The fourth band colour gives the tolerance as follows:

**GOLD**     $\pm$     **5%**

**SILVER**    $\pm$     **10%**

### 2. Preferred Values for Resistors – E24 series


10, 11, 12, 13, 15, 16, 18, 20, 22, 24, 27, 30, 33, 36, 39, 43, 47, 51, 56, 62, 68, 75, 82, 91.

3. **Resistance** =  $\frac{\text{voltage}}{\text{current}}$  ;  $R = \frac{V}{I}$ .

4. **Effective resistance**,  $R$ , of two resistors  $R_1$  and  $R_2$  in series is given by  $R = R_1 + R_2$ .

5. **Effective resistance**,  $R$ , of two resistors  $R_1$  and  $R_2$  in parallel is given by  $R = \frac{R_1 R_2}{R_1 + R_2}$ .

### 6. Voltage Divider

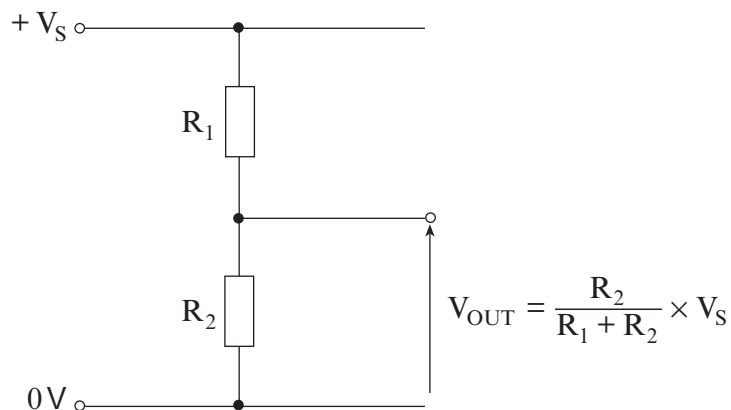

7. **Power** = voltage  $\times$  current;  $P = VI = I^2R = \frac{V^2}{R}$ .

8. **LED** The forward voltage drop across an LED is 2V.

9. **NPN Transistors**    (i) **Current gain** =  $\frac{\text{Collector current}}{\text{Base current}}$ ;  $h_{FE} = \frac{I_C}{I_B}$ .

(ii) The forward voltage drop across the base emitter junction is 0.7V.

**10. Amplifiers**

Voltage gain:  $A = \frac{V_{\text{OUT}}}{V_{\text{IN}}}$

Non-inverting amplifier:  $A = 1 + \frac{R_F}{R_1}$





Inverting amplifier:  $A = -\frac{R_F}{R_{\text{IN}}}$

Summing amplifier:  $V_{\text{OUT}} = -R_F \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots \right)$


Answer **all** questions.

1. Which graph shows the output signal for a monostable set up to produce a delay of 11 s?  
(Tick (✓) the correct answer.)

[1]

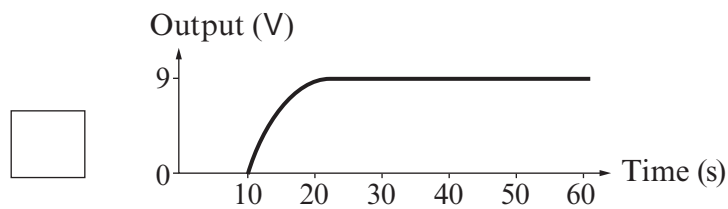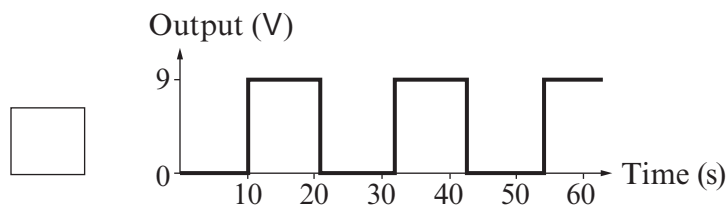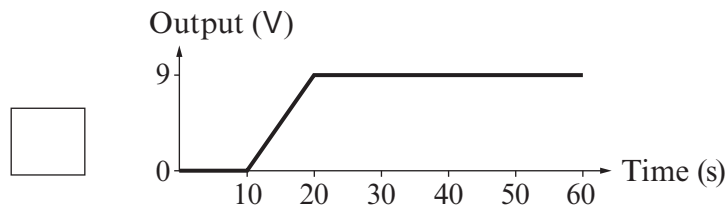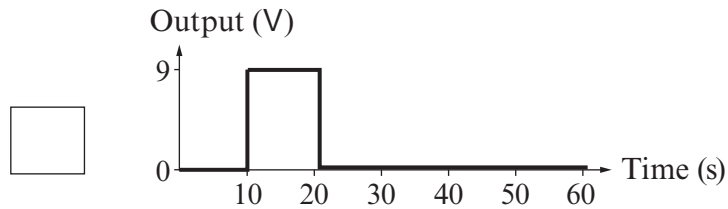

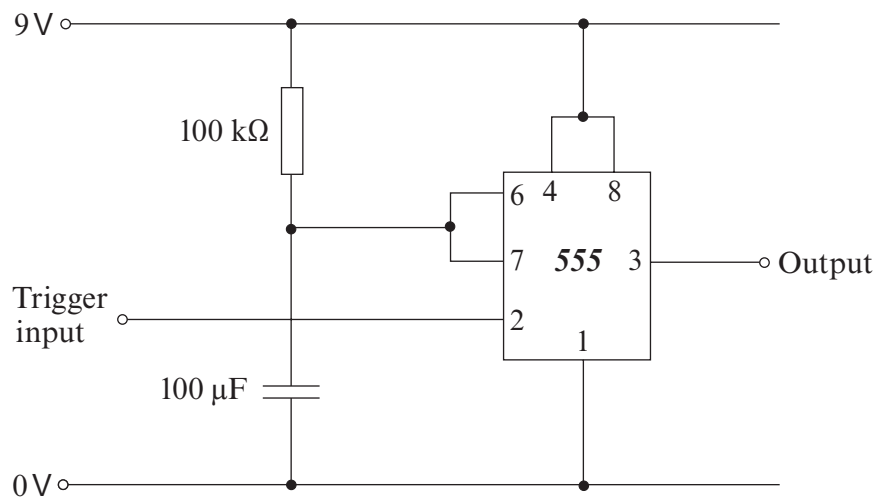2. The circuit diagram shows a 555 timer set up as a monostable to give a time delay of 11 seconds.




The 100 kΩ resistor is replaced with a 200 kΩ resistor. What is the new time delay?  
(Tick (✓) the correct answer.)

[1]

- 1.1 s
- 5.5 s
- 11 s
- 22 s
- 110 s

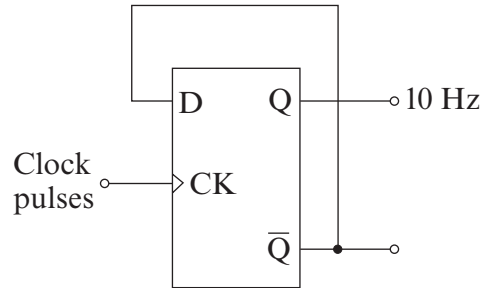3. The diagram shows a D-type flip-flop used in a divide-by-two circuit. Pulses from the Q output have a frequency of 10 Hz.



Give the frequency of the signals at:

- (a) the clock input; ..... Hz [1]
- (b) the  $\bar{Q}$  output. .... Hz [1]

4. Which **one** of the following systems **must** contain an astable circuit? (Tick (✓) the correct answer.) [1]


- A bath alarm flashes an LED on and off when the bath water is too hot.
- In a kitchen timer, a buzzer comes on and stays on until a reset switch is pressed.
- In a game scorer, a lamp lights as soon as one team reaches a score of 5.
- A car alarm sounds the horn continuously for 2 minutes when someone rocks the car.

5. An electronic toothbrush warns the user that the battery voltage is too low by sounding a buzzer for three seconds.


The control system does this by generating a single square pulse with an amplitude of 5V and a period of 3s.

Complete the graph by drawing this pulse. *The trace is started for you.*



[2]

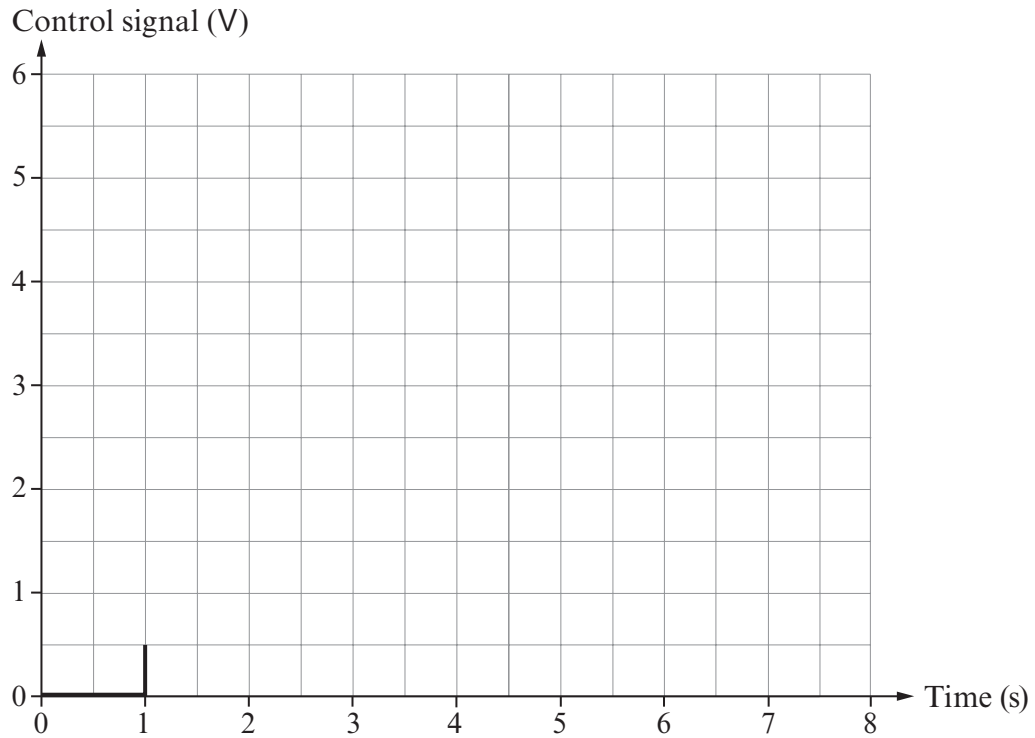

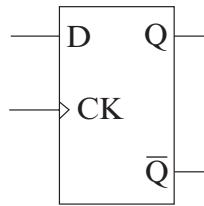6. This D-type flip-flop is rising-edge triggered.



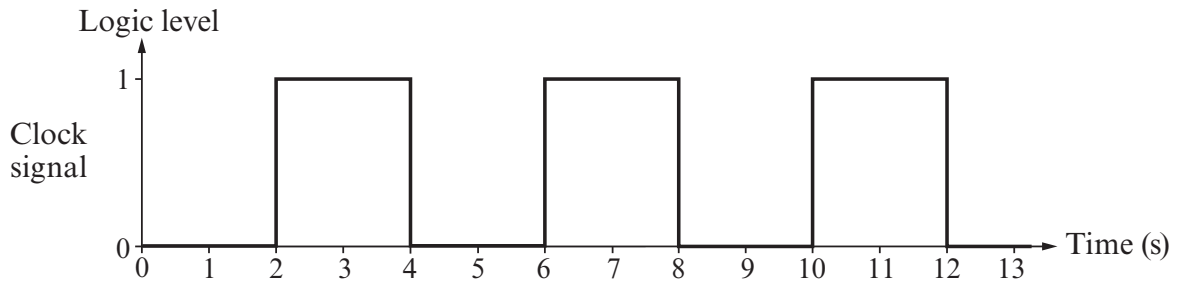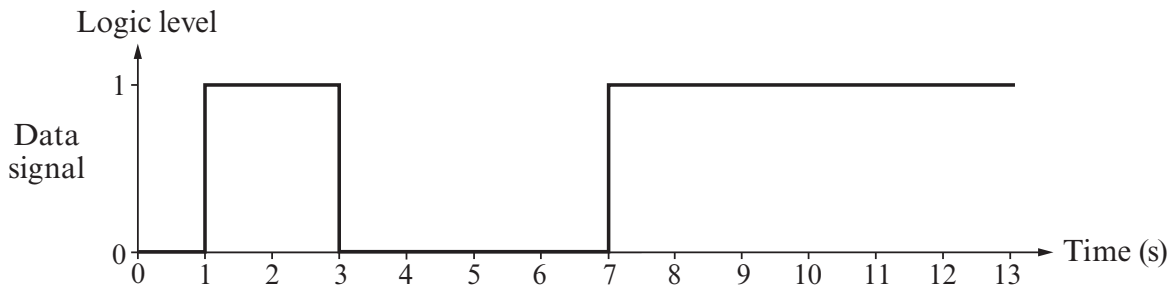The graphs show the data and clock signals.



What logic level is present on the Q output:

- (a) at time 5s; ..... [1]
- (b) at time 9s; ..... [1]
- (c) at time 13s? ..... [1]
- (d) Which line of the table gives the signals on the  $\bar{Q}$  output at the times shown?  
(Tick (✓) the correct answer.) [1]



	time = 5 s	time = 9 s	time = 13 s
<input type="checkbox"/>	0	1	0
<input type="checkbox"/>	0	1	1
<input type="checkbox"/>	1	0	0
<input type="checkbox"/>	1	0	1



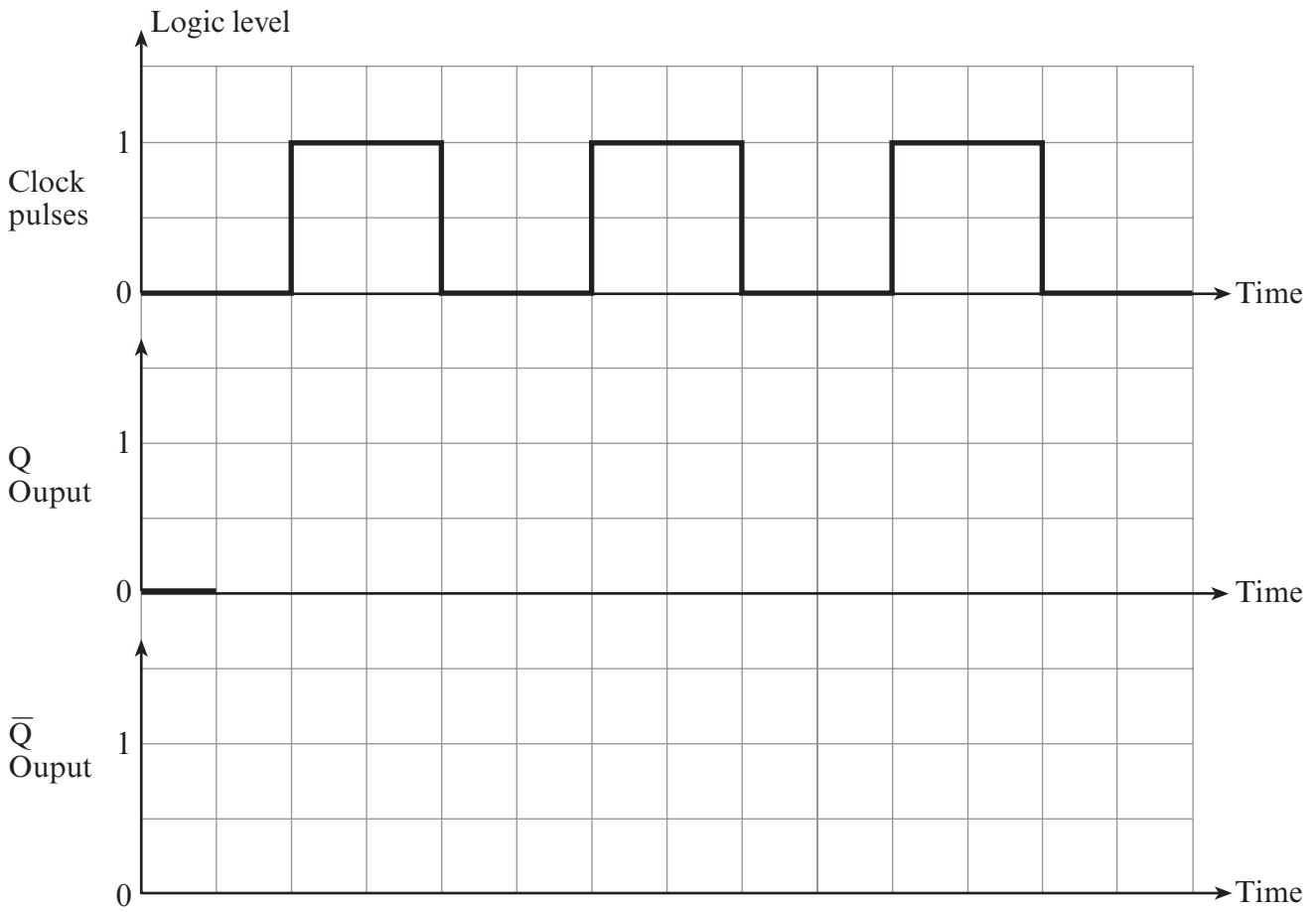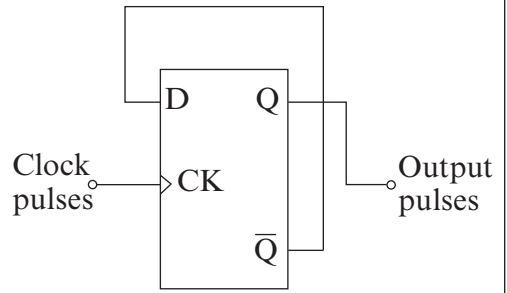
7. The diagram shows a D-type flip-flop set up as a one-bit counter. The Q output starts at logic 0.

The upper graph shows the clock pulses applied to the counter.

Complete the corresponding output signals at the Q and  $\bar{Q}$  terminals. [3]



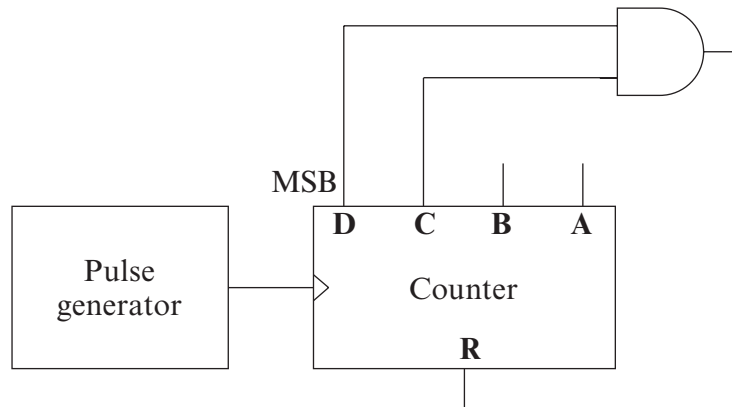8. The diagram shows a four-bit up counter. Output **D** is the most significant bit (MSB).



The table shows the initial sequence of output signals caused by clock pulses from the pulse generator.

Clock pulses received	Outputs			
	D	C	B	A
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0

- (a) Which line shows the signals at the outputs after four clock pulses have been received? (Tick (✓) the correct answer.) [1]

	Clock pulses received	Outputs			
		D	C	B	A
<input type="checkbox"/>	4	0	0	1	1
<input type="checkbox"/>	4	0	1	0	0
<input type="checkbox"/>	4	0	1	0	1
<input type="checkbox"/>	4	0	1	1	0

- (b) How many clock pulses are needed to make the **D** output produce a logic 1 signal?  
(Tick (✓) the correct answer.) [1]

5

6


7

8

- (c) The counter resets when the Reset input receives a logic 1 signal.  
Which output combination will reset the counter?  
(Tick (✓) the correct answer.) [1]

Outputs				
	<b>D</b>	<b>C</b>	<b>B</b>	<b>A</b>
<input type="checkbox"/>	0	1	0	1
<input type="checkbox"/>	0	1	1	0
<input type="checkbox"/>	1	0	0	1
<input type="checkbox"/>	1	1	0	0

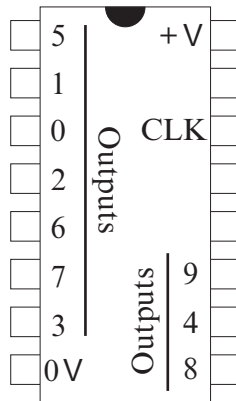9. In one type of counter, each output is activated in turn when the clock pulses arrive.




A typical pinout is shown in the diagram.

Which type of counter IC does this describe? ..... [1]

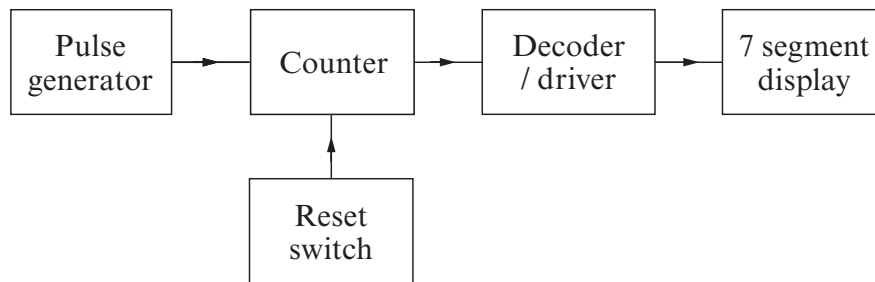10. The diagram shows a system that displays the number of pulses received from a pulse generator.


A reset switch is used to restart the count.



Which counter could be used in this system without requiring extra connections to reset it when the count passes 9? (Tick (✓) the correct answer.) [1]

- up/down counter
- a binary counter
- a BCD counter
- a decade counter

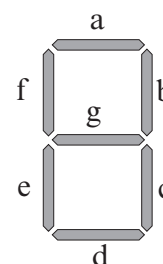11. The diagram shows a 7-segment display.  
A logic 1 signal makes a segment light up.



- (a) Identify the character displayed by the signals shown.

[1]

Segments							Character displayed
a	b	c	d	e	f	g	
1	1	1	0	0	0	0	


- (b) Complete the signals needed to display the letter 'H'.

[1]


Segments							Character displayed
a	b	c	d	e	f	g	
							H

12. Complete the diagram for an amplifier system using some of the sub-systems given. You can use each sub-system **once, more than once or not at all**.

[3]

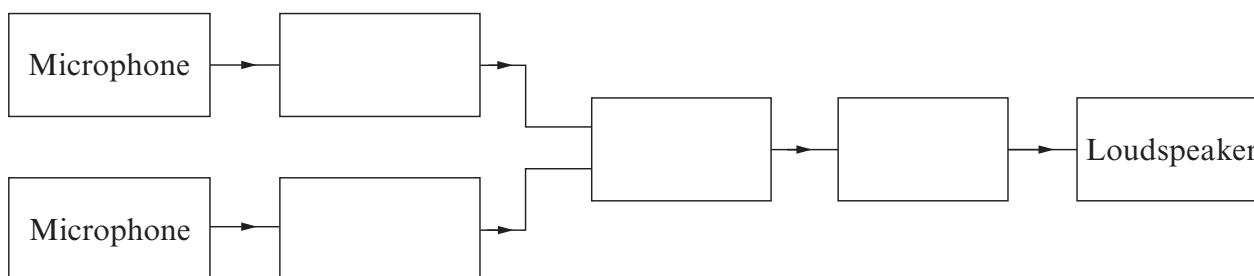

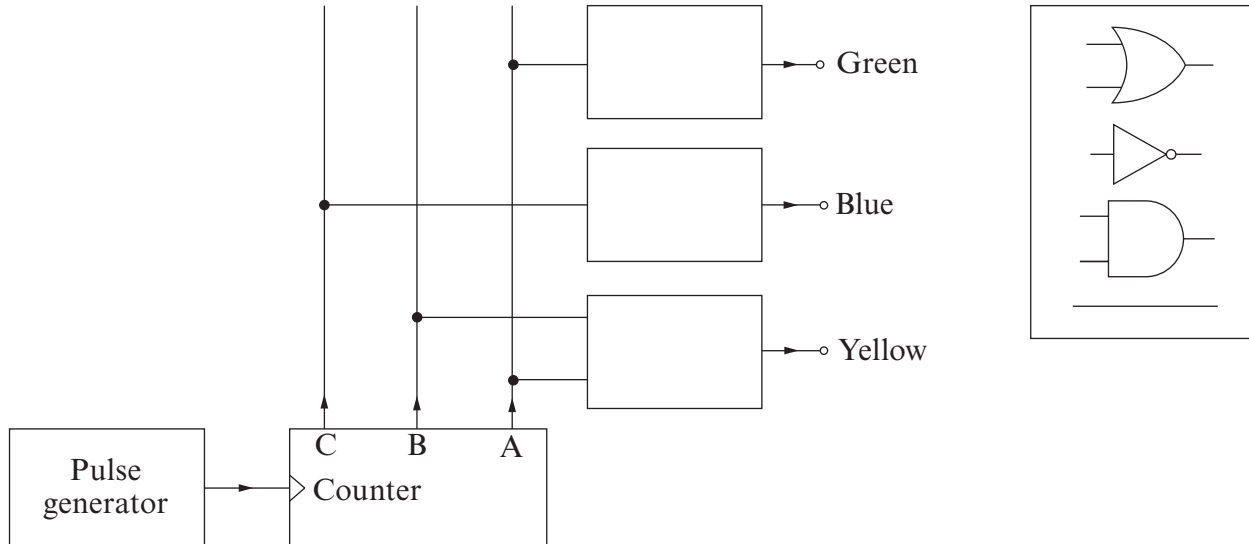13. The diagram shows part of the control system for a set of coloured lights. Each light is switched on when it receives a logic 1 signal.





Complete the diagram by adding three of the components provided. The required sequence of lights is shown in the table.

[3]


Pulses from pulse generator	Counter outputs			Lights		
	C	B	A	Yellow	Blue	Green
0	0	0	0	0	1	0
1	0	0	1	1	1	1
2	0	1	0	1	1	0
3	0	1	1	1	1	1
4	1	0	0	0	0	0
5	1	0	1	1	0	1
6	1	1	0	1	0	0
7	1	1	1	1	0	1

14. A non-inverting amplifier has a voltage gain of 4.  
 The upper graph shows the signal applied to the input of the amplifier.  
 Use the axes provided to draw the corresponding output signal.

[3]

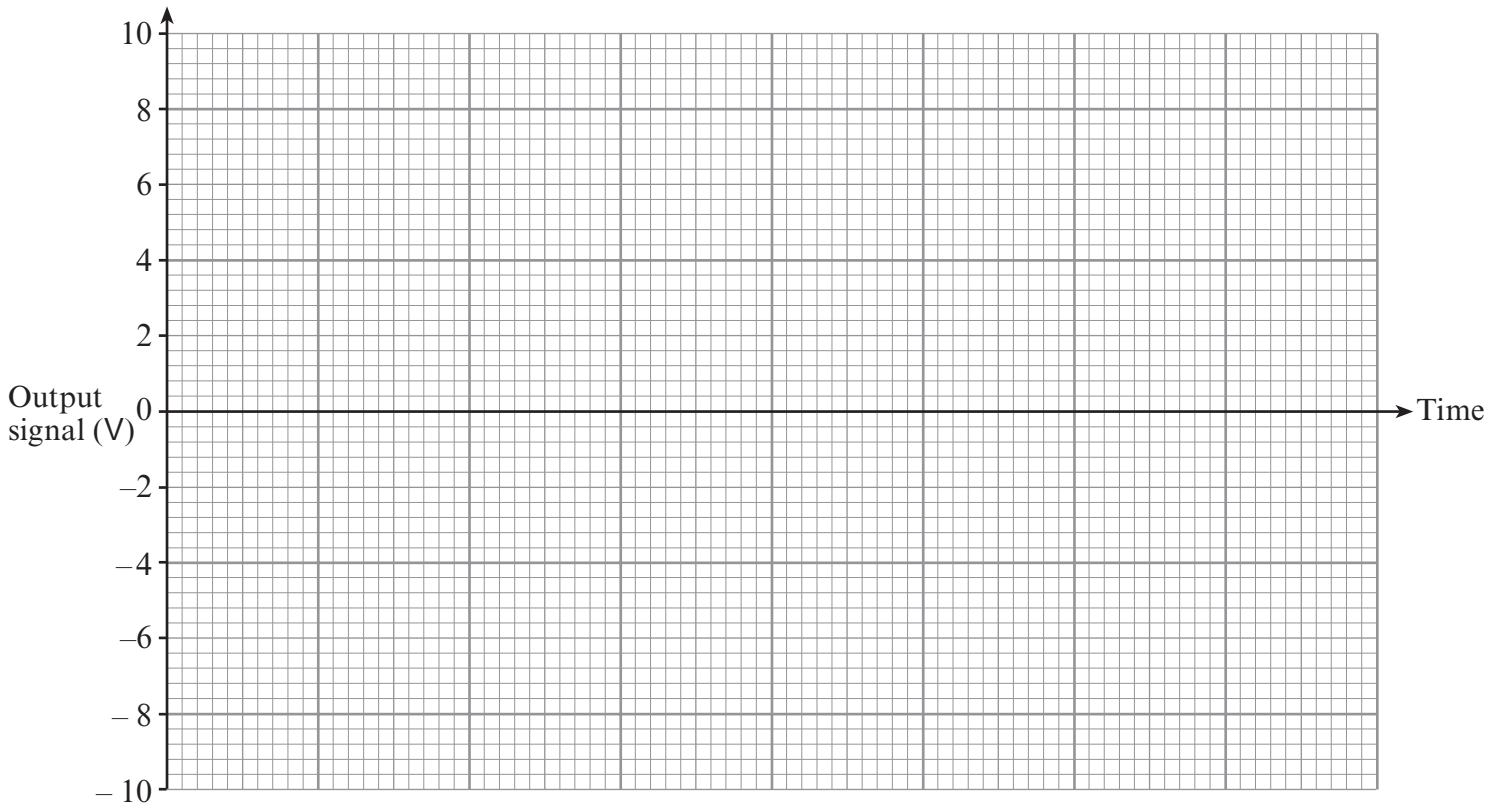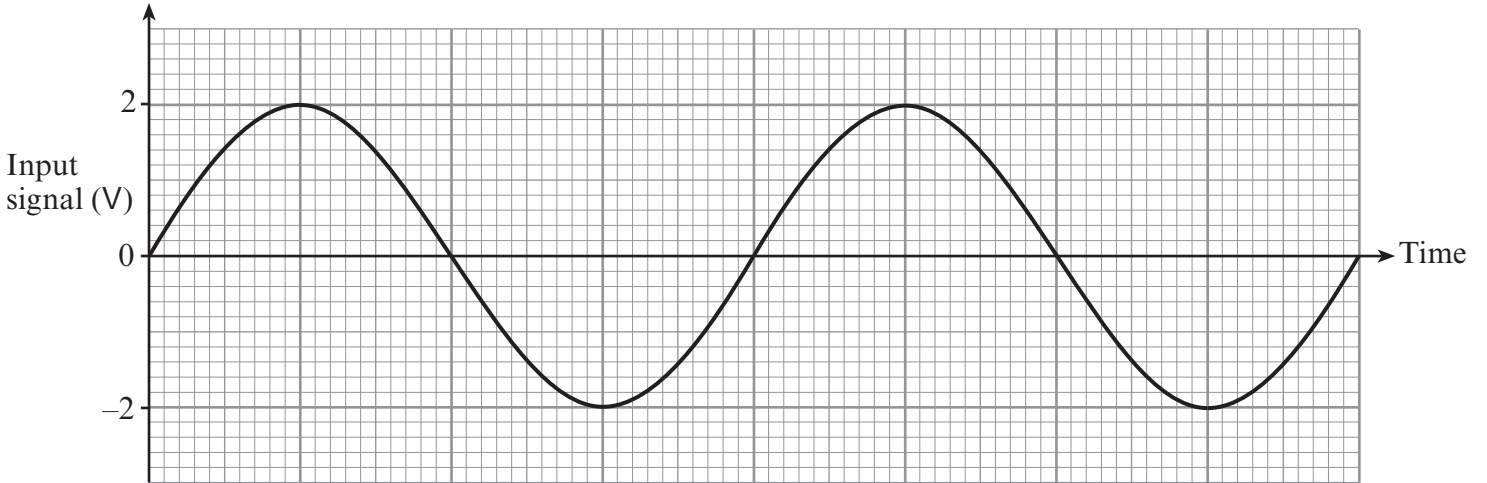


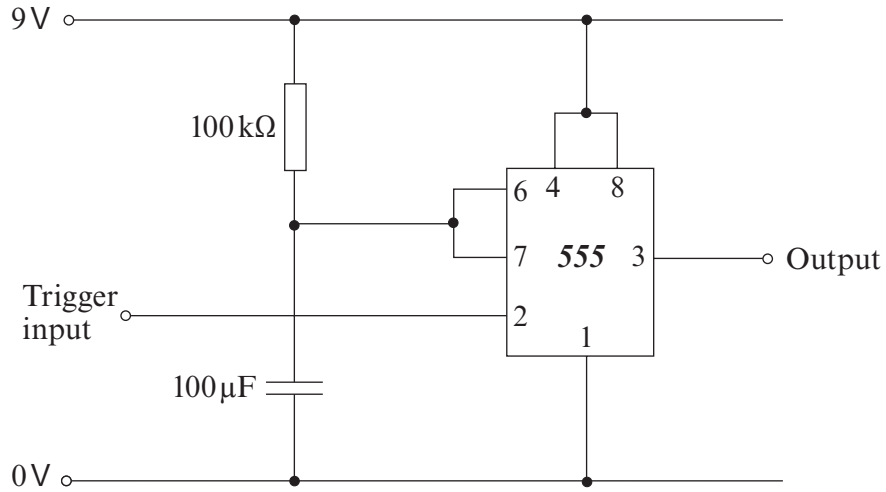15. The monostable circuit shown in the diagram is triggered by the falling-edge of a signal applied to the trigger input.




This can be achieved by using push-to-make or push-to-break switches.

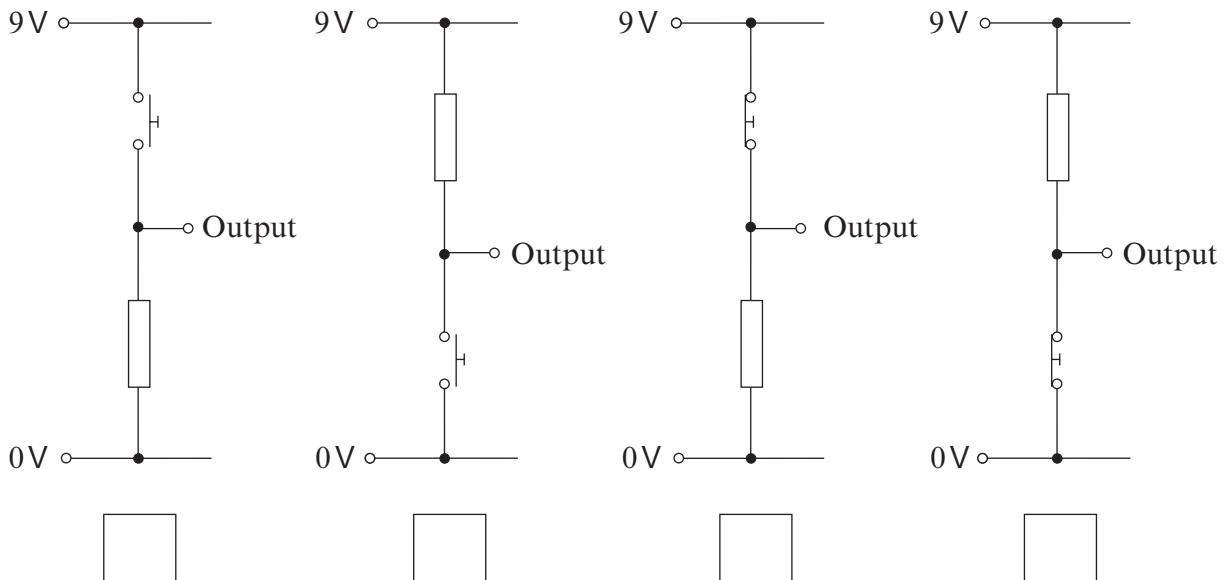Which **two** of the following produce a falling-edge signal at the output when the switch is pressed? (Tick (✓) the correct answers.) [2]






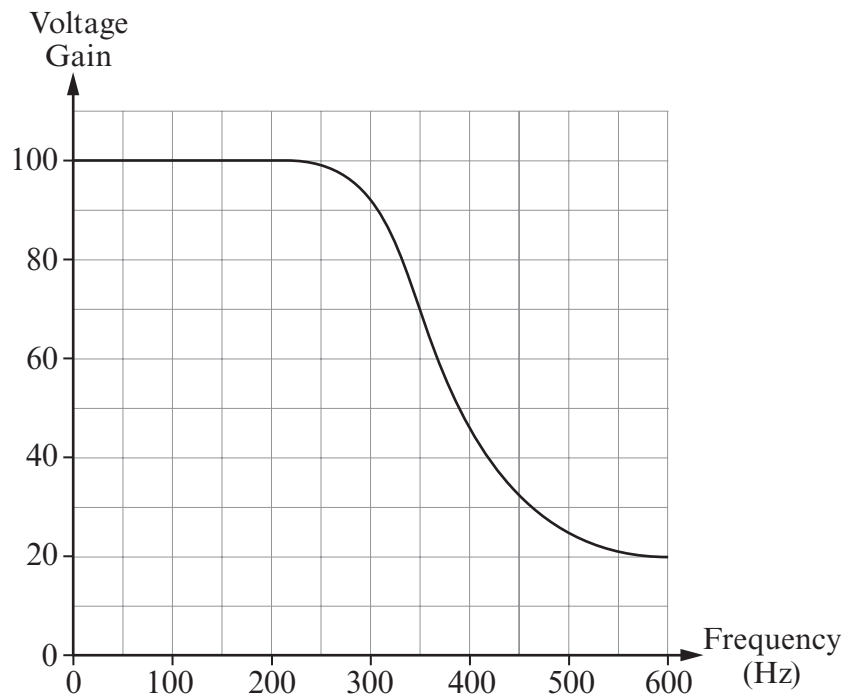16. The graph shows the frequency response of a voltage amplifier.




What is the bandwidth of this amplifier in Hz? ..... [1]

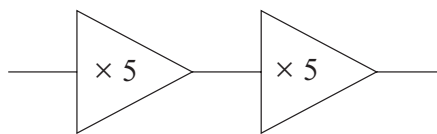17. Two multistage amplifiers are shown. They use identical op-amps, which are configured to give the gains shown.



System A

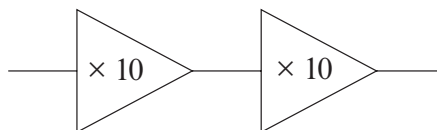

System B

Which system, A or B, has the bigger gain? .....

Which system, A or B, has the bigger bandwidth? ..... [1]

18. The output signal from a voltage amplifier is 'clipped'.


Which is the best solution to remove the clipping? (Tick (✓) the correct answer.)

[1]

- Increase the power supply voltage to the amplifier.
- Reduce the power supply voltage to the amplifier.
- Increase the bandwidth of the amplifier.
- Reduce the bandwidth of the amplifier.

19. Which combination of resistors would give the following non-inverting amplifier a voltage gain of 10? (Tick (✓) the correct answer.)

[1]

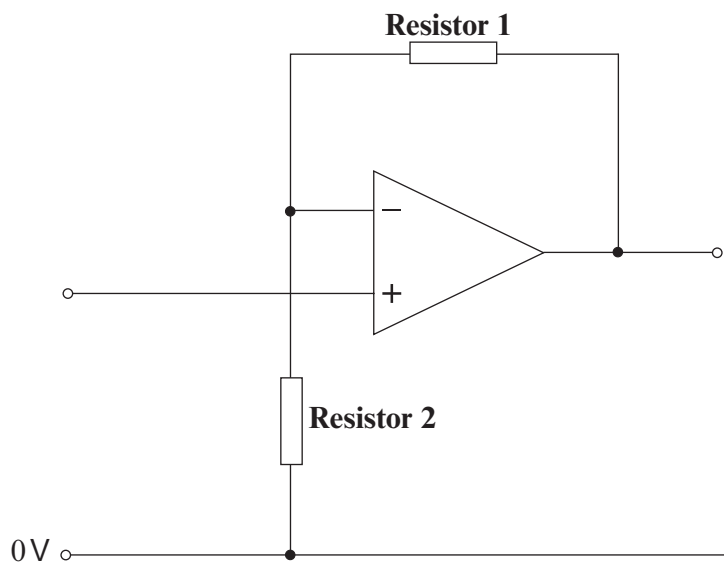


	Resistor 1	Resistor 2
<input type="checkbox"/>	9 k $\Omega$	1 k $\Omega$
<input type="checkbox"/>	1 k $\Omega$	9 k $\Omega$
<input type="checkbox"/>	1 k $\Omega$	10 k $\Omega$
<input type="checkbox"/>	10 k $\Omega$	1 k $\Omega$

20. Here is part of a data sheet for a Schmitt Inverter.

When connected to 5V supply:

- Logic 0 = 0V
- Logic 1 = 5V
- The output changes from logic 1 to logic 0 when a **rising** input voltage reaches 3V
- The output changes from logic 0 to logic 1 when a **falling** input voltage reaches 1V

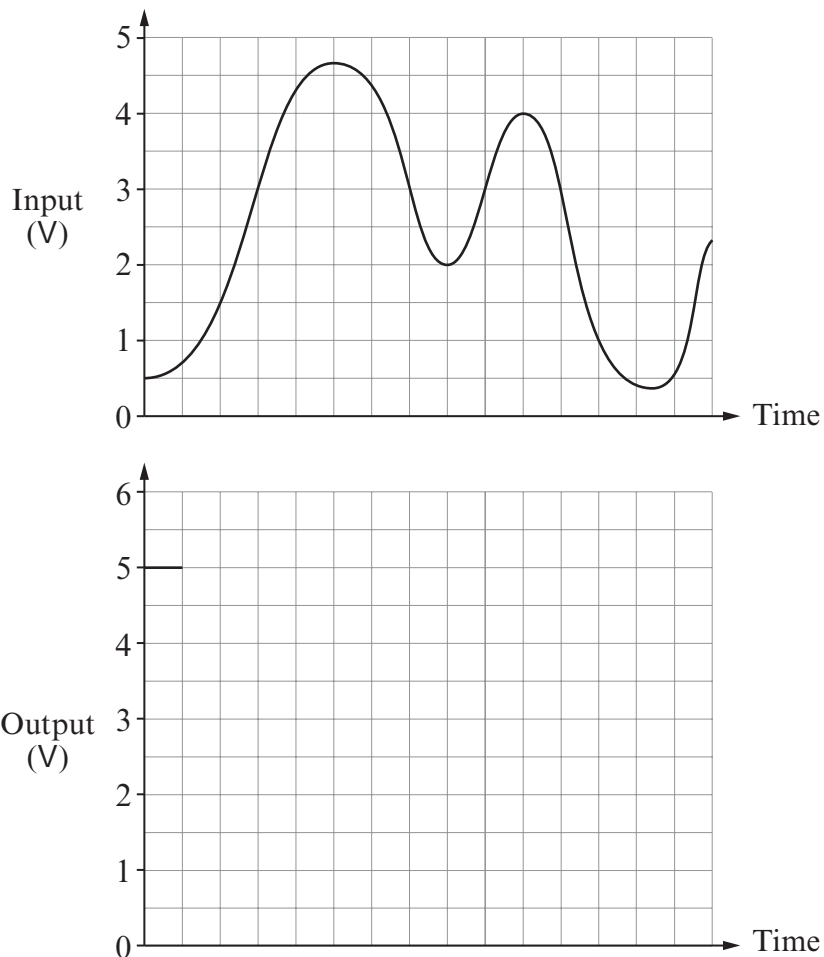The input signal for the Schmitt Inverter is shown below.




Use the axes provided to complete the corresponding output signal.

[3]

21. The transistor switch in the diagram acts as an interface between a logic system and three lamps.

Each lamp is rated at 12V, 100 mA.

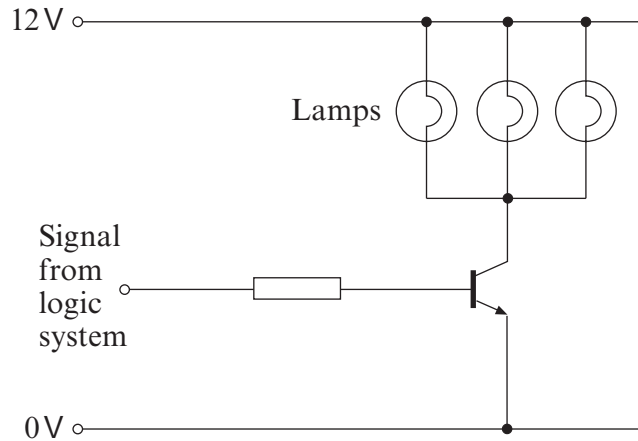

(a) What is the collector current when the three lamps are fully lit?


Collector current = ..... mA [1]

(b) Using the following table, which transistor is capable of driving the three lamps, whilst drawing the smallest current from the logic system?

(Tick (✓) the correct answer.) [1]

	Transistor	Current gain, $h_{FE}$	Collector current, $I_C$ max
<input type="checkbox"/>	A	50	120
<input type="checkbox"/>	B	100	120
<input type="checkbox"/>	C	50	500
<input type="checkbox"/>	D	150	500

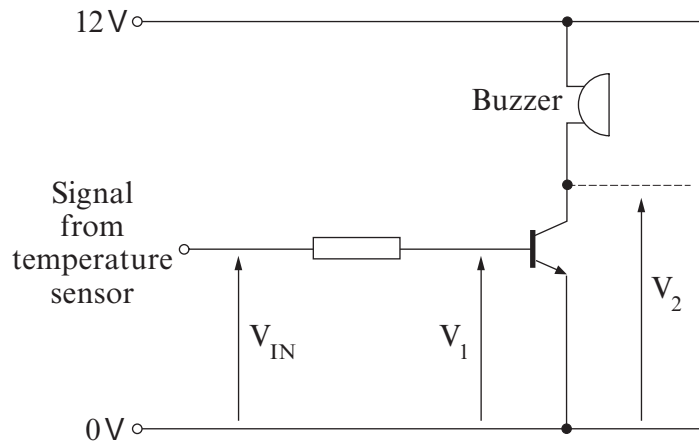22. A simple fire alarm uses a transistor switch.




Complete the table to show the voltages  $V_1$  and  $V_2$  for the input voltages  $V_{IN}$  given.

[4]

	$V_{IN}$	$V_1$	$V_2$
(a)	0.2V		
(b)	1.2V		

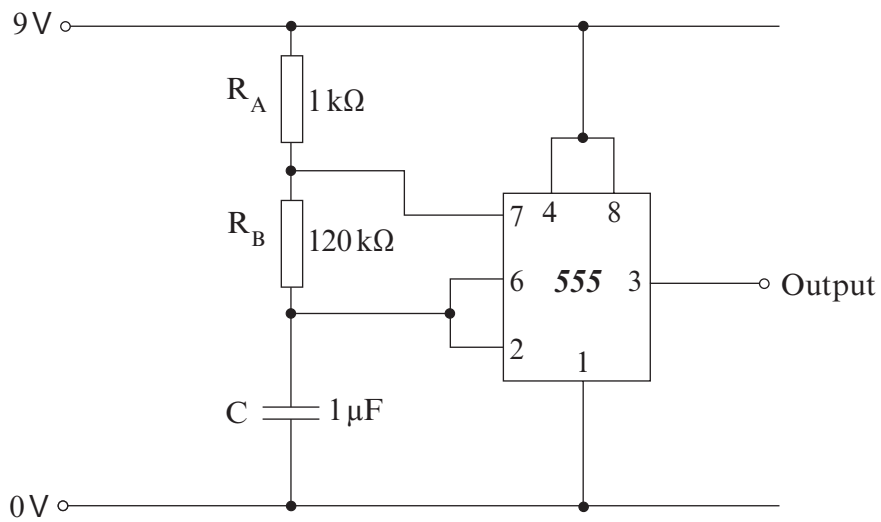23. The circuit diagram shows an astable circuit.



The output frequency can be calculated using the formula:


$$f = \frac{0.72}{R_B \times C}$$

Calculate the output frequency.

Output frequency = ..... Hz

[1]

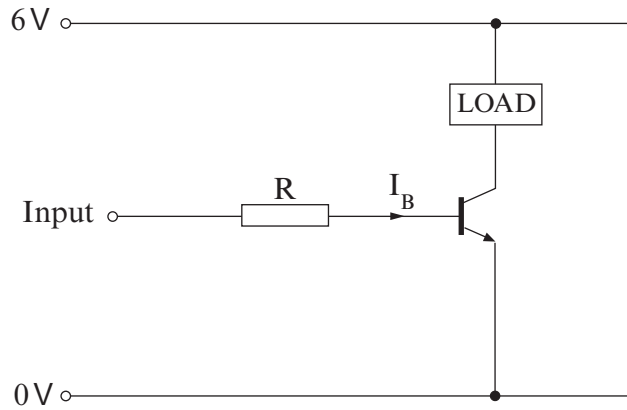24. The diagram shows a transistor switch circuit.  
The input voltage  $V_{IN} = 5.2\text{V}$  and  $V_{BE} = 0.7\text{V}$ .



- (a) Calculate the voltage drop across resistor R.

Voltage drop = ..... V [1]

- (b) Calculate the ideal value of resistor R, in  $k\Omega$  that gives a base current,  $I_B$  of 2 mA. [1]

.....

.....

.....


25. Amplifier systems often contain a mixer to combine signals.

The diagram shows part of the circuit of a mixer, used to combine signals **1** and **2**.

The box on the right contains the available components.


Draw the correct component in each of the dotted boxes.

[4]

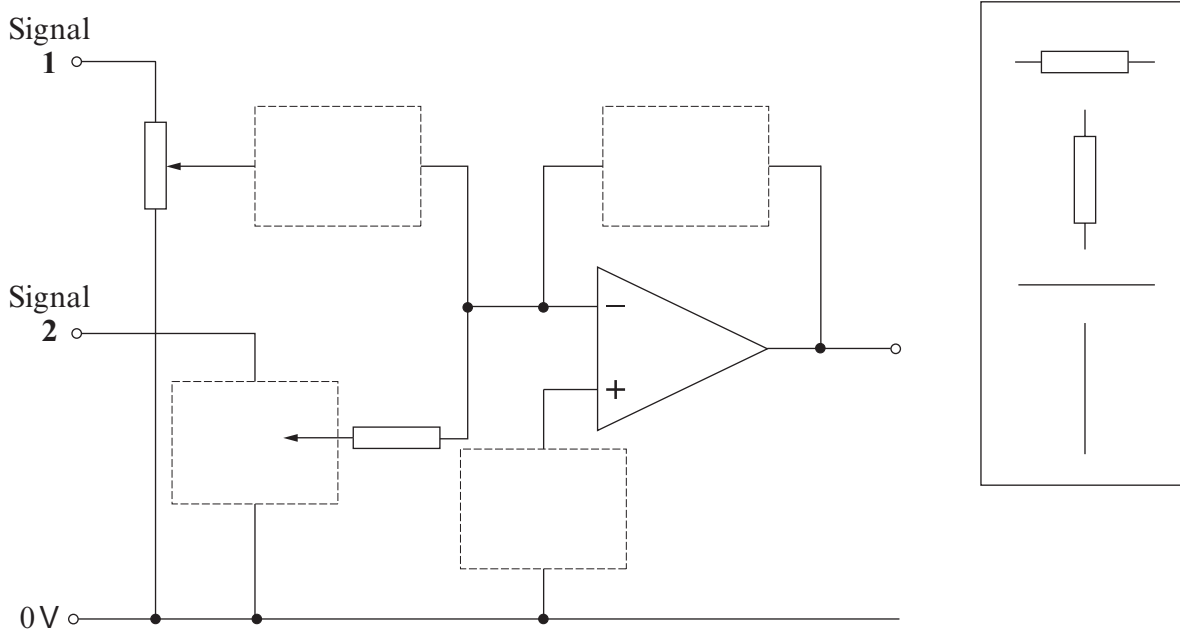



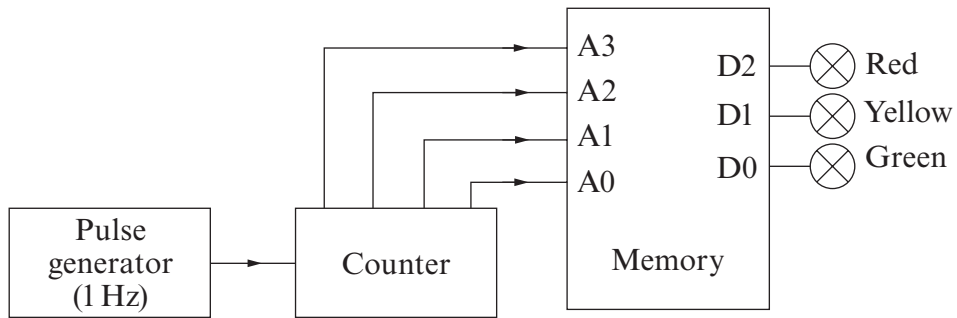26. The block diagram shows a simple traffic light system controlled by a memory IC.



The data stored in the memory IC is shown in the following table:

A3	A2	A1	A0	D2	D1	D0
0	0	0	0	1	0	0
0	0	0	1	1	0	0
0	0	1	0	1	0	0
0	0	1	1	1	1	0
0	1	0	0	1	1	0
0	1	0	1	0	0	1
0	1	1	0	0	0	1
0	1	1	1	0	1	0
1	0	0	0	0	1	0
1	0	0	1	Reset		

(a) For how many seconds does the red light stay on after the counter is reset?

..... s

[1]

(b) How long does the whole sequence take before it is reset?

..... s


[1]

(c) This memory IC has 4 address pins, A3, A2, A1 and A0. What is the maximum number of steps that can be stored in this memory IC?

.....

[1]

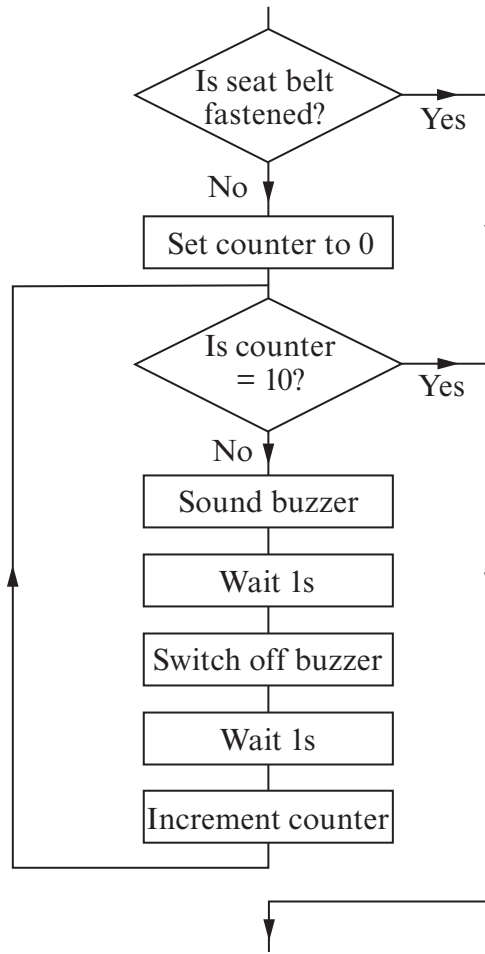27. Here is part of the flowchart for a car safety system. It warns the driver that the seat belt is not fastened.



(a) What is the effect of the first two boxes? [2]

.....

.....

.....

.....

(b) The seat belt is not fastened. Explain in detail what the buzzer does. [3]

.....

.....

.....

.....

.....

.....

**THERE ARE NO MORE QUESTIONS IN THE EXAMINATION**