

Candidate Name	Centre Number	Candidate Number

WELSH JOINT EDUCATION COMMITTEE
General Certificate of Secondary Education



CYD-BWYLLGOR ADDYSG CYMRU
Tystysgrif Gyffredinol Addysg Uwchradd

293/01

ELECTRONICS

MODULE TEST E1

FOUNDATION TIER

P.M. THURSDAY, 25 May 2006

(45 minutes)

For Examiner's use only

Total Mark	
-----------------------	--

ADDITIONAL MATERIALS

In addition to this examination paper you may need a calculator.

INSTRUCTIONS TO CANDIDATES

Write your name, centre number and candidate number in the spaces at the top of this page.

Answer **all** the questions in the spaces provided in this booklet.

INFORMATION FOR CANDIDATES

The number of marks is given in brackets at the end of each question or part-question.

No certificate will be awarded to a candidate detected in any unfair practice during the examination.

INFORMATION SHEET

This information may be of use in answering the questions.

1. Resistor Colour Codes

BLACK	0	GREEN	5
BROWN	1	BLUE	6
RED	2	VIOLET	7
ORANGE	3	GREY	8
YELLOW	4	WHITE	9

The fourth band colour gives the tolerance as follows:

GOLD $\pm 5\%$

SILVER $\pm 10\%$


2. Preferred Values for Resistors

E 12 SERIES OF PREFERRED VALUES 10; 12; 15; 18; 22; 27; 33; 39; 47; 56; 68; 82 and multiples thereafter
--

3. Resistance = $\frac{\text{voltage}}{\text{current}}$; $R = \frac{V}{I}$.

4. Effective resistance, R, of two resistors R_1 and R_2 in series is given by $R = R_1 + R_2$.

5. Voltage Divider

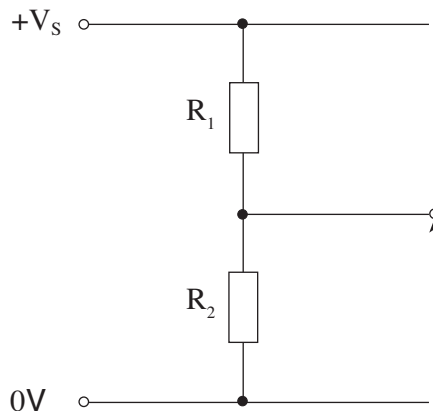

$$V_{\text{OUT}} = \frac{R_2}{R_1 + R_2} \times V_s$$

6. Power = voltage \times current; $P = VI$

7. LED The forward voltage drop across a LED is 2V.

8. Transistors

The forward voltage drop across the base emitter junction is 0.7V.

Answer **all** questions in the spaces provided.

1. Some electronic sub-systems are listed below:

OR gate *light sensor* *latch* *bulb*


(a) Which **one** of these is an output sub-system? [1]


(b) Which **one** of these is an input sub-system? [1]

(c) Which **one** of these keeps the output on until reset? [1]

2. Here is a list of electronic components:

transistor *LED* *variable resistor* *LDR*

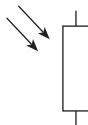(a) Which component has this symbol?  [1]
Answer

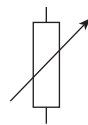(b) Which component has this symbol?  [1]
Answer

(c) Which component from the list would you use to sense changes in light level?
Answer [1]

3. Four types of mechanical switches are listed below.

tilt *micro* *toggle* *magnetic*

Choose the most appropriate switch from the list for the following jobs.

(a) To be used with a magnet as part of a bicycle speedometer.
Answer

(b) To warn drivers of off-road vehicles that the vehicle may be in danger of toppling over.
Answer

[2]

Turn over.


4. Put the three currents in order of size, starting with the **smallest**, and ending with the **biggest**.

- 1 milliamp (mA)*
- 1 amp (A)*
- 1 microamp (μ A)*

..... → →

[2]

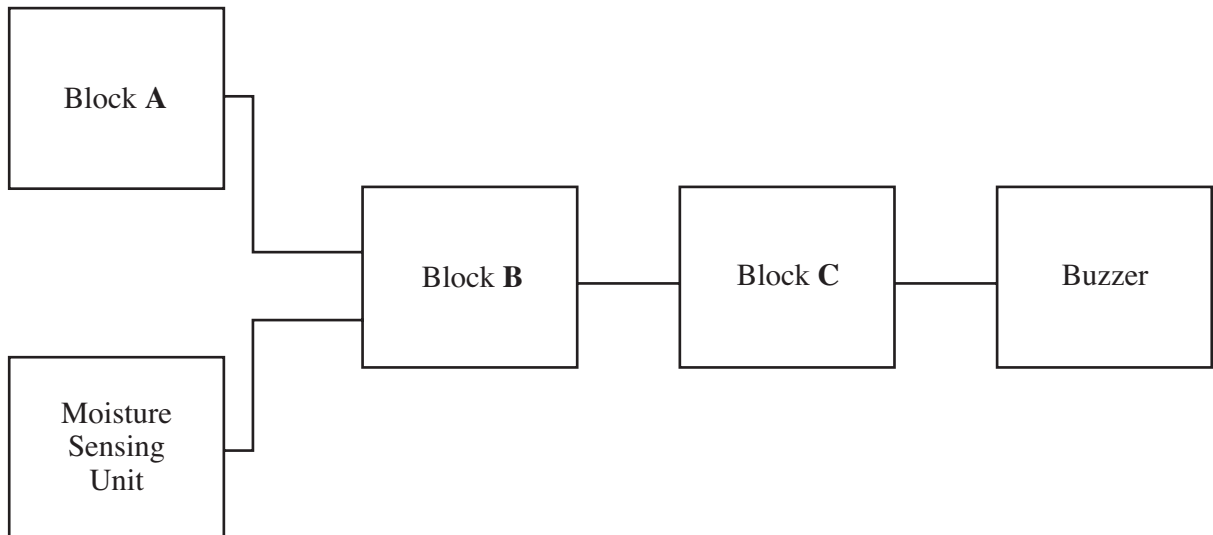5. Here is a system to switch on a lamp if it is too dark or too wet.



You can choose any of the following sub-systems to use for blocks **A**, **B** and **C**:-


- | | |
|--------------------------|---------------------------------------|
| Temperature sensing unit | Time delay |
| OR gate | Transistor switch / transducer driver |
| Pulse unit | Light sensing unit |

Which sub-system is:

- (a) a suitable unit for block **A**?
- (b) a suitable unit for block **B**?
- (c) a suitable unit for block **C**?

[3]

6. Look at the following diagram.

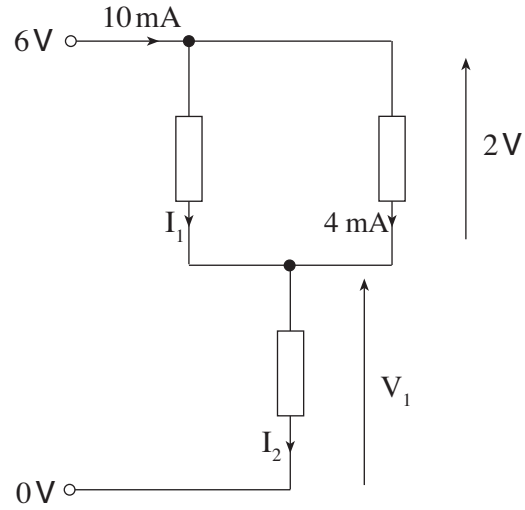


Write down the values of the following:

- (a) I_1 mA
 (b) I_2 mA
 (c) V_1 V

[3]

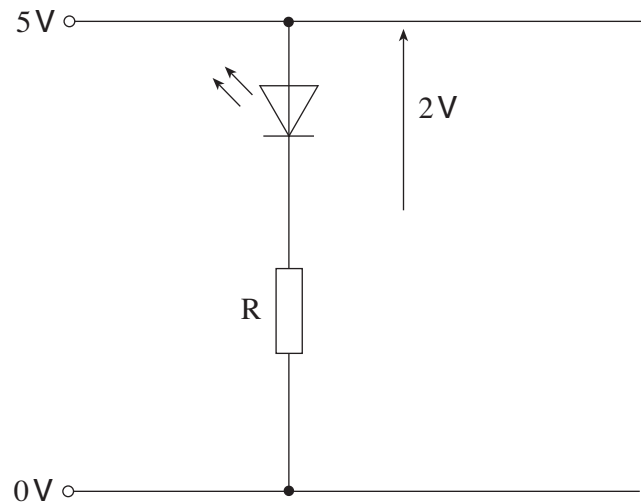7. The LED in the following circuit needs a current of **10 mA** and forward voltage drop of **2 V** across it to make it light correctly.



- (a) How much power is used in the LED?

Choose the correct answer from the following list:

50 mW 20 mW 50 W 20 W

..... [1]

- (b) The LED is on.

- (i) What is the current through resistor R ?

.....

- (ii) What is the voltage across resistor R ?

.....

[2]

- (c) Use the formula in the information sheet on page 2 to calculate a suitable resistance for resistor R. [2]

.....


.....

- (d) Choose a suitable preferred value for resistor R from the E12 series in the information sheet on page 2. [1]

.....


8. The resistor colour code is given in the information sheet on page 2.

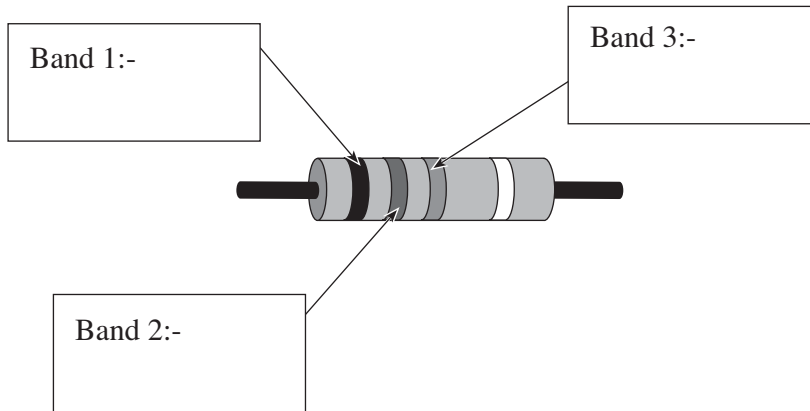- (a) Use the information to work out the colour code for a **10 kΩ** resistor. Write the colours in the correct spaces on the diagram below.



[3]

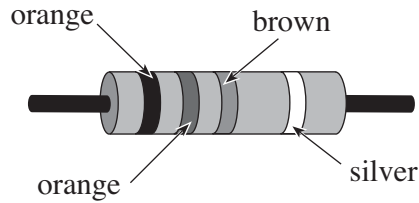
- (b) Use the colour code to work out the resistance of the following resistor .



Resistance **in ohms** =

[2]

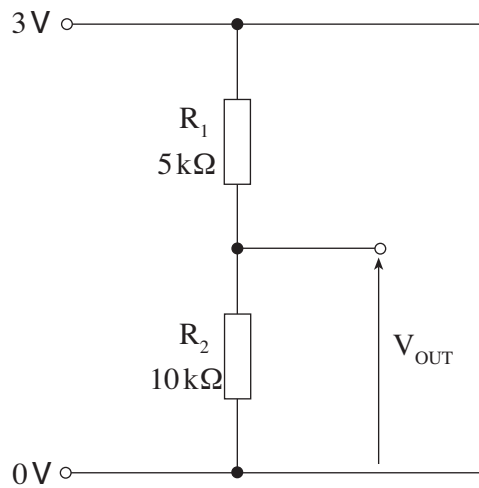- (c) The **10 kΩ** resistor is used with a **5 kΩ** resistor to make a voltage divider:



- (i) What is the combined resistance of R_1 and R_2 ? [1]


.....

- (ii) Use the equation given in the information sheet on page 2 to calculate the value of voltage V_{OUT} . [2]

.....

.....

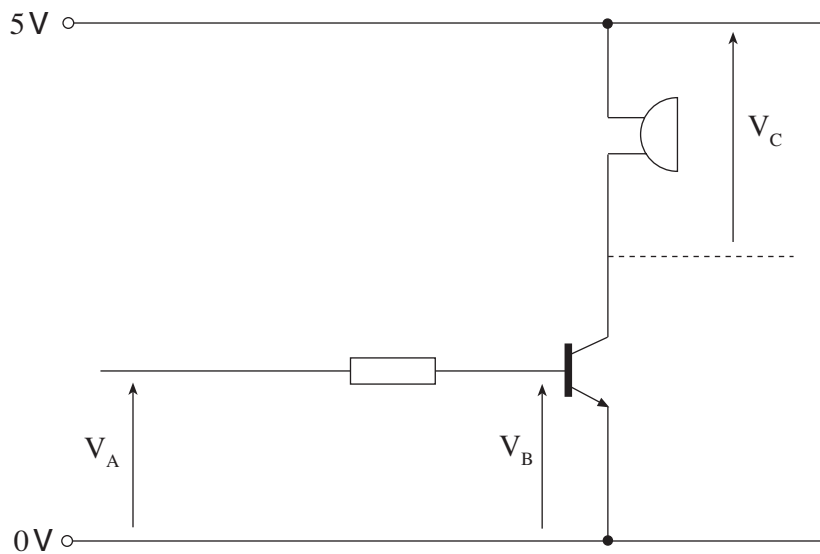9. The following circuit diagram shows part of a system used to switch on a buzzer.



The transistor is **just** saturated when the input voltage V_A is 2.5 V.

The input voltage V_A is set to

- (i) 0.5 V,
- (ii) 3.5 V.


Complete the following table to show:

- the voltages V_B and V_C ;
- whether the buzzer will be **On** or **Off**.

	V_A	V_B	V_C	Buzzer On/Off?
(i)	0.5 V			
(ii)	3.5 V			

[5]

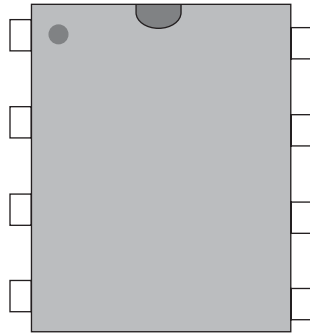
10. (a) The diagram shows a comparator IC seen from above.




- (i) Label pin 1 with the number 1.
- (ii) Label pin 7 with the number 7.

[2]

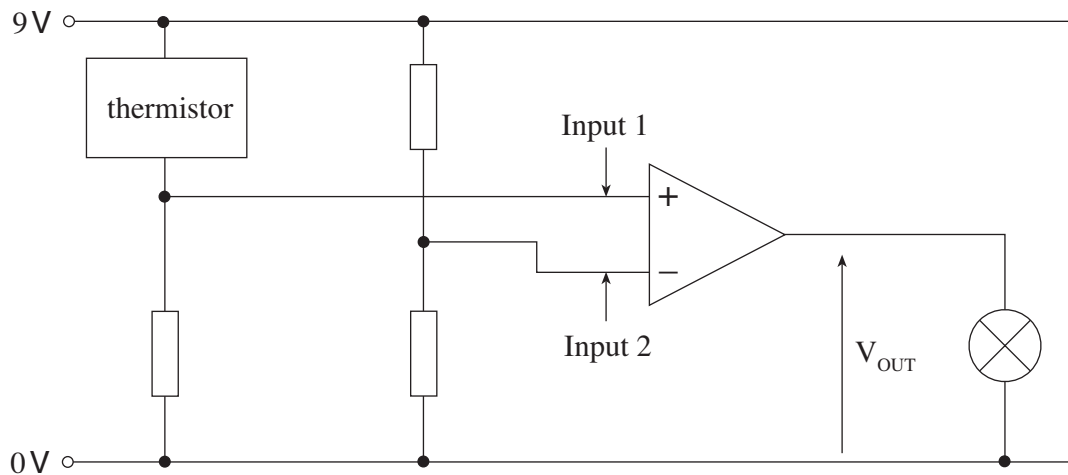(b) A warning system is used in a shop to warn the assistant if the temperature in the freezer becomes too warm. The circuit diagram for this is shown below.



 - (i) The circuit makes use of a thermistor. Draw the circuit symbol for a thermistor in the space below. [1]



- (ii) The output V_{OUT} of the comparator saturates at +6V and 0V.

Complete the table for the given values of the input voltages.

Input 1 (V)	Input 2 (V)	Output V_{OUT} (V)
3.2	4.0	
4.5	2.1	

[2]