

Candidate Name	Centre Number	Candidate Number

WELSH JOINT EDUCATION COMMITTEE  
General Certificate of Secondary Education



CYD-BWYLLGOR ADDYSG CYMRU  
Tystysgrif Gyffredinol Addysg Uwchradd

294/01

**ELECTRONICS**

**MODULE TEST E2**

**FOUNDATION TIER**

A.M. THURSDAY, 7 June 2007

(45 minutes)

**For Examiner's use only**

<b>Total Mark</b>	
-----------------------	--

**ADDITIONAL MATERIALS**

In addition to this examination paper you may need a calculator.

**INSTRUCTIONS TO CANDIDATES**

Write your name, centre number and candidate number in the spaces at the top of this page.

Answer **all** the questions in the spaces provided in this booklet.

**INFORMATION FOR CANDIDATES**

The number of marks is given in brackets at the end of each question or part-question.

No certificate will be awarded to a candidate detected in any unfair practice during the examination.

Answer **all** questions.

1. There are three types of electronic subsystem, known as *Input*, *Process* and *Output*.

Here are three subsystems:


Subsystem	Type ( <i>Input, Process, or Output</i> )
Lamp unit	
Light Sensing Unit	
Comparator	

For each one, decide which type it is.

Add the word *Input*, *Process* or *Output* to show what you have decided.

[3]

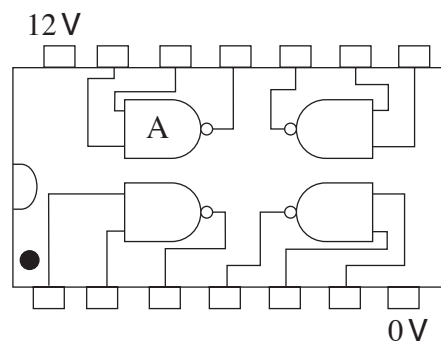2. The diagram shows the pinout for an IC (integrated circuit.)




- (a) How many logic gates are there on this IC? .....
- (b) How many inputs does each gate have? .....
- (c) Label pin 1 of the IC.
- (d) What is the number of the pin connected to the output of gate A? .....
- (e) Choose the type of logic gate found on this IC from the following list:

AND      OR      NOT      NAND      NOR

Answer .....

[5]

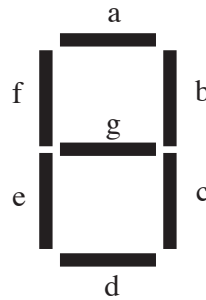
3. (a) The diagram shows the arrangement of the LEDs in a seven-segment display.



Complete the following table to show the number displayed when different segments are lit. [3]

SEGMENTS							NUMBER DISPLAYED
a	b	c	d	e	f	g	
1					0		<b>7</b>
							<b>9</b>
1	1	1	1	0	0	1	

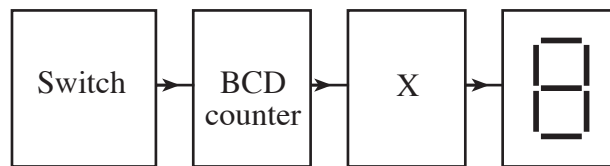- (b) Here is the block diagram for a counting system. The system shows how many times the switch has been pressed.



Subsystem X converts the output of the counter to light the correct LEDs in the seven-segment display.

Choose the best subsystem to do this from the following list: [1]


*monostable          decoder / driver          AND gate          transducer driver*

Answer .....

4. (a) Here is a list of logic gates:

AND OR NOT NAND NOR

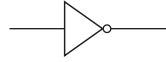(i) Which of the gates has the following symbol?



Answer .....

[1]

(ii) Which of the gates has the following truth table?

A	B	Q
0	0	0
0	1	0
1	0	0
1	1	1

Answer .....

[1]


(iii) Which of the gates has the opposite effect to (inverts) an OR gate?

Answer .....

[1]


(b) Complete the truth table for the following logic system:

[2]

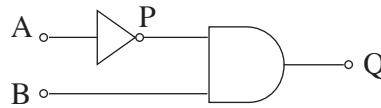


A	B	P	Q
0	0		
0	1		
1	0		
1	1		

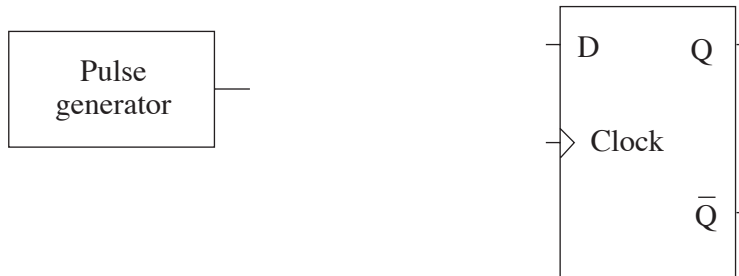
5. The diagram shows a pulse generator and a D-type flip-flop.



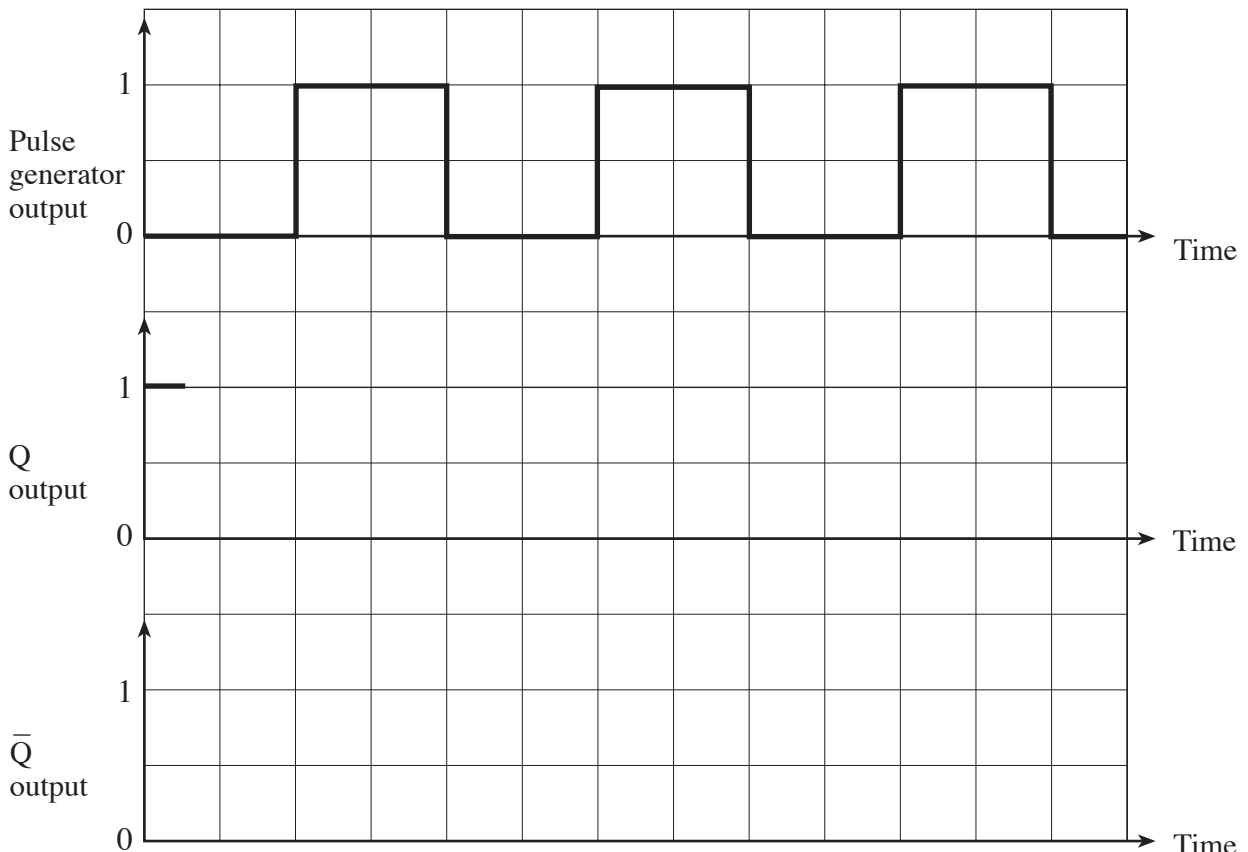- (a) Draw the two connections needed to make the D-type perform a divide-by-two action. [2]
- (b) The frequency of the signal at the Q output is 100 Hz.
  - (i) What is the frequency of the  $\bar{Q}$  output? .....
  - (ii) What is the frequency of the pulse generator output? ..... [2]
- (c) The D-type flip-flop is rising-edge triggered.
  - (i) Label a rising-edge on the pulse generator output graph. [1]
  - (ii) The Q output is initially at logic 1. Complete the graph to show the signal at the Q output. [3]
  - (iii) Draw the graph to show the signal at the  $\bar{Q}$  output. [1]



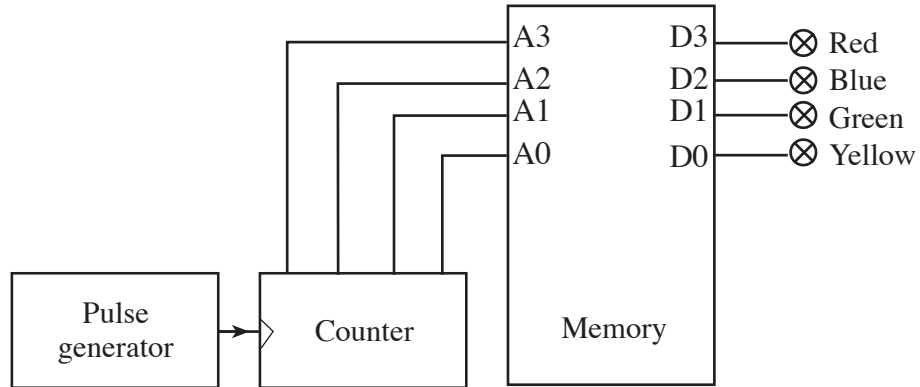
6. The block diagram shows a system which generates a sequence of lights. The sequence repeats over and over again. It uses a memory IC to store the sequence. The pulse generator and counter select each memory location in turn.



The memory stores the following data:

Address				Data			
A3	A2	A1	A0	D3	D2	D1	D0
0	0	0	0	0	0	0	0
0	0	0	1	1	0	0	0
0	0	1	0	1	1	0	0
0	0	1	1	1	1	1	0
0	1	0	0	1	1	1	1
0	1	0	1	Reset			

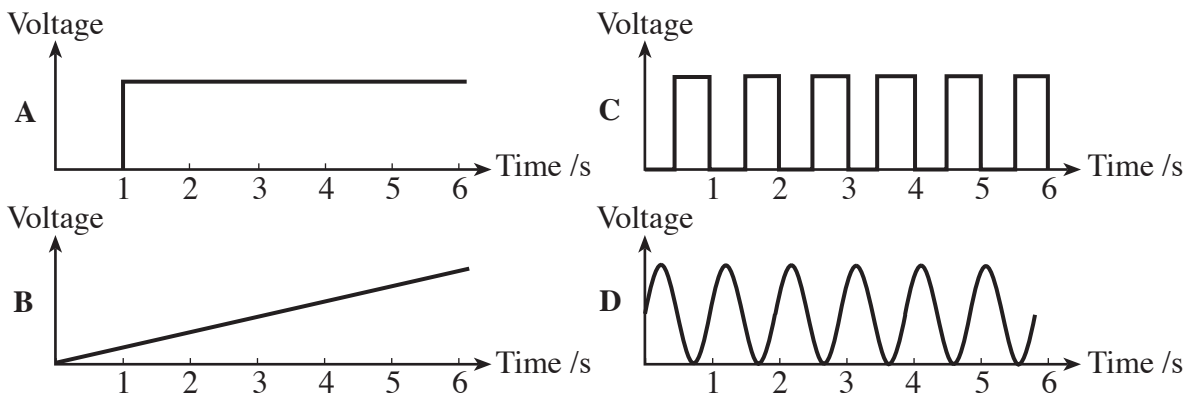- (a) The pulse generator has a frequency of 1Hz. Which of the following shows the output signal from the pulse generator?




Answer .....

[1]

- (b) Complete the following table by adding either *Off* or *On* to show the sequence of lights produced by the system. [4]

Red	Blue	Green	Yellow
<i>Off</i>			

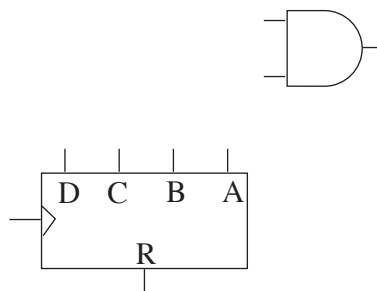- (c) The counter resets when the reset pin receives a logic 1 signal. Output A is the least significant bit of the counter output. Complete the circuit diagram to make the counter reset when the output reaches 0101. [3]



7. A logic system has two input sensors, **A** and **B**, and three outputs **P**, **Q** and **R**. The truth table is shown below.

<b>B</b>	<b>A</b>	<b>P</b>	<b>Q</b>	<b>R</b>
0	0	1	1	1
0	1	1	1	1
1	0	1	1	0
1	1	1	0	0

- (a) Which output can be produced by connecting one of the inputs to a NOT gate? [1]
- .....
- (b) Which output does not need a logic gate to produce it? [1]
- .....
- (c) Look at the remaining output. It is produced by connecting inputs **A** and **B** to a logic gate. What kind of logic gate is needed? [1]
- .....
- (d) Complete the diagram to show how this logic system can be made. [3]

