

Candidate Name	Centre Number	Candidate Number

WELSH JOINT EDUCATION COMMITTEE  
General Certificate of Secondary Education



CYD-BWYLLGOR ADDYSG CYMRU  
Tystysgrif Gyffredinol Addysg Uwchradd

294/02

**ELECTRONICS**  
**MODULE TEST E2**  
**HIGHER TIER**

P.M. FRIDAY, 12 January 2007

(45 minutes)

**For Examiner's use only**

<b>Total Mark</b>	
-----------------------	--

**ADDITIONAL MATERIALS**

In addition to this examination paper you may need a calculator.

**INSTRUCTIONS TO CANDIDATES**

Write your name, centre number and candidate number in the spaces at the top of this page.

Answer **all** the questions in the spaces provided in this booklet.


**INFORMATION FOR CANDIDATES**

The number of marks is given in brackets at the end of each question or part-question.

No certificate will be awarded to a candidate detected in any unfair practice during the examination.

Answer **all** questions.

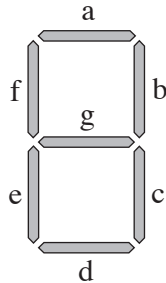1. The diagram shows the arrangement of the LEDs in a seven-segment display.



Complete the following table, which shows the number/letter displayed when different segments are lit.

Segment							Letter/Number displayed
a	b	c	d	e	f	g	
1	0						<b>F</b>
							<b>3</b>
0	1	1	0	1	1	1	

[3]


2. The diagram shows a pulse generator and a D-type flip-flop.



- (a) (i) The D-type must be connected so that it performs a *divide-by-two* action on pulses from the pulse generator.  
Draw the two connections needed to do this.
- (ii) The frequency of the signal at the Q output is 200 Hz.  
What is the frequency of the pulse generator? ..... [2]

(b) A D-type flip-flop can also be used for **data transfer**.

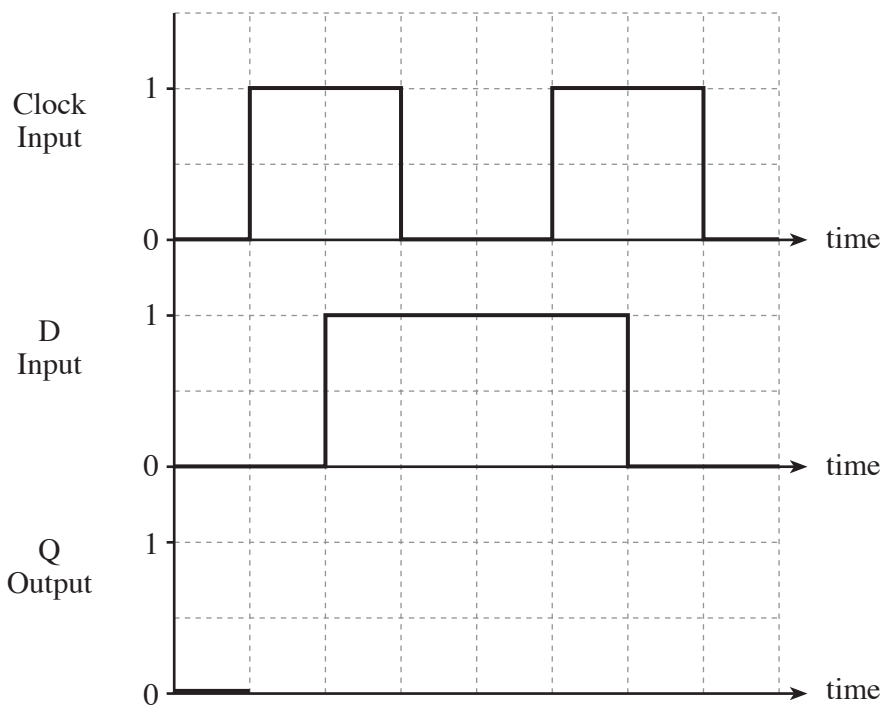- (i) The D-type is *rising-edge* triggered. Label a rising-edge on the *Clock Input* graph.




- (ii) The signal shown on the graph is applied to the D input.

Complete the graph to show the waveform obtained at the Q output.

[3]

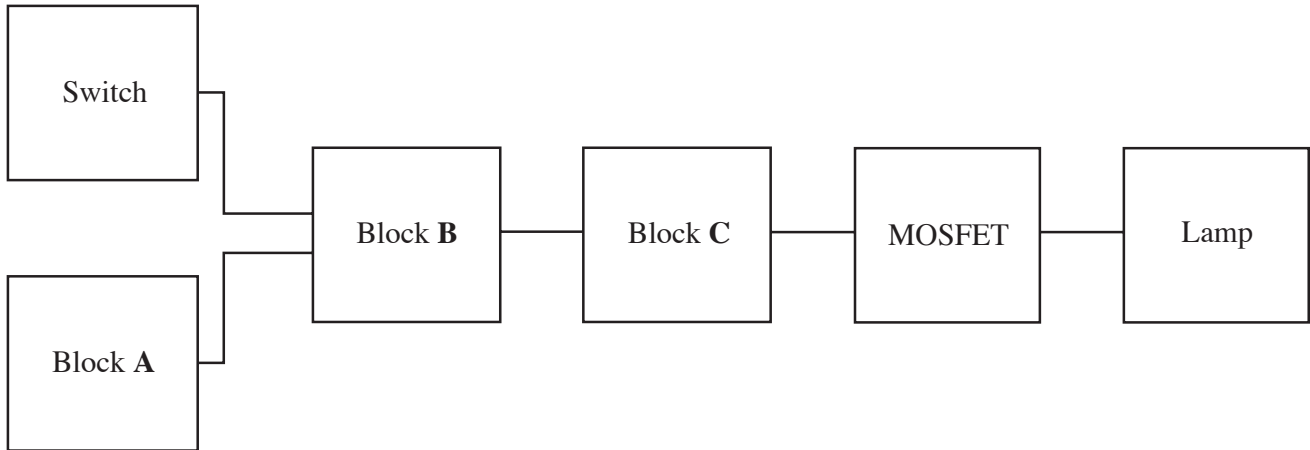3. (a) Here is a system that controls a lamp on a stairway. The lamp comes on when the switch is pressed **but only** if it is dark. The lamp switches off automatically after 1 minute.



You can choose any of the following sub-systems to use for blocks **A**, **B** and **C**:-

- Temperature sensing unit
- Light sensing unit
- OR gate
- Delay unit
- Pulse unit
- AND gate

Which sub-system is

- (i) a suitable unit for block **A**? .....
- (ii) a suitable unit for block **B**? .....
- (iii) a suitable unit for block **C**? ..... [3]

- (b) Complete the circuit diagram to show how the MOSFET is connected to Block **C** and the lamp.

9V ○—————

Ouput from  
Block C ○——



0V ○—————

(c) The lighting control system is an example of electronics being used to conserve energy.

(i) Describe **another** example of electronics being used to conserve energy.

.....  
.....

(ii) Describe **one** benefit of electronics to a hospital patient.

.....  
.....

[2]

4. A logic system has two input sensors A and B, and three outputs P, Q and R. The truth table showing how the input sensors control the outputs is shown below.

B	A	P	Q	R
0	0	0	1	1
0	1	0	0	1
1	0	0	0	0
1	1	1	0	0

- (a) (i) Look at the P output. Which type of logic gate will provide this?

Logic gate is .....

- (ii) Look at the Q output. Which type of logic gate will provide this?

Logic gate is .....

- (iii) Look at the R output. It is the inverse of one of the inputs. Write down an expression to describe this output.

R = .....

[3]

- (b) You have a selection of AND, OR, NOT, NOR and NAND gates available. Draw a labelled diagram to show how the logic system can be made.

A ○—

—○ P

—○ Q

B ○—

—○ R


[3]

- (c) A memory IC could be used to give the same output as the logic system. Give one advantage, other than cost, of designing an electronic system using a memory IC instead of logic gates. [1]

.....

.....

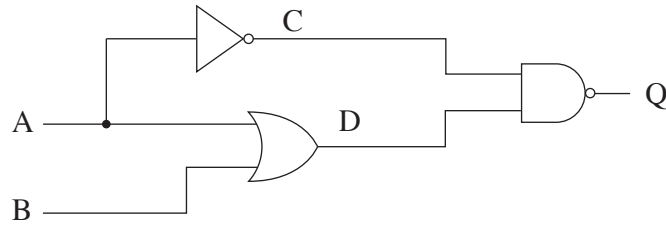5. (a) Complete the truth table for the following logic system.




B	A	C	D	Q
0	0			
0	1			
1	0			
1	1			

[3]

- (b) Redraw the system to produce the same output, but using only NAND gates.


[2]

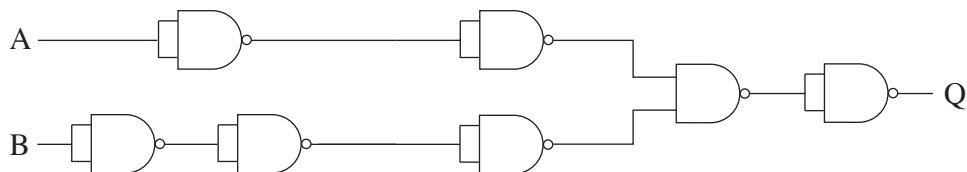- (c) Here is another system of NAND gates. Simplify it by crossing out any redundant gates.






[2]

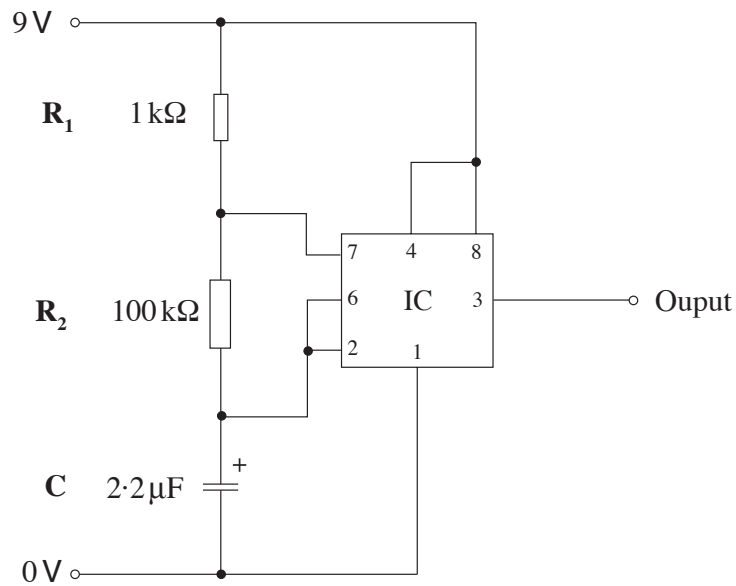6. Here is the diagram for an astable circuit based on a 555 timer IC.



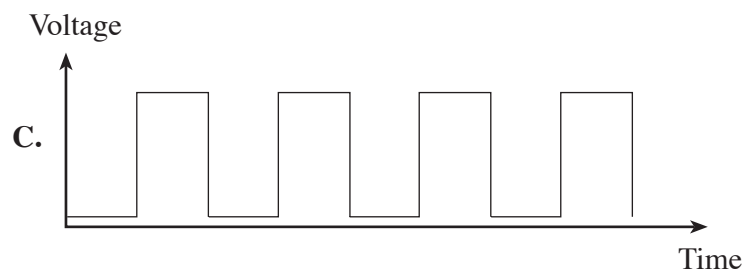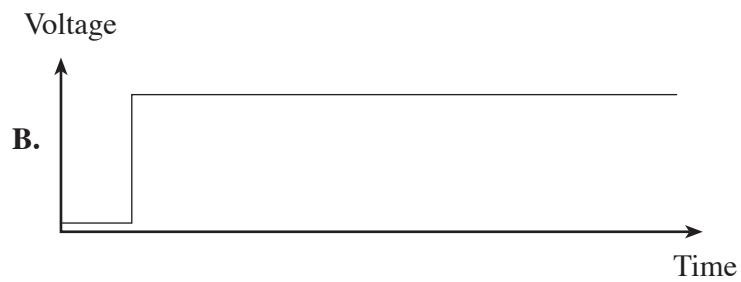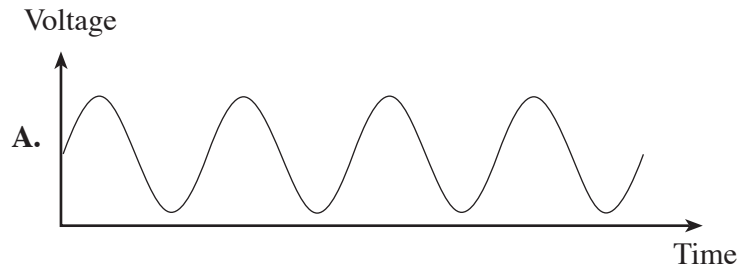(a) Which of the following is the output waveform produced by an astable circuit?



Answer .....

[1]



- (b) The **approximate** value of frequency  $f$  of the pulse generator is given by the formula.

$$f = \frac{0.7}{R_2 C} \quad (\text{where } f \text{ is in Hz, } R_2 \text{ is in } M\Omega \text{ and } C \text{ is in } \mu\text{F}).$$

Use this formula to calculate the frequency of the pulse generator.

.....


.....

.....

[3]


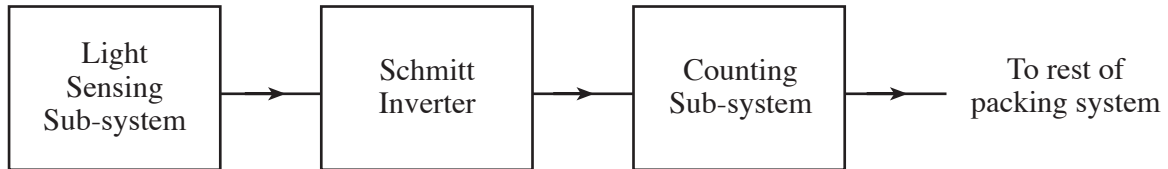
7. A company packs DVDs into boxes, five to a box.

Part of the packing system is shown in the following block diagram.



- The counting sub-system contains a 3-bit binary counter and an AND gate
- The system must reset when the **fifth** DVD passes the light sensor
- Taking the reset pin to logic 1 resets the counter
- Bit A of the counter is the least significant bit
- The counter is initially reset

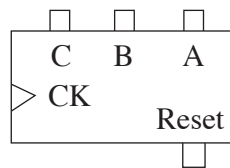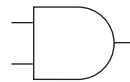(a) Complete the diagram below to show how the AND gate is connected to the counter to allow it to reset correctly.



[3]

- (b) The Schmitt inverter *cleans up* the signal produced by the light sensor. Here is part of a data sheet for a Schmitt Inverter:


When connected to 5 V supply:

- Logic 0 = 0 V
- Logic 1 = 5 V
- The output changes from logic 1 to logic 0 when a **rising** input voltage reaches 3 V
- The output changes from logic 0 to logic 1 when a **falling** input voltage reaches 1 V

The signal produced by the light sensor is shown in **Graph 1**.

Complete **Graph 2** to show the signal obtained at the output of the Schmitt Inverter.

**Graph 1**

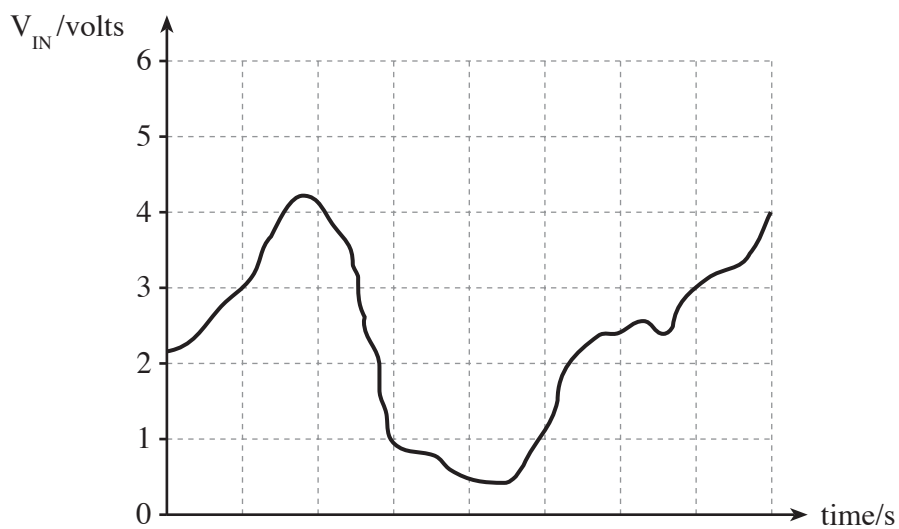

**Graph 2**

