

Candidate Name	Centre Number	Candidate Number
		0



GCSE

293/02

ELECTRONICS

MODULE TEST E1

HIGHER TIER

P.M. FRIDAY, 23 May 2008

45 minutes

For Examiner's use only	
Total Mark	

ADDITIONAL MATERIALS

In addition to this examination paper you may need a calculator.

INSTRUCTIONS TO CANDIDATES

Write your name, centre number and candidate number in the spaces at the top of this page.

Answer **all** the questions in the spaces provided in this booklet.

INFORMATION FOR CANDIDATES

The number of marks is given in brackets at the end of each question or part-question.

INFORMATION SHEET

This information may be of use in answering the questions.

1. Resistor Colour Codes

BLACK	0	GREEN	5
BROWN	1	BLUE	6
RED	2	VIOLET	7
ORANGE	3	GREY	8
YELLOW	4	WHITE	9

The fourth band colour gives the tolerance as follows:
GOLD $\pm 5\%$
SILVER $\pm 10\%$

2. Preferred Values for Resistors


E 12 SERIES OF PREFERRED VALUES
 10; 12; 15; 18; 22; 27; 33; 39; 47; 56; 68; 82 and multiples thereafter

3. **Resistance** = $\frac{\text{voltage}}{\text{current}}$; $R = \frac{V}{I}$.

4. **Effective resistance**, R , of two resistors R_1 and R_2 in series is given by $R = R_1 + R_2$.

5. **Effective resistance**, R , of two resistors R_1 and R_2 in parallel is given by $R = \frac{R_1 R_2}{R_1 + R_2}$.

6. Voltage Divider

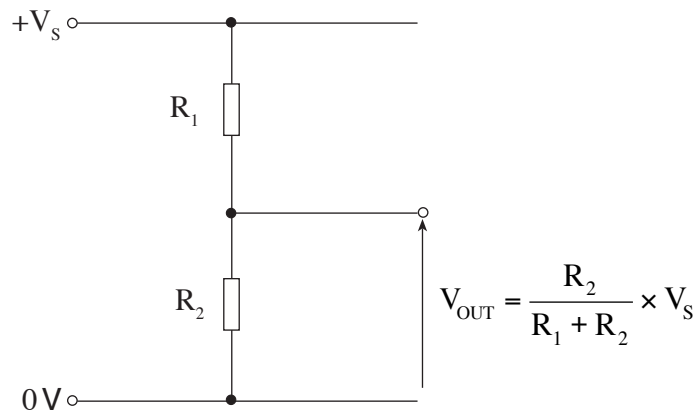

7. **Power** = voltage \times current; $P = VI = I^2 R = \frac{V^2}{R}$.

8. **LED** The forward voltage drop across a LED is 2V.


9. Transistors

(i) **Current gain** = $\frac{\text{Collector current}}{\text{Base current}}$; $h_{\text{FE}} = \frac{I_C}{I_B}$.

(ii) The forward voltage drop across the base emitter junction is 0.7V.

Answer **all** questions in the spaces provided.

1. The diagram shows a 4.7kΩ resistor.

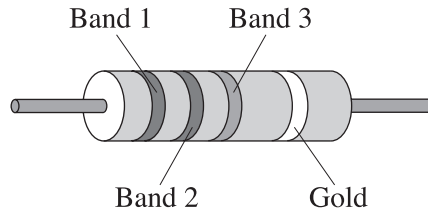


(a) Change 4.7kΩ into ohms. [1]

.....

(b) Use the resistor colour code to select the colours of: [3]

Band 1 Band 2 Band 3

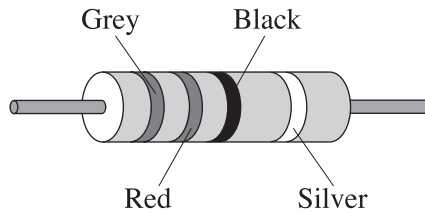(c) A **different** resistor is shown below




(i) What is its resistance? Ω [2]

(ii) Use the tolerance band to calculate the maximum value of resistance for this resistor. [1]

.....

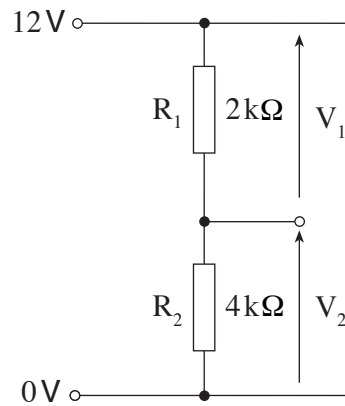2. The circuit diagram shows a voltage divider.



(a) What is the combined resistance of R_1 and R_2 ? [1]

(b) Calculate voltage V_2 . [2]


Hint: The equation is given on page 2.

.....

(c) A second $4\text{k}\Omega$ resistor is connected in parallel with R_2 .
 What is the combined resistance of the two $4\text{k}\Omega$ resistors? [1]

.....

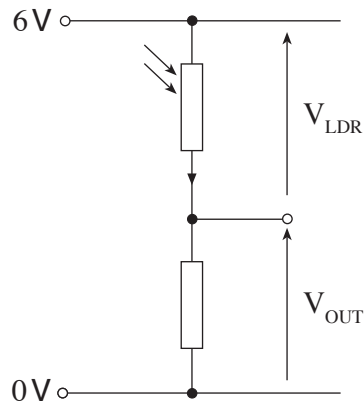3. Here is the circuit diagram for a light-sensing unit.




A bright light is now shone on the LDR.
As a result, what happens to:

- (a) the resistance of the LDR? [1]


- (b) the voltage V_{LDR} across the LDR? [1]

- (c) the output voltage V_{OUT} ? [1]

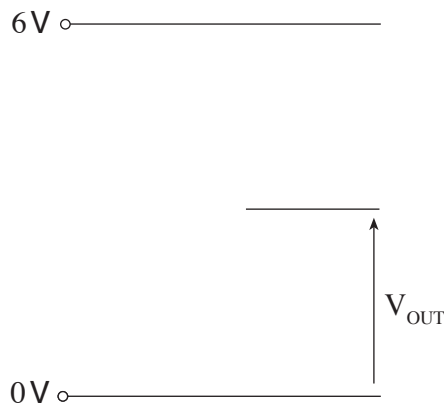- (d) Complete the circuit diagram for a temperature sensing unit that has an output voltage which decreases when the temperature rises. [3]



4. The diagram shows part of a circuit.

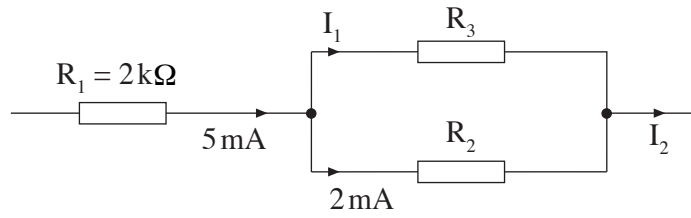


- (a) Calculate current I_1 . [1]

- (b) Calculate current I_2 . [1]

- (c) Calculate the voltage across resistor R_1 . [2]
Hint: The equation is given on page 2.

BLANK PAGE

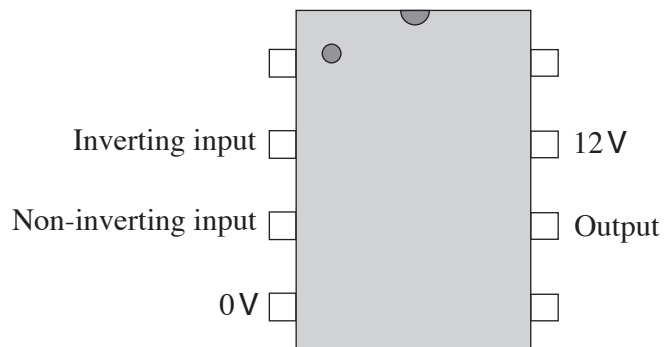
5. The diagram shows the pinout for a comparator IC.



(a) The comparator output saturates at 12V and 0V.

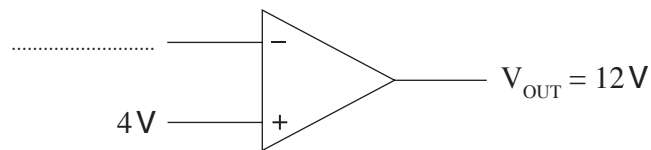
(i) The non-inverting input is set to 4V.

Write down a voltage at the inverting input that will make the output voltage 12V. [1]



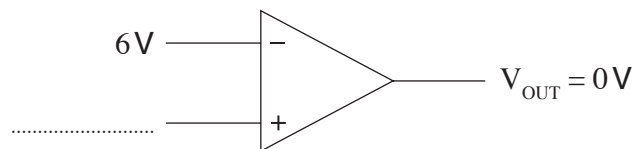
(ii) The inverting input is set to 6V.

Write down a voltage at the non-inverting input that will make the output voltage 0V. [1]



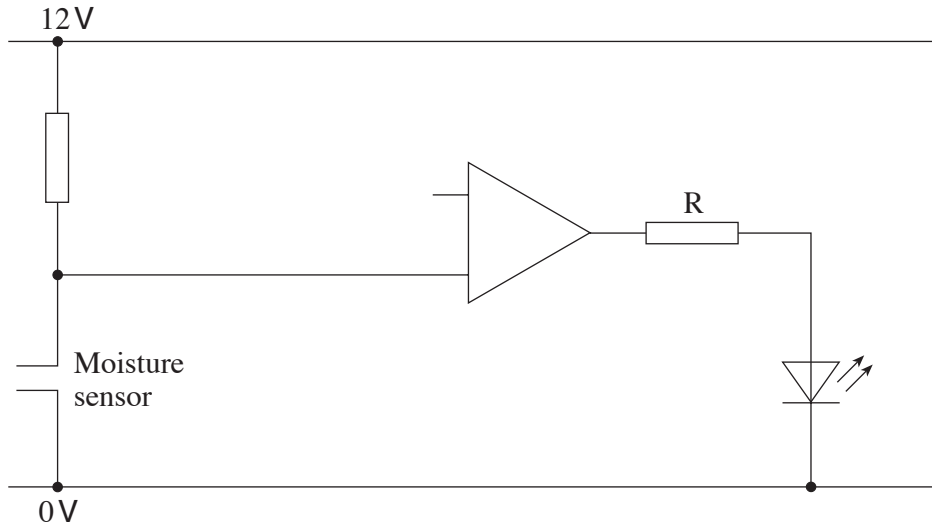
- (b) A moisture sensor is placed in a plant pot. It is connected to the comparator, which lights an LED when the soil in the plant pot is too dry.

Part of the circuit diagram is shown below.



- (i) Add component(s), connected to provide a variable voltage at the other input of the comparator. [1]
- (ii) The LED should light when the moisture sensor is **too dry**, giving it a high resistance. Add '+' and '-' labels to the comparator to identify the non-inverting and inverting inputs. [1]
- (c) The LED in the moisture sensor is lit, and has a 2V voltage drop across it. The current must be limited to a maximum of 20 mA.
- (i) What is the voltage drop across the resistor R? [1]
- (ii) What is the maximum current through resistor? [1]
- (iii) Calculate the resistance of resistor R. [1]
-
- (iv) Use the list of preferred values on page 2. Select the preferred value needed to limit the current to 20 mA. [1]
- (d) What is the advantage of using a comparator rather than a transistor switch for the moisture detector? [1]
-
-
-

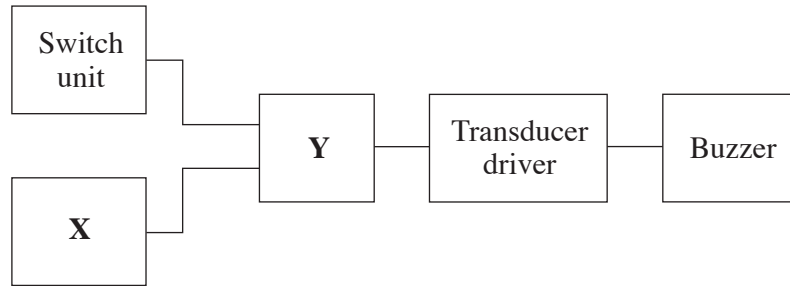
6. Here is the block diagram for a burglar alarm.



The alarm is triggered when a burglar stands on a pressure pad (the switch unit.).
The buzzer then beeps on and off repeatedly.

- (a) Subsystem X makes the buzzer beep on and off repeatedly.
What is the name for this subsystem? [1]
- (b) Subsystem Y combines the signals from subsystem X and the switch unit so that the buzzer pulses only when the burglar stands on the pressure pad.
What is the name for this subsystem? [1]
- (c) The design is faulty because the buzzer stops beeping as soon as the burglar steps off the pressure pad.
 - (i) What additional subsystem is needed to make sure that the buzzer continues to beep on and off repeatedly even after the burglar steps off the pressure pad? [1]
.....
 - (ii) Redraw the block diagram including this subsystem in its correct position. [1]

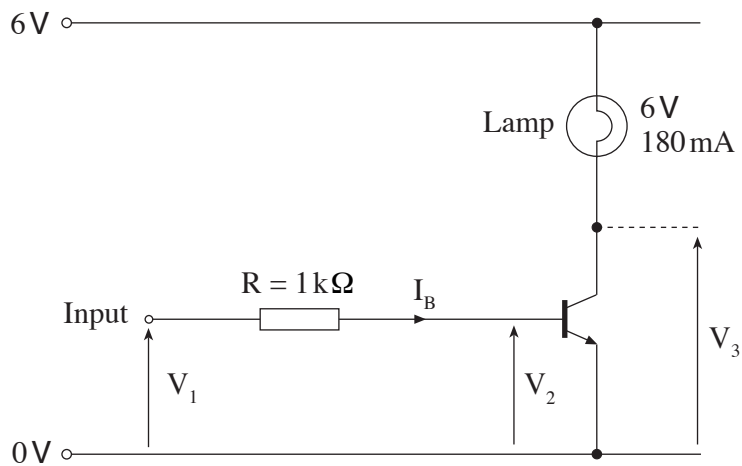7. The circuit diagram shows a transistor switch used as a transducer driver.



- (a) The bulb is rated at 6V 180mA.
Calculate the power dissipated in the bulb when it is switched on fully. [1]

- (b) A transistor with a current gain (h_{FE}) of 90 is used in this circuit.
The input voltage V_1 is increased until the transistor is **just saturated**.

Calculate:

- (i) the base current I_B ; [2]

.....

.....

- (ii) the voltage across the base resistor; [2]

.....

.....

- (iii) the new input voltage V_1 . [1]

.....

.....