

Candidate Name	Centre Number	Candidate Number
		0



GCSE

294/02

ELECTRONICS

MODULE TEST E2

HIGHER TIER

P.M. FRIDAY, 6 June 2008

45 minutes

For Examiner's use only

Total Mark	
-----------------------	--

ADDITIONAL MATERIALS

In addition to this examination paper you may need a calculator.

INSTRUCTIONS TO CANDIDATES

Write your name, centre number and candidate number in the spaces at the top of this page.


Answer **all** the questions in the spaces provided in this booklet.

INFORMATION FOR CANDIDATES

The number of marks is given in brackets at the end of each question or part-question.

Answer **all** questions

 1. The diagram shows the arrangement of the LEDs in a seven-segment display.



Complete the following table.

Segments							Number Displayed
a	b	c	d	e	f	g	
1	1	1					7
1	1	1	1	0	0	1	

[2]

2. (a) Complete the truth tables for the following logic gates:

- (i) a **NOT** gate

[1]


Input	Output
0	
1	

- (ii) an **AND** gate

[1]


Inputs		Output
0	0	
0	1	
1	0	
1	1	

 (b) Complete the following truth table for this system. [2]




Input A	Input B	X	Q
0	0		
0	1		
1	0		
1	1		

 (c) (i) Complete the diagram to show how a NAND gate can be made to behave as a NOT gate. [1]



(ii) Draw a diagram to show the NAND gate equivalent of an AND gate [1]

 
(iii) Here is a logic system built using only NAND gates.



Cross out all redundant gates

[1]

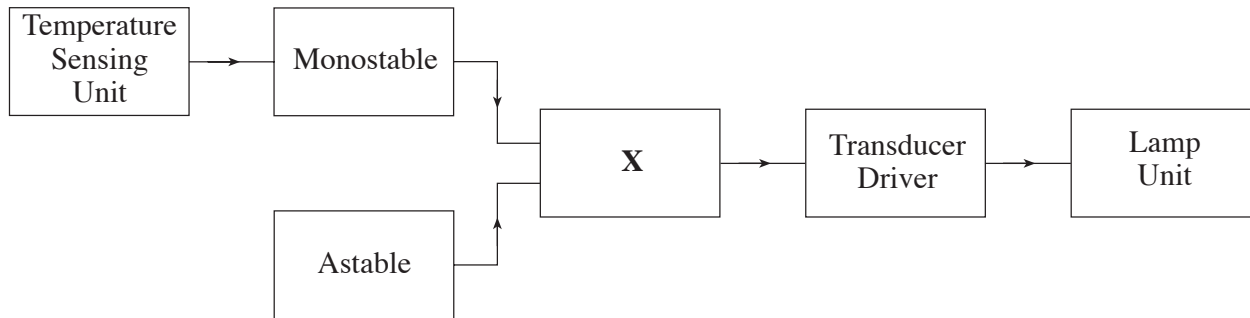3. Here is the block diagram for a freezer alarm.



The lamp does not light when the freezer is cold enough.
 The lamp flashes on and off repeatedly when the freezer is too hot.
 The monostable outputs a logic 1 signal for 30s when the freezer gets too hot.

(a) What type of logic gate is required in block **X**?

[1]

Answer

(b) What is the job of the astable in this system?

Choose one of the following answers:


- A. It makes the Lamp Unit pulse on and off over and over again.
- B. It outputs a steady logic 1 signal when the freezer gets too hot.
- C. It keeps the Lamp Unit switched on for 30s and then switches it off automatically.
- D. It buffers the output of the monostable, providing enough current to light the lamp.

[1]

Answer

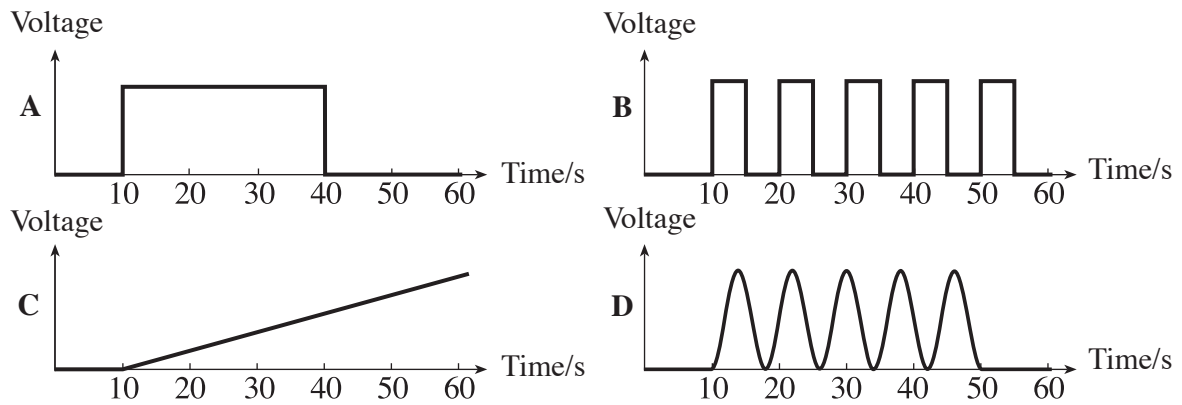(c) The temperature in the freezer rises and triggers the monostable.

Which of the following shows the output signal from the monostable?



[1]

Answer

(d) The monostable time delay can be found from the formula

$$T = 1.1 RC \text{ (where } T \text{ is in seconds, } R \text{ is in } M\Omega \text{ and } C \text{ is in } \mu\text{F)}$$

This can be re-arranged into the form:

$$R = \frac{T}{1.1C}$$

The monostable circuit uses a $470 \mu\text{F}$ capacitor.


Calculate the value of resistance needed to produce a time delay of 30 s.

[2]

.....

.....

 4. The block diagram shows the design of a security light, which turns on automatically when it gets dark.



- (a) The Light Sensing Unit gives out a logic 0 signal in the dark.

- (i) The Schmitt Inverter inverts the signal from the Light Sensing Unit.

Explain what this sentence means.

[1]

.....

- (ii) What is the other use of the Schmitt Inverter in this system?

[1]

.....

- (b) Here is part of a data sheet for a Schmitt Inverter:



When connected to 5 V supply:

- Logic 0 = 0 V
- Logic 1 = 5 V
- The output changes from logic 1 to logic 0 when a **rising** input voltage reaches 3 V
- The output changes from logic 0 to logic 1 when a **falling** input voltage reaches 1 V


The input signal for the Schmitt Inverter is shown below.

Use the axes provided to draw the resulting output signal produced by the Schmitt Inverter.

[4]

  

 - (c) (i) Complete the circuit diagram to show how a transistor switch can be used to interface the Schmitt Inverter to the bulb. [3]



- (ii) A thyristor is often used as an interface device. Why is it **not** suitable in this system? [1]

.....

.....

5. An electronic system has two input sensors **A** and **B**, and three outputs **P**, **Q** and **R**. The truth table showing how the input sensors control the outputs is shown below.

B	A	P	Q	R
0	0	1	1	1
0	1	1	1	0
1	0	0	1	0
1	1	0	0	0

- (a) Which of the following expressions correctly describes the **P** output? [1]

A **NOT A** **B** **NOT B**


Answer

- (b) Which of the following expressions correctly describes the **Q** output? [1]

A AND B **A OR B** **A NAND B** **A NOR B**

Answer

 - (c) Complete the following diagram to show how the **R** output can be obtained using a single logic gate. [1]




- (d) **Another** electronic system uses a memory IC rather than logic gates to control output devices from input sensors.

The memory IC has 4 address pins and 8 data pins.

- (i) How many outputs can be connected to the memory IC? [1]
 (ii) How many memory locations are there on the memory IC? [1]

 6. (a) The D-type flip-flop can be used for data transfer, under the control of the clock. The D-type flip-flop is rising-edge triggered.




The signal shown in the first graph is sent into the D input.

The second graph shows the pulses sent into the clock input.

Use the axes provided to draw the signals at the Q and \bar{Q} outputs.


The Q output is initially at logic 1.

[3]

 


(b) A binary counter can be built from a series of D-type flip-flops, or can be obtained as a dedicated counter IC.

 (i) The following diagram shows a pulse generator and two **rising-edge** triggered D-type flip-flops



Draw on the diagram the connections required to make a 2-bit up-counter, connected to the pulse generator. [3]

 (ii) The graph shows clock pulses applied to the 2-bit up-counter. Use the axes provided to draw the signals which would appear at the outputs of the two flip-flops. [3]
Initially the Q_A output and the Q_B output are both at logic 0.




(c) The next diagram shows a counter IC, used to control a lighting sequence.

The sequence is given in the table.

Pulse number	Lamp State		
	Z	Y	X
0	Off	Off	Off
1	Off	Off	On
2	Off	On	Off
3	Off	On	On
4	On	Off	Off
5	On	Off	On
6	Off	Off	Off
7	Off	Off	On
Sequence continues			

A lamp is switched on when the corresponding counter output is logic 1.

 A partly completed circuit diagram is shown below.



Complete the circuit diagram by adding suitable connections from the counter to the AND gate. [2]