



Rewarding Learning

General Certificate of Secondary Education  
2014

--	--	--	--	--

Candidate Number

--	--	--	--

StudentBounty.com

## Technology and Design

Unit 2:  
Systems and Control

Element 1: Electronic and  
Microelectronic Control Systems

ML

[GTD21]

TUESDAY 3 JUNE, AFTERNOON

### TIME

1 hour, plus your additional time allowance.

### INSTRUCTIONS TO CANDIDATES

Write your Centre Number and Candidate Number in the spaces provided at the top of this page.

Write your answers in the spaces provided in this question paper.

Questions which require drawing or sketching should be completed using an HB pencil. All other questions must be completed in blue or black ink only.

Answer **all** questions.

### INFORMATION FOR CANDIDATES

The total mark for this paper is 80.

Figures in brackets printed down the right-hand side of pages indicate the marks awarded to each question or part question.

**DO NOT WRITE ON THIS PAGE**


## Formulae for GCSE Technology and Design

You should use, where appropriate, the formulae given below when answering questions which include calculations.

1 Potential Difference = current  $\times$  resistance ( $V = I \times R$ )

2 For potential divider
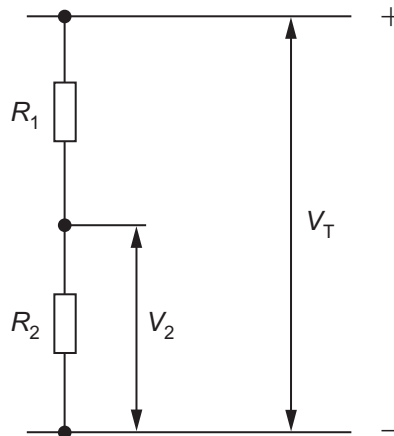
$$V_2 = \frac{R_2}{R_1 + R_2} \times V_T$$



3 Series Resistors  $R_T = R_1 + R_2 + R_3 \text{ etc}$

Parallel Resistors  $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$  or  $R_T = \frac{R_1 \times R_2}{R_1 + R_2}$

4 Time Constant  $T = R \times C$

[Turn over







(d) Potential divider circuits form part of timing circuits as shown in Fig. 5. A timing circuit produces either an astable or monostable output.

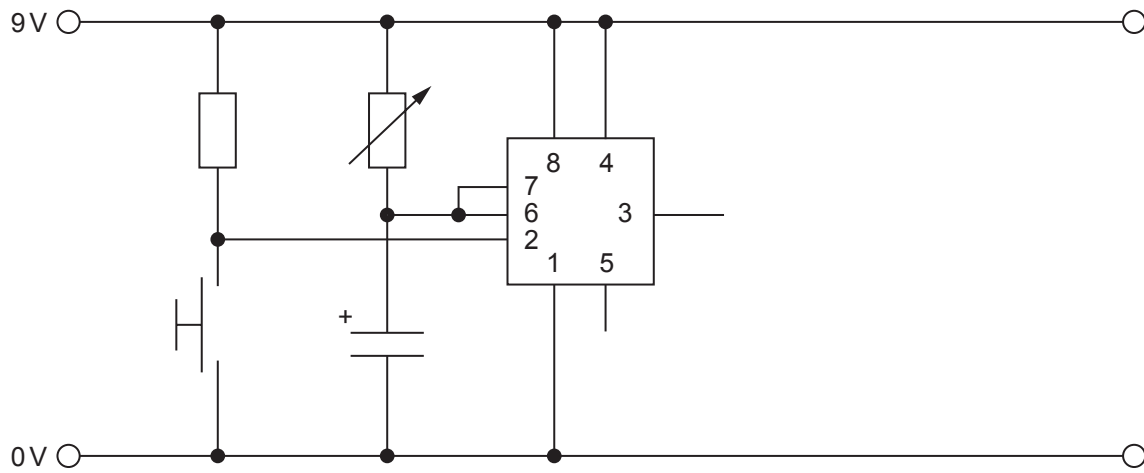


Fig. 5

(i) Explain what an astable output is and what a monostable output is.

Astable output \_\_\_\_\_  
 \_\_\_\_\_  
 \_\_\_\_\_ [2]

Monostable output \_\_\_\_\_  
 \_\_\_\_\_  
 \_\_\_\_\_ [2]

(ii) Does the circuit in Fig. 5 produce a monostable or an astable output?


\_\_\_\_\_ [2]

Examiner Only	
Marks	Remark





- 2 The incomplete circuit diagram in **Fig. 6** shows part of a primary PIC circuit and a secondary circuit. The secondary circuit requires a 12 volt supply and a 12 volt motor.

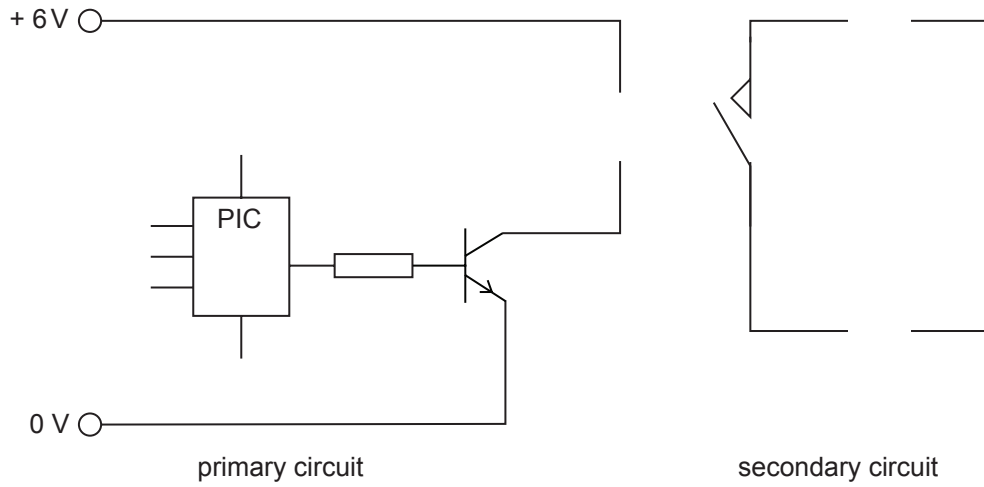

**Fig. 6**

- (a) (i) Complete **Fig. 6** by inserting symbols for a relay coil, a diode, a 12 volt supply and a motor in the correct locations. [4]

- (ii) What is the purpose of the diode in the circuit?

\_\_\_\_\_ [1]

- (iii) Suggest a reason for the use of a secondary circuit.

\_\_\_\_\_ [1]

Examiner Only

Marks Remark

[Turn over



Tables 1 and 2 show the inputs and outputs which are used in the PIC circuit.

**Table 1**

PIC Inputs	Not used	Not used	Start/Play Switch	Display Switch	Loop Contacts Steel Wire
BIT	4	3	2	1	0

**Table 2**

PIC Outputs	Not used	Not used	Not used	Buzzer	Not used	Green LED	Yellow LED	Red LED
BIT	7	6	5	4	3	2	1	0

**Examiner Only**

**Marks Remark**

--	--

[Turn over









---

**THIS IS THE END OF THE QUESTION PAPER**

---







**DO NOT WRITE ON THIS PAGE**

8687.04 ML

**DO NOT WRITE ON THIS PAGE**



**DO NOT WRITE ON THIS PAGE**

8687.04 ML

**DO NOT WRITE ON THIS PAGE**

For Examiner's use only	
Question Number	Marks
1	
2	

<b>Total Marks</b>	
--------------------	--

Examiner Number

Permission to reproduce all copyright material has been applied for.  
In some cases, efforts to contact copyright holders may have been unsuccessful and CCEA will be happy to rectify any omissions of acknowledgement in future if notified.

177996