

- f. The Barkhausen criterion for sustained oscillations is given by _____
- (A) $A\beta = 1$ (B) $|A\beta| \geq 1$
 (C) $|A\beta| < 1$ (D) $\angle A\beta = 180^\circ$
- g. The purpose of phase-log compensation is to _____.
- (A) make the op-amp stable at very high values of gain
 (B) make the op-amp stable at very low values of gain
 (C) reduce the unity gain frequency
 (D) increase the bandwidth
- h. The output time period of a transistorised monostable multivibrator using base resistor R_b and coupling capacitor C_b for the output transistor is given by _____.
- (A) $R_b C_b$ (B) $0.69 R_b C_b$
 (C) $2 R_b C_b$ (D) $1.38 R_b C_b$
- i. If the load resistance of a capacitor filtered full-wave rectifier is reduced, the ripple voltage _____.
- (A) increases (B) decreases
 (C) is not affected (D) has a different frequency
- j. The digital circuit as shown in Fig. 1 works as

 


Fig. 1

- (A) JK flip-flop (B) Clocked R-S flip-flop
 (C) T flip-flop (D) Ring counter

**Answer any FIVE Questions out of EIGHT Questions.
 Each question carries 16 marks.**

- Q.2** a. Sketch a family of Common-Base output characteristics for a transistor and indicate the active, cut-off and saturation regions. Explain the shapes of the curves qualitatively. (8)
- b. A Zener diode as shown in Fig. 2 has $V_Z = 12\text{ V}$, determine the minimum and maximum Zener currents as well as the output voltage, when (i) the Zener diode is considered to be ideal one (ii) the Zener resistance of the Zener diode is $7\ \Omega$. Comment on the results of the output voltage. (8)

 


Fig. 2

- Q.3** a. Draw the Hybrid- Π model for a transistor in Common Emitter configuration at high frequencies and explain the different parameters involved in the circuit. (8)
- b. Draw the small-signal T-equivalent circuit of cascode amplifier and derive an expression for its voltage gain. Determine the voltage gain (A_V) of the cascoded amplifier. If $r'_e = 6.73\Omega$ and $R_C = 1.8k\Omega$. (8)
- Q.4** a. Draw the small signal AC equivalent circuit of source follower at high frequencies and derive an expression for the input admittance and output admittance. What are the applications of source follower? (9)
- b. A class B Push-pull power amplifier is supplied with $V_{CC} = 50$ V. The signal swings the collector voltage down to $V_{min} = 5$ V, and the total dissipation (P_d) in both transistors is 40 W. Find
 (i) the DC power input (ii) the AC power output (iii) conversion efficiency. (7)
- Q.5** a. What type of feedback is used in emitter follower? Draw the circuit of an emitter follower and show that the output voltage follows the input voltage. (6)
- b. The gain of an amplifier is 100 and its bandwidth is 10 kHz. If 10% of negative feedback is applied in the basic amplifier, determine:
 (i) the gain with negative feedback (ii) the bandwidth with negative feedback. (4)
- c. Draw the circuit diagram of Hartley Oscillator using BJT and briefly explain how the oscillations are maintained in this oscillator. (6)
- Q.6** a. Define slew rate and explain its importance in op-amp. (5)
- b. Draw the circuit of an op-amp integrator and derive an expression for its output voltage. Also draw the output waveform for square wave input waveform. (7)
- c. Find the output voltage V_o for the op-amp circuit as shown in Fig. 3. (4)

 


Fig. 3

- Q.7**
- Draw the circuit of an astable multivibrator using op-amp and describe its operation with the help of output waveform. (7)
 - Design a Schmitt Trigger with $V_{UT} = 5 \text{ V}$ and $V_{LT} = -5 \text{ V}$. What is the hysteresis voltage? Assume $V_{sat} = \pm 10 \text{ V}$ (4)
 - Draw the block diagram for IC555 Timer and explain briefly, the components used. (5)
- Q.8**
- Draw the circuit of Transistor Shunt Voltage Regulator and explain its operation. What are its limitations? (7)
 - Draw the circuit of Full-wave Bridge Rectifier and explain its operation with the help of input and output waveforms. What is P.I.V. for this rectifier? (9)
- Q.9**
- State and prove de-Morgan's theorems. (5)
 - Minimize the four-variable logic function $f(A, B, C, D) = \sum m(0,1,2,3,5,7,8,9,11,14)$ using Karnaugh Map. (6)
 - What is a half-adder? Draw the logic diagram of a half-adder and explain its operation with the help of truth table. (5)