

Subject: VLSI DESIGN

Time: 3 Hours

DECEMBER 2010

Max. Marks: 100

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q. 1. must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after half an hour of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

a. MOS transistor with implant channel is called as \_\_\_\_\_.

- (A) bipolar (B) enhancement  
(C) BiCMOS (D) depletion

b. Substrate in nMOS is \_\_\_\_\_.

- (A) N type (B) P type  
(C) polysilicon (D) metal

c. Switching speed of MOS transistor is inversely proportional to \_\_\_\_\_ of the channel.

- (A) square of length (B) length  
(C) square root of length (D) three times of length

d.  $Z_{pd}/Z_{pu}$  for an nMOS inverter driven by another nMOS inverter is \_\_\_\_\_.

- (A) 1/6 (B) 1/16  
(C) 1/8 (D) 1/4

e. latch up in CMOS circuit exists in \_\_\_\_\_.

- (A) P-well only (B) n-well only  
(C) P-well and n-well (D) twin tup

f. Feature size of MOS transistor is \_\_\_\_\_.


- (A)  $2\lambda \times 2\lambda$  (B)  $\lambda \times \lambda$   
(C)  $4\lambda \times 4\lambda$  (D)  $\frac{\lambda}{2} \times \frac{\lambda}{2}$

- g. Standard unit capacitance value  $C_g$  for  $5\ \mu\text{m}$  MOS transistor is \_\_\_\_\_.
- (A) 0.0005 pF (B) 0.04 pF  
(C) 0.01 pF (D) 0.02 pF
- h. Overall delay  $fd$  for nMOS cascaded inverter driven by large capacitive load is \_\_\_\_\_.
- (A)  $3.5\ eN\ \tau$  (B)  $4.5\ eN\ \tau$   
(C)  $1.5\ eN\ \tau$  (D)  $2.5\ eN\ \tau$
- i. Gate Area  $A_g$  is scaled by \_\_\_\_\_.
- (A)  $1/\alpha$  (B)  $1/\beta$   
(C)  $1/\alpha^2$  (D)  $1/\beta^2$
- j. In constant field scaling model \_\_\_\_\_.
- (A)  $\alpha = \frac{1}{\beta}$  (B)  $\beta = 1$   
(C)  $\beta = \alpha$  (D)  $\alpha = 1$

**Answer any FIVE Questions out of EIGHT Questions.  
Each question carries 16 marks.**

- Q.2** a. With neat diagram explain the working of enhancement mode nMOS transistor. (8)  
b. Design the inverter using CMOS logic. Explain its characteristics also. (8)
- Q.3** a. Derive an expression for  $I_{ds}$  in non saturated and saturated region. (10)  
b. What is body effect? Explain briefly how threshold voltage  $V_t$  will be affected by body effect. (6)
- Q.4** a. Obtain pull up to pull down ratio for a nMOS inverter driven through one or more pass transistor. (10)  
b. Explain the working of MOSFET. (6)
- Q.5** a. Write  $\lambda$  based design rules for wires and transistor. (8)  
b. Define sheet resistance and standard capacitance for a feature size transistor. (8)
- Q.6** a. Derive an expression for total delay for N-cascaded inverters driving a large capacitive load. (8)

- b. Two nMOS inverters are cascaded to drive a capacitive load  $C_L = 16C_g$  as shown in Fig.1. Calculate pair delay in terms of  $\tau$ . (8)

 

Inverter 1


$L_{pu1} = 16 \lambda$   
 $W_{pu1} = 2 \lambda$   
 $L_{pd1} = 2 \lambda$   
 $W_{pd1} = 2 \lambda$

Inverter 2

$L_{pu2} = 2 \lambda$   
 $W_{pu2} = 2 \lambda$   
 $L_{pd2} = 2 \lambda$   
 $W_{pd2} = 8 \lambda$

**Fig. 1**

- Q.7** a. Obtain scaling factor for the following:  
 (i) Parasitic capacitance (ii) Channel resistance (iii) Gate delay  
 (iv) Saturation current (8)
- b. Design a two-line to four-line decoder circuit to the mask layout level and determine its boundary box. (8)
- Q.8** a. Design two input NOR gate using CMOS. (6)
- b. Write an example of an inverter showing that the power dissipation decreases at the expense of area. (10)
- Q.9** a. Write a note on design styles in VLSI. (6)
- b. Obtain test-vector for the Fig.2, using sensitised path based testing. (10)

 

**Fig.2**