

## DipIETE – CS (OLD SCHEME)

Code: DC02  
Time: 3 Hours

Subject: FUNDAMENTALS OF ELECTRONICS  
Max. Marks: 100

**DECEMBER 2010**

StudentBounty.com

**NOTE:** There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after half an hour of the commencement of the examination.
- Out of the remaining EIGHT Questions, answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

**Q.1 Choose the correct or the best alternative in the following: (2×10)**

a. Under normal operating voltage, the reverse current in a silicon diode is about

- (A) 10 mA. (B) 1  $\mu$  A.  
(C) 1000 mA. (D) none.

b. In full-wave rectification, if the input frequency is 50 Hz, then the output frequency will be

- (A) 50 Hz (B) NONE  
(C) 100 Hz (D) 75 Hz

c. The emitter of a transistor is doped

- (A) heavily (B) lightly  
(C) moderately (D) None

d. The silicon transistors are more widely used than germanium transistors because

- (A) they have smaller leakage current  
(B) they have smaller depletion layers  
(C) they have smaller heat dissipation  
(D) they have larger current carrying capacity

e. In the initial stage of a transistor amplifier, the zero signal collector current  $I_c$

- (A) 0.5 mA (B) 1.0 mA  
(C) 1.5 mA (D) 2.0 mA

f. A biasing circuit has a stability factor of 40. If due to temperature change,  $I_{co}$  changes by 1  $\mu$ A then  $I_c$  will by

- (A) 20  $\mu$ A (B) 40  $\mu$ A  
(C) 80  $\mu$ A (D) None



- b. Write in brief and give an example about the following:  
 (i) Noise margin  
 (ii) Fan in Fan out  
 (iii) Propagation delay. (8)
- Q. 7** a. With the help of suitable circuit diagram, explain the working of a single stage transistor amplifier. (8)
- b. What is an oscillator? What are the essential parts of an oscillator? (8)
- Q. 8** a. Discuss the steps for IC fabrication. (8)
- b. What is CMRR? With the help of suitable circuit diagram explain working of op – amp as differentiator. (2+6)
- Q. 9** a. Convert following binary numbers into hexadecimal numbers.  
 (i) 1101 0110  
 (ii) 1111 1001 (8)
- b. Show that:  
 (i)  $AB + AC + \overline{B}\overline{C} = AC + \overline{B}\overline{C}$   
 (ii)  $(A + B)(\overline{A} + C) = AC + \overline{A}B$  (8)