

DiplETE – ET (OLD SCHEME)

Code: DE07
Time: 3 Hours

Subject: NETWORK AND TRANSMISSION LINES
Max. Marks: 100

DECEMBER 2010

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after half an hour of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

a. A capacitor has a capacitance of 5 μF, calculate the energy stored in it if a d.c voltage of 100 V is applied across it.

- (A) 2.5×10^{-2} joules (B) 2×10^{-2} joules
(C) 2.5×10^{-3} joules (D) 0.5×10^{-2} joules

b. If the two capacitance C_1 & C_2 are in parallel then what will be the total capacitance:-

- (A) $\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$ (B) $C = C_1 + C_2$
(C) $C = \frac{C_1 + C_2}{C_1 C_2}$ (D) $C = \frac{C_1 C_2}{C_1 + C_2}$

c. What will be the form factor of a sinusoidal voltage wave:-

- (A) 2.22 (B) 1.92
(C) 1.11 (D) 1.10

d. Laplace transform of unit step function is:-

- (A) $\frac{1}{s}$ (B) s
(C) $\frac{1}{s^2}$ (D) $\frac{1}{s^3}$

e. Laplace transform of parabolic function:-

- (A) $\frac{2}{s^2}$ (B) $\frac{2}{s^3}$
(C) $\frac{1}{s^3}$ (D) $\frac{1}{s^2}$

- Q.3** a. Define unit impulse function $\delta(t)$, unit step function $u(t)$ and ramp function (8)
 b. In the Laplace domain, a function is given by- (8)

$$F(S) = M \left[\frac{(S + \alpha) \sin \theta}{(S + \alpha)^2 + \beta^2} + \frac{\beta \cos \theta}{(S + \alpha)^2 + \beta^2} \right]$$

Show, by initial value theorem

$$\lim_{t \rightarrow 0} f(t) = M \sin \theta$$

- Q.4** a. In the circuit of Fig.1, find the power loss in the 1Ω resistor by Thevenin theorem (8)

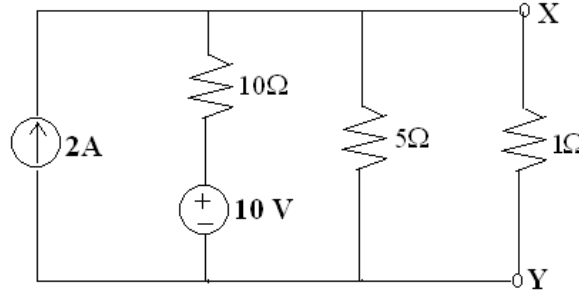


Fig.1

- b. Find the value of R in the circuit of Fig.2 such that maximum power transfer takes place. What is the amount of this power? (8)

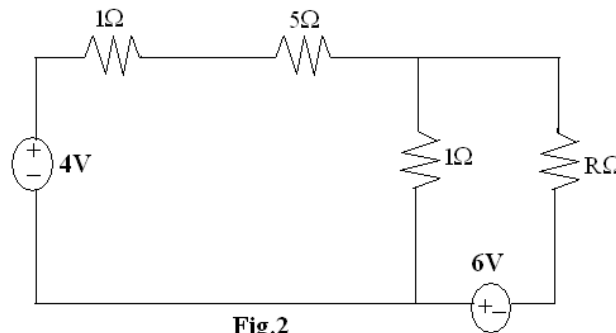


Fig.2

- Q.5** a. Derive the condition of reciprocity or symmetry in h parameter representation. (8)
 b. In the circuit shown in Fig.3, find the h parameter. (8)

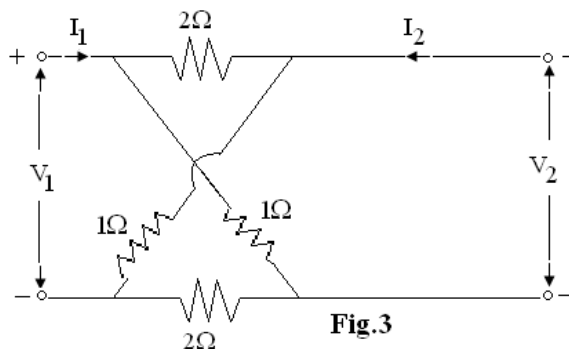


Fig.3

- Q.6** a. A 50 Hz sinusoidal voltage $V=311 \sin \omega t$ is applied to a RL series circuit if the magnitude of resistance is 5Ω and that of inductance is 0.02H.
- (i) Calculate the R.M.S or effective value of steady state current and relative phase angle.
 - (ii) obtain the expression for the instantaneous current.
 - (iii) compute the effective magnitude and phase of voltage drop appearing across each circuit element. (8)
- b. Define the concept of selectivity & bandwidth and their values in terms of Q and ω_0 . (8)

- Q.7** a. Determine the relationship between the resonance frequency f_0 and the half-power frequency f_1 and f_2 in a series resonating circuit. (8)
- b. Show that no value of R_L in the circuit shown in Fig.4 will make it resonant. (8)

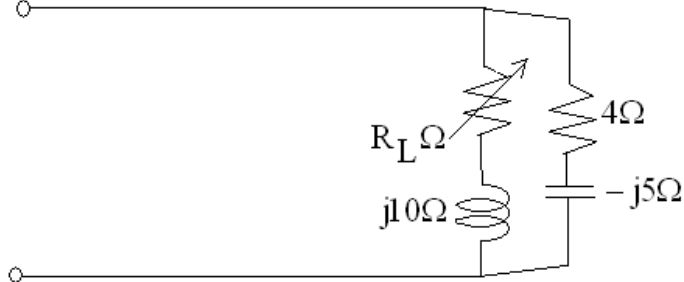


Fig.4

- Q.8** a. Drive the general equation of a transmission line characteristics impedance (Z_0) (8)
- b. Define single stub & double stub matching. And also explain the utility of smith chart for transmission lines.. (8)
- Q.9** a. Define symmetrical and asymmetrical attenuator and give the design parameters of π type attenuator. (8)
- b Design a T & Π section constant K high pass filter having cut off freq. of 12 KHz and nominal impedance. (8)
 $R_0 = 500\Omega$ also find its characteristics impedance and phase constant at 24 KHz.