

Code: AE08

Subject: CIRCUIT THEORY &amp; DESIGN

**AMIETE – ET (OLD SCHEME)**

Time: 3 Hours

**DECEMBER 2011**

Max. Marks: 100

**NOTE: There are 9 Questions in all.**

- Please write your Roll No. at the space provided on each page immediately after receiving the Question Paper.
- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 Minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

**Q.1 Choose the correct or the best alternative in the following: (2×10)**

a. The following constitutes a bilateral element

- (A) A resistor (B) A diode  
(C) A transistor (D) A graph

b. A constant voltage source with 10 V and series internal resistance of 100 ohm is equivalent to a current source of

- (A) 100 mA in parallel with 100 ohm  
(B) 1000 mA in parallel with 100 ohm  
(C) 100 A in parallel with 10 ohm  
(D) 100 mA in parallel with 1000 ohm

c. Kirchoff's Voltage Law (KVL) is indicating conservation of

- (A) Power (B) Energy  
(C) Flux (D) Charge

d. Which of the following quantities possess the dimension of time?

- (A) RC (B) L/R  
(C) (LC)<sup>1/2</sup> (D) All of the above

e. Superposition theorem is not applicable in:

- (A) Voltage responses (B) Power responses  
(C) Current responses (D) All of the above three

Code: AE08

Subject: CIRCUIT THEORY &amp; DESIGN

- f. A series resonant circuit is inductive at  $f = 1200$  Hz. The circuit will be capacitive some where at
- (A)  $f > 1200$  Hz  
 (B)  $f < 1200$  Hz.  
 (C)  $f$  equal to 1200 Hz and by adding a resistance in series  
 (D)  $f = 600 + f_0$  ( where  $f_0 =$  resonance frequency).
- g. If the load connected to the source is inductive for a maximum transfer of power from source to load, the source impedance should be
- (A) Inductive (B) Capacitive  
 (C) Resistive (D) Combination of L & C
- h. The junction of two or more branches is known as
- (A) graph (B) node  
 (C) ground (D) chord
- i. An attenuator is
- (A) R- L-C network (B) R's network  
 (C) R-L network (D) R-C network
- j. An ideal filter should have
- (A) Zero attenuation in the pass band  
 (B) Zero attenuation in the attenuation band.  
 (C) Infinite attenuation in the pass band  
 (D) None of the above

**Answer any FIVE Questions out of EIGHT Questions.**  
**Each question carries 16 marks.**

- Q.2** a. Explain the following:
- (i) Ideal Voltage Source  
 (ii) Energy and power in an inductor.  
 (iii) Resonance  
 (iv) Pole-zero diagram (8)
- b. A circuit consist of a voltage source  $v(t) = V e^{(-\alpha t)}$   $t > 0$  ; a switch (k), and R-L elements all connected in series. Draw the circuit. If at  $t=0$  the switch is closed. Find  $i(t)$  for
- (i)  $\alpha \neq R/L$  and (ii)  $\alpha = R/L$ . (8)
- Q.3** a. State and prove Reciprocity theorem. Also, state the applications of Reciprocity theorem. (8)

Code: AE08

Subject: CIRCUIT THEORY &amp; DESIGN

- b. Explain Duality. Obtain dual network for the circuit shown in Fig.1. (4+4)

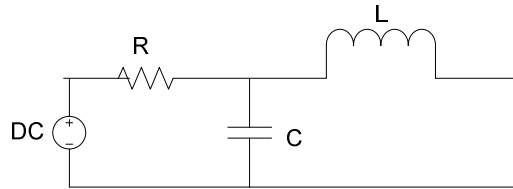


Fig. 1

- Q.4** a. A resistive network is described by the following set of Nodal equations. Develop the possible network and calculate the nodal voltages.

$$\begin{aligned} 7V_1 - 3V_2 - 4V_3 &= -11 \\ -3V_1 + 6V_2 - 2V_3 &= 3 \\ -4V_1 - 2V_2 + 11V_3 &= 25 \end{aligned} \quad (12)$$

- b. A 0.2 H inductor is in parallel with a 100 Ohm resistor. The inductor current is 4 A at  $t=0$ . Determine the inductor current  $i_L(t)$  at 0.8 m sec. (4)

**Q.5** a. Realise  $T(s) = \frac{s^2}{(s+2)(s+5)}$  (8)

- b. With the help of flow-chart, explain the method of determining the steady – state response using phasors. (8)

**Q.6** a. From the following  $Z(s)$  develop a reliable network  $Z(s) = \frac{2(s^2+1)(s^2+9)}{s(s^2+4)}$  (8)

- b. “Total average power supplied to one port network from the source is the sum of  $P_{av}$  for each element of the network”. Prove it. (8)

- Q.7** a. Differentiate the term network analysis and network synthesis. Realise a RLC network whose driving point impedance is given by

$$Z(s) = \frac{(s^2 + 2s + 6)}{s(s+3)} \quad (2+6)$$

- b. Find the Foster-I and Cauer-II form, from the following impedance function

$$Z(s) = \frac{2(s+1)(s+3)}{(s+2)(s+6)} \quad (4+4)$$

- Q.8** a. Discuss the frequency scaling. (4)

- b. Explain basic synthesis procedure. (4)

Code: AE08

Subject: CIRCUIT THEORY &amp; DESIGN

- c. Obtain the Z- parameter for the Circuit shown in the Fig.2. Draw the Z- parameter equivalent model. State whether the network is reciprocal or symmetrical. Assume  $R_1 = 1$  ohm and  $R_2 = 2$  ohms. (8)

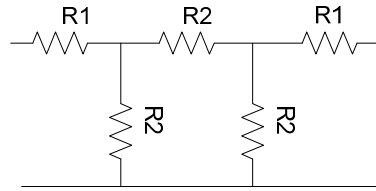


Fig. 2

- Q.9 a. Describe the method of frequency transformation with a typical example. (8)
- b. Differentiate single tuned and double tuned circuit. A tank circuit have a capacitor of 100 pF and an inductor of 150  $\mu$  H. The resistance of the inductor is 5  $\Omega$ . Calculate
- resonant frequency
  - impedance at resonance
  - Q-factor
  - bandwidth. (8)