

Time: 3 Hours

DECEMBER 2011

Max. Marks: 100

NOTE: There are 9 Questions in all.

- Please write your Roll No. at the space provided on each page immediately after receiving the Question Paper.
- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 Minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.


Q.1 Choose the correct or the best alternative in the following: (2×10)

- a. The rate of change of an integrator's output voltage in response to a step input is set by
- (A) The RC time constant
(B) The amplitude of the step input
(C) The current through the capacitor
(D) all of these
- b. In a 4-bit binary weighted input DAC, if the lowest valued resistor is $1\text{K}\Omega$, the highest valued input resistor is
- (A) $1\text{K}\Omega$ (B) $4\text{K}\Omega$
(C) $8\text{K}\Omega$ (D) $16\text{K}\Omega$
- c. The type of ADC with the fastest conversion time is the
- (A) Dual slope (B) Single slope
(C) Simultaneous (D) Successive approximation
- d. The output of a particular op-amp increases 8V in $12\mu\text{s}$. The slew rate is
- (A) $96\text{V}/\mu\text{s}$ (B) $0.67\text{V}/\mu\text{s}$
(C) $1.5\text{V}/\mu\text{s}$ (D) None of these
- e. The frequency at which the open loop gain is equal to one is called
- (A) The upper critical frequency (B) Cutoff frequency
(C) The notch frequency (D) The unity gain frequency
- f. In ECL negative supply voltage is used because of
- (A) Reduction in noise at the output (B) Saving in power
(C) Case of wired-OR operation (D) Increase in speed of operation

- g. The figure of merit of a logic family is given by
- (A) Gain x bandwidth
 - (B) Propagation delay time x power dissipation
 - (C) Fan-out x propagation delay time
 - (D) Noise margin x power dissipation
- h. When a flip flop is reset, its output will be
- (A) $Q = 0, \bar{Q} = 1$
 - (B) $Q = 1, \bar{Q} = 0$
 - (C) $Q = 0, \bar{Q} = 0$
 - (D) $Q = 1, \bar{Q} = 1$
- i. In a T FLIP FLOP the output frequency is
- (A) Same as the input frequency
 - (B) One-half of its inputs frequency
 - (C) Double the input frequency
 - (D) None of the above
- j. D flip flop can be used as a
- (A) Differentiator
 - (B) Divider circuit
 - (C) Delay Switch
 - (D) None of the above


Answer any FIVE Questions out of EIGHT Questions.
Each question carries 16 marks.

Q.2 a.

 

- (i) What are the waveforms at the two outputs of the circuits of Fig.1?
- (ii) What is the peak to peak amplitude of output1?
- (iii) What is the peak to peak amplitude of output2?
- (iv) What is the frequency of each output waveform? (8)

 - b. Determine the input and output impedances of the amplifier in the Fig.2. The op-amp data sheet gives $Z_{in} = 2M\Omega$, $Z_{out} = 75\Omega$, and $A_{oi} = 200,000$. Also find the closed loop gain. (8)



Code: AE09

Subject: ANALOG & DIGITAL ELECTRONICS

- Q.3** a. Name the basic parts of an active filters. Explain how Butterworth, Chebyshev and Bessel responses differ. (8)
- b. Determine the critical frequency of the low pass filter in the Fig.3, and set the value of R_1 for an approximate Butterworth response. (8)

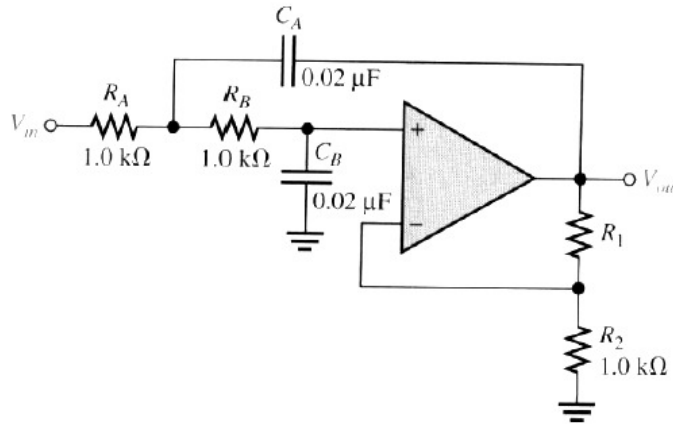


Fig.3

- Q.4** a. Draw Log and antilog amplifier with a BJT. Explain the purpose of transistor perform in the log and antilog amplifier circuits. (8)
- b. Describe the operation of digital to analog R/2R ladder DAC. Discuss resolution, accuracy, linearity, monotonicity and settling time. (8)
- Q.5** a. (i) For the transistor switching circuit in Fig.4, what is V_{CE} When $V_{IN} = 0V$.
 (ii) What minimum value of I_B is required to saturate this Transistor if β_{DC} is 200? Assume $V_{CE(sat)} = 0V$.
 (iii) Calculate the maximum value of R_B when $V_{IN} = 5V$. (8)

 


Fig.4

- b. Why switching speed of a BJT is limited. How a schottky transistor can improve it? (8)

Code: AE09**Subject: ANALOG & DIGITAL ELECTRONICS**

- Q.6** a. Realize the following boolean expression using 4:1 MUX(S) only.
 $Z = A'B'C'D' + A'BCD' + AB'CD' + AB'C'D + AB'C'D' + ABCD$ (8)
- b. Implement a full adder with a decoder and two OR gates. (8)
- Q.7** a. Design a combinational circuit using a ROM that accepts a 2-bit number and generates an output binary number equal to the square of the input number (6)
- b. Compare TTL and ECL logic family and explain how TTL is interface to ECL. (10)
- Q.8** a. Draw and explain the operation of four bit universal shift register. (8)
- b. Draw and explain the operation of four bit Johnson counter. (8)
- Q.9** a. A simple function of three inputs is given by the following expression:
 $F(H) = (\overline{AB} + C)H$
- (i) Construct the logic circuit by using AND/NOR/INV logic. Assume that the inputs arrive active high.
- (ii) Construct the CMOS circuit for the function given in part (i).
- (iii) Obtain the physical truth table for the circuit of part (ii).
- (iv) Obtain the positive logic truth table for the circuit of part (ii). (8)
- b. A system needs a $4K \times 8$ memory system. But the requirement is such that a single $2K \times 8$ RAM IC be used and the two consecutive $2K$ memory addresses should be overlapped to this device only? (8)