

Code: AE27

Subject: DIGITAL HARDWARE DESIGN

AMIETE – ET (OLD SCHEME)

Time: 3 Hours

DECEMBER 2011

Max. Marks: 100

NOTE: There are 9 Questions in all.

- Please write your Roll No. at the space provided on each page immediately after receiving the Question Paper.
- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 Minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)a. Which of the following converter is used for *quantization*

- (A) CAD (B) DAC
(C) CDA (D) ADC

b. In *Gray code*, bit-vectors corresponding to consecutive digit values differ by

- (A) 4-bits (B) 5-bits
(C) 1-bit (D) 2-bit

c. Each time an event occurs on any of the signals in the sensitivity list, the statements within a ----- are executed in a sequential order.

- (A) procedure (B) process
(C) function (D) block

d. Logic blocks, interconnection switches and I/O blocks are features of

- (A) PLA (B) ROM
(C) PSA (D) FPGA

e. The number of decoder modules in a coincident decoder are

- (A) 2 (B) 4
(C) 8 (D) 16

f. The output function of Moore machine is given by:

- (A) $z(t) = H(S(-t))$ (B) $z(t) = H(S(t))$
(C) $z(t) = H(S(-t), x(t))$ (D) $z(t) = H(S(t), x(t))$

Code: AE27

Subject: DIGITAL HARDWARE DESIGN

- g. ----- module is the *control unit* of microprogrammed controller.
- (A) Control-store address register (B) Control-store address generator
(C) Microcontroller (D) Control store
- h. A switching function is said to be ----- if and only if it is invariant under any permutation of its variables.
- (A) symmetric (B) unate
(C) canonical (D) threshold
- i. If the width of the trigger pulse is greater than the propagation time of the flip-flop, then flip-flop continues to toggle and results in unpredictable output. This feature is known as
- (A) race around condition (B) unknown condition
(C) stuck around condition (D) None of the above
- j. Datapaths provide connection between various components in a data sub-system consisting of -----
- (A) switches and storage modules (B) wires and functional modules
(C) switches and functional modules (D) wires and switches

Answer any FIVE Questions out of EIGHT Questions.

Each question carries 16 marks.

- Q.2** a. Explain module level, logical level and physical level of implementation in a digital system. (5)
- b. Mention any five features of high level specification of combinational systems. (5)
- c. Explain the following features in combinational systems:
(i) Karnaugh's map
(ii) Tabulation method (3+3 = 6)
- Q.3** a. Describe a system that counts the number of 1's in a four-bit vector x . Give the following:
(i) High-level using arithmetic expression (5)
(ii) Table of arithmetic expression (5)
- b. Reduce the following switching expression to 4 literals:
 $abc\bar{d} + ab\bar{c} + bc\bar{d} + ab\bar{c}\bar{d} + acd + a\bar{b}cd$ (3)
- c. Mention any two features of the following:
(i) Methods to minimize a switching functions
(ii) Symmetric function
(iii) Threshold logic
(iv) Unate function (8)
- Q.4** a. Expand the features of VHDL. Explain how entity and architectures are related with a block diagram. (3+4)

Code: AE27

Subject: DIGITAL HARDWARE DESIGN

- b. Give an example to illustrate mixed style modeling using VHDL. (6)
- c. Compare functions and procedures in VHDL. (3)
- Q.5** a. Explain coincident decoding and tree decoding used in decoder networks. (8)
- b. What is a shift register? Explain various types of shift registers and give their respective applications. (8)
- Q.6** a. Compare Moore and Mealy state machines. Give their applications. (6)
- b. Explain any two methods used in simplification of incompletely specified synchronous machines. (6)
- c. Explain the asynchronous state machine and its mode of operations. (4)
- Q.7** a. Explain data subsystem. Mention various components used in data subsystem. Explain the role of storage and functional modules in data subsystem. (8)
- b. Write short notes on ASM Charts. (4)
- c. Compare explicit and implicit microinstruction sequencing. (4)
- Q.8** a. Determine the state diagram for the sequential system described by the following expressions: (6)
- $$s(t+1) = \begin{cases} s(t) & \text{if } x = a \\ (s(t)+1) \bmod 5 & \text{if } x = b \\ 2 & \text{if } x = c \end{cases}$$
- $$z(t) = \begin{cases} 0 & \text{if } s(t) \text{ is even} \\ 1 & \text{otherwise} \end{cases}$$
- The system has five states labeled 0,1,2,3, and 4.
- b. Give the advantages and disadvantages of programmable modules. (6)
- c. Explain various types of hazards in asynchronous sequential circuits. (4)
- Q.9** a. Write short notes for any **THREE** of the following: (3×4 = 12)
- Microinstruction format
 - Microinstruction timing
 - Signal and variables in VHDL
 - Priority Encoders
- b. Express the complement of $E(x, y, z) = \Pi M(1,4,6,7)$ as sum of minterms and product of maxterms. (4)