

**DiplETE – ET (NEW SCHEME) – Code: DE57****Subject: NETWORKS AND TRANSMISSION LINES**

Time: 3 Hours

**DECEMBER 2011**

Max. Marks: 100

**NOTE: There are 9 Questions in all.**

- Please write your Roll No. at the space provided on each page immediately after receiving the Question Paper.
- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 Minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

**Q.1 Choose the correct or the best alternative in the following: (2×10)**

- a. A practical current source consists of
- (A) An ideal current source in series with an impedance  
 (B) An ideal current source in parallel with an impedance  
 (C) Both are correct  
 (D) None of the above
- b. Compensation theorem is applicable to
- (A) linear networks only                      (B) non linear networks only  
 (C) linear and nonlinear networks        (D) none of the above
- c. Peak value of a certain sine wave voltage is 10 V, peak to peak value is
- (A) 10 V    (B) 20 V  
 (C) 5 V    (D) 7.07 V
- d. The maximum value of the coefficient of coupling is
- (A) 100%    (B) 80%  
 (C) more than 100%                              (D) 90%
- e. The inverse Laplace transform of  $\frac{1}{s}(1 - e^{-as})$  is
- (A)  $u(t) - u(t-a)$                               (B)  $u(t)$   
 (C)  $u(t-a)$                                         (D) 0
- f. The Transfer function of a system having pole-zero plot as in Fig. 1 is
- (A)  $\frac{(s-1)}{s(s^2+4)}$     (B)  $\frac{s}{(s-1)(s^2+4)}$   
 (C)  $\frac{s(s-1)}{s^2+4}$     (D)  $\frac{s^2+2}{(s+1)(s-1)}$


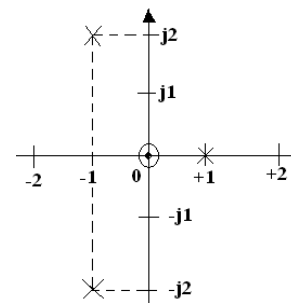


Fig. 1


- g. The h parameters  $h_{11}$  and  $h_{12}$  are obtained
- (A) by shorting output terminals      (B) by opening output terminals  
(C) by shorting input terminals      (D) by opening input terminals
- h. If the network short circuit impedance is 16 ohm and open circuit impedance is 25 ohm. Then characteristic impedance of a network is
- (A) 4  $\Omega$       (B) 20  $\Omega$   
(C) 5/4  $\Omega$       (D) infinite
- i. The propagation constant of a symmetrical T and  $\Pi$  section
- (A) are equal      (B) not equal  
(C) None of the above      (D) both (A) and (B)
- j. If K is the voltage reflection coefficient then SWR standing wave ratio s is
- (A)  $\frac{1-|K|}{1+|K|}$       (B)  $\frac{1+|K|}{1-|K|}$   
(C)  $1+|K|$       (D)  $1-|K|$

**Answer any FIVE Questions out of EIGHT Questions.**  
**Each question carries 16 marks.**

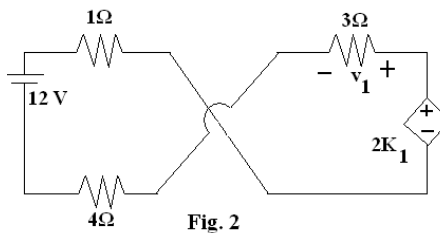- Q.2** a. For the circuit shown in Fig.2, find the power absorbed by each of the elements. (8)



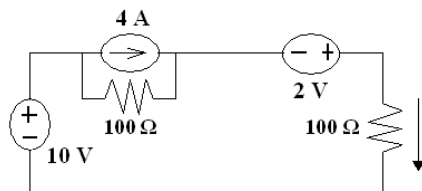- b. Two inductively coupled coils have self inductance  $L_1 = 50$  mH,  $L_2 = 200$  mH. If the coefficient of coupling is 0.5 (i) find the value of mutual inductance between the coils (ii) what is the maximum possible mutual inductance? (4)
- c. Explain the transformation of sources using transformation find the current I in the load of 100  $\Omega$  (Fig.3). (4)



- Q.3** a. Determine the Laplace transform (Fig. 4) of  $f(t)=t$  for  $0 < t < 1$   
 $=0$  for  $t > 1$  (8)

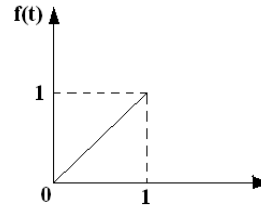


Fig. 4

- b. Verify the initial value theorem for (i)  $2 - e^{5t}$  (ii) final value theorem for  $2 + e^{-3t} \cos 2t$ . (4+4)

- Q.4** a. A 220 V, 100 Hz ac source supplies a series LCR circuit with a capacitor and a coil. If the coil has  $50 \text{ m}\Omega$  resistance and 5 mH inductance, find the quality factor and half power frequencies of the circuit. (8)

- b. Find the short circuit admittance parameters for the circuit as shown in Fig.5. (8)

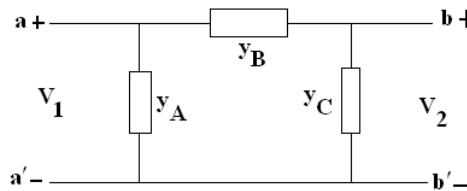


Fig. 5

- Q.5** a. Derive the equations for the elements of an  $m$  derived T &  $\pi$  sections. (8)

- b. A  $50 \Omega$  resistor is connected in series with an inductor having internal resistance, a capacitor and 100 V variable frequency at a frequency of 200 Hz, a maximum current of 0.7 A flows through the circuit and voltage across the capacitor is 200 V. Determine the circuit constants (Fig.6). (8)

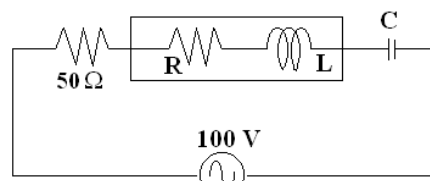


Fig.6

- Q.6** a. Determine the primary line constants of a transmission line / km for a 100 km distortion less line having characteristic impedance  $Z_o = 600 \Omega$  terminated in a pure resistive load of  $400 \Omega$ . When the line is operated at an angular frequency  $\omega = 5000 \text{ rad/s}$ ,  $\alpha$  and  $\beta$  were measured to be  $2 \times 10^{-3}$  neper/km  $5 \times 10^{-3} \text{ rad/km}$  respectively. (8)

- b. Derive open circuit and short circuit impedance of infinite length transmission line and hence write the expressions for  $\alpha$  and  $\beta$  of the lines. (8)

- Q.7** a. A certain lossless transmission line has a characteristic impedance of  $40 \Omega$ . Determine the standing wave ratio with the following end impedances  
 (i)  $Z_L=800 \Omega$  (ii)  $Z_L=650-j475 \Omega$ . (8)
- b. Explain the principle behind single stub impedance matching on a line. Discuss its limitations also. (8)

- Q.8** a. An inductance of  $30 \text{ mH}$  and two shunt capacitances of value  $0.25 \mu\text{F}$  each are used to form a  $\Pi$  section filter. Find  
 (i) type of filter (ii) cut-off frequency,  $f_c$   
 (iii)  $\alpha$  at  $10 \text{ kHz}$  (iv)  $\beta$  at  $10 \text{ kHz}$  (Fig.7) (8)

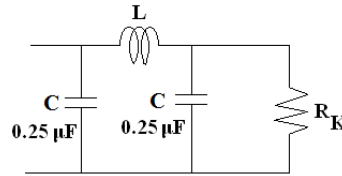


Fig.7

- b. Write short notes on: symmetrical (i) T attenuator and (ii)  $\Pi$  attenuator. (8)
- Q.9** a. State the principle of duality. Obtain the dual of given network (Fig.8). (8)

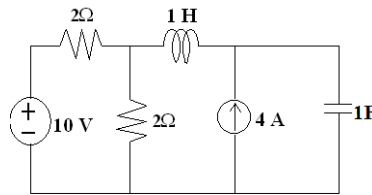


Fig.8

- b. State Milliman theorem. Obtain the equivalent voltage source ( $V_s$ ) and resistance ( $R_s$ ) (Fig.9). (8)

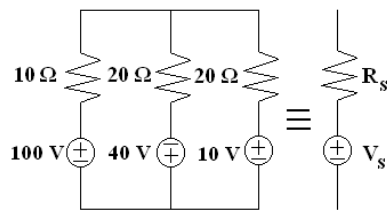


Fig.9