

**DiplETE – ET (NEW SCHEME) – Code: DE59****Subject: ELECTRONIC INSTRUMENTATION  
AND MEASUREMENT**

Time: 3 Hours

Max. Marks: 100

**DECEMBER 2011****NOTE: There are 9 Questions in all.**

- Please write your Roll No. at the space provided on each page immediately after receiving the Question Paper.
- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 Minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

**Q.1 Choose the correct or the best alternative in the following: (2×10)**

a. Dead zone in a certain pyrometer is 0.125% of span. Calibration is 400° C to 1000° C. The temperature change that might occur before it is detected is

- (A) 1° C (B) 0.5° C  
(C) 0.75° C (D) 1.5° C

b. A  $4\frac{1}{2}$  digital voltmeter is used for voltage measurement. On 10 V range, 0.6983 is displayed as \_\_\_\_\_

- (A) 6.983 (B) 0.698  
(C) 0.6983 (D) 6.98

c. A D'Arsonval meter of 200  $\Omega$  and of 0-1 mA sensitivity is to work as voltmeter of full scale rating 10 V. The value of multiplier should be

- (A) 1 k $\Omega$  (B) 10 k $\Omega$   
(C) 9800 k $\Omega$  (D) 900  $\Omega$

d. A.C. bridge circuits are used for the measurement of

- (A) inductance (B) capacitor  
(C) storage factor (D) all of the above

e. A thermometer is calibrated as 150° C to 200° C. The accuracy is specified within  $\pm 0.25\%$  of instrument span. The maximum static error is

- (A)  $\pm 0.2^\circ\text{C}$  (B)  $\pm 0.05^\circ\text{C}$   
(C)  $\pm 0.125^\circ\text{C}$  (D)  $\pm 1.25^\circ\text{C}$

- f. A 600 V voltmeter is specified to be accurate within  $\pm 2\%$  of full scale. The limiting error when the instrument is used to measure a voltage of 250 V is
- (A) 4.8% (B) 5.4%  
(C) 6.2% (D) 2.8%
- g. Digital instrument have input impedance of the order of
- (A) 1  $\Omega$ . (B) k  $\Omega$   
(C) M  $\Omega$ . (D) m  $\Omega$
- h. Dummy strain gauges are used for
- (A) Compensation of temperature changes  
(B) Increasing the sensitivity of bridge in which they are included  
(C) Compensating for different expansion  
(D) Calibration of strain gauges
- i. Capacitive transducers are normally used for
- (A) static measurements (B) dynamic measurements  
(C) both (A) and (B) (D) transient measurements
- j. A resistance potentiometer is a
- (A) first order instrument (B) zero order instrument.  
(C) second order instrument (D) none of the above

**Answer any FIVE Questions out of EIGHT Questions.  
Each question carries 16 marks.**

- Q.2** a. Explain the following terms:
- (i) Repeatability (ii) Resolution  
(iii) Precision and (iv) Linearity (8)
- b. Discuss the following types of static error occurs in measuring instrument
- (i) Gross error (ii) Systematic error and  
(iii) Random error. (8)
- Q.3** a. Derive the expression for the measurement of capacitance and loss angle of a lossy capacitor using Schering's Bridge. (8)
- b. A Wheatstone Bridge is shown in Fig. 1. The value of resistances are  $P=1 \text{ k}\Omega$ ,  $S=5\text{k}\Omega$ ,  $G=100\Omega$ ,  $R=1\text{K}\Omega$ . Thevenin source generates voltage  $E_0=24\text{mV}$  and the galvanometer current is  $13.6\mu\text{A}$ . Calculate the value of Q. (8)

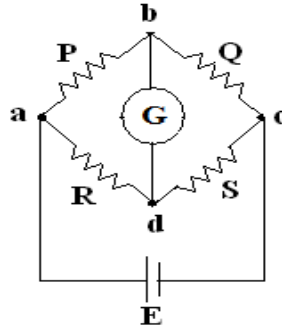


Fig. 1

- Q.4** a. Discuss different types of thermocouples with neat diagram. Give its limitations (8)
- b. Convert a basic D'Arsonval movement with an internal resistance of  $50\ \Omega$  and a full scale deflection current of  $2\text{mA}$  into a multirange d.c voltmeter with voltage ranges of  $0\text{-}10\ \text{V}$ ,  $0\text{-}50\ \text{V}$ ,  $0\text{-}100\ \text{V}$  and  $0\text{-}250\ \text{V}$  (8)

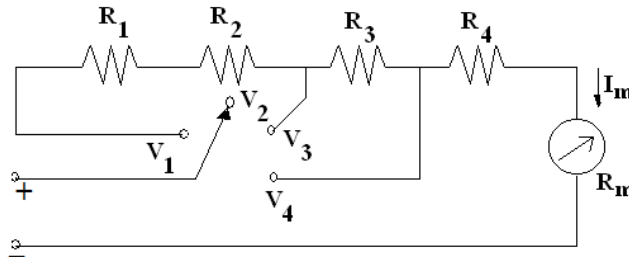


Fig. 2

- Q.5** a. An integrator contains a  $100\ \text{k}\Omega$  and  $1\ \mu\text{F}$  capacitor. If the voltage applied to the integrator input is  $1\ \text{V}$ . What voltage will be present at the output of integrator after  $1\ \text{sec}$ ? Now, if an reference voltage is applied to the same integrator at time  $t_1$  is  $5\ \text{V}$  in amplitude. What is the time interval of  $t_2$ . (8)
- b. Explain the working of a digital phase meter. (8)
- Q.6** a. Bring out the salient features of a pulse generator with a neat block diagram. (8)
- b. Briefly discuss the basic elements of a storage oscilloscope. (8)
- Q.7** a. What is harmonic distortion? With a neat block diagram, explain the features of a fundamental –suppression distortion meter. (8)
- b. Write a note on calorimetric method of measurement of RF power. (8)
- Q.8** a. Explain the principle, advantages and working of potentiometric recorders. (8)
- b. What are the general features to be considered when selecting recorder for a particular application. (8)

- Q.9** a. With respect to signal conditioning of the inputs, explain
- (i) Ratiometric Conversion. (8)
  - (ii) Logarithmic Conversion. (8)
- b. What is LVDT? Describe its operating principle. Also discuss its advantages and disadvantages. (8)